



# D- $\Sigma$ Digital Control for Improving Stability Margin under High Line Impedance

**Tsai-Fu Wu**

Professor, National Tsing Hua University, Taiwan

Elegant Power Electronics Applied Research Laboratory (EPEARL)

Aug. 26, 2015

---

Elegant Power Electronics Applied Research Laboratory (EPEARL)





# Outline


- # Introduction
- # D- $\Sigma$  Digital Control
- # Filter-Capacitor Current Compensation
- # Stability Analysis
- # Experimental Results
- # Conclusions





# # Introduction


## ➤ Harmonized AC and DC Microgrid

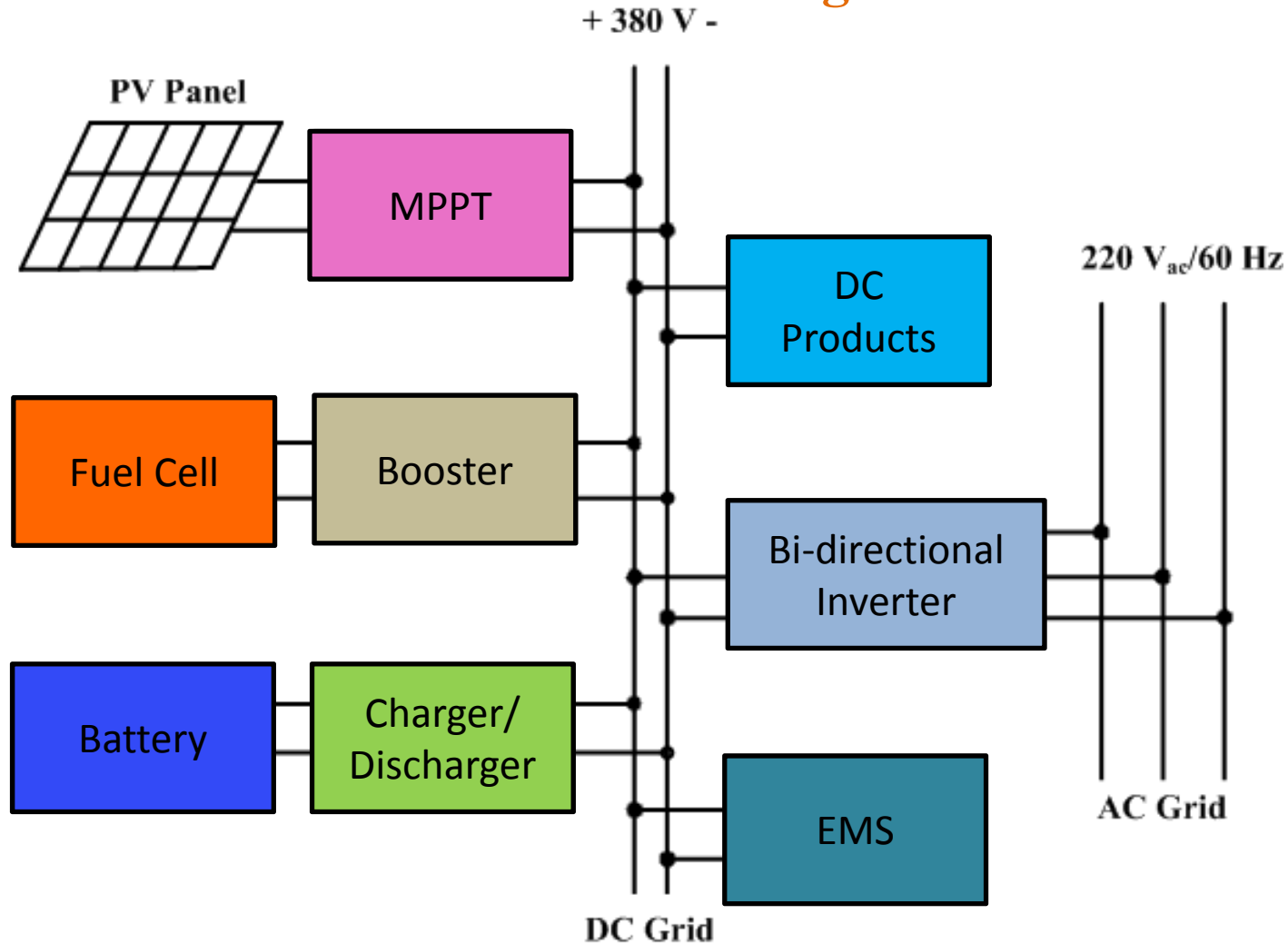



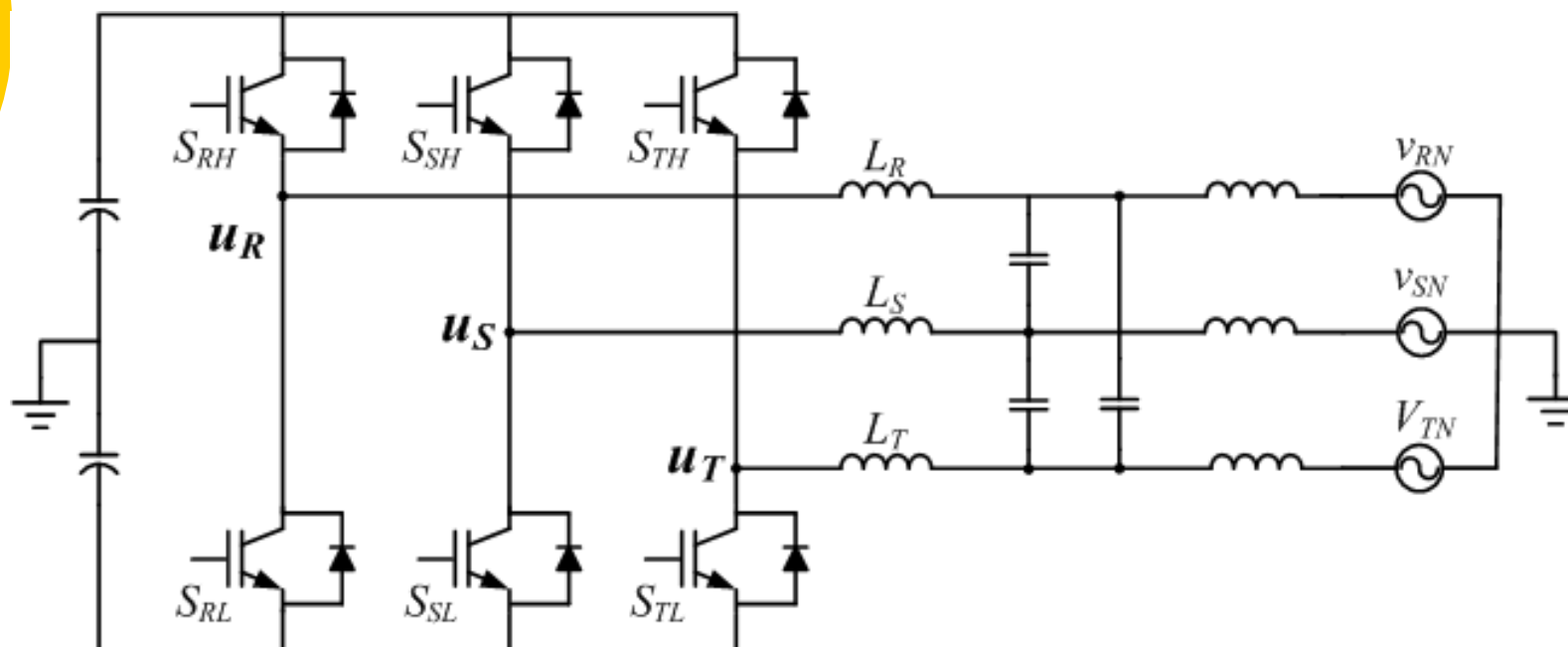
## ➤ Bi-directional Inverter

- $3\Phi 4W$  Inverter (= 3 x 1  $\Phi$  2W Inverters)






- **1 $\Phi$ 2W Inverter**

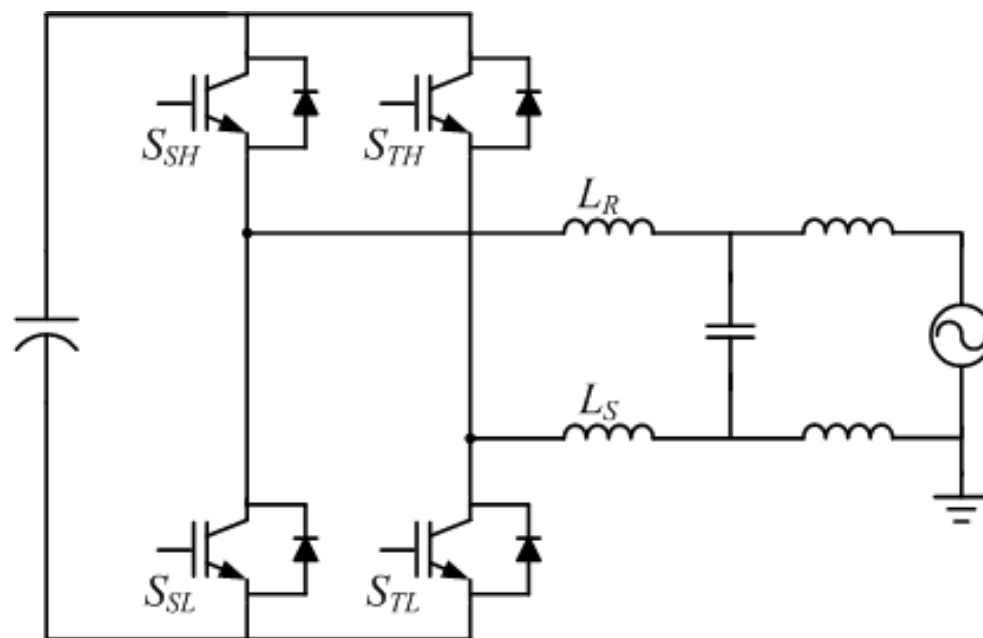





## ➤ SPWM and Bi-Polar Operation

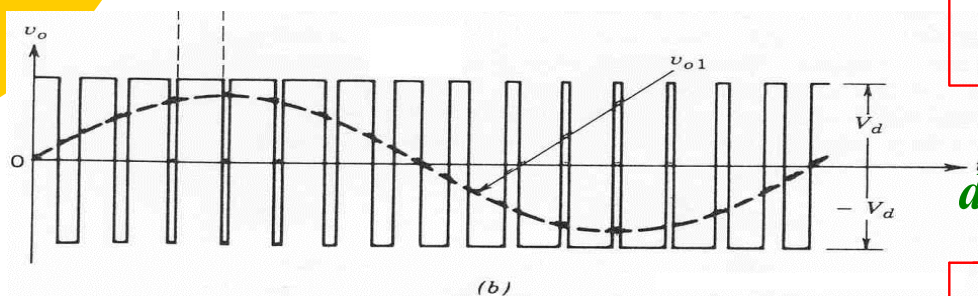

*magnetize*

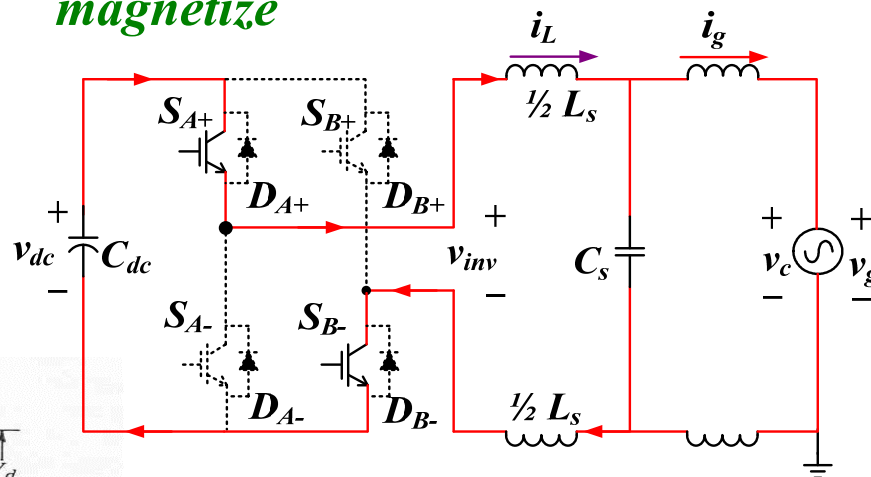

*demagnetize*

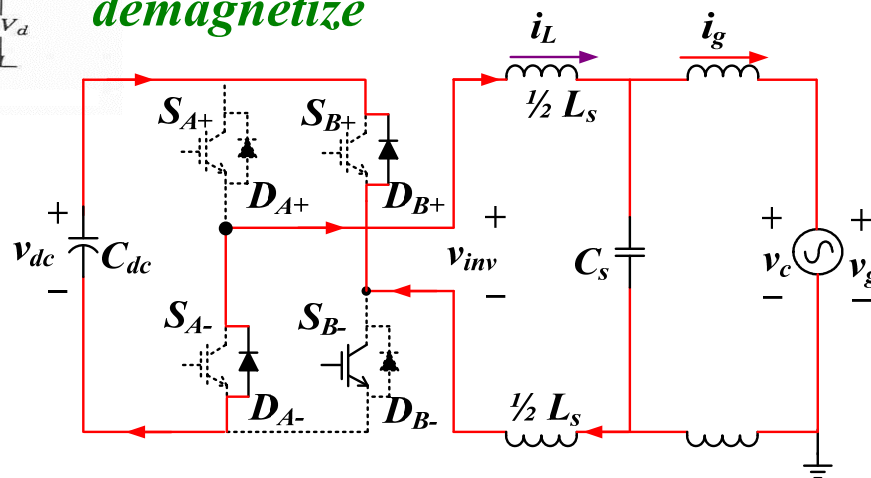





## # D- $\Sigma$ Digital Control

### ➤ Major Characteristics

- 1) No need of frame transformation (for three-phase systems), the D- $\Sigma$  digital control determining control laws directly.
- 2) Unlike predictive control, the D- $\Sigma$  digital control using all of the information known *a priori*.
- 3) Similar to deadbeat control, the D- $\Sigma$  digital control determining control law directly without modulation.
- 4) **Unlike deadbeat control, the D- $\Sigma$  digital control having a controller to cover wide filter inductance, dc-bus voltage and switching frequency variations.**
- 5) Like fuzzy control, the D- $\Sigma$  digital control being named based on the processes of control-law derivation.








## ➤ Unique Features

- 1) **Direct digital control -- link error to control directly.**
- 2) **Current source – achieve high stability margin.**
- 3)  **$G_C \bullet G_P = I$  – cancel parameter variation effects.**
- 4) **Wide bandwidth – up to switching frequency.**




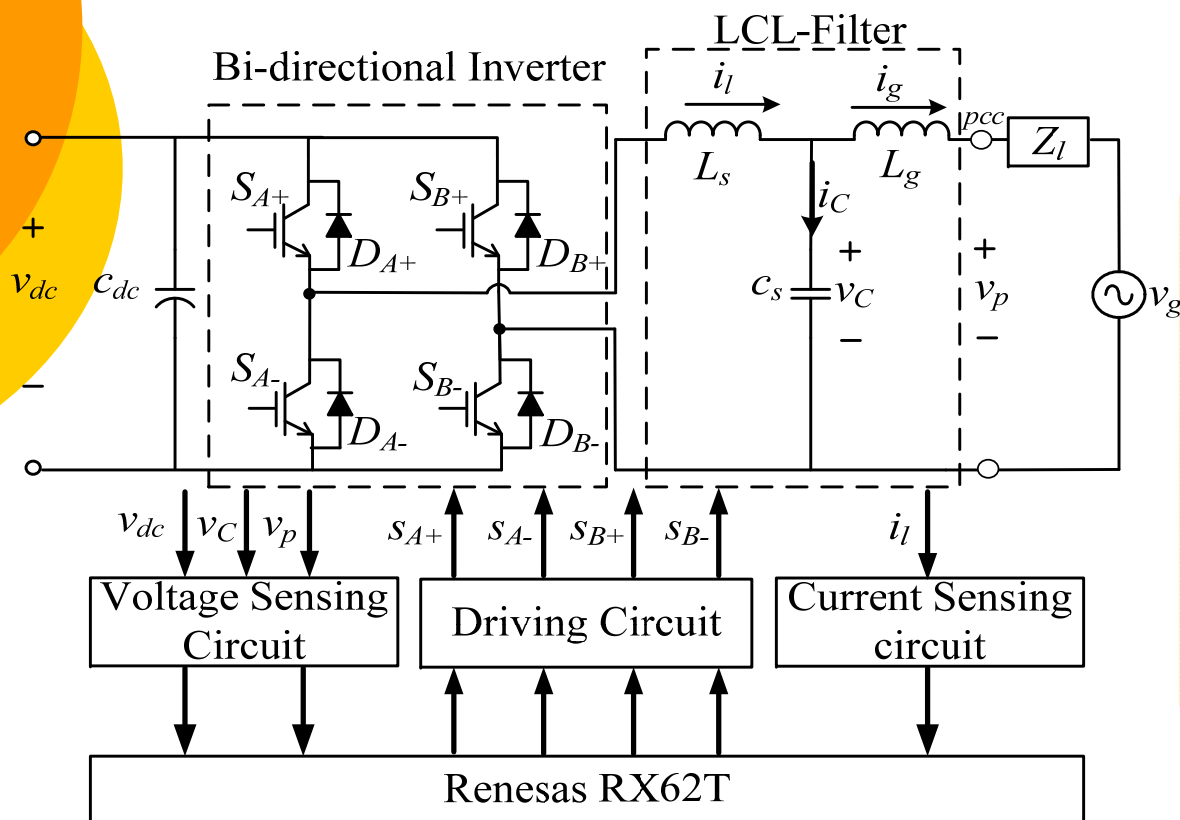
## ➤ Single-Phase Bi-directional Inverter



- D-Σ digital control
- Cover wide inductance variation and grid voltage distortion.
- Shape grid-current sinusoidally.
- Achieve wide BW ( $= f_s$ ).

Circuit diagram of a single-phase bi-directional inverter with LCL filter and its control blocks.



## ➤ Derivation of Control Laws

### A. Grid-Connection Mode

Two buck converters operated in +tive and -tive half line cycles, respectively.

### B. Rectification Mode

Two boost converters operated in +tive and -tive half line cycles, respectively.

### D- Σ Approach (Grid –Connection Mode)

Division (D) of Switching Period:

$$\Delta i_{L_s, magnetize} = \frac{v_{dc} - v_c}{L_s(i_l)} d T_s$$

+ ) and

Control law for grid-connection mode:

$$d_{GC} = \frac{1}{2} + \frac{v_c}{2v_{dc}} + \frac{\Delta i_L \cdot L_s(i_l)}{2v_{dc} \cdot T_s}$$

$$d_{Rec} = 1 - d_{GC} = \frac{1}{2} - \frac{v_c}{2v_{dc}} - \frac{\Delta i_L \cdot L_s(i_l)}{2v_{dc} \cdot T_s}$$


Control law for rectification mode:

$$\Delta i_{L_s, demagnetize} = \frac{v_{dc} + v_c}{L_s(i_l)} (1-d) T_s$$

Summation: Σ



## # LC or LCL Filter

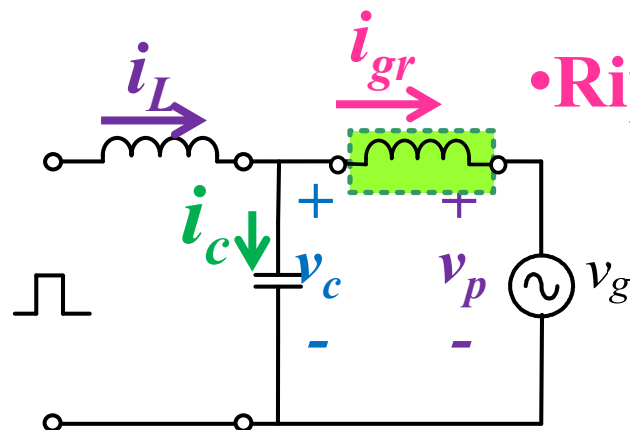

• Ripple Current

✓ LCL Filter

LC filter network at the inverter output side.


$$d_{GC} = \frac{1}{2} + \frac{v_c}{2v_{dc}} + \frac{\Delta i_L(n+1) \cdot L_s(i_L)}{2v_{dc} \cdot T_s}$$

$$\begin{aligned} \Delta i_L(n+1) &= I_{gr}(n+1) - i_{Lfb}(n) \\ &= (I_{gr}(n) - i_{Lfb}(n)) + (I_{gr}(n+1) - I_{gr}(n)) \end{aligned}$$

$$I_{gr} = I_M \sin(n\omega T_s)$$


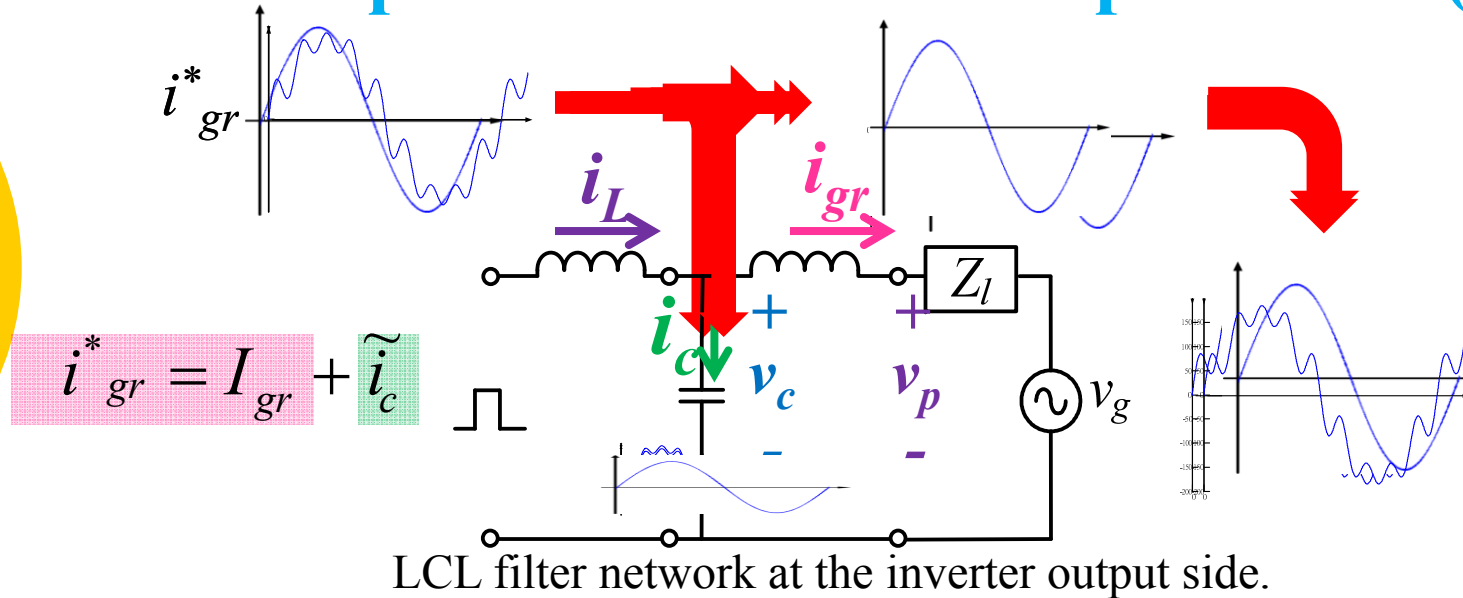
# # Filter-Capacitor Current Compensation (FCCC)



$$d_{GC} = \frac{1}{2} + \frac{v_c}{2v_{dc}} + \frac{\Delta i_L(n+1) \cdot L_s(i_L)}{2v_{dc} \cdot T_s}$$

$$\Delta i_L(n+1) = i_{gr}^*(n+1) - i_{Lfb}(n)$$

$$\Delta i_L(n+1) = I_{gr}(n+1) - i_{Lfb}(n)$$

$$\tilde{i}_c = \frac{C_s (\tilde{v}_c(n+1) - v_c(n))}{T_s}$$

$$I_{gr} = I_M \sin(n\omega T_s)$$


$$\tilde{v}_c(n+1) = v_p(n) + \frac{L_g (I_{gr}(n+1) - I_{gr}(n-1))}{T_s}$$




# # Stability Analysis

## ➤ s-domain model

D-Σ Control

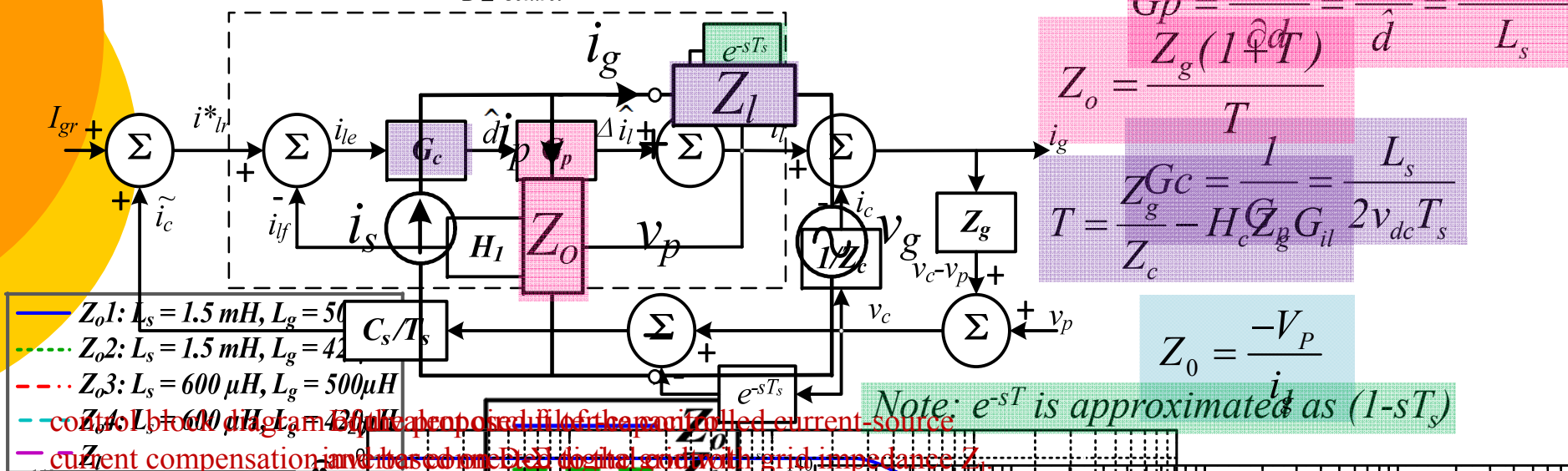

### equivalent transformation

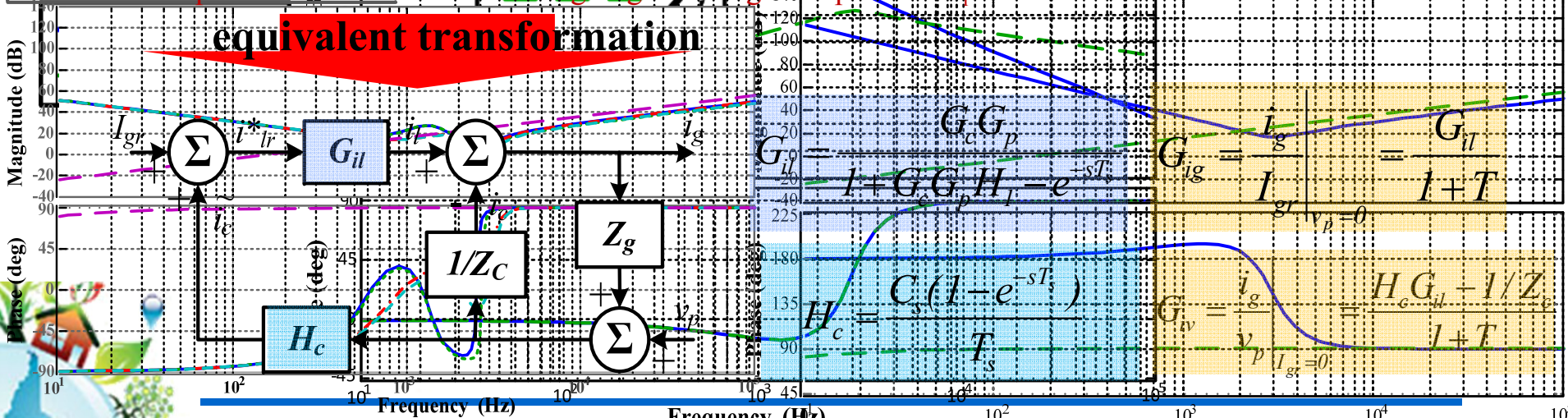




## ➤ Specifications

### SYSTEM PARAMETERS OF THE EXPERIMENT SET-UP

Parameters	Symbols	Values
DC-bus voltage	$V_{DC}$	360 ~ 400 V
AC output voltage	$V_N$	220 V <sub>rms</sub>
Maximum rated power	$P_{max}$	5 kW
Line frequency	$f_l$	60 Hz
Inverter inductors	$L_s$	3 mH ~ 650 $\mu$ H
Filter capacitor	$C_s$	5 $\mu$ F
Power switch	IGBT IRG4PC50SPbF	$V_{CE(on) \text{ typ.}} = 1.28 \text{ V}$ , $V_{CES} = 600\text{V}$ , and $I_{C(TC=25^\circ\text{C})} = 70 \text{ A}$
Power diode (silicon carbide)	CREE C3D20060D	$V_{F(TJ=25^\circ\text{C}) \text{ typ.}} = 1.5 \text{ V}$ Zero-Recovery Time
Switching frequency	$f_s$	20 kHz



## ➤ Prototype

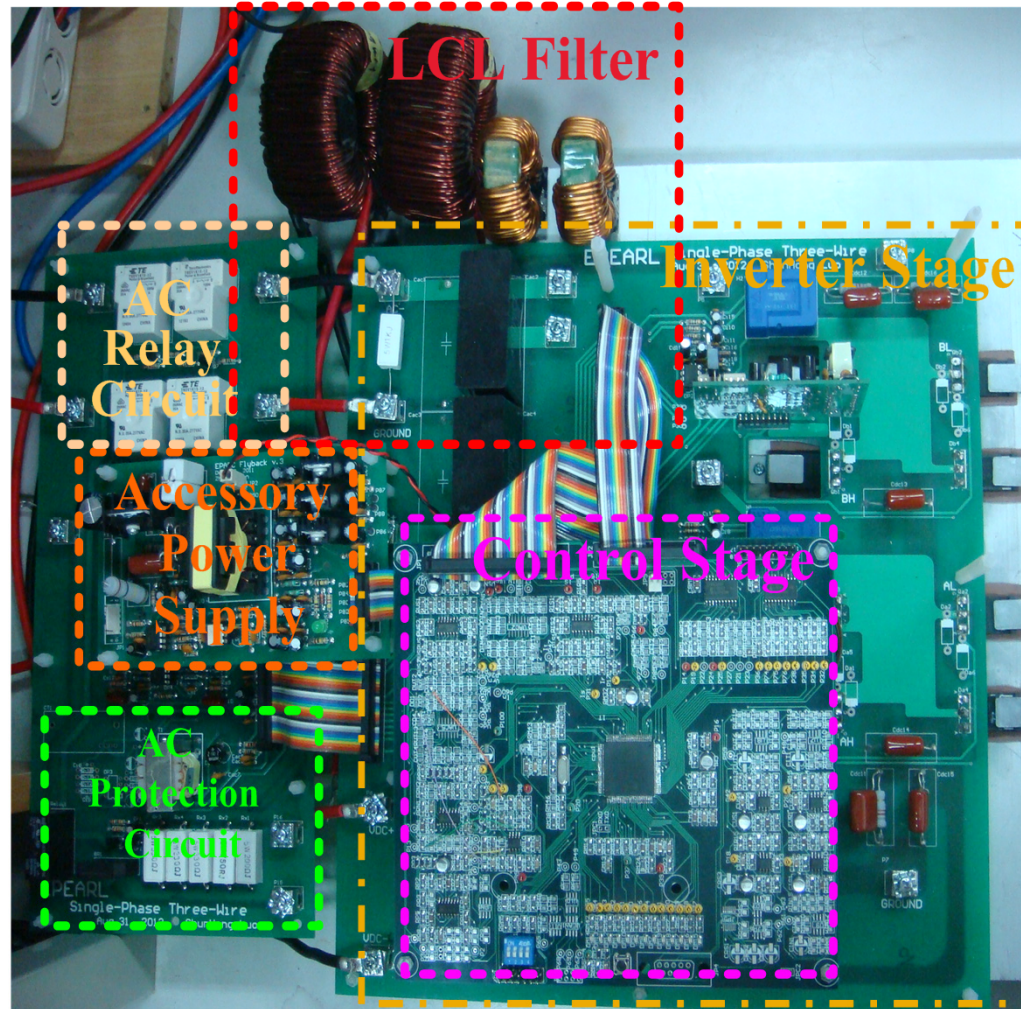


Photograph of the designed single-phase bi-directional inverter system




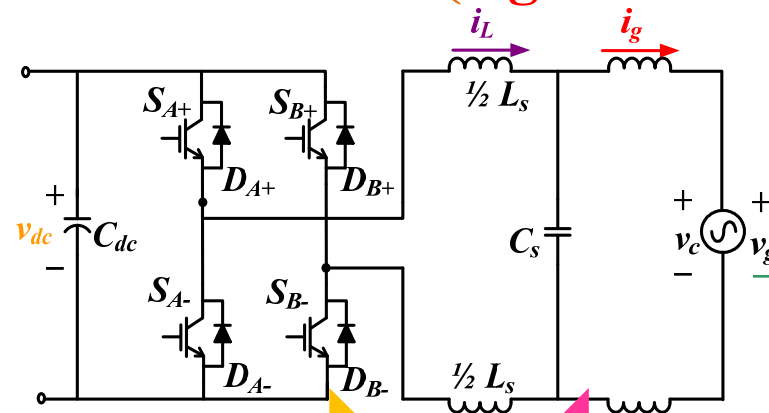
## ➤ Experimental Results ( $V_g$ with no harmonics)




GC mode

GC mode (5 kW)

Rectification mode


Rectification mode (5 kW)

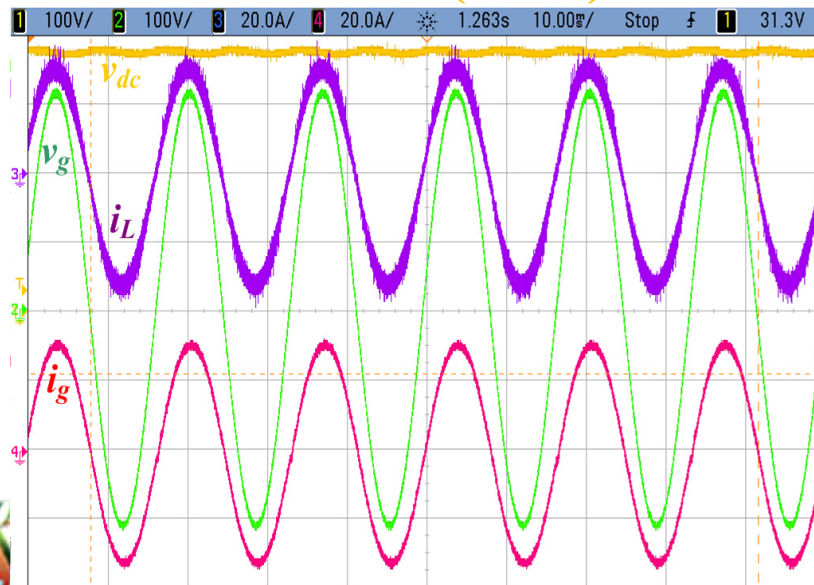



( $i_L$  and  $i_g$ : 20A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)


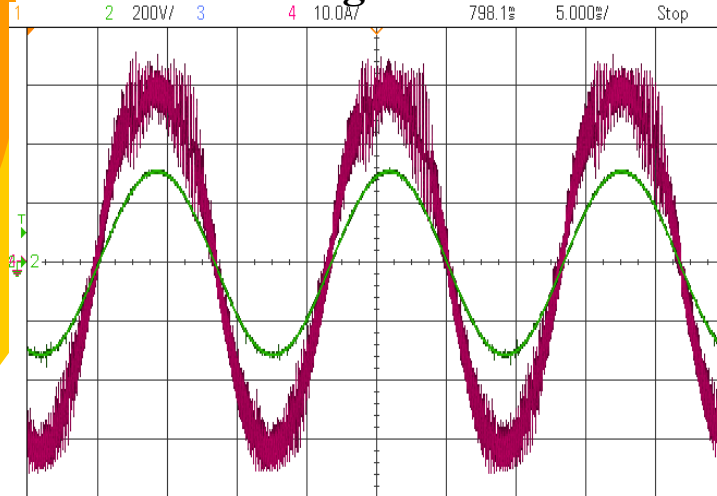
## Without considering inductance variation



## Considering inductance variation

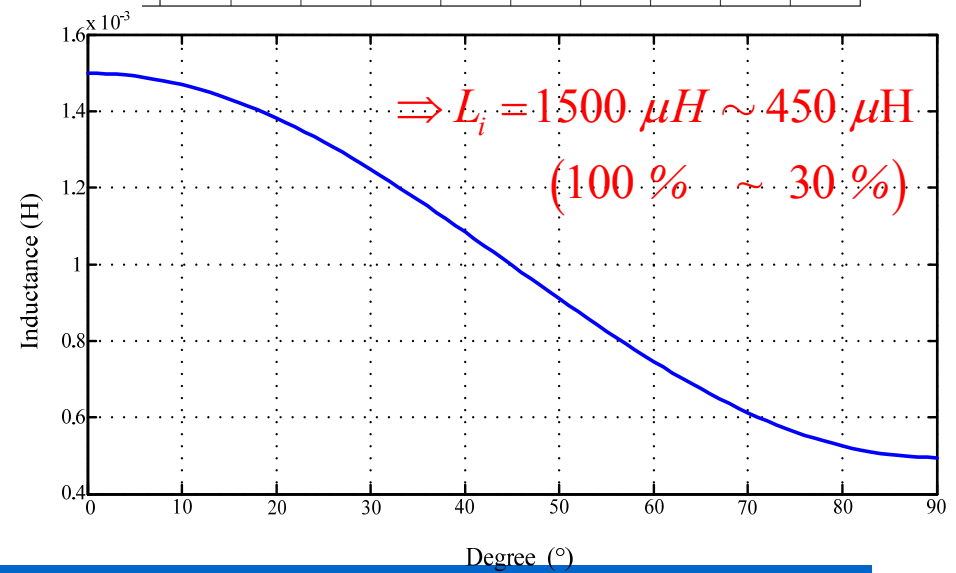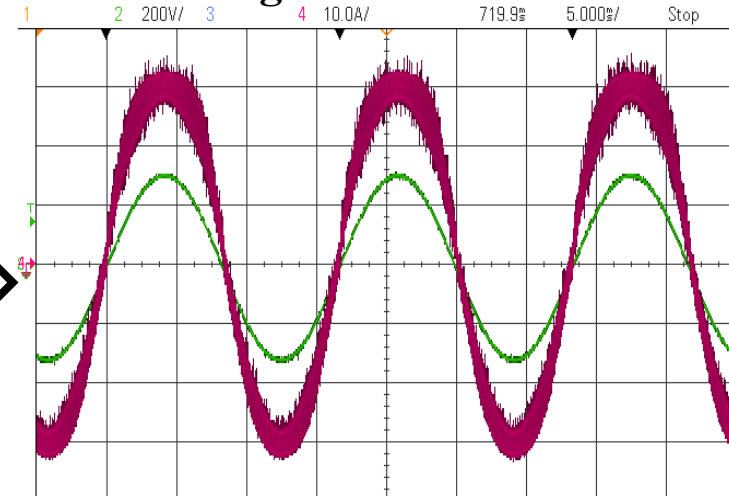




## ➤ Experimental Results (GC mode) ( $V_g$ with harmonics)


✓ *Case I:* ( $V_{THD} : 18.5\%$ )

Harmonic order	%
5	9.8
7	15.8
8	2.16

Without FCCC  $I_{THD} : 18.8\%$

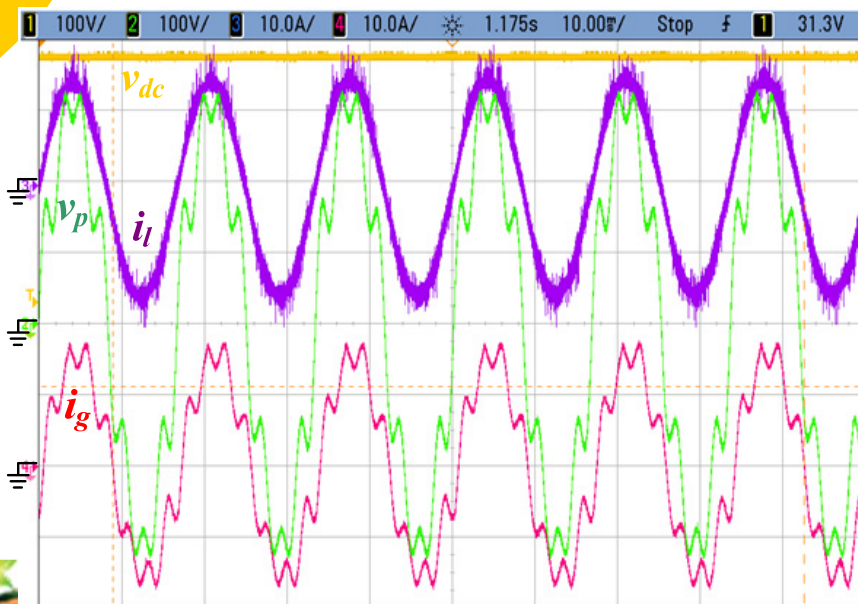

With FCCC  $I_{THD} : 3.2\%$

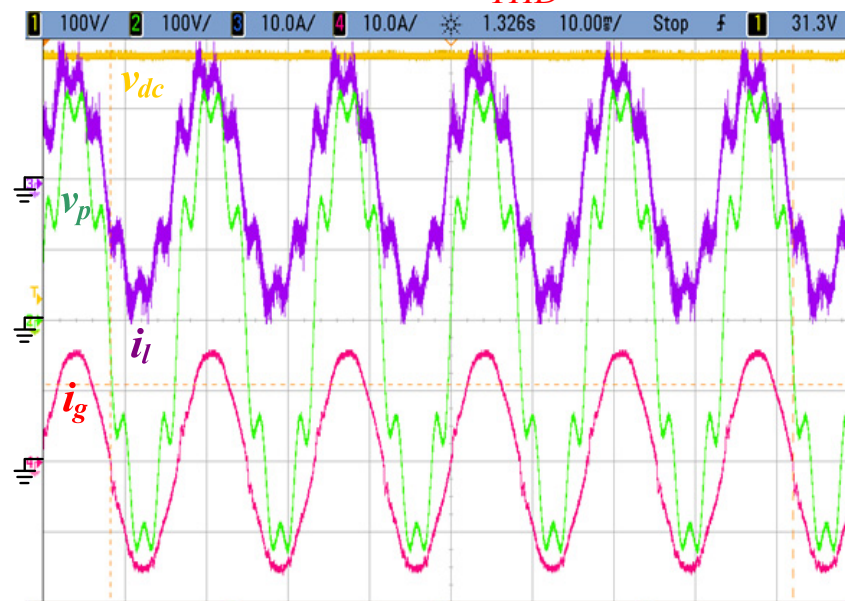


( $i_L$  and  $i_g$ : 10A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)




✓ *Case II: ( $V_{THD} : 6.4%$ )*

Harmonic order	%	Harmonic order	%
3	4.9	11	1.4
5	1.6	15	2
7	2.7	17	1.1

Without FCCC  $I_{THD} : 9.4%$

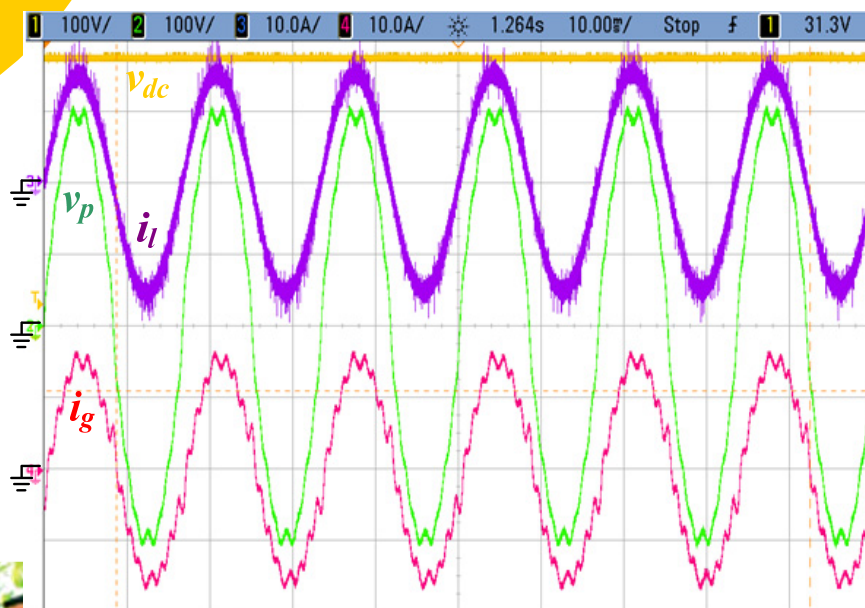

With FCCC  $I_{THD} : 3.8%$

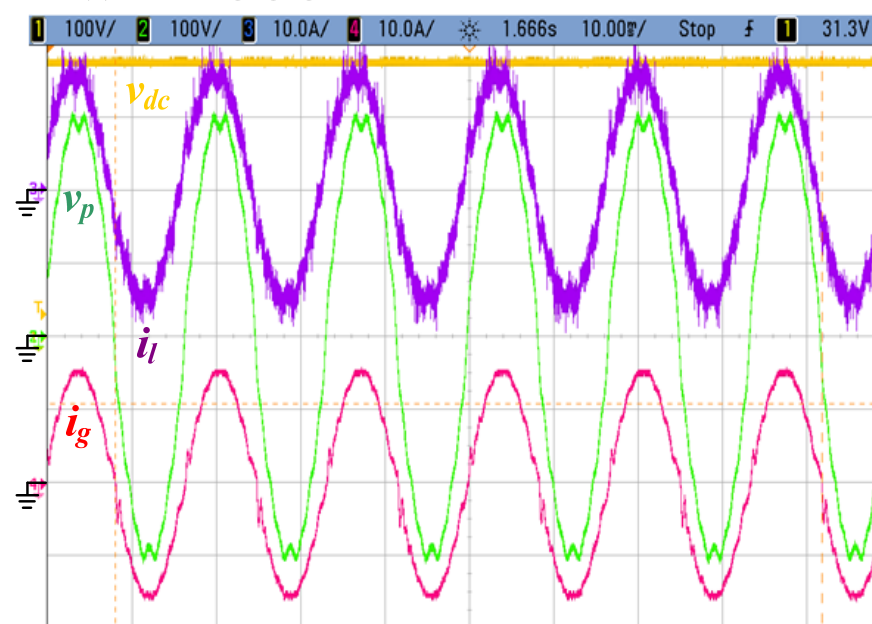


( $i_L$  and  $i_g$ : 10A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)




✓ *Case III: ( $V_{THD} : 17.8%$ )*

Harmonic order	%
3	17.8

Without FCCC  $I_{THD} : 17.7%$

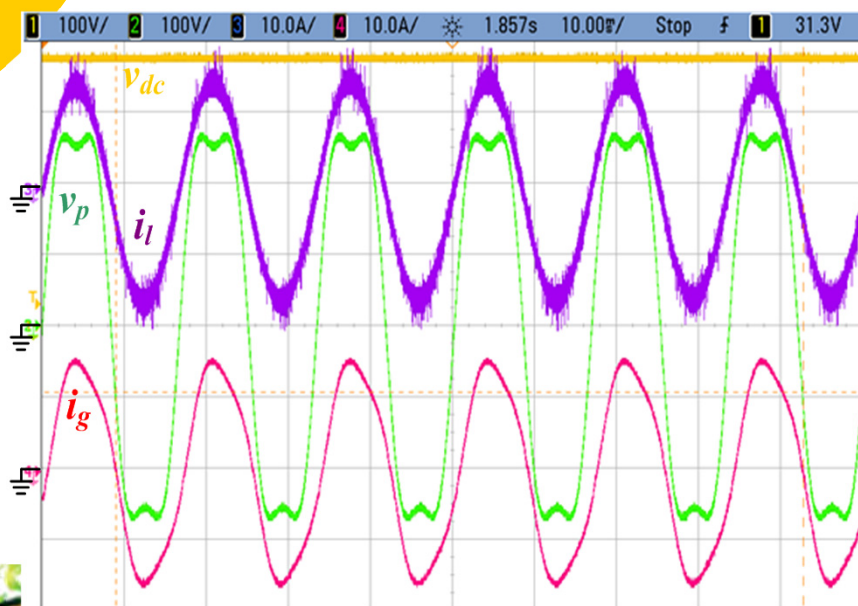

With FCCC  $I_{THD} : 2.1%$

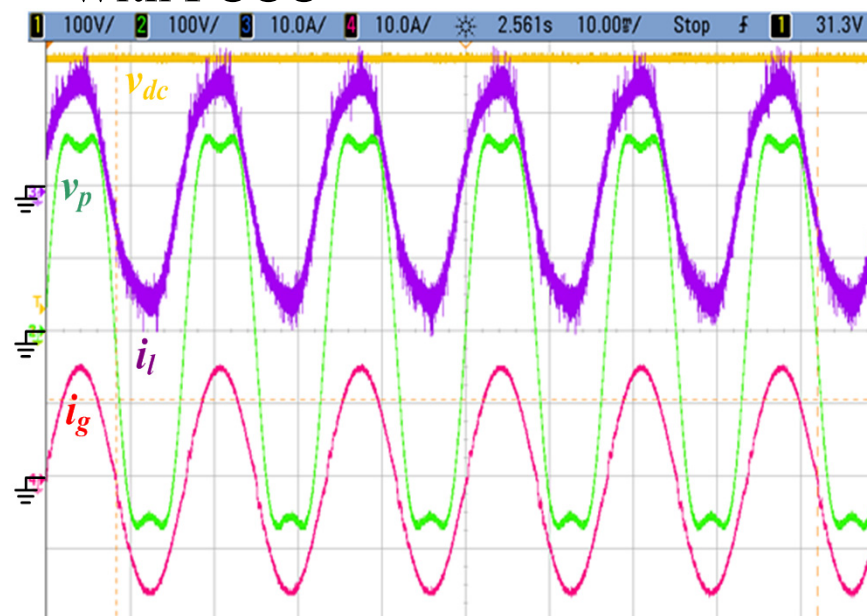


( $i_L$  and  $i_g$ : 10A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)




✓ *Case IV: ( $V_{THD} : 4.9\%$ )*

Harmonic order	%	Harmonic order	%
7	4.6	21	0.9
9	1	39	0.7

Without FCCC  $I_{THD} : 5.1\%$

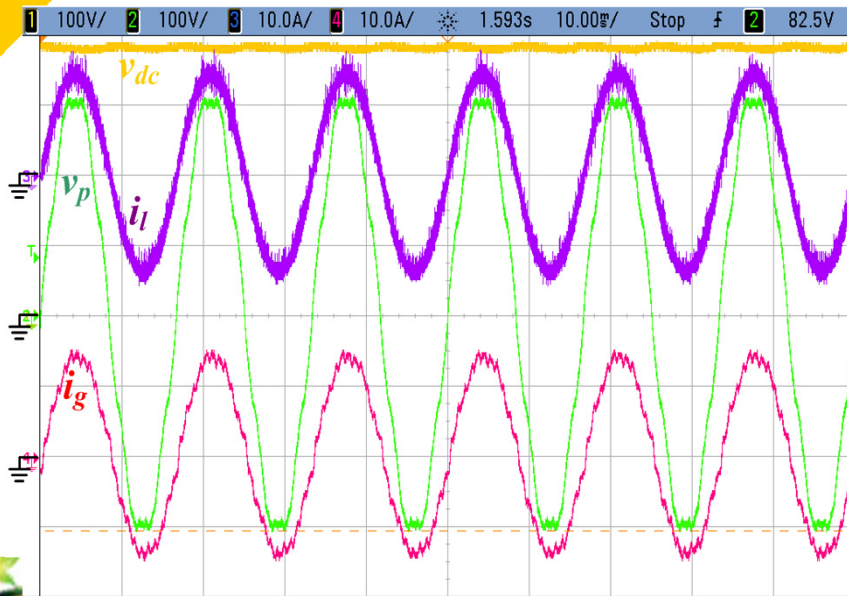

With FCCC  $I_{THD} : 2.5\%$

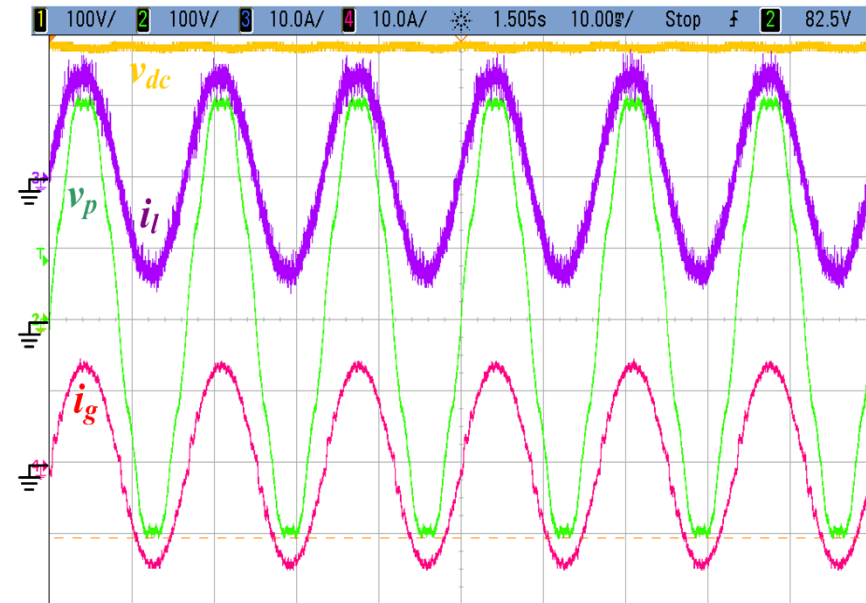

( $i_L$  and  $i_g$ : 10A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)




## Experimental Results (Rectification mode) ( $V_g$ with harmonics)


✓ Case I: ( $V_{THD} : 18.4%$ )

Harmonic order	%
5	9.8
7	15.8
8	2.16

Without FCCC  $I_{THD} : 18.7%$

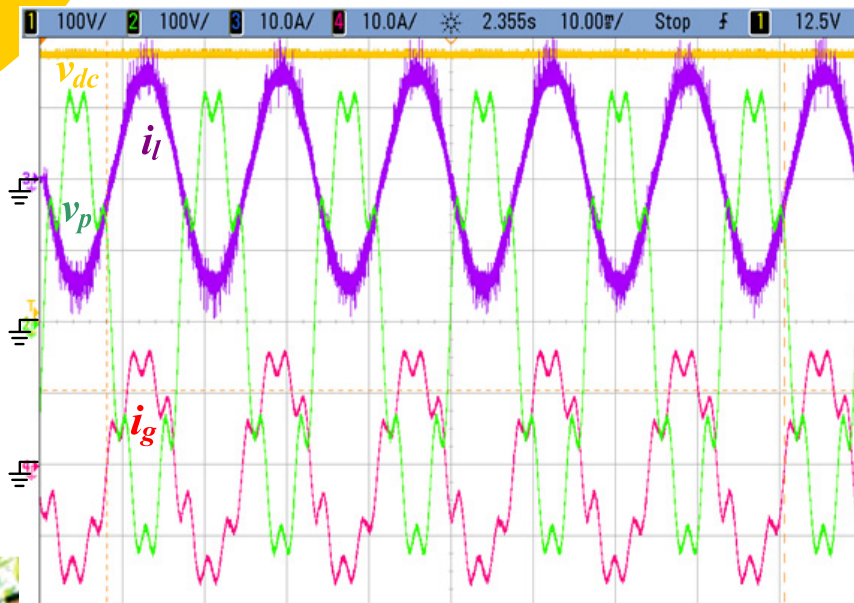

With FCCC  $I_{THD} : 2.8%$

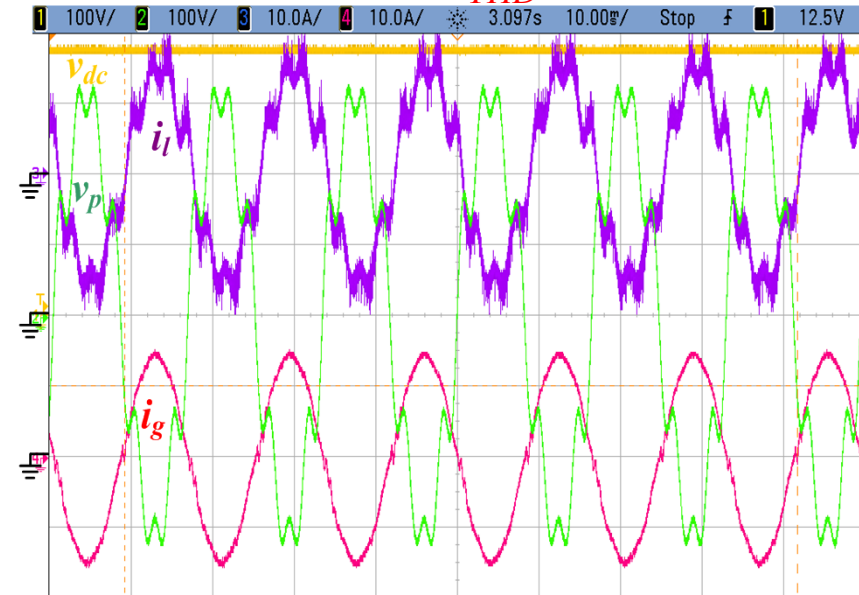


( $i_L$  and  $i_g$ : 10A/div;  $v_g$  and  $v_{dc}$ : 100V/div; time: 10ms/div)




✓ *Case II: ( $V_{THD} : 16.4%$ )*

Harmonic order	%	Harmonic order	%
3	4.9	11	1.4
5	1.6	15	2
7	2.7	17	1.1

Without FCCC  $I_{THD} : 9.3%$

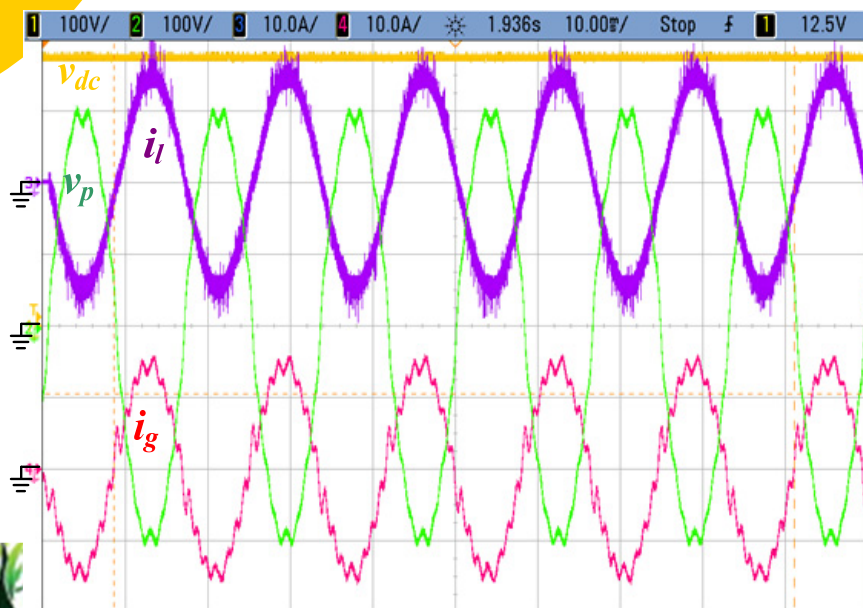

With FCCC  $I_{THD} : 3.3%$

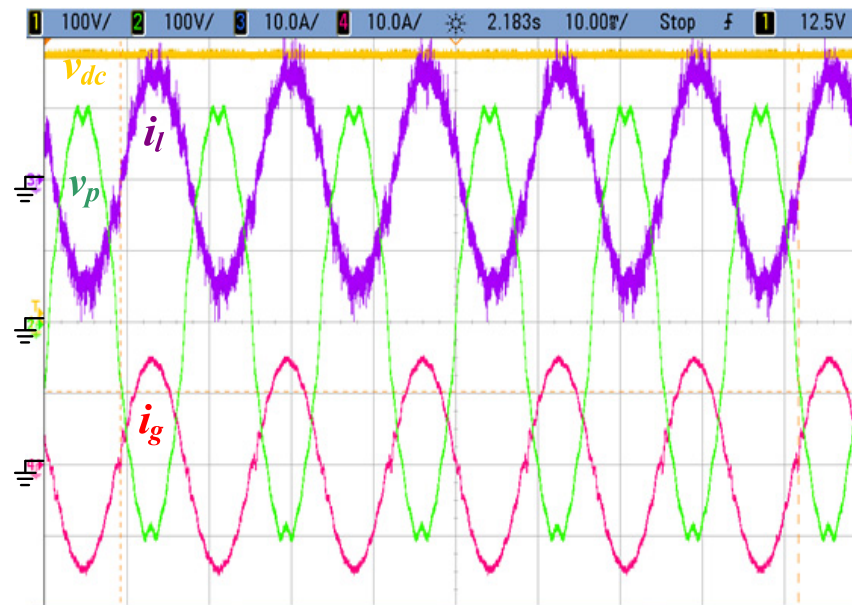

( $i_L$  and  $i_g$ : 10A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)







✓ *Case III: ( $V_{THD} : 17.7%$ )*

Harmonic order	%
3	17.8

Without FCCC  $I_{THD} : 17.8%$

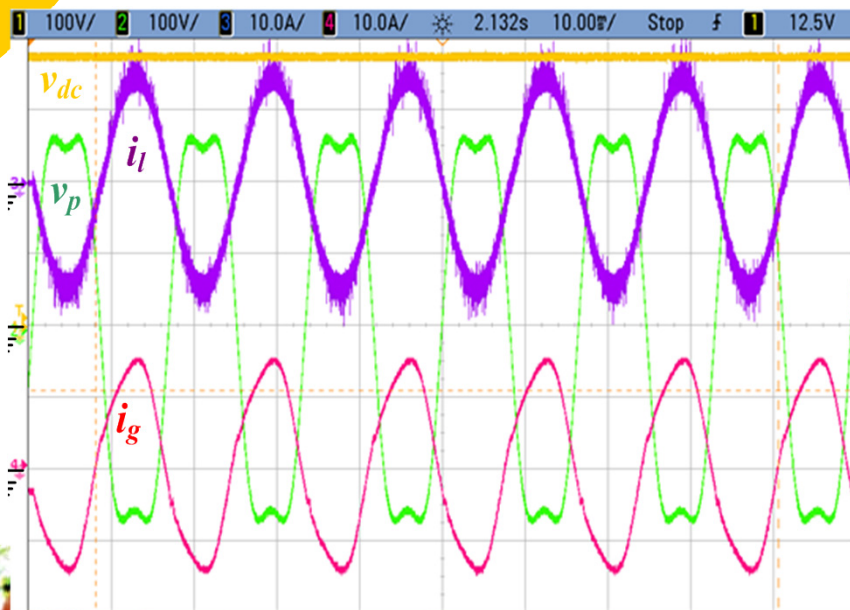

With FCCC  $I_{THD} : 2.0%$

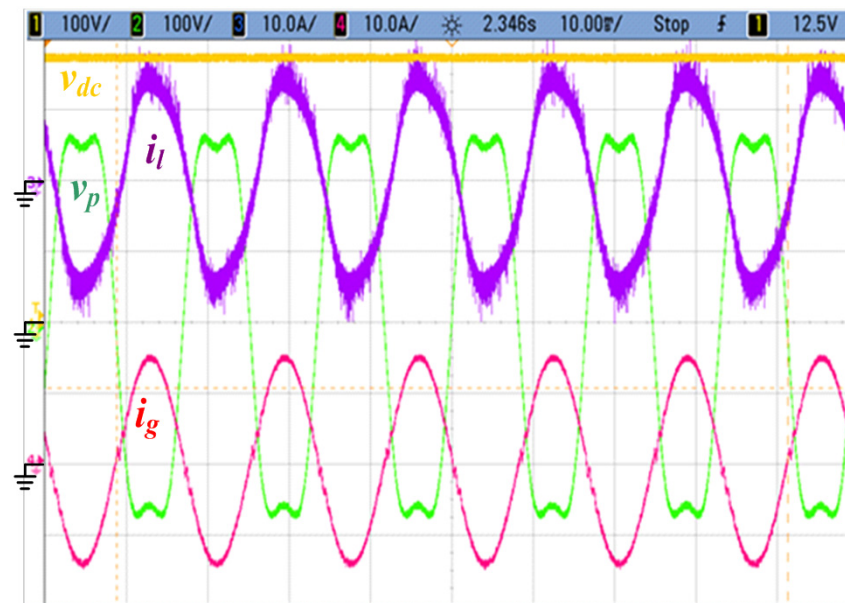


( $i_L$  and  $i_g$ : 10A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)




✓ *Case IV: ( $V_{THD} : 4.9%$ )*

Harmonic order	%	Harmonic order	%
7	4.6	21	0.9
9	1	39	0.7

Without FCCC  $I_{THD} : 5.0%$

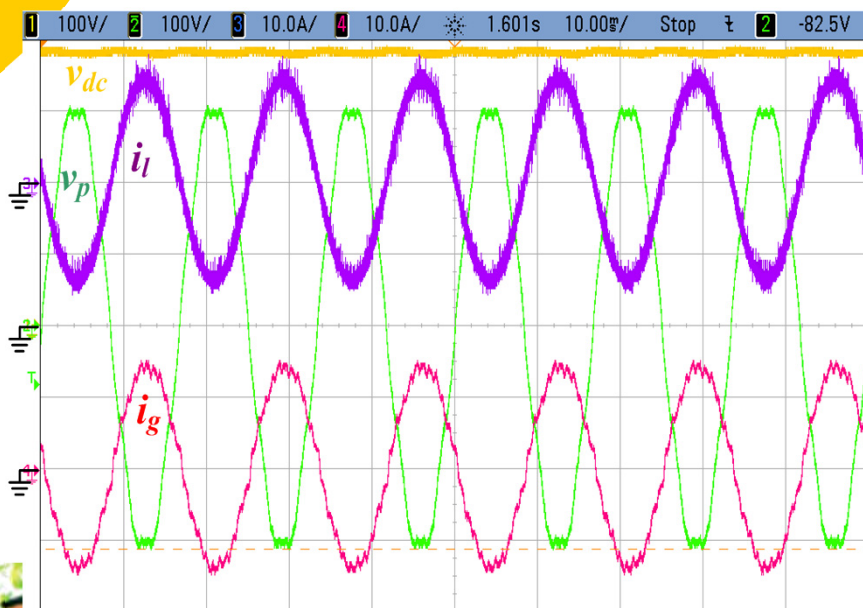

With FCCC  $I_{THD} : 2.6%$

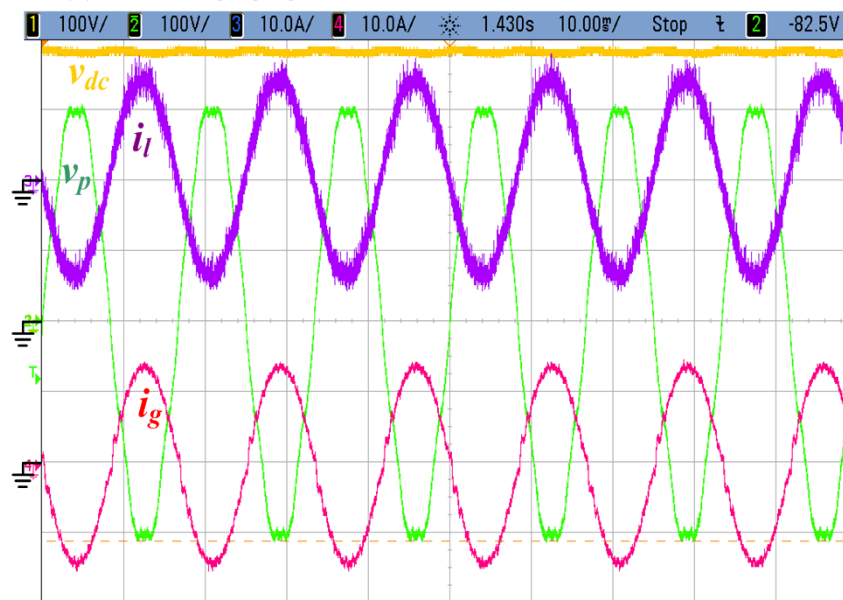

( $i_L$  and  $i_g$ : 10A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)




## ➤ Experimental Results (step current change)

10 A




20 A

(a) with low-THD  $v_g$

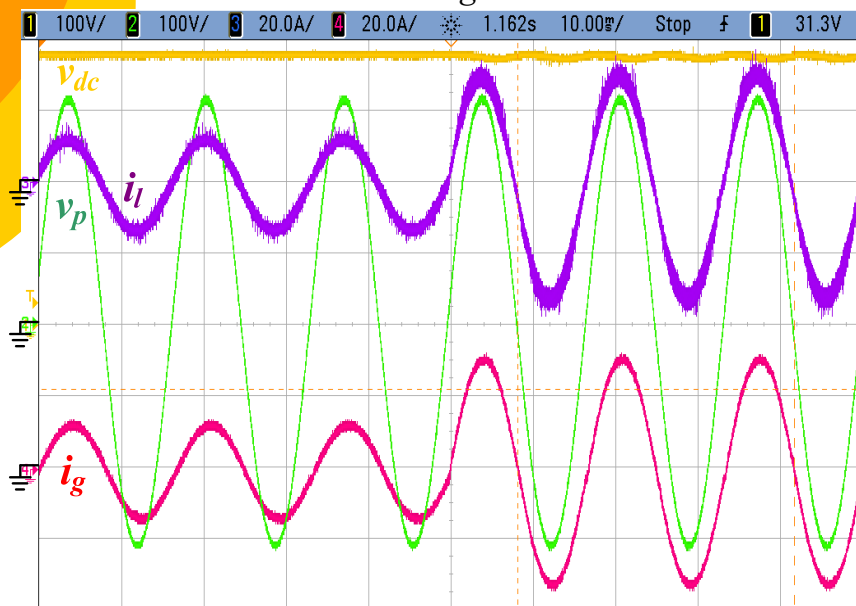

(b) with high-THD  $v_g$

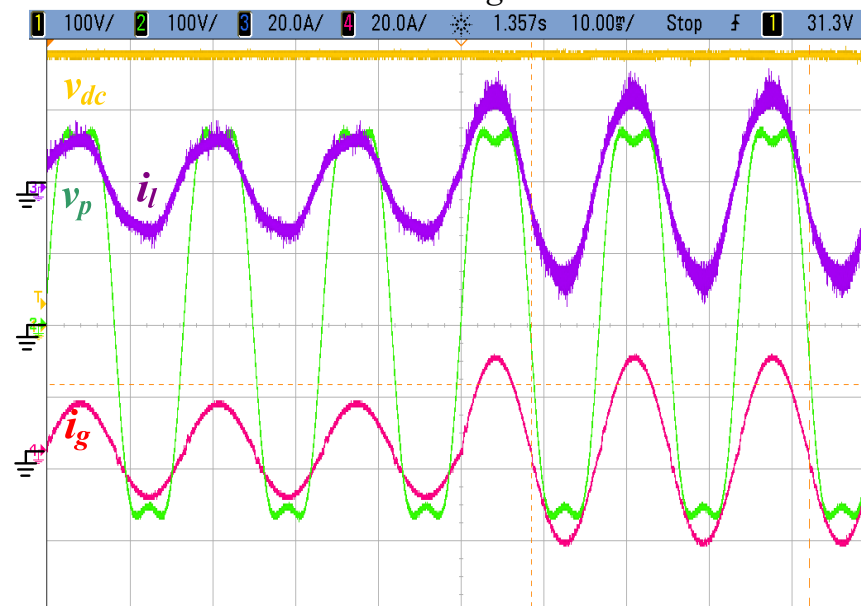

( $i_L$  and  $i_g$ : 20A/div;  $v_g$  and  $v_{dc}$ : 100v/div; time: 10ms/div)





# # Conclusions

## Four test conditions of grid distortion

Case	Harmonic order	%	Measured Item	Without FCCC (GC Mode)	With FCCC (GC Mode)	Without FCCC (Rect. Mode)	With FCCC (Rect. Mode)
Case I	5	9.8	PF	0.95	0.98	0.95	0.97
	7	15.8	V <sub>THD</sub> (%)	18.5	18.4	18.4	18.4
	8	2.16	I <sub>THD</sub> (%)	18.8	3.2	18.7	2.8
Case II	3	4.9	PF	0.98	0.99	0.98	0.99
	5	1.6					
	7	2.7	V <sub>THD</sub> (%)	6.4	6.4	6.4	6.4
	11	1.4					
	15	2					
	17	1.1	I <sub>THD</sub> (%)	9.4	3.8	9.3	3.3
Case III	3	17.8	PF	0.95	0.98	0.96	0.97
			V <sub>THD</sub> (%)	17.8	17.7	17.7	17.8
			I <sub>THD</sub> (%)	17.7	2.1	17.8	2.0
Case IV	7	4.6	PF	0.97	0.98	0.97	0.98
	9	1					
	21	0.9	V <sub>THD</sub> (%)	4.9	5.1	4.9	5.0
	39	0.7					



- 1) With D- $\Sigma$  digital control, the controller can tune loop gains corresponding to inductance variation cycle by cycle.
- 2) D- $\Sigma$  digital control can cover wide inductance, dc-bus voltage and line voltage variations, and achieve precise inverter current tracking.
- 3) With the filter capacitor-current compensation, the grid current can be shaped sinusoidally under distorted grid voltage.
- 4) D- $\Sigma$  digital control can improve stability margin, close to  $90^\circ$ , when injecting current to the grid under high line impedance.





*Thanks*

