



Decoding and Synthesizing Transformerless PWM Converters

Tsai-Fu Wu

Professor, National Tsing Hua University, Taiwan
Elegant Power Electronics Applied Research Laboratory
(EPEARL)

Aug. 27, 2015



Outline

I. Introduction

- **Six PWM Converters (DC-DC Conversion)**
- **Six-PWM-Converter Derived Converters (High Step-up or Step-down)**
- **Single-Stage converters (PFC + Electronic Ballast)**
- **Buck Derived Isolated PWM Converters (DC-DC Conversion with DC Transformer)**
- **Z-Source Converters (Step-up Conversion & Inversion)**
- **Soft-Switching PWM Converters (DC-DC Conversion)**
- **Resonant Converters (DC-AC & DC-DC Conversion)**
- **Non-PWM Converters (DC-DC Conversion)**
- **Compound Concept**



II. Input-Output Transfer Curves (Codes)

- **Step-down**
- **Step-up**
- **Step-up and -down**
- **Positive and Negative Step-up and -down**

III. Origin of Converters

- **Source-Load Approach**
- **Proton-Meson Approach**
- **Resonance Approach**
 - **Lossy Power Transfer (Non-PWM)**
 - **Lossless Power Transfer (PWM)**
- **The Original Converter**



IV. Graft Scheme

- **Conventional Approaches Deriving Converters**
- **Grafted Switches and Grafted Diodes**
- **Illustration of Grafting Converters**

V. Layer Scheme

- **Buck Family**
- **Boost Family**
- **Universal Forms**





VI. Decoding and Synthesizing PWM Converters

- **Some Fundamentals**
- **Fundamental PWM Converters**
- **Layered PWM Converters**
- **Grafted PWM Converters**
- **Summary and Discussion**

VII. Other PWM Converters

- **PWM Converters with DC Transformers**
- **Resonant Converters**
- **Single-Stage Interleaved**
- **Discussion**
- **Analogy of PWM Converters to DNA**



VIII. Conclusions

- Resonance is the main principle of high-efficiency power transfer.
- **Converters were evolved and deduced from the original converter, buck converter.**
- Hopefully, no more trial and error in synthesizing PMW Converters.





I. Introduction

➤ Six PWM Converters

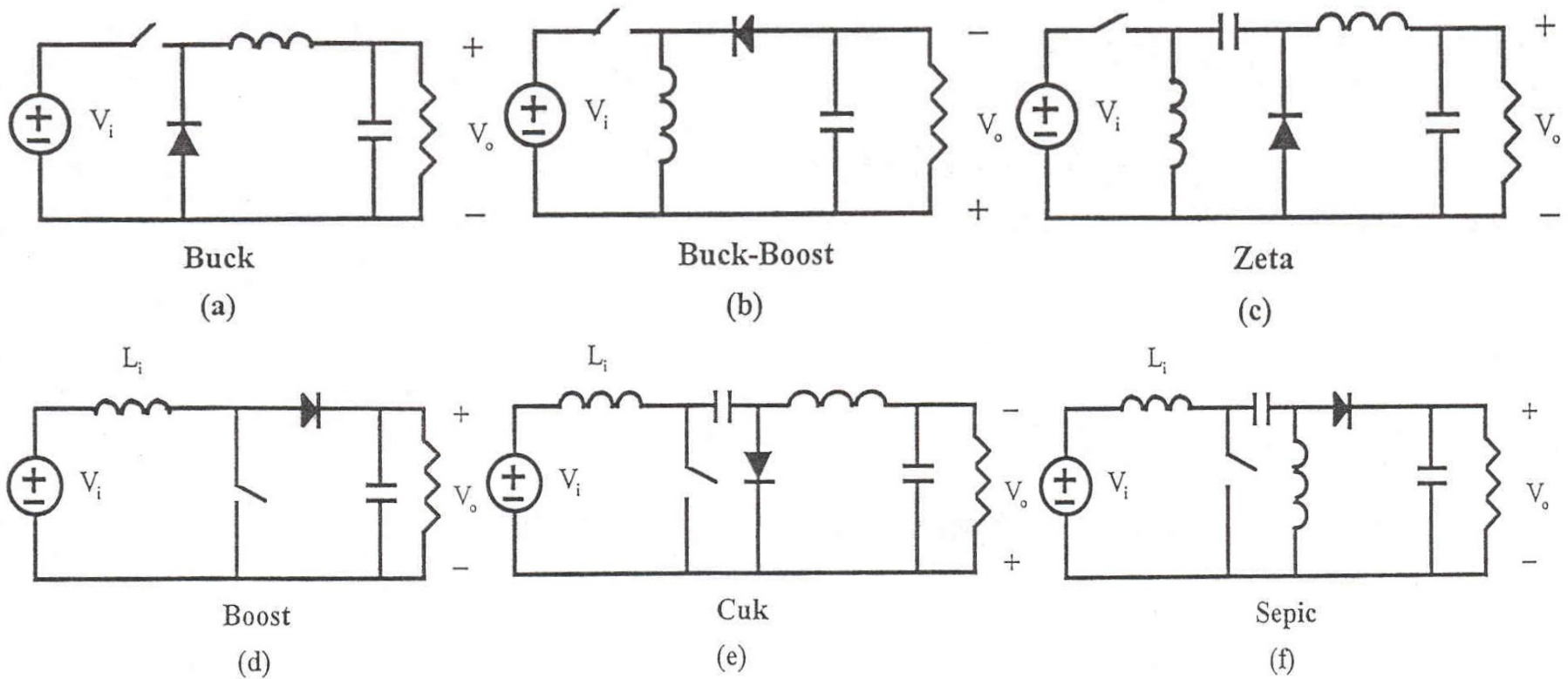


Fig. 1.



➤ Six-PWM-Converter Derived Converters

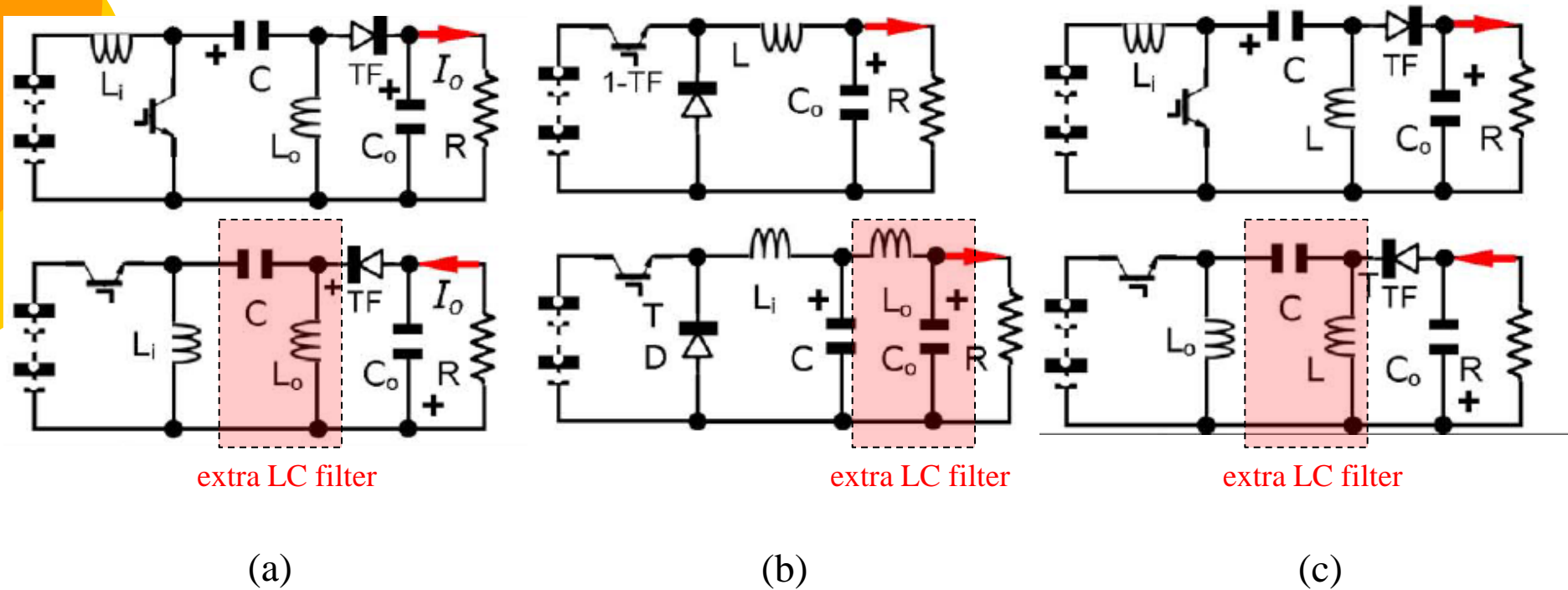


Fig. 2.



➤ Switched Cap./Ind. Hybrid Converters

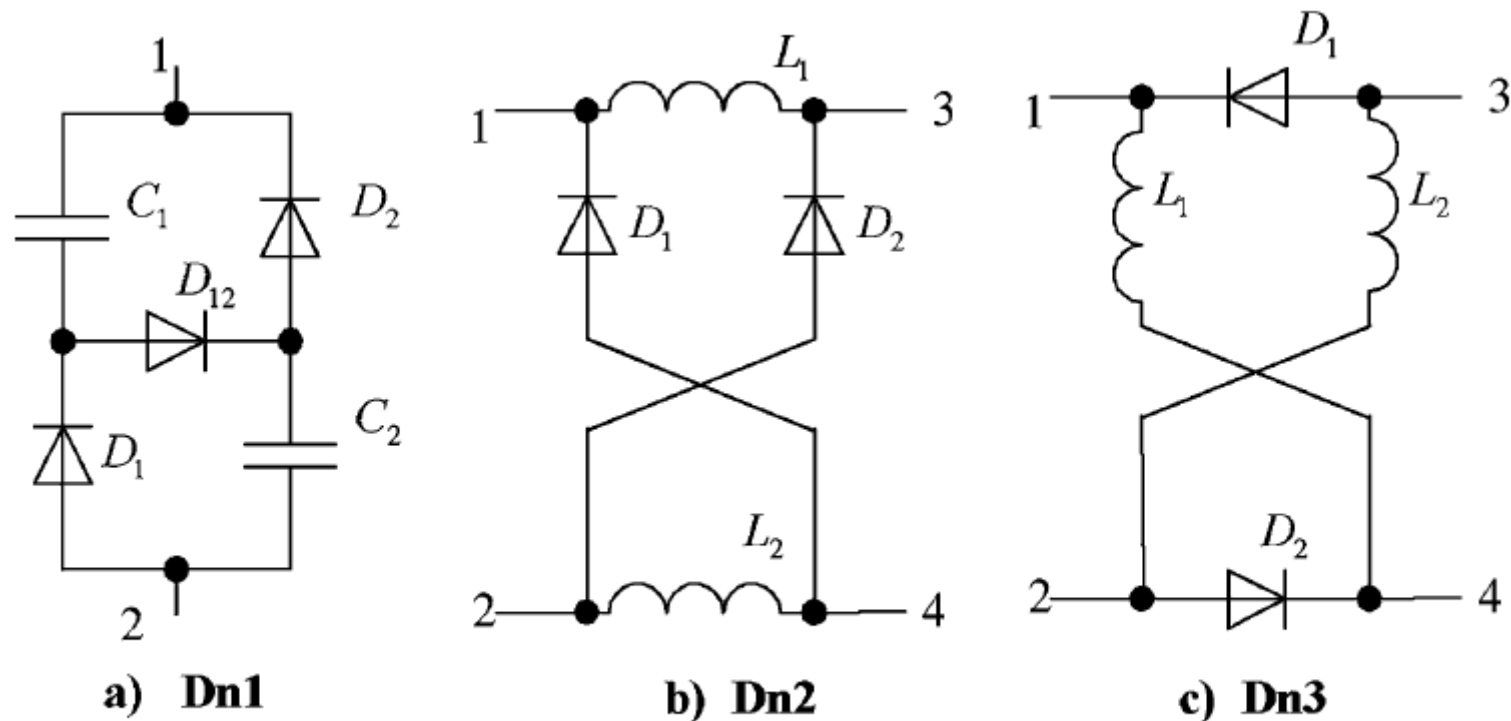


Fig. 3. Step-down basic switching structures.

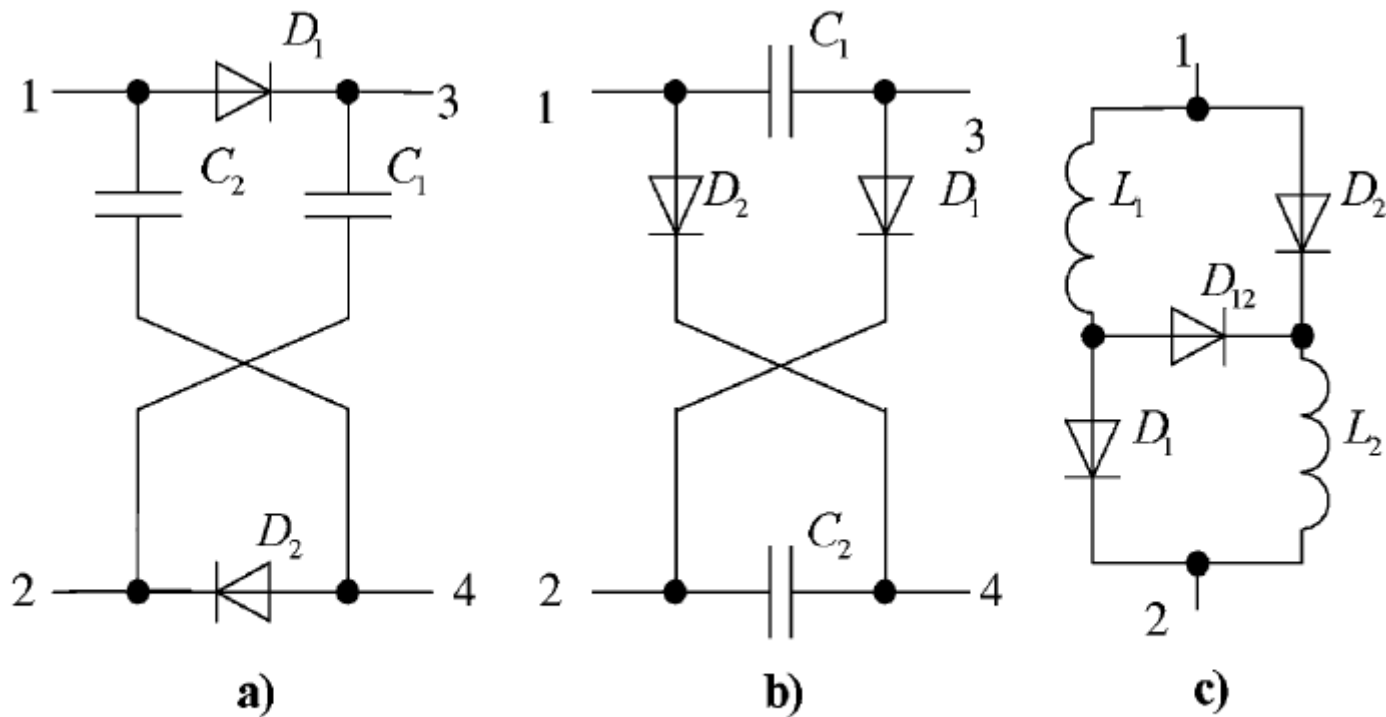


Fig. 4. Step-up basic switching structures. (a) Up1. (b) Up2. (c) Up3.



TABLE I
POSSIBLE REALIZATIONS OF HYBRID CONVERTERS
WITH C-/L-SWITCHING STRUCTURES

C/L-switching struc Converter	Dn1	Dn2	Dn3	Up1	Up2	Up3
Buck	☀	☀				
Boost				☀		☀
Buck- Boost	☀			☀		☀
Cuk	☀	☀			☀	☀
Sepic	☀		☀			☀
Zeta		☀			☀	☀

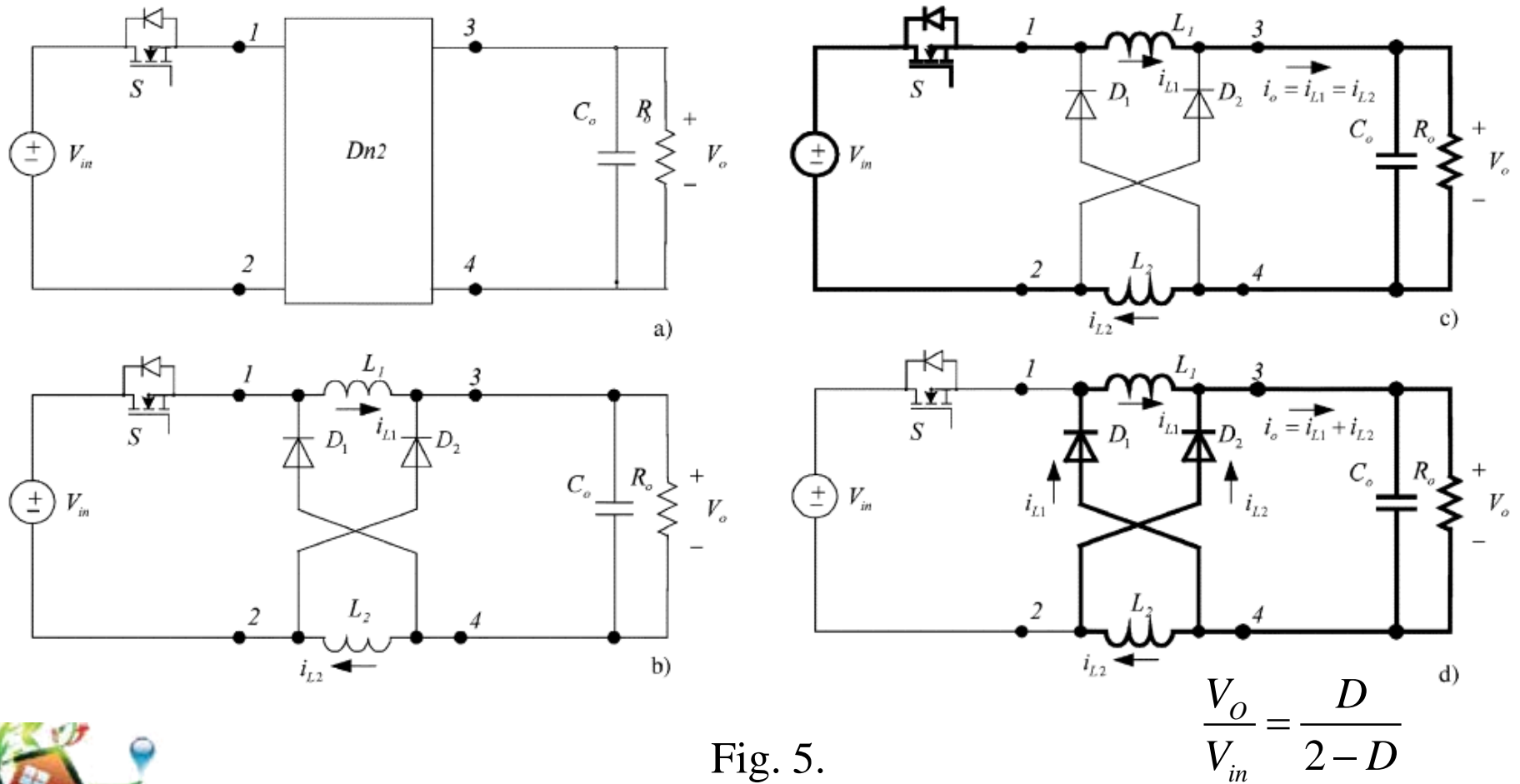


Fig. 5.

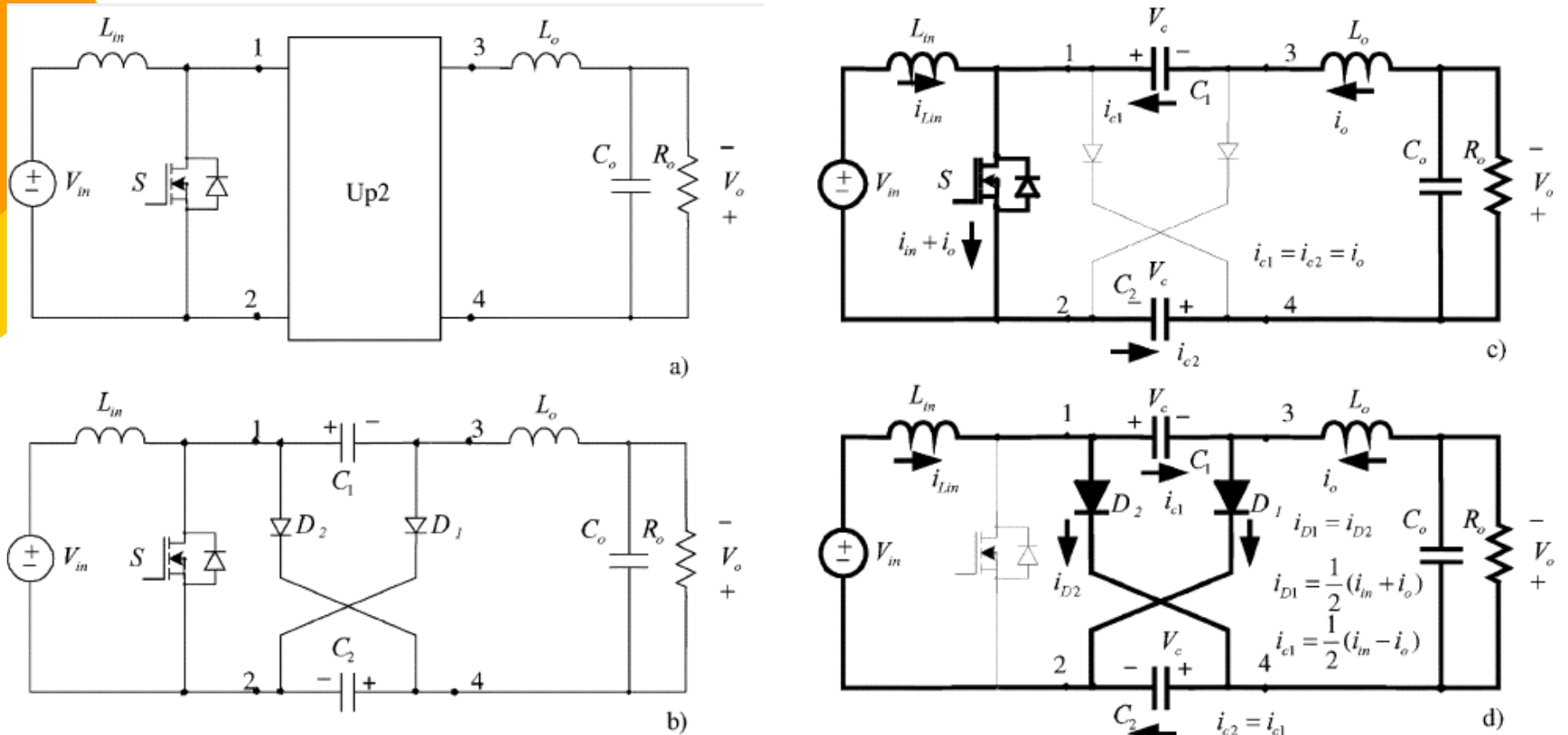


Fig. 6.

$$\frac{V_o}{V_{in}} = \frac{1+D}{1-D}$$

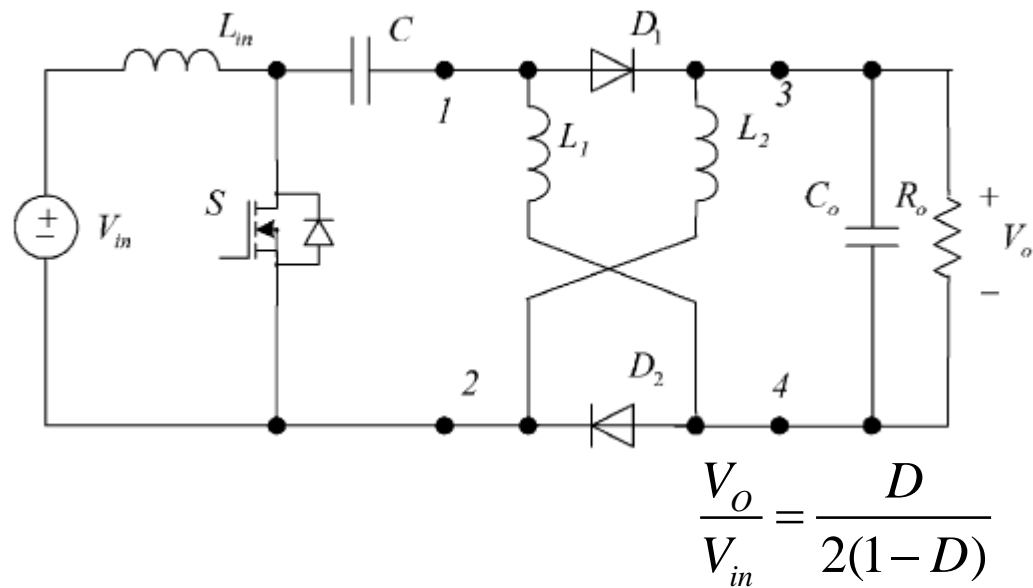


Fig. 7.



➤ Single-Stage Converters

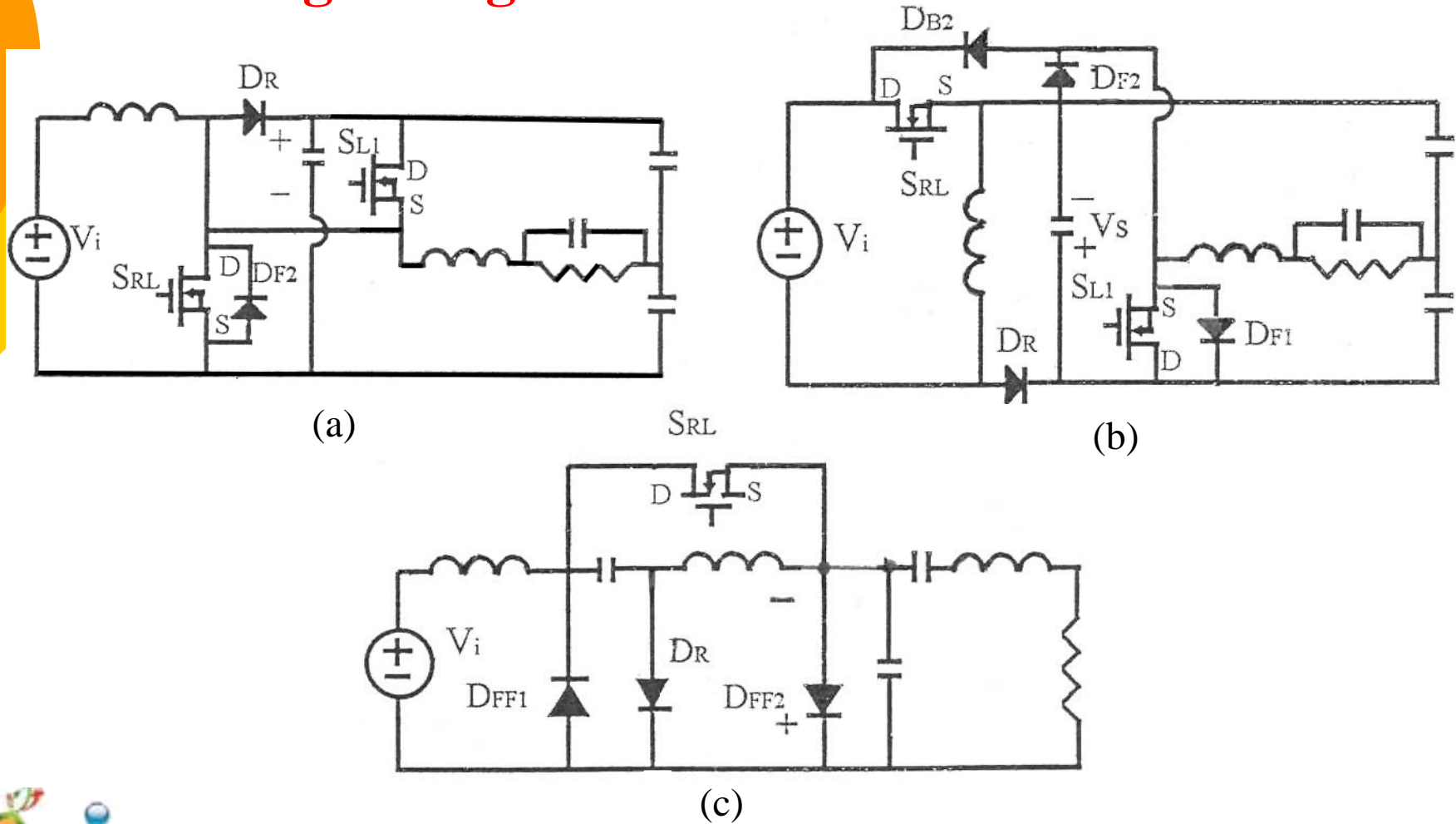


Fig. 8.



➤ Buck Derived PWM Converters



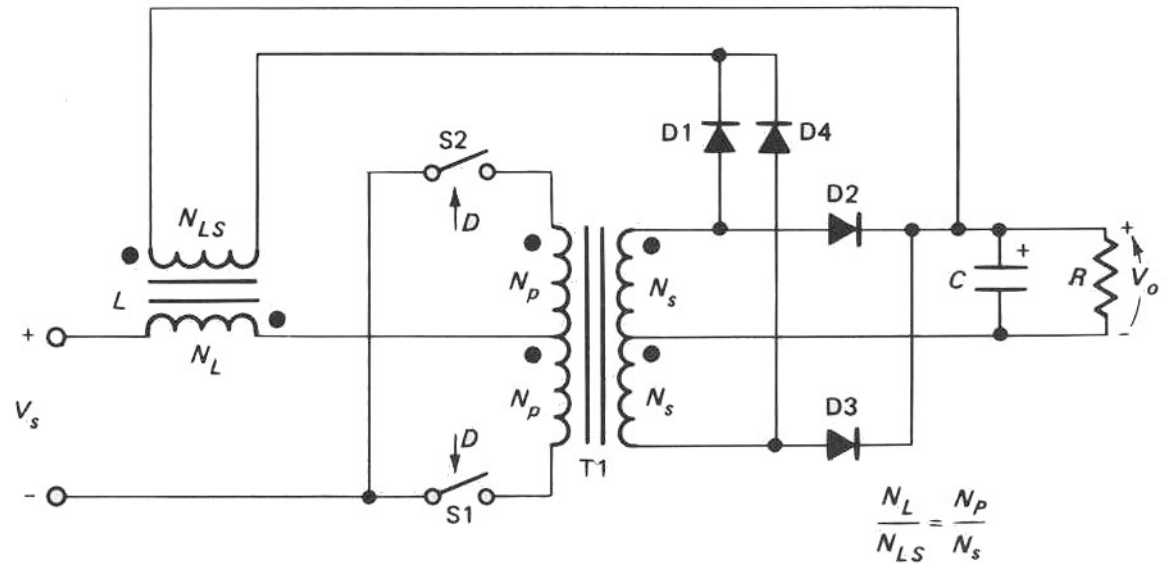



Fig. 9.

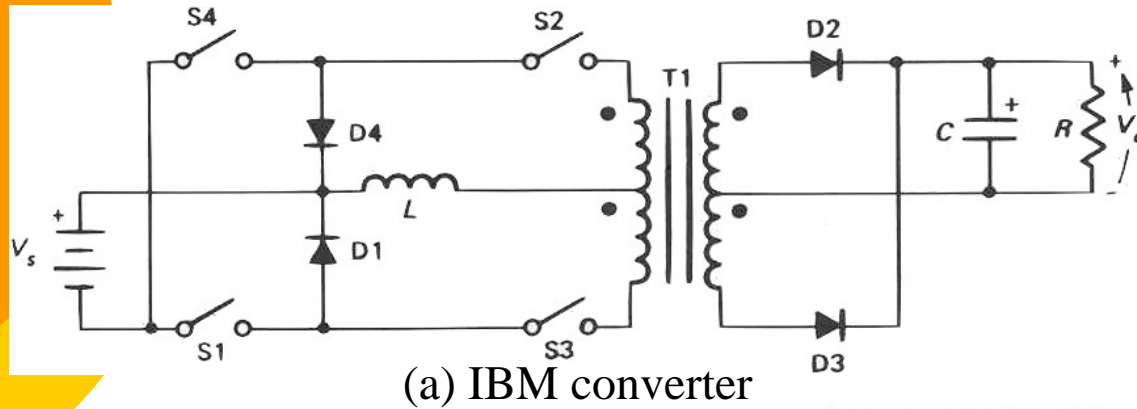


➤ Z-source Converters

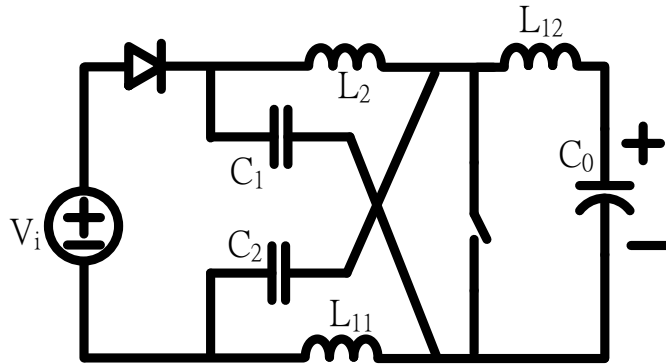

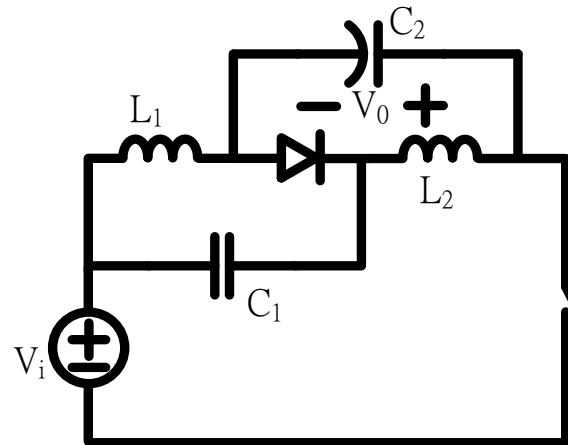
(a) Voltage-fed Z-source $\frac{V_0}{V_i} = \frac{1-D}{1-2D}$



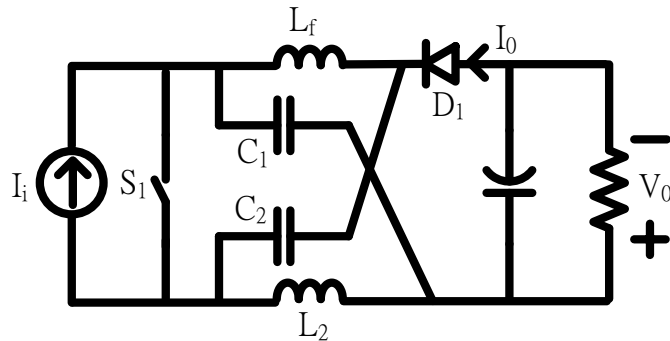(b) Quasi Z-source $\frac{V_0}{V_i} = \frac{D}{1-2D}$



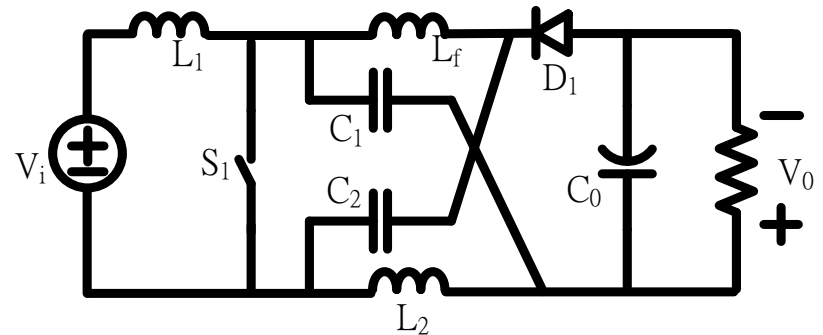(c) Current-fed Z-source $\frac{I_0}{I_i} = \frac{1-D}{2D-1}$




$$\frac{V_0}{V_i} = \frac{2D-1}{1-D}$$


Fig. 10.



➤ Soft Switching PWM Converters

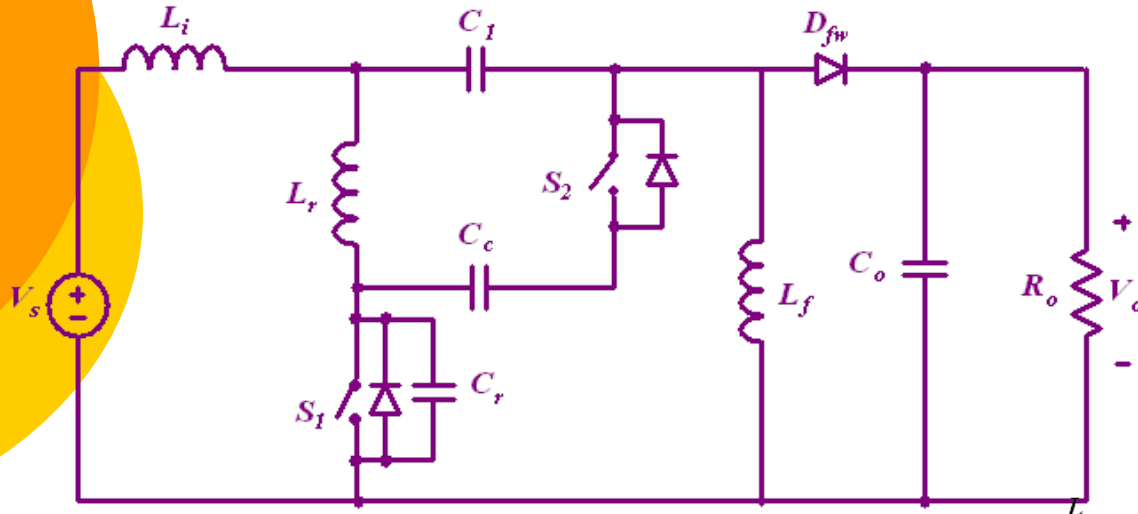

Active soft-switching SEPIC converter

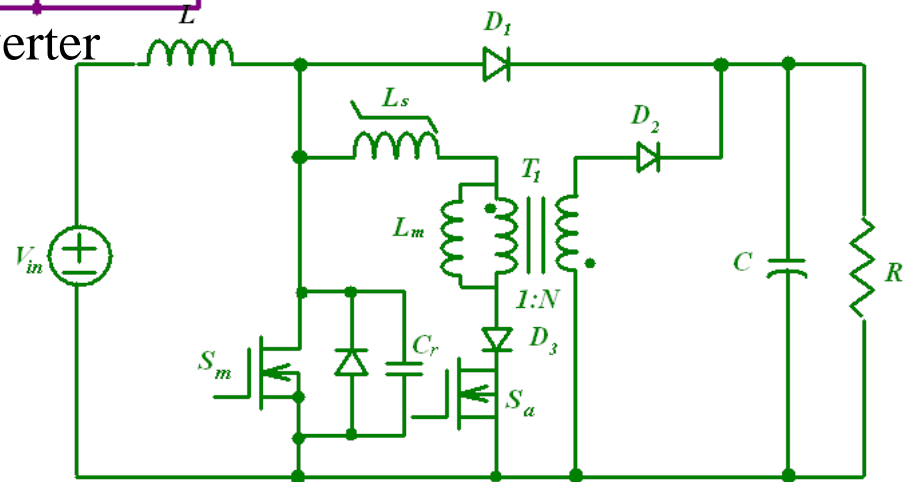


Boost + flyback


Fig. 11.



➤ Resonant Converters

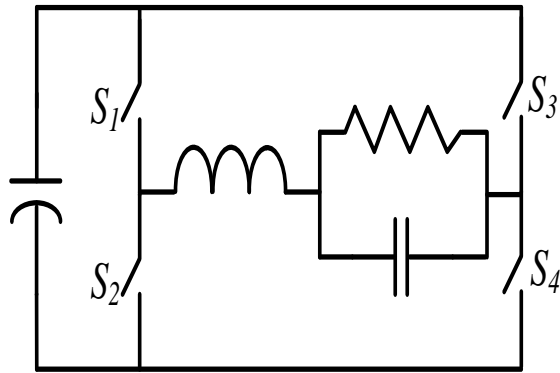

(a) Series-Parallel

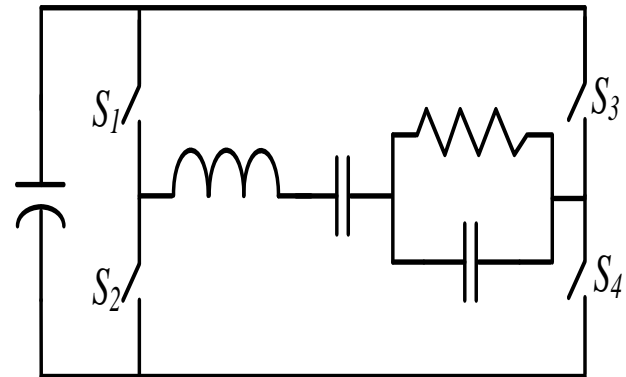


(b) LCC


Fig. 12.




➤ Non-PWM Converters

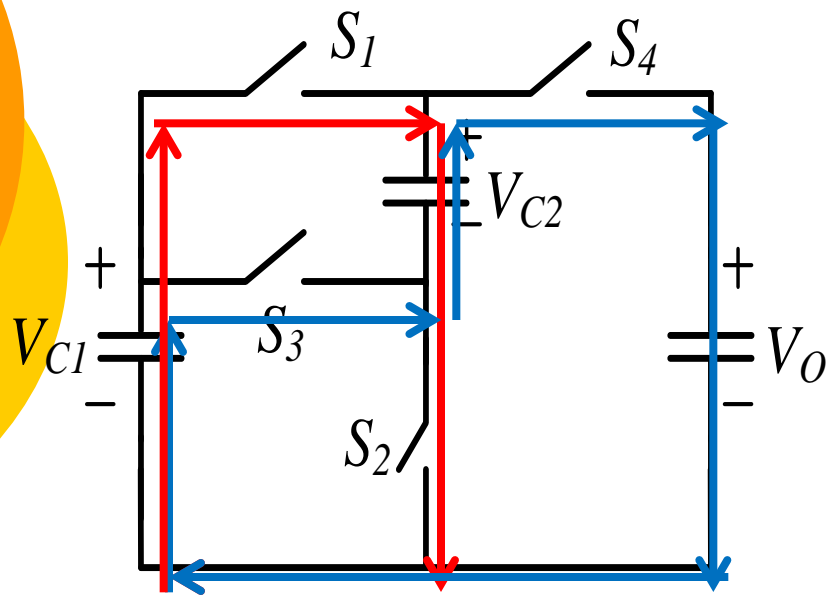

(a) Two Lift

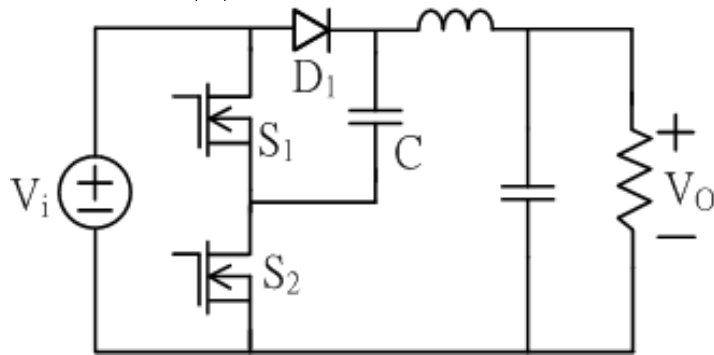

(b) KY Converter (Non-PWM Converter)

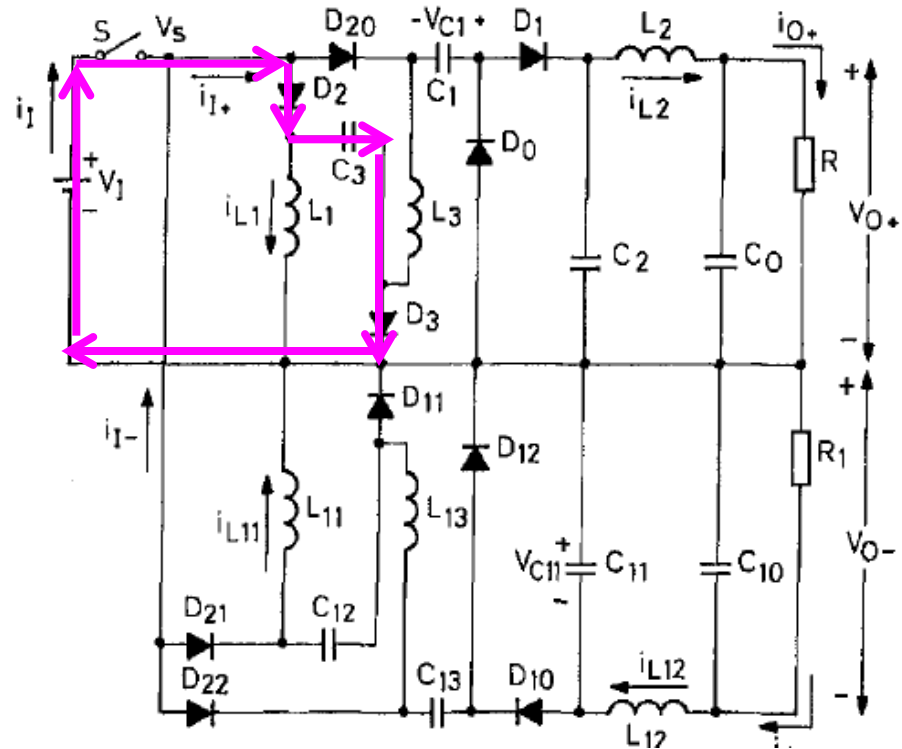

(c) Re-Lift Circuit

Fig. 13.




How to Synthesize PWM Converters?





➤ Compound Concept

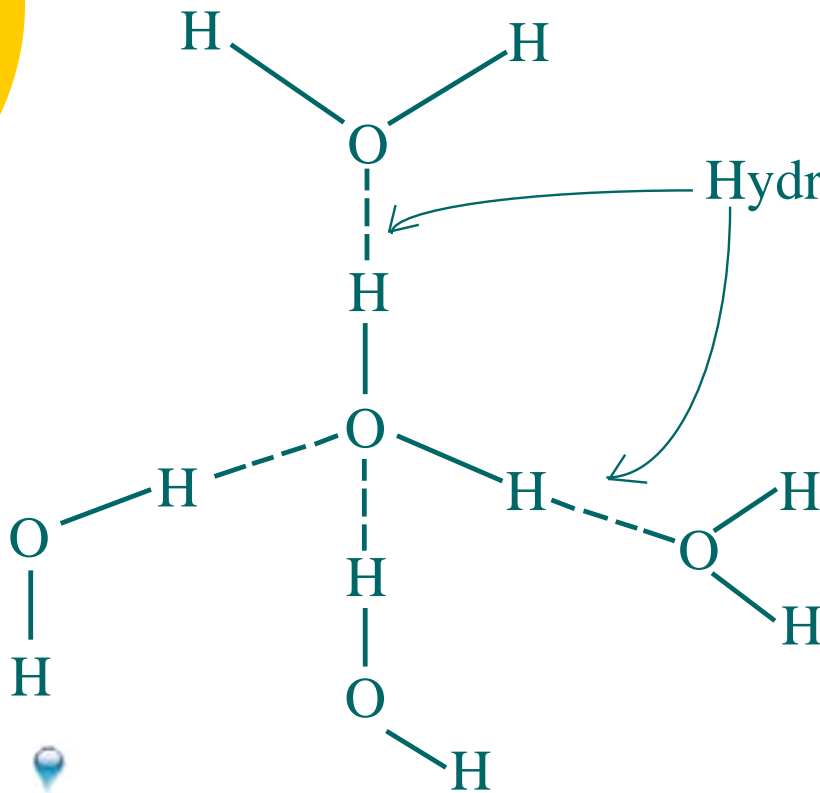

Converter → Element

What is the mechanism of binding converters to be a compound converter?



Decoding






A. Approach 1—Component-Interconnection Expression

- 1) Representing $D \times \frac{1}{1-D}$ in an expression which can inter-connect all components in a certain configuration.

$$\left[\text{Buck} \right] \textcircled{?} \left[\text{Boost} \right] = \left[\text{Buck-Boost} \right]$$

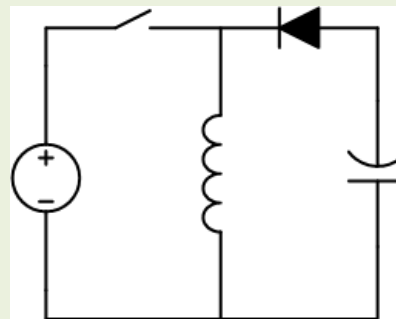- 2) Based on the above expression, sketch the final version of the desired converter.




Buck-Boost




2) Approach 2—Transfer-Gain Code Expression

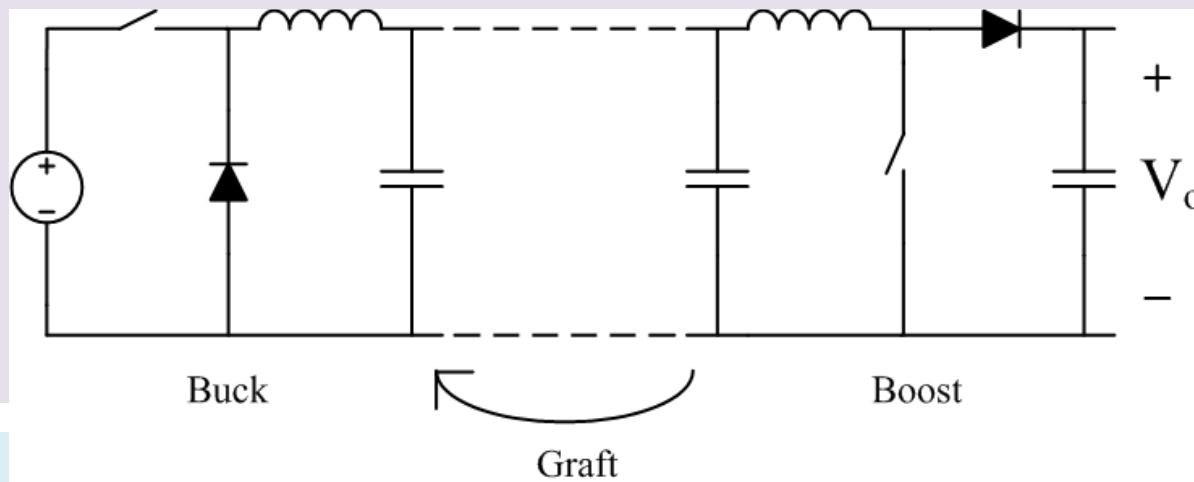- 1) Decode $D \times \frac{1}{1-D}$ into two transfer gain codes: D and $1/(1-D)$ and realize these two codes with two converters.



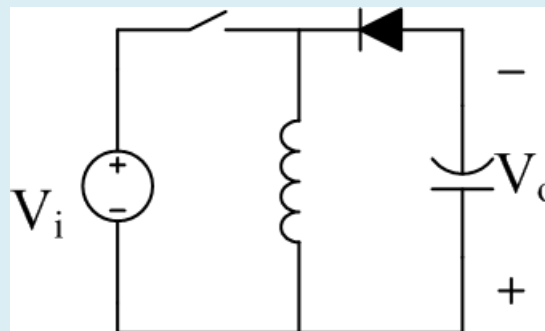- 2) How to synthesize the two converters to become a single one?





Two questions to ask:

1. How to select effective codes?
2. Is there existing an original converter?





II. Input-Output Transfer Curves (Codes)

➤ Step-Down

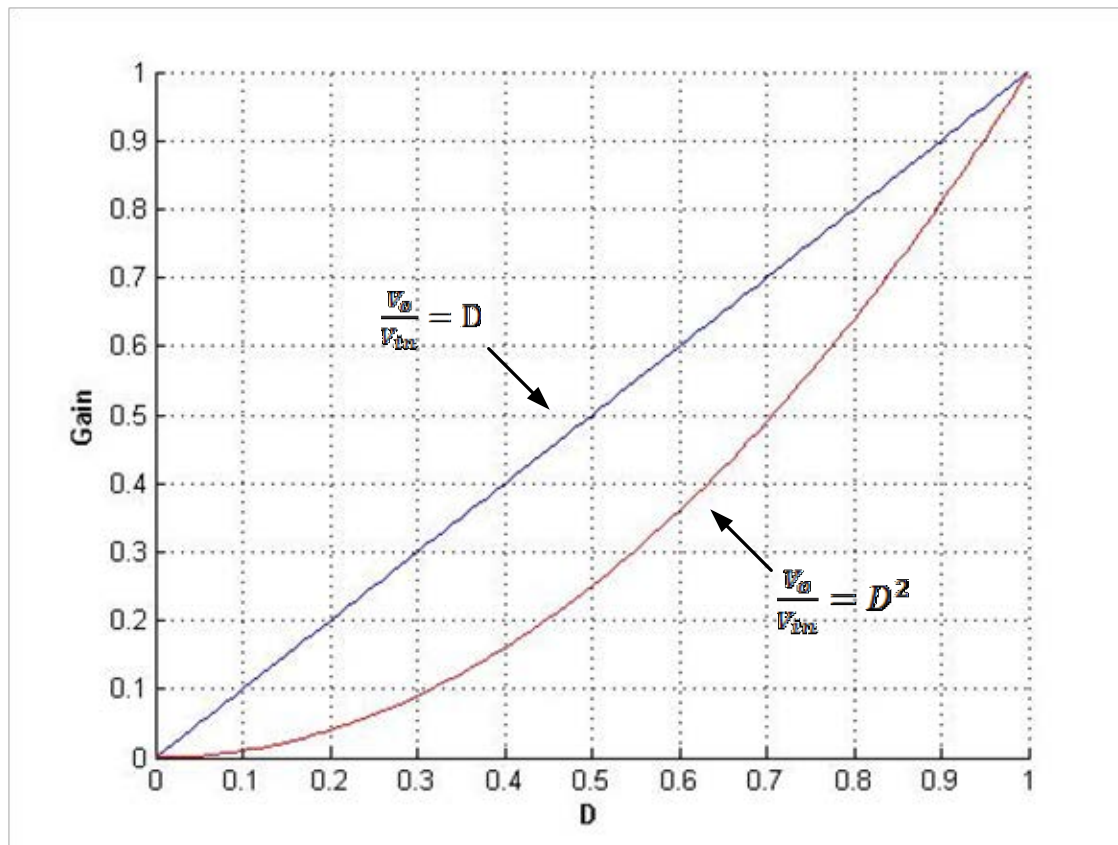


Fig. 1.



Step-Up

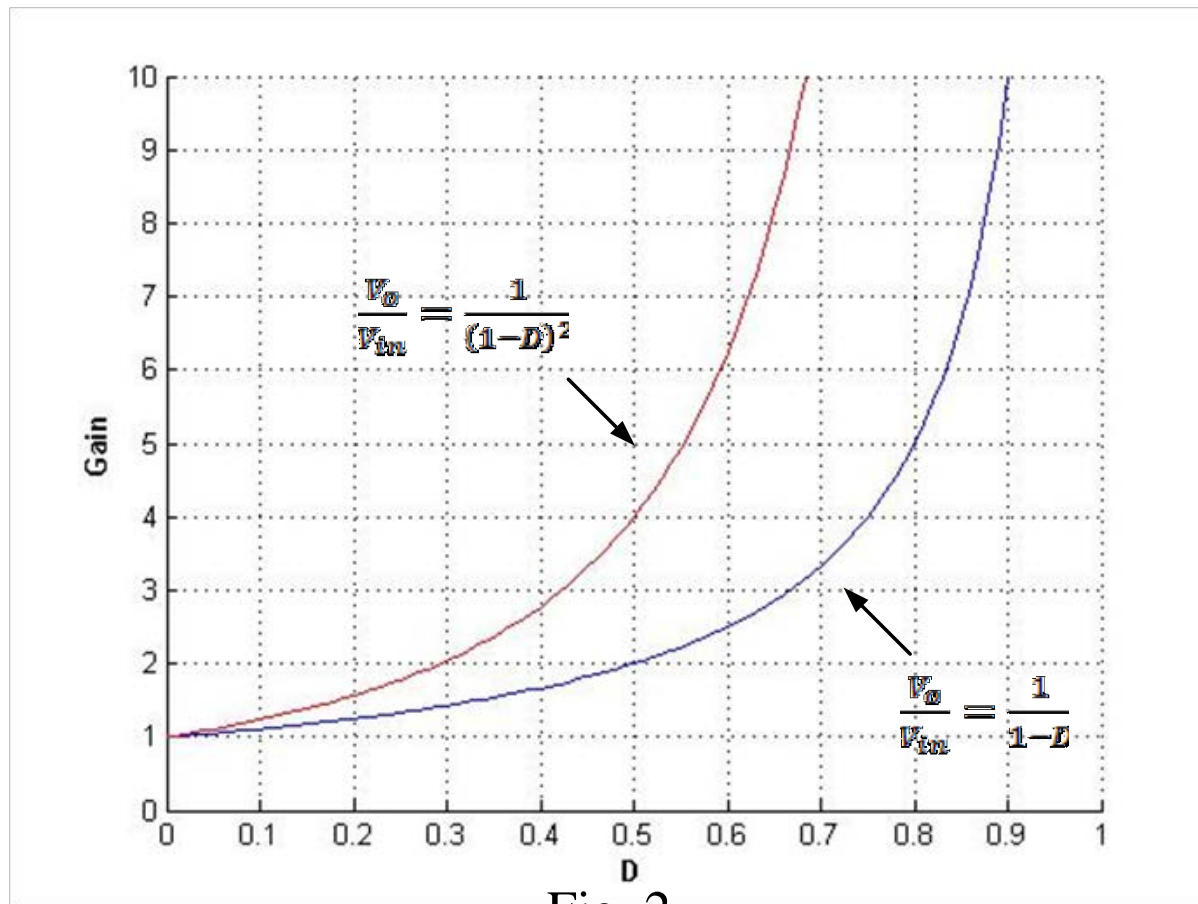


Fig. 2.



Step-Up and Step-Down


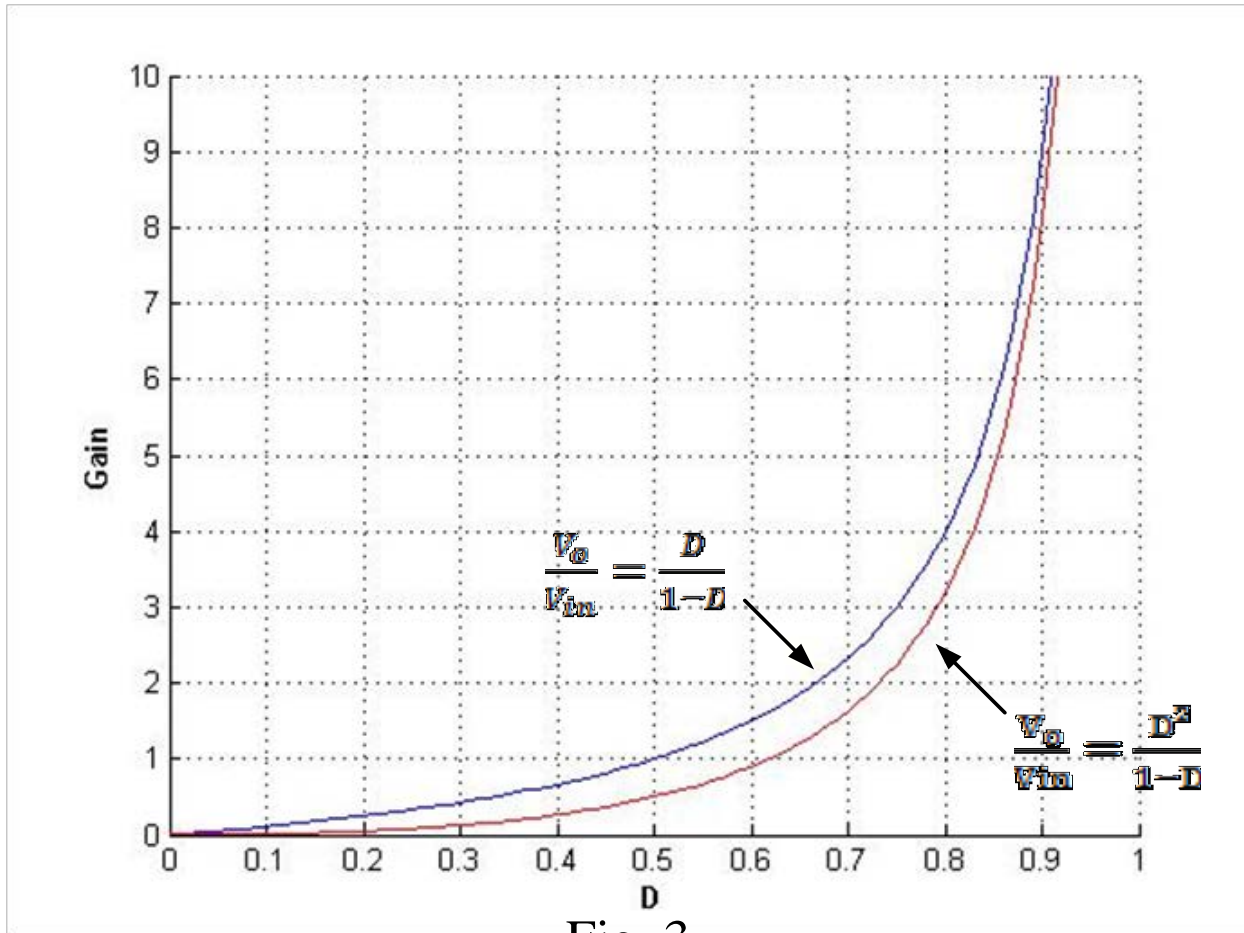


Fig. 3.

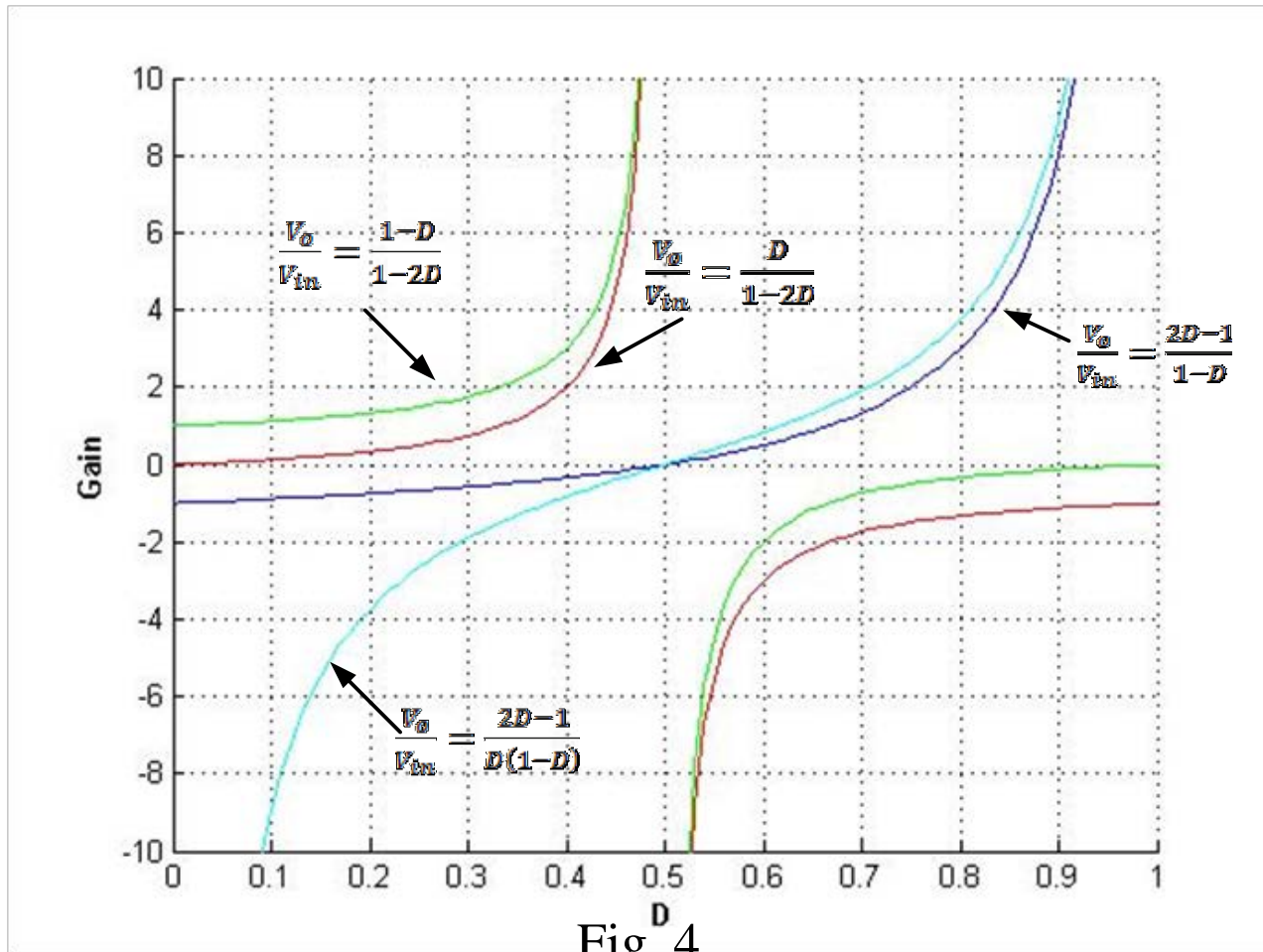

± Step-Up and Step-Down





III. Origin of Converters

➤ **Source-Load Approach**

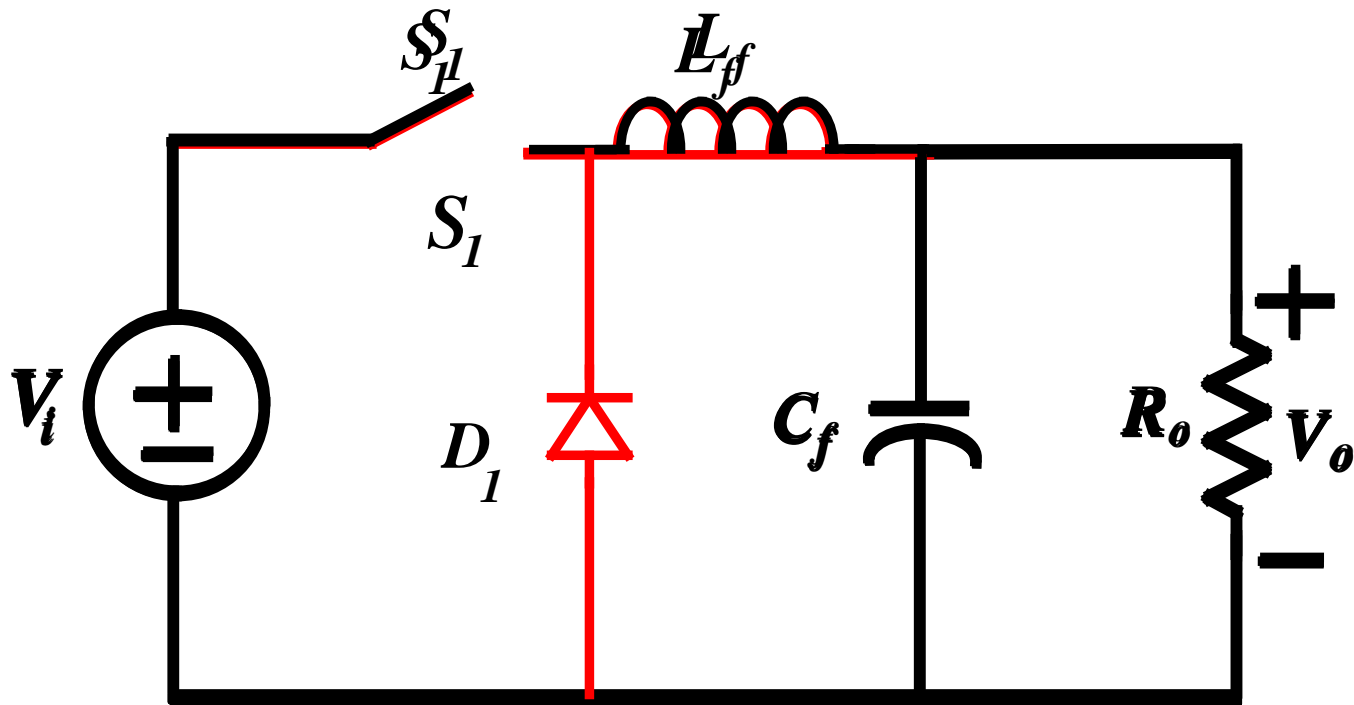


Fig. 1.




Proton-Meson Approach




Hideki Yukawa

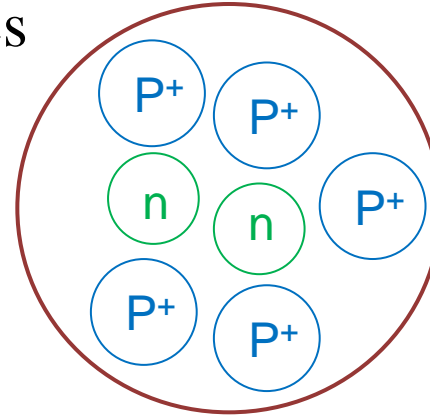- ◆ Awarded the 1949 Nobel Prize in Physics



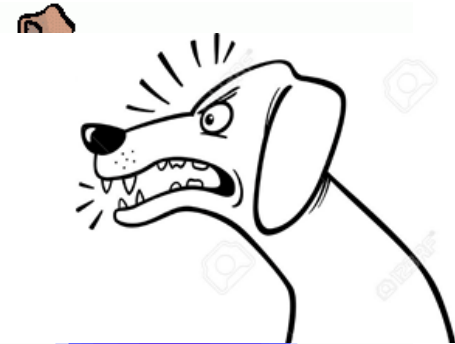Protons are dogs and Neutrons are rawhide knotted bones.



Meson is the carrier of the nuclear force that holds nuclei together.



- Buck Converter


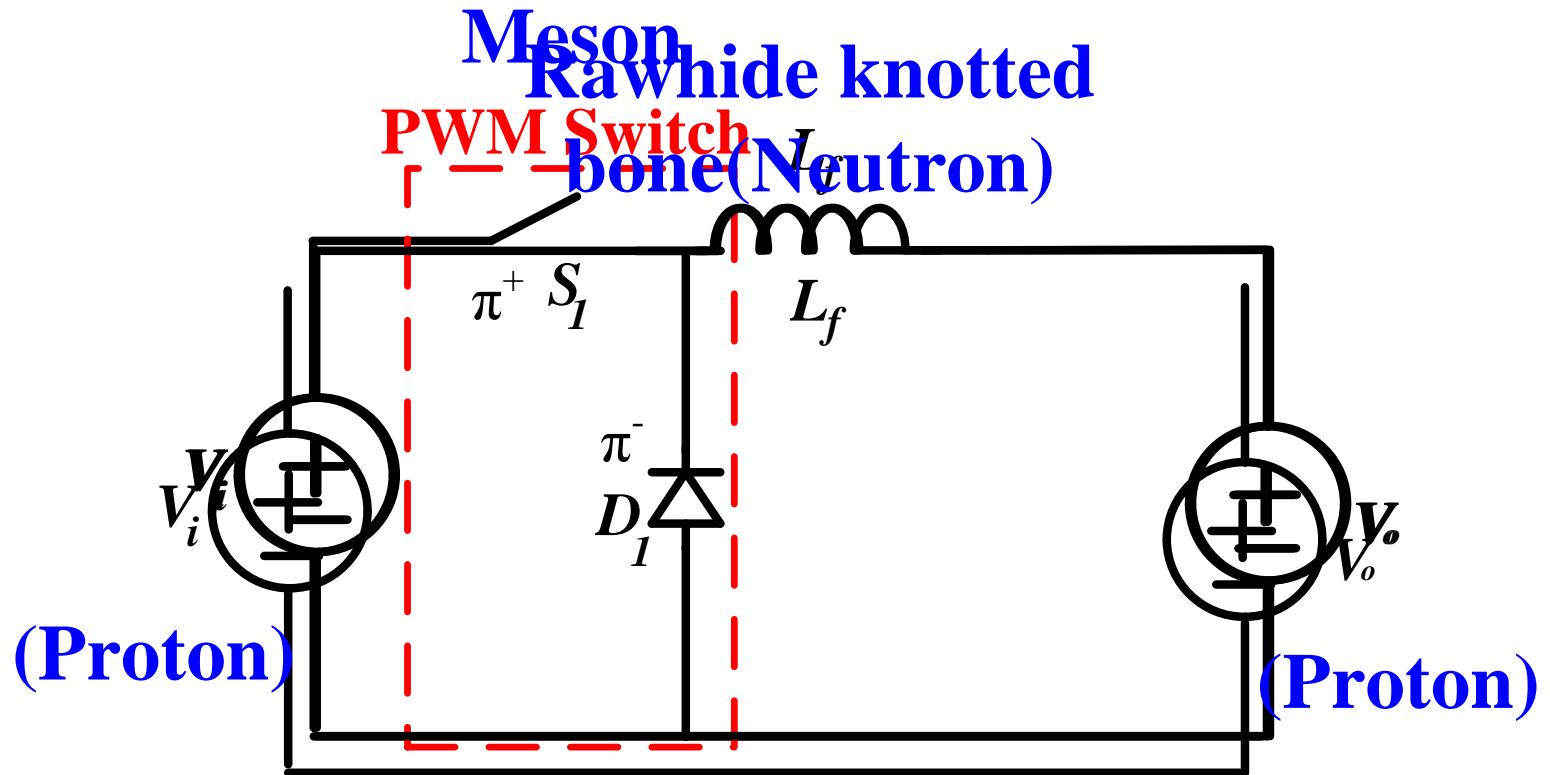



Fig. 2.

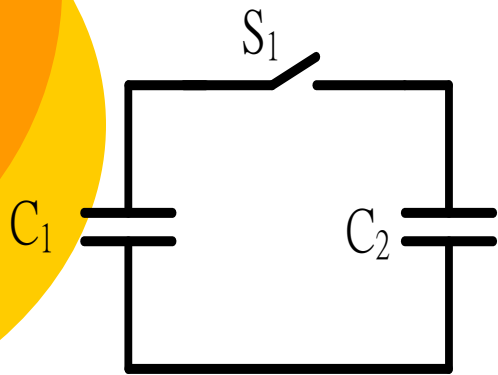


Resonance Approach



(a) lossy

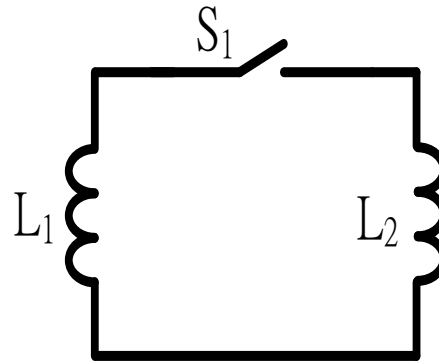

(b) lossy

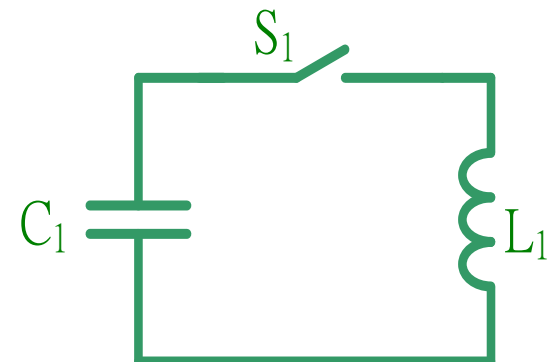


(c) lossless


Fig. 3. Three types of configurations of power transfer between capacitor and inductor.



The Original Converter

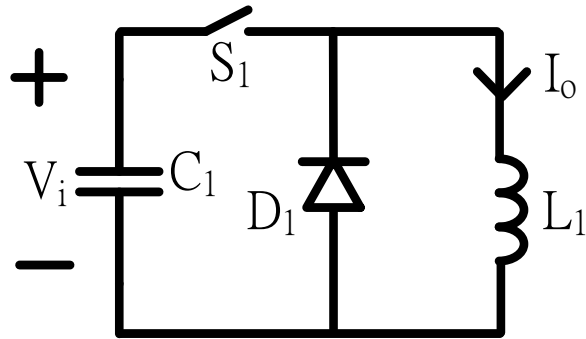

(a)

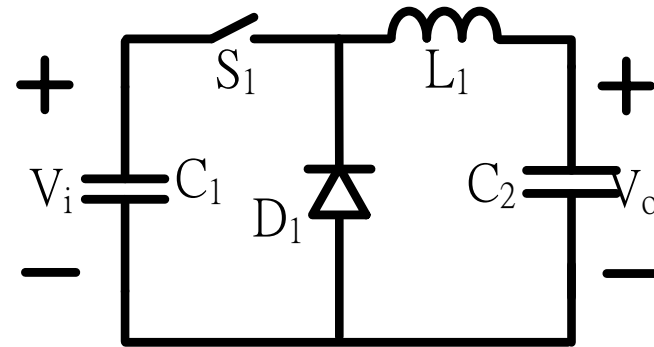

(b)

Fig. 4. A practical example applying the resonance concept.



IV. Graft Scheme

- **Conventional Approaches to Deriving Converters**
 - P cell and N cell [20]

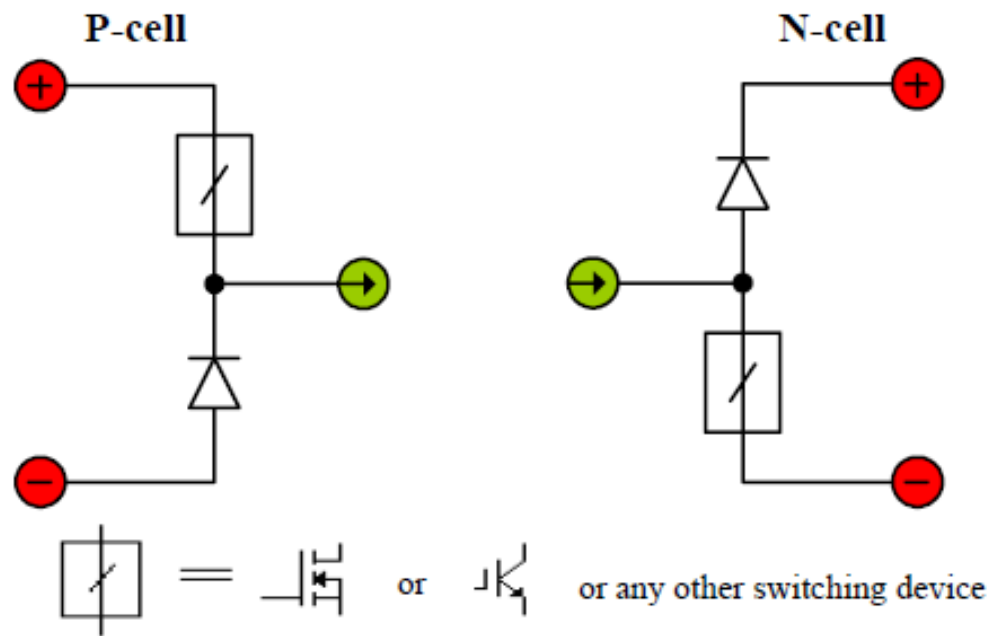

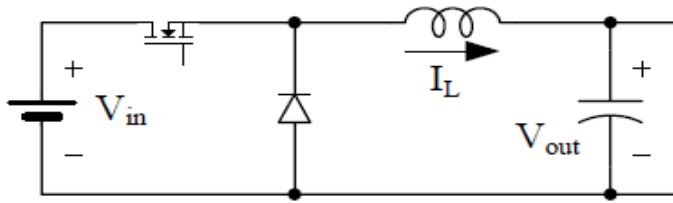
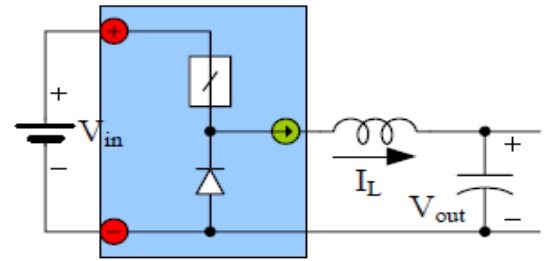



Fig. 1. Two basic switching cells: P-cell and N-cell. Terminal (+) connects to the positive lead of a voltage-source or capacitor, (-) connects to the negative lead of a voltage-source or capacitor, (→) connects to the positive lead of a current-source or inductor, and (←) connects to the negative lead of a current-source or inductor. The switching device  can be a MOSFET, IGBT, or other controlled semiconductor switching device.




(a) Buck converter




(b) P-cell buck converter

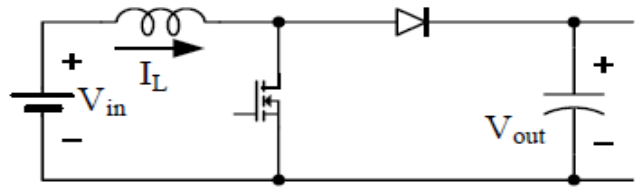


(c) Boost converter

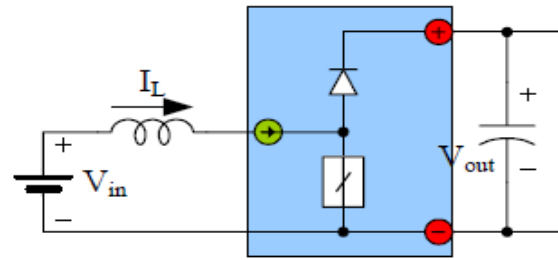


(d) N-cell boost converter

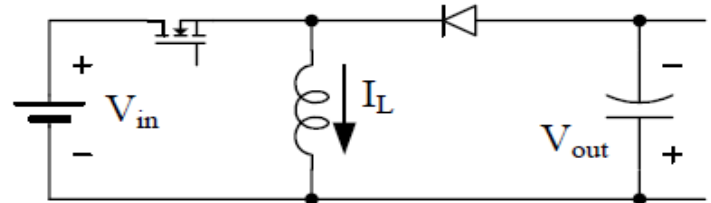


(e) Buck-boost converter

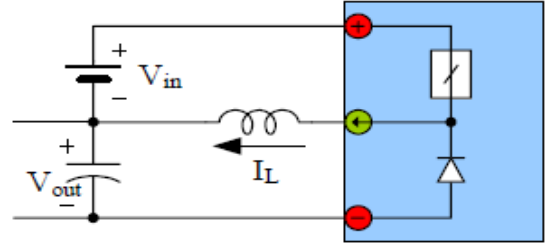

(f) P-cell buck-boost converter

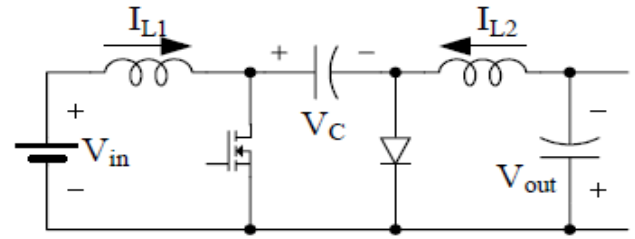

(g) Cuk converter

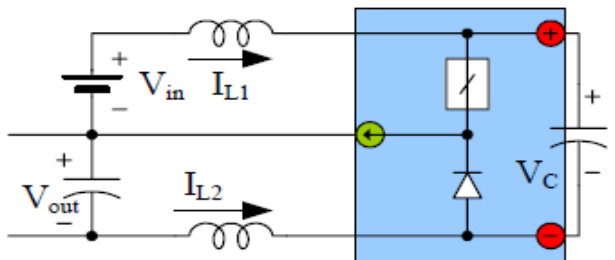

(h) P-cell Cuk converter

Fig. 2. The dc-dc converters and their construction by the basic cells.



- Canonical Switching Cells [24], [29]

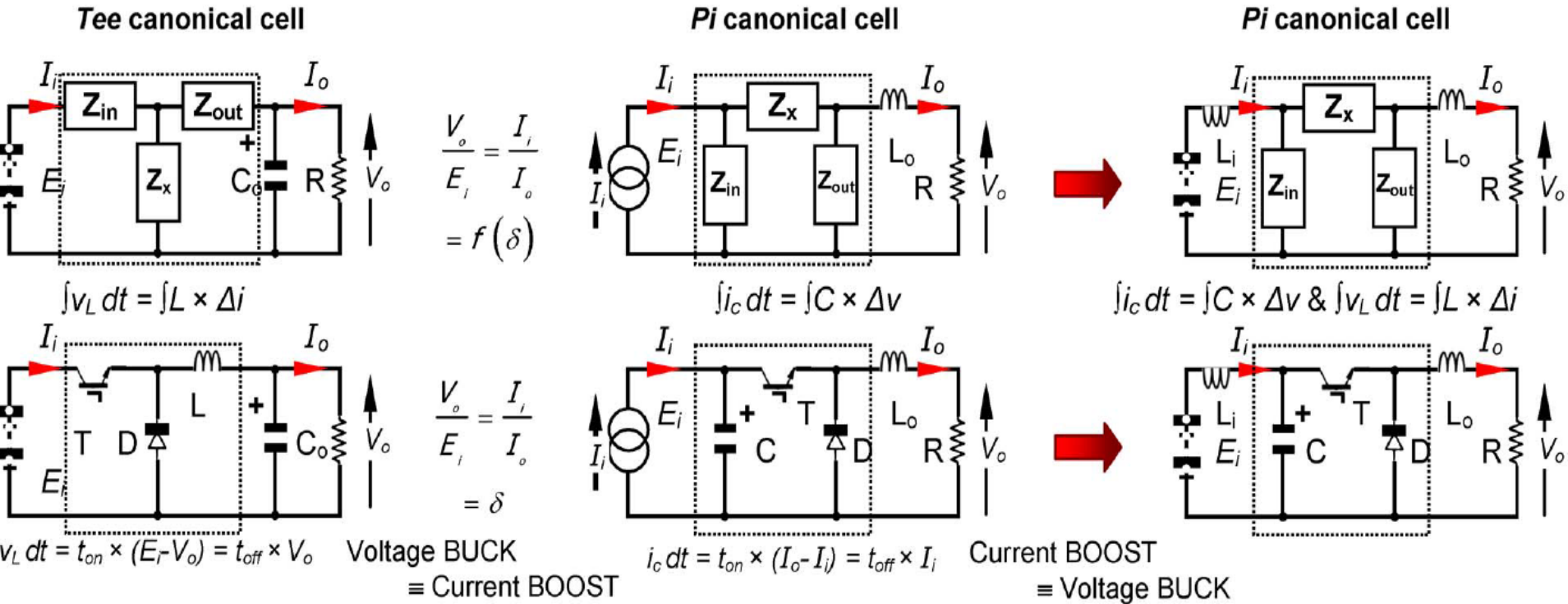


Fig. 3.

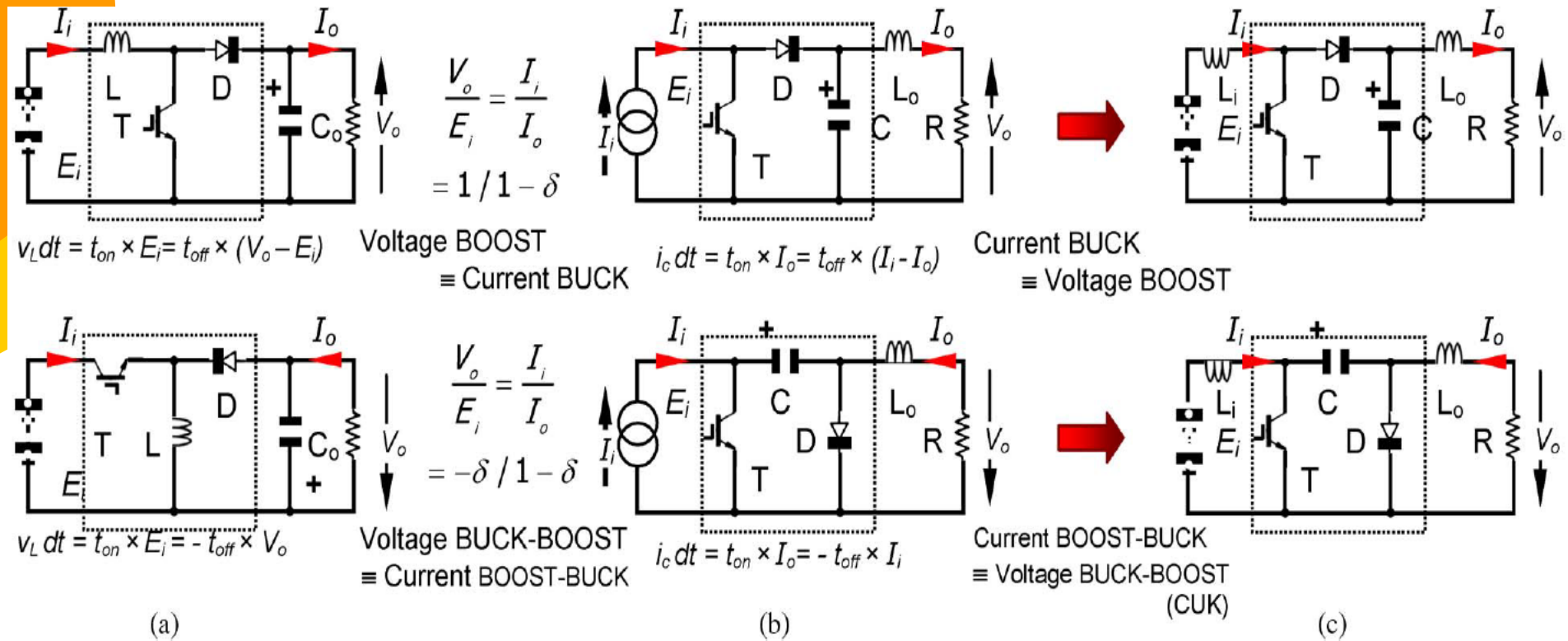


Fig. 4.



- Switched-Cap./Ind. Cells [48]

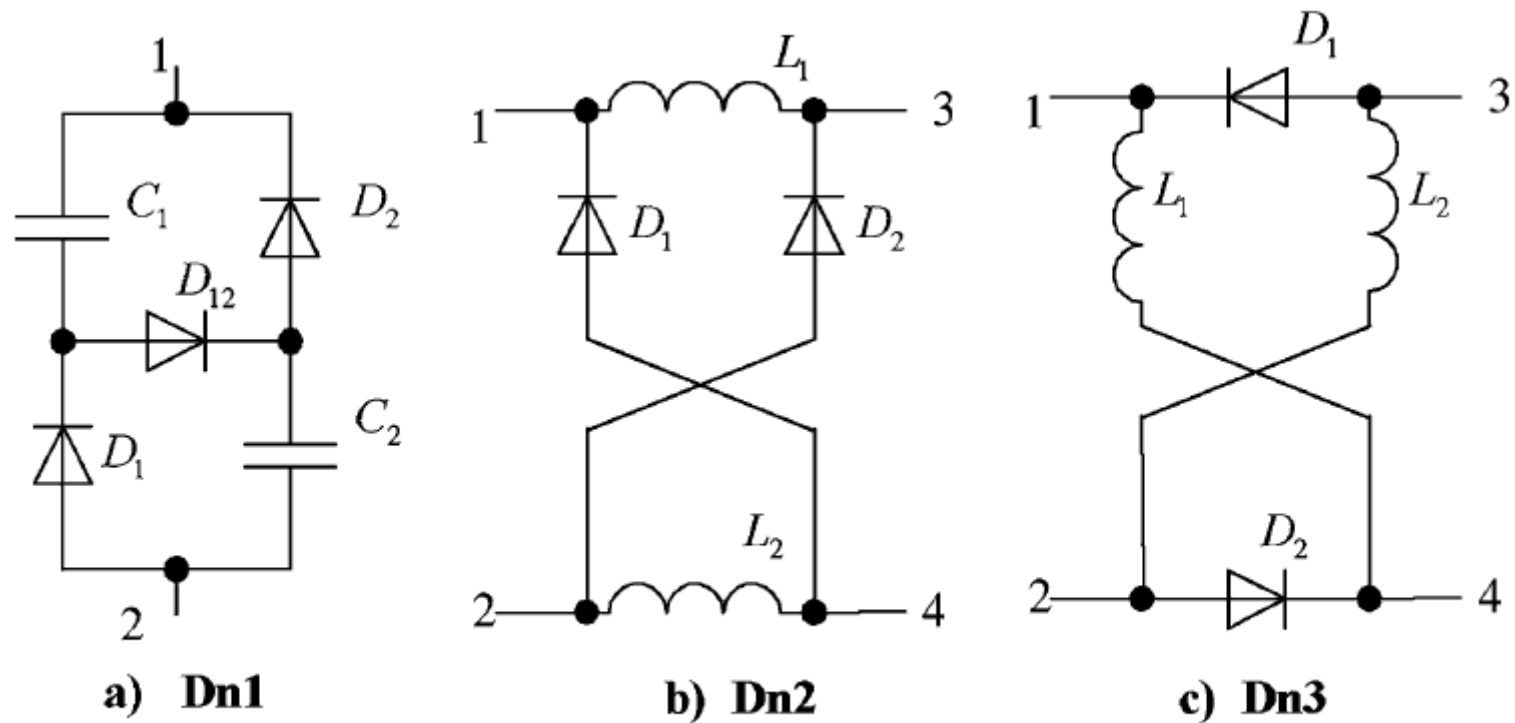


Fig. 5. Step-down basic switching structures.

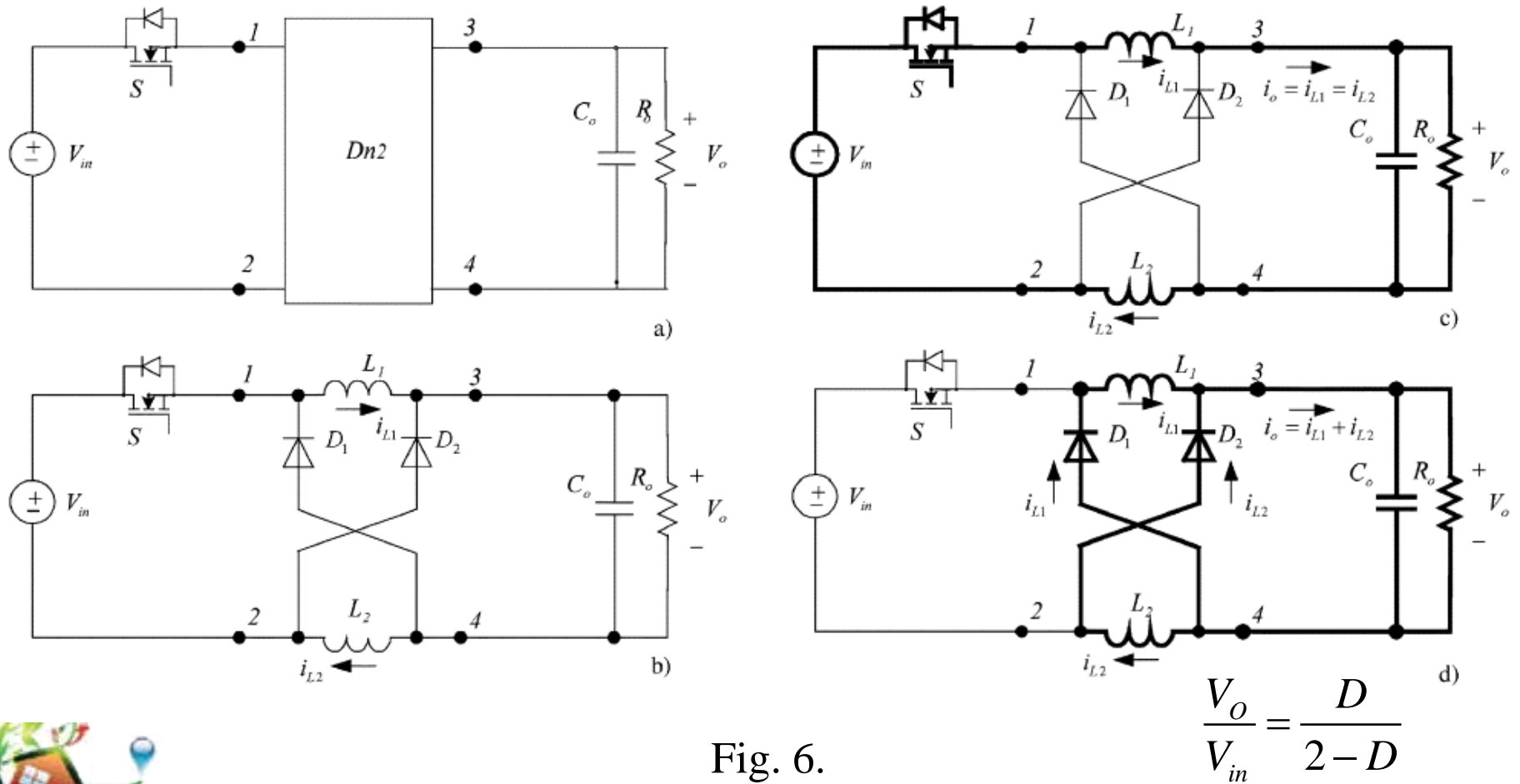


Fig. 6.



• Synchronous Switches [3]

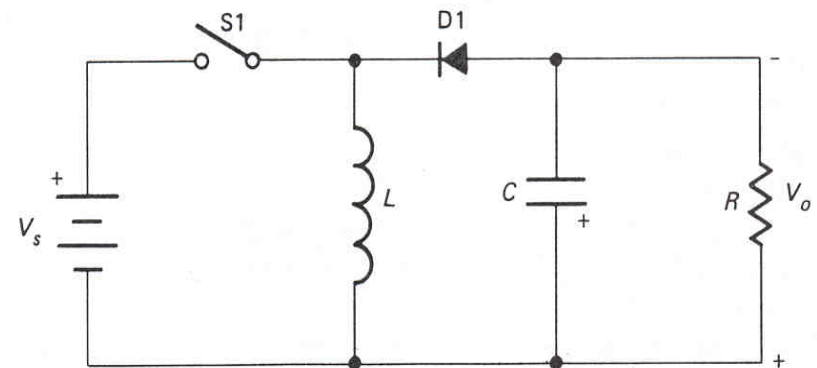
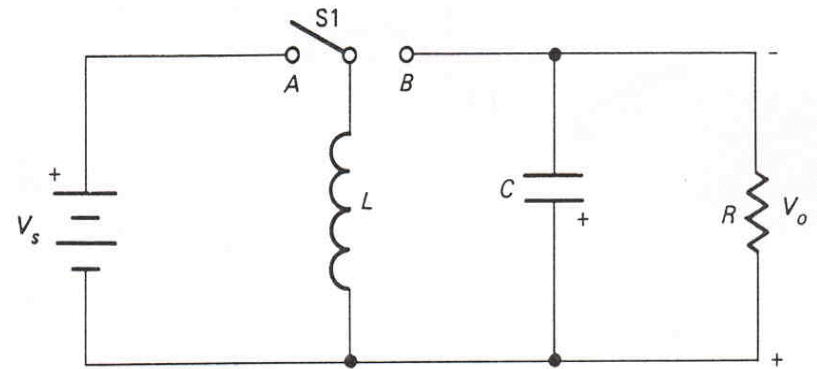
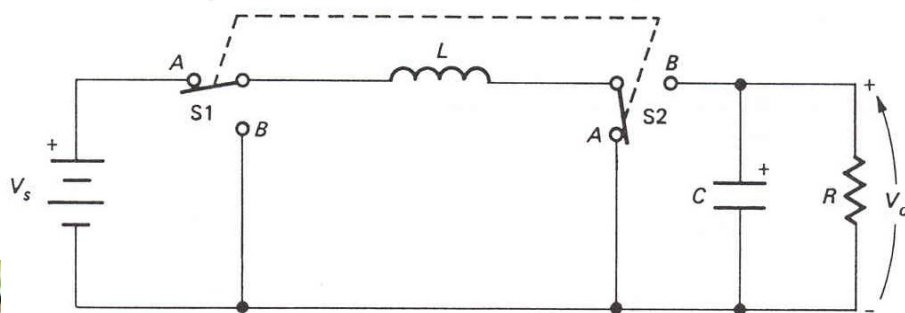
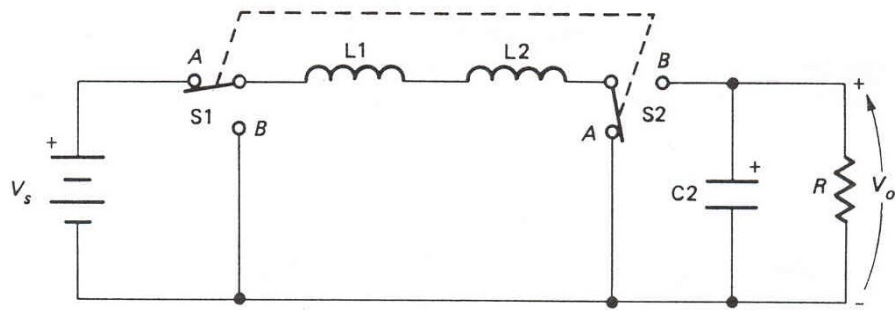
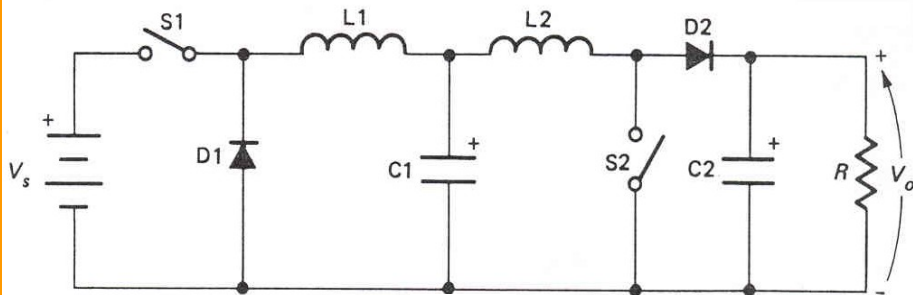


Fig. 7. Evolution of the buck-boost converter

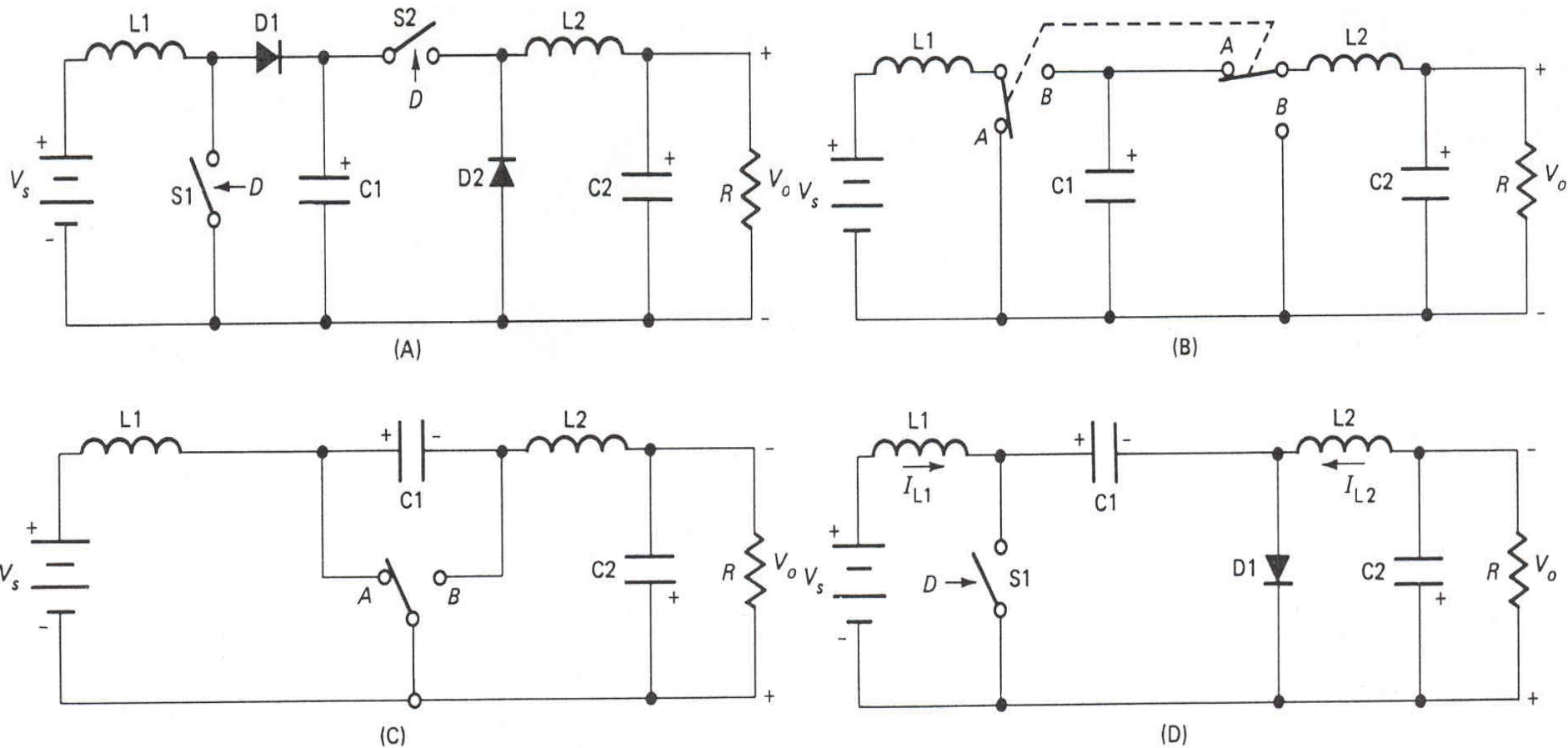


Fig. 8. Evolution of the Ćuk converter.



with Grafted Switches

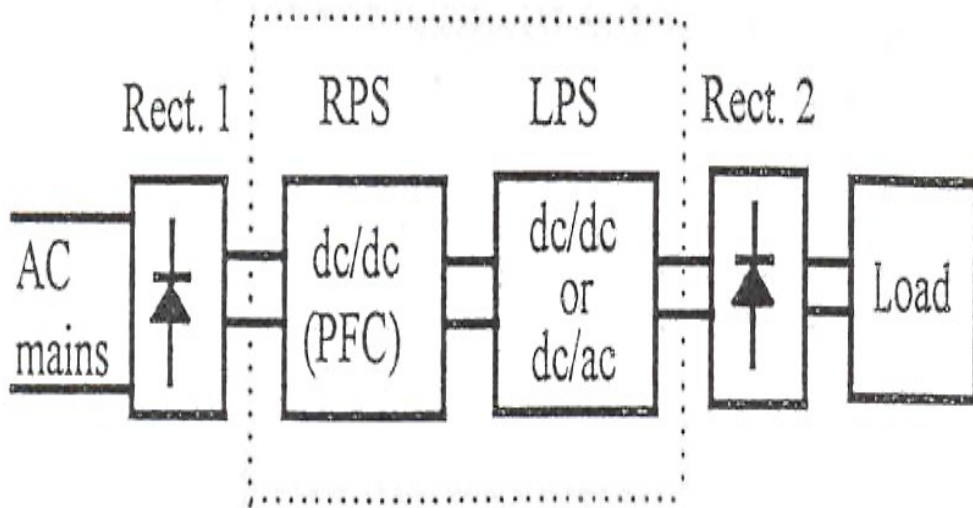


Fig. 9.


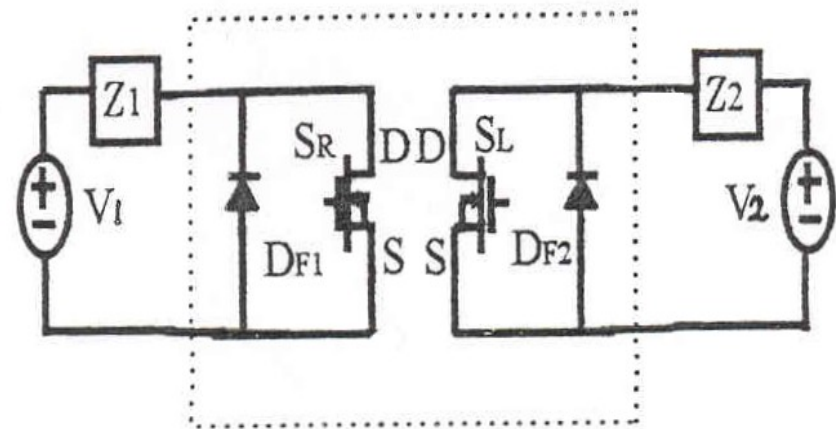


Fig. 10.

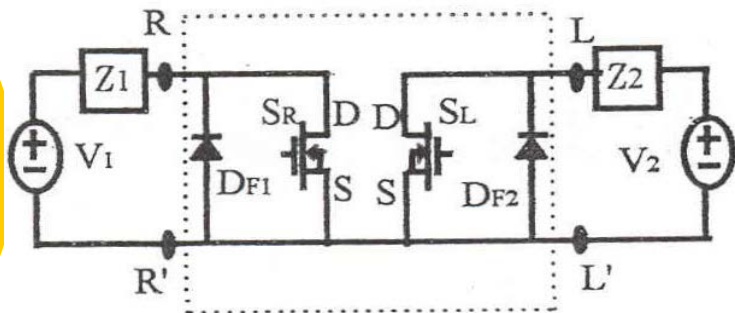




- T-type Grafted Switches



S-S:T-type


(a)

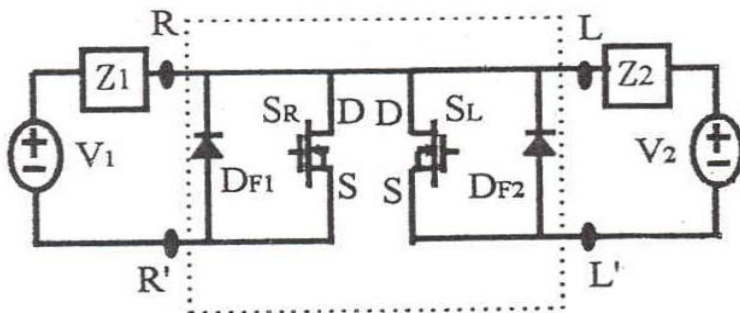


D-D:IT-type

(b)

Fig. 11.

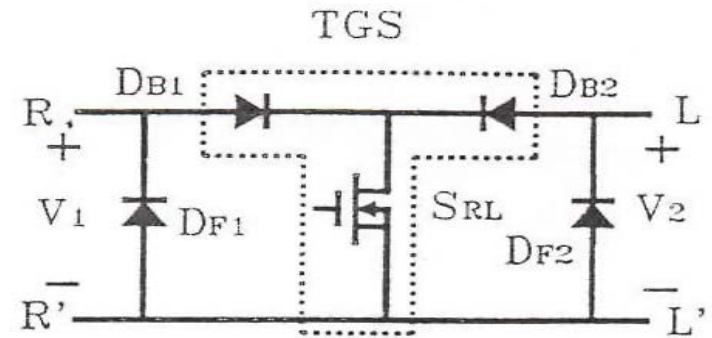

(a)

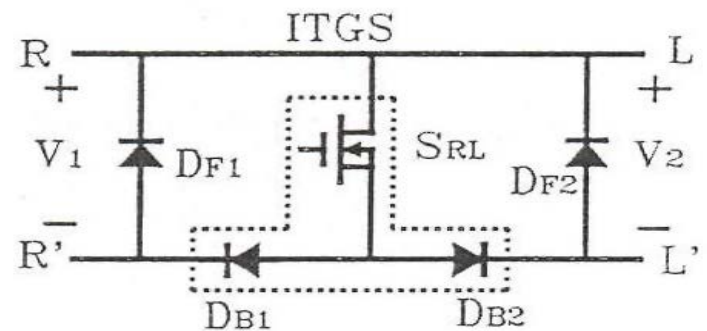


(b)


Fig. 12.



• π -type Grafted Switches

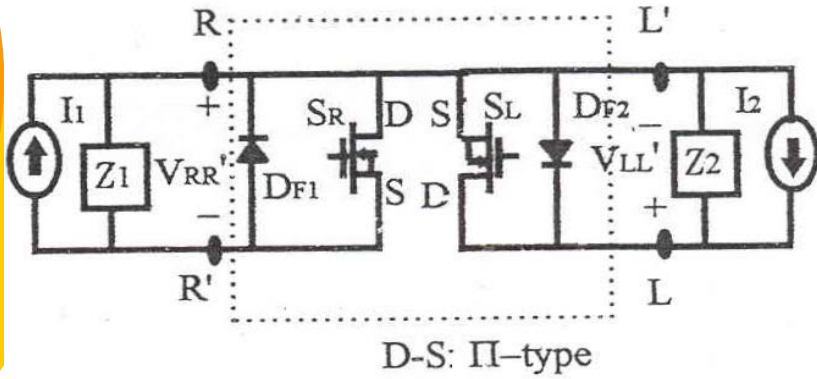


(c)

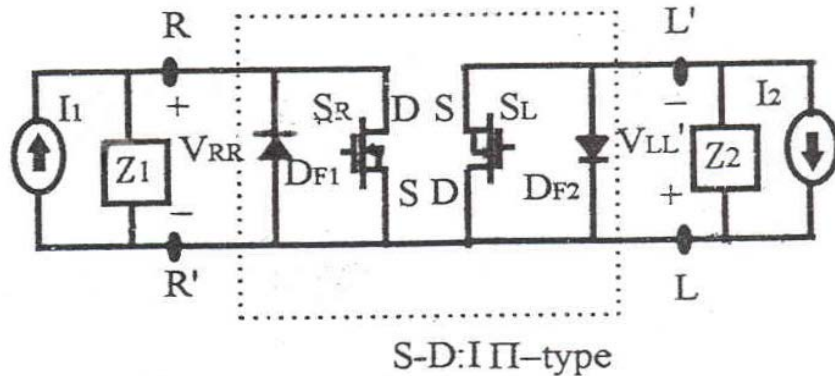


(d)

Fig. 13.

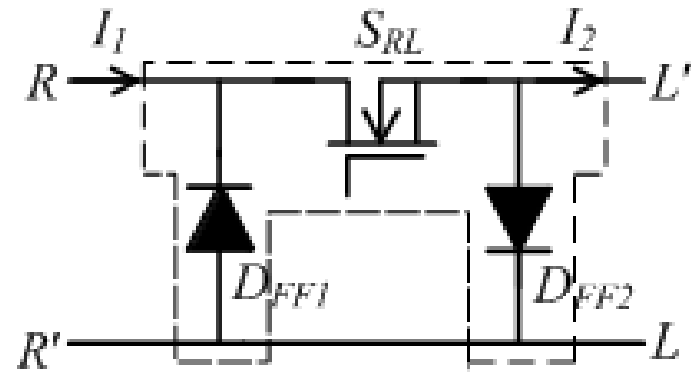

(c)

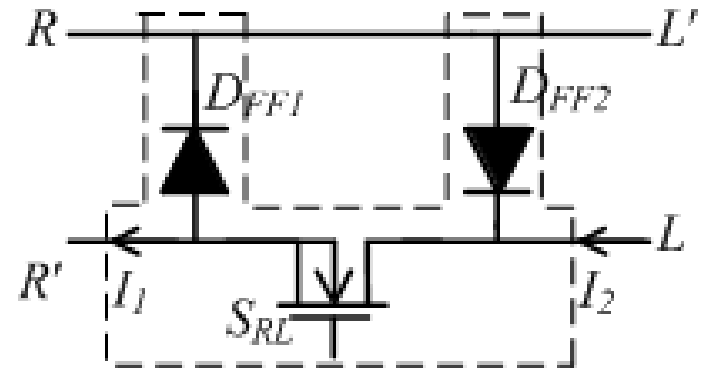

(d)

Fig. 14.



Table 1

Relationship between voltage sources	Original Switches		Degenerated T-type Grafted Switch (DTGS)	Degenerated Inverted T-type Grafted Switch (DITGS)
	S1	S2		
$V_1 > V_2$	U	U		
	U	B		
	B	U		
	B	B		



Table 2

Relationship between voltage sources	Original Switches		Degenerated T-type Grafted Switch (DTGS)	Degenerated Inverted T-type Grafted Switch (DITGS)
	S1	S2		
$V_1 < V_2$	U	U		
	U	B		
	B	U		
	B	B		



Table 3

Relationship between voltage sources	Original Switches		Degenerated T- type Grafted Switch (DTGS)	Degenerated Inverted T-type Grafted Switch (DITGS)
	S1	S2		
$V_1 = V_2$	U	U		
	U	B		
	B	U		
	B	B		



Table 4

Relationship between current sources	Original Switches		Degenerated Π -type Grafted Switch (DIIGS)	Degenerated Inverted Π -type Grafted Switch (DIINGS)
	S1	S2		
$I_1 > I_2$	U	U		
	U	B		
	B	U		
	B	B		
$I_1 < I_2$	U	U		
	B	U		
	U	B		
	B	B		



Table 5

Relationship between current sources	Original Switches		Degenerated Π -type Grafted Switch (DPIGS)	Degenerated Inverted Π -type Grafted Switch (DIPIGS)
	S1	S2		
$I_1 = I_2$	U	U		
	U	B		
	B	U		
	B	B		



Table 6. Duality between T-type and II-type grafted switches

TGS and ITGS	IIGS and IIIGS
1. D_{B1} , D_{B2} and S_{RL} share a node.	1. D_{FF1} , D_{FF2} and S_{RL} form a loop.
2. D_{Bi} blocks the voltage difference between V_1 and V_2 when both switches S_R and S_L are in the off states.	2. D_{FFi} circulates the current difference between I_1 and I_2 when both switches S_R and S_L are in the on states.
3. Required to determine the V_1 and V_2 when S_R and S_L are in the off states.	3. Required to determine the I_1 and I_2 when S_R and S_L are in the on states.
4. Power processors are represented by TECs.	4. Power processors are represented by NECs.





Illustration of Buck-Boost Integration

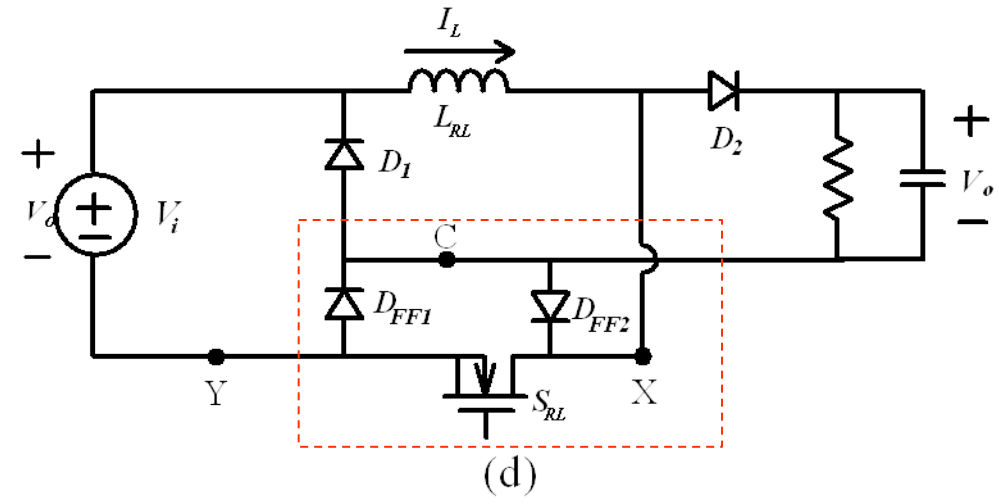
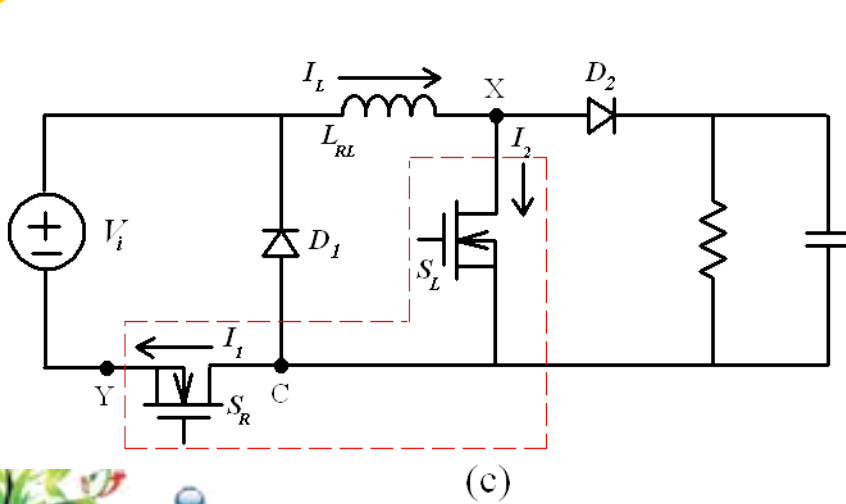
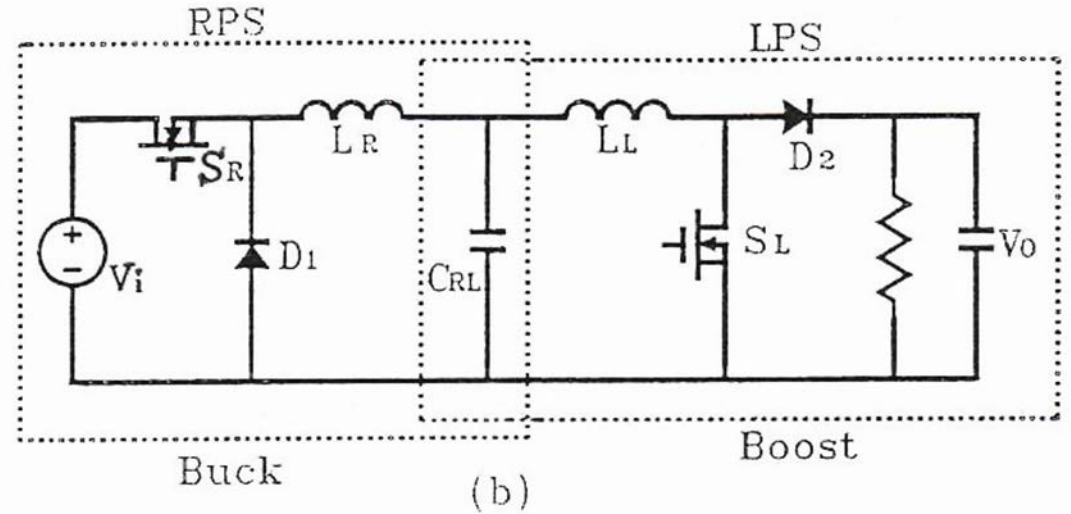
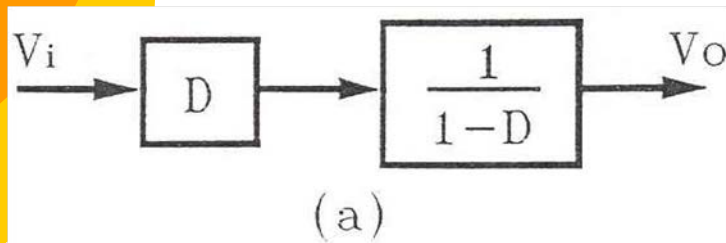


Fig. 15.


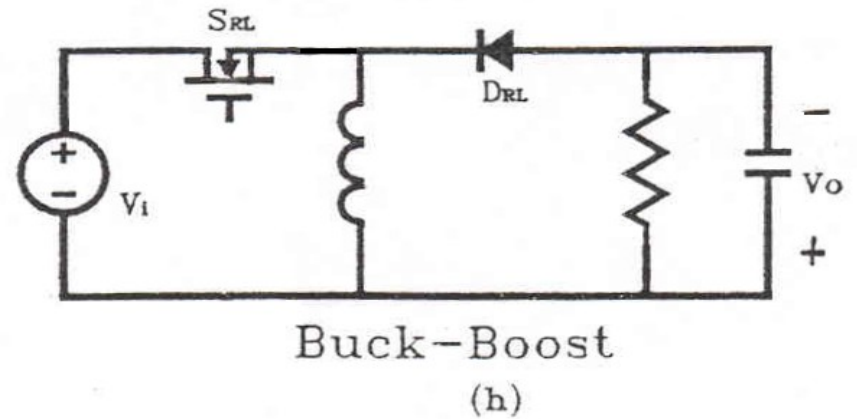
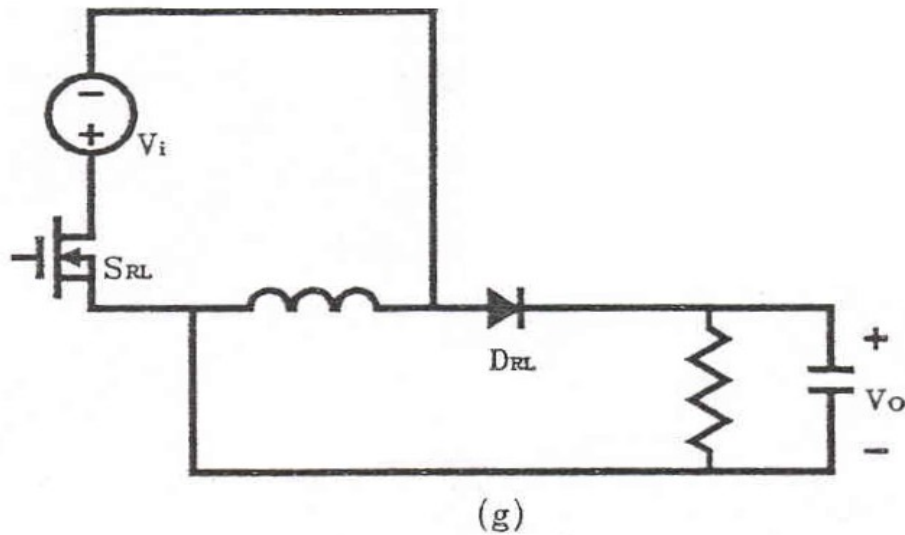
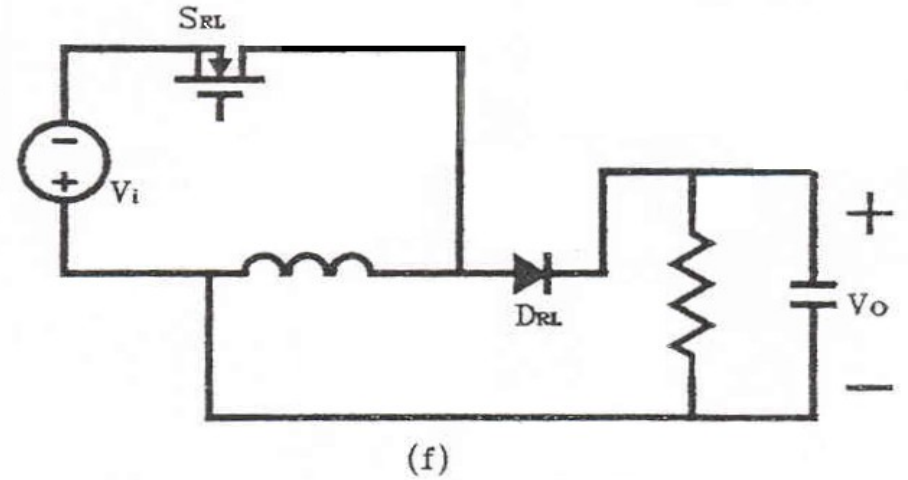


Fig. 15. (continued)

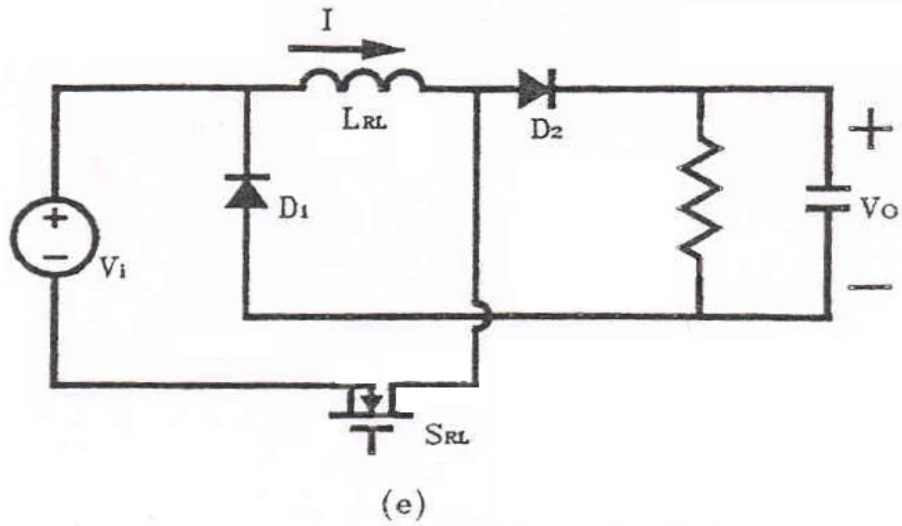

Illustration of Boost-Buck (Ćuk) Integration

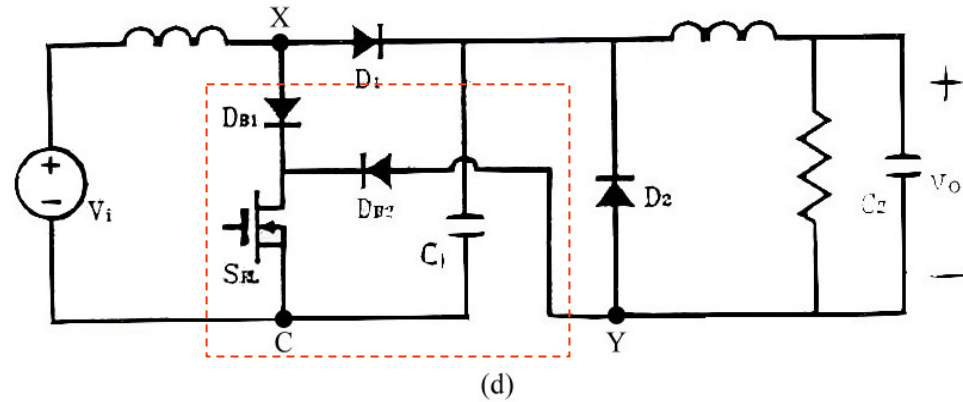
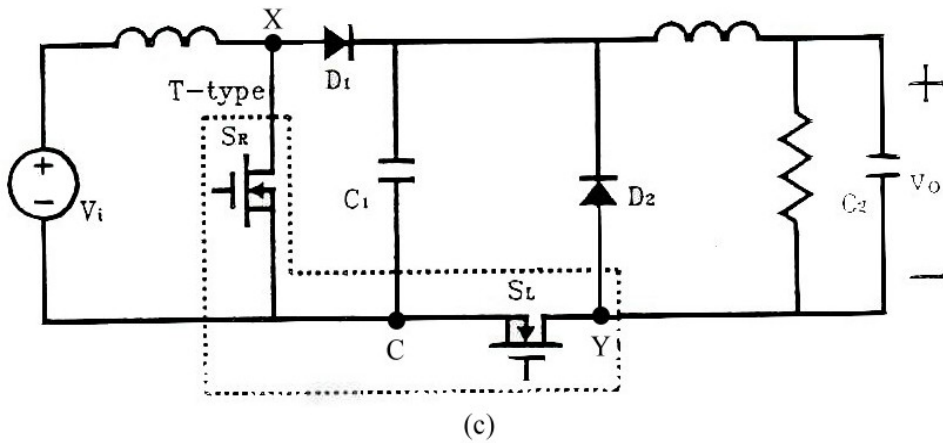
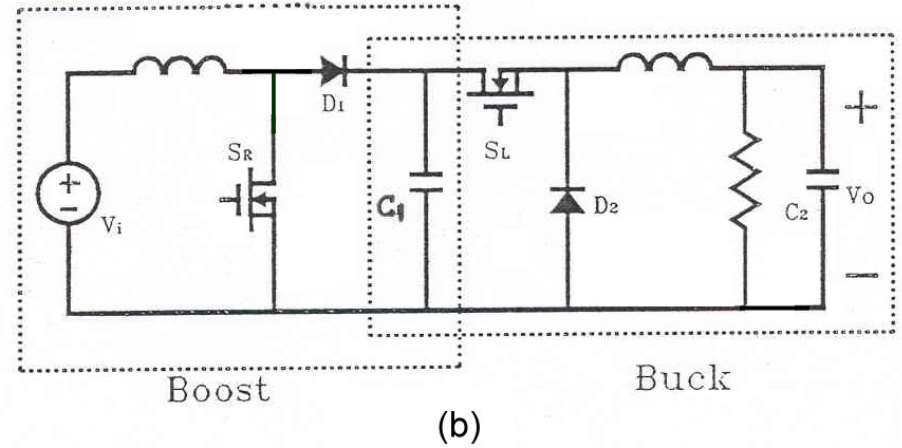
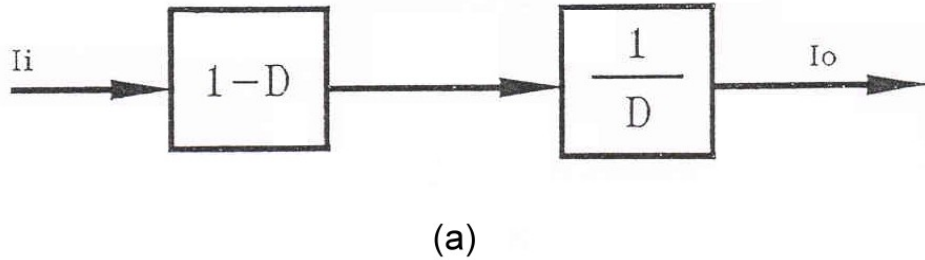


Fig. 16.



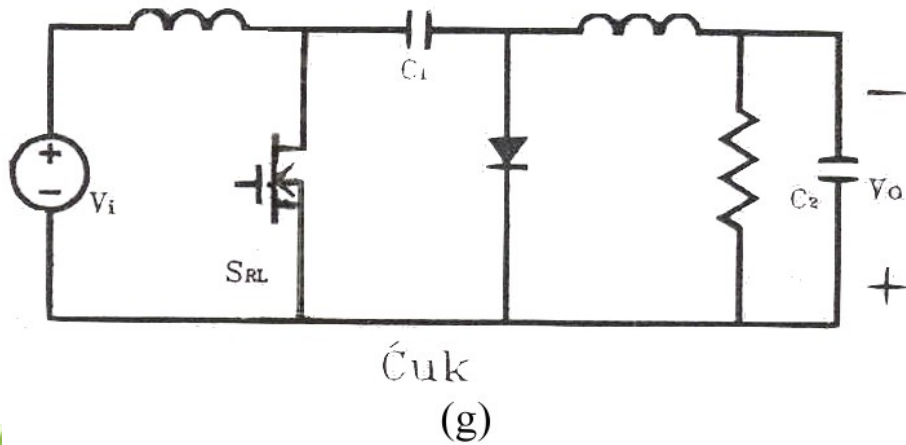
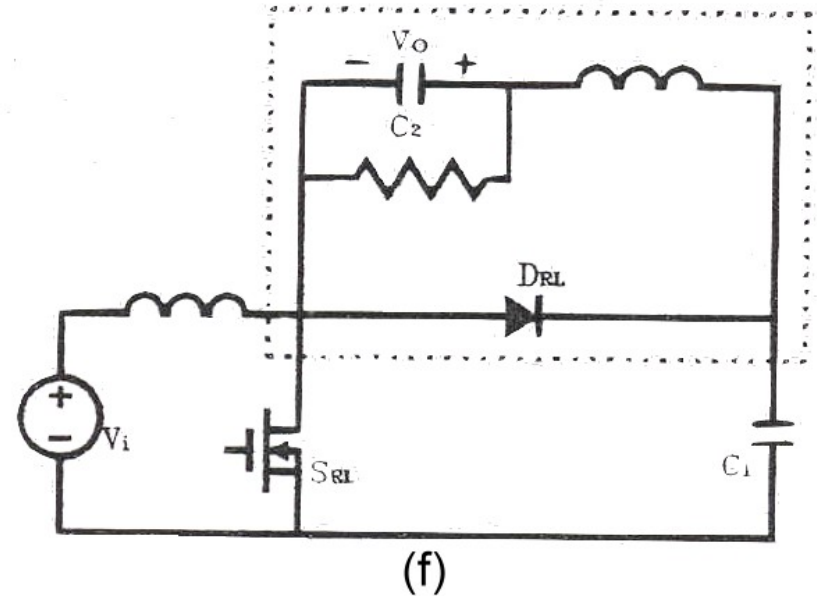


Fig. 16. (continued)

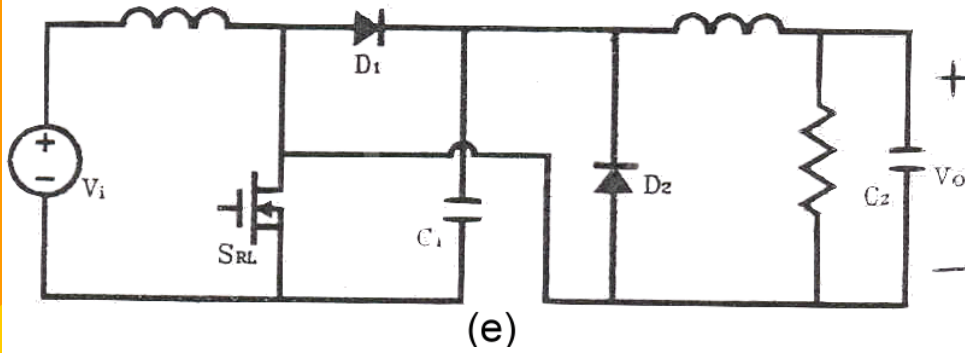

Illustration of Buck-Boost-Buck (Zeta) Integration

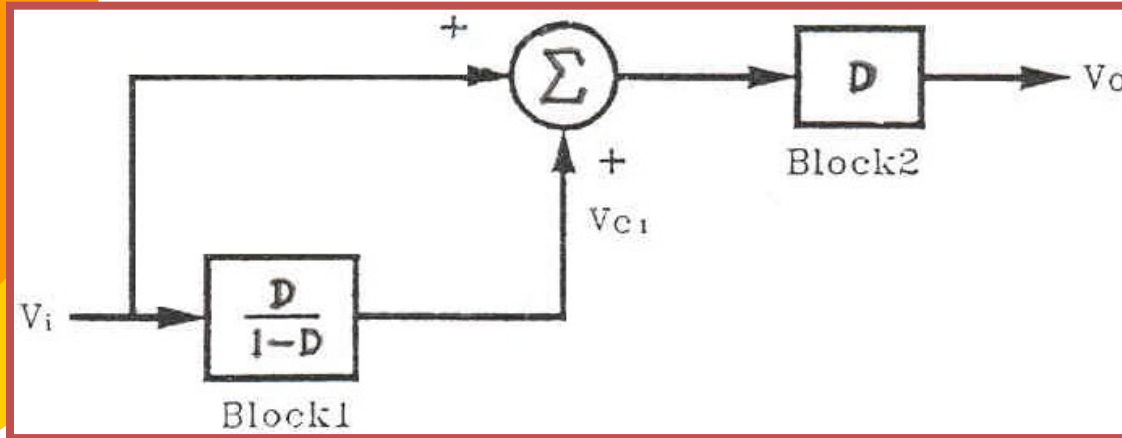

(a)



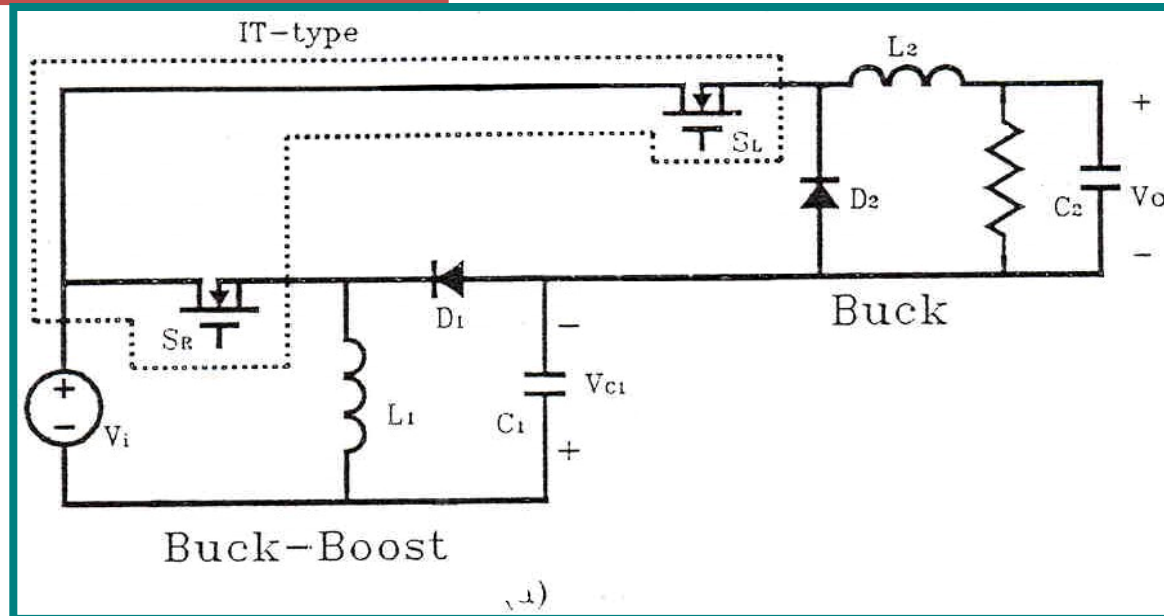



Fig. 17.

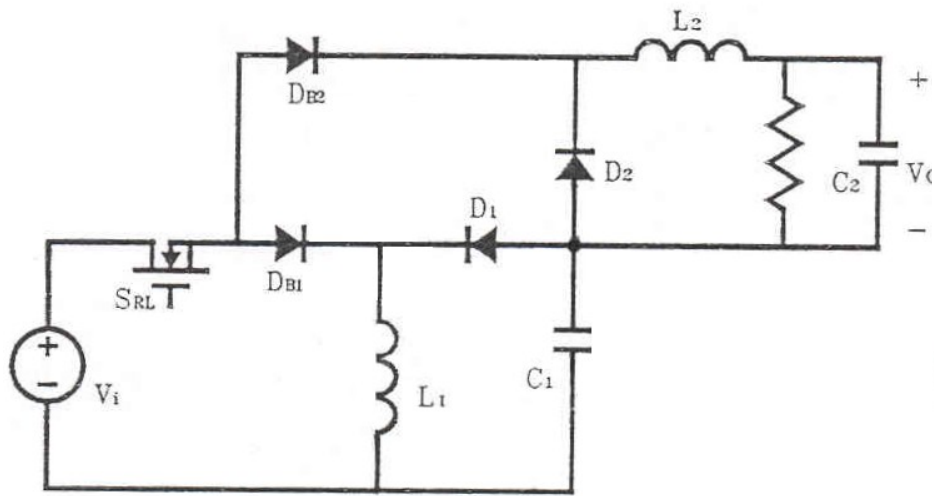


(c)

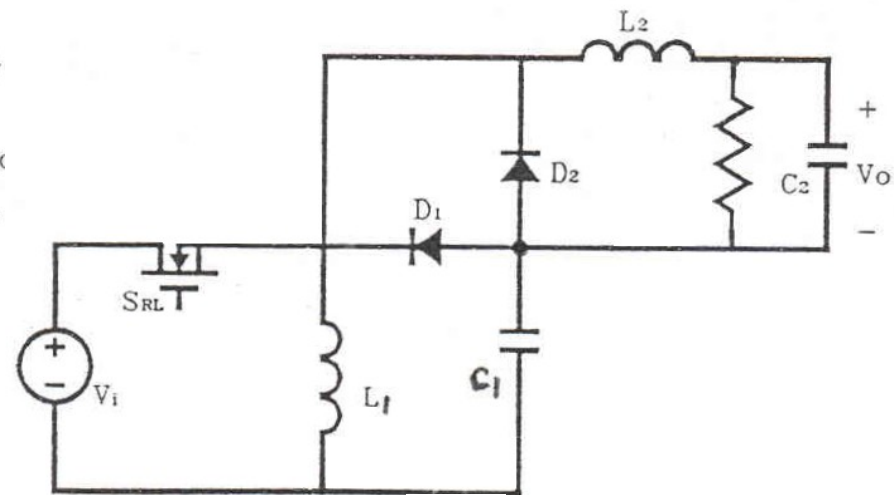

(d)

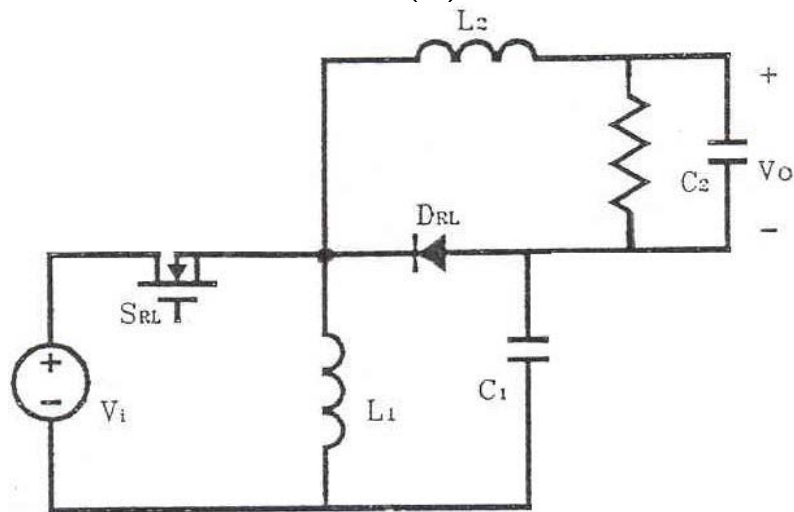

(e)

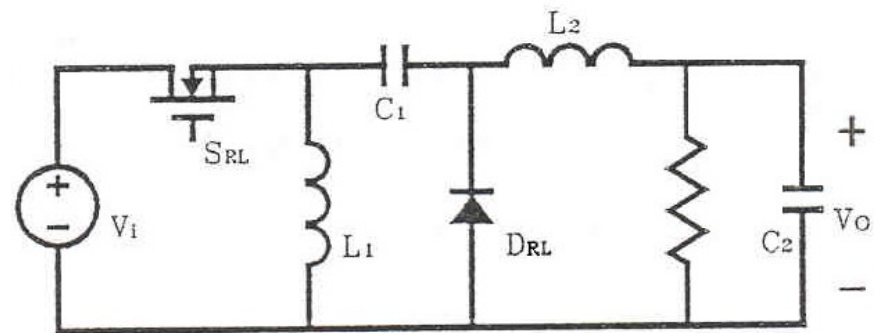

Zeta

(f)

Fig. 17. (continued)



Illustration of Boost-Buck-Boost (SEPIC) Integration

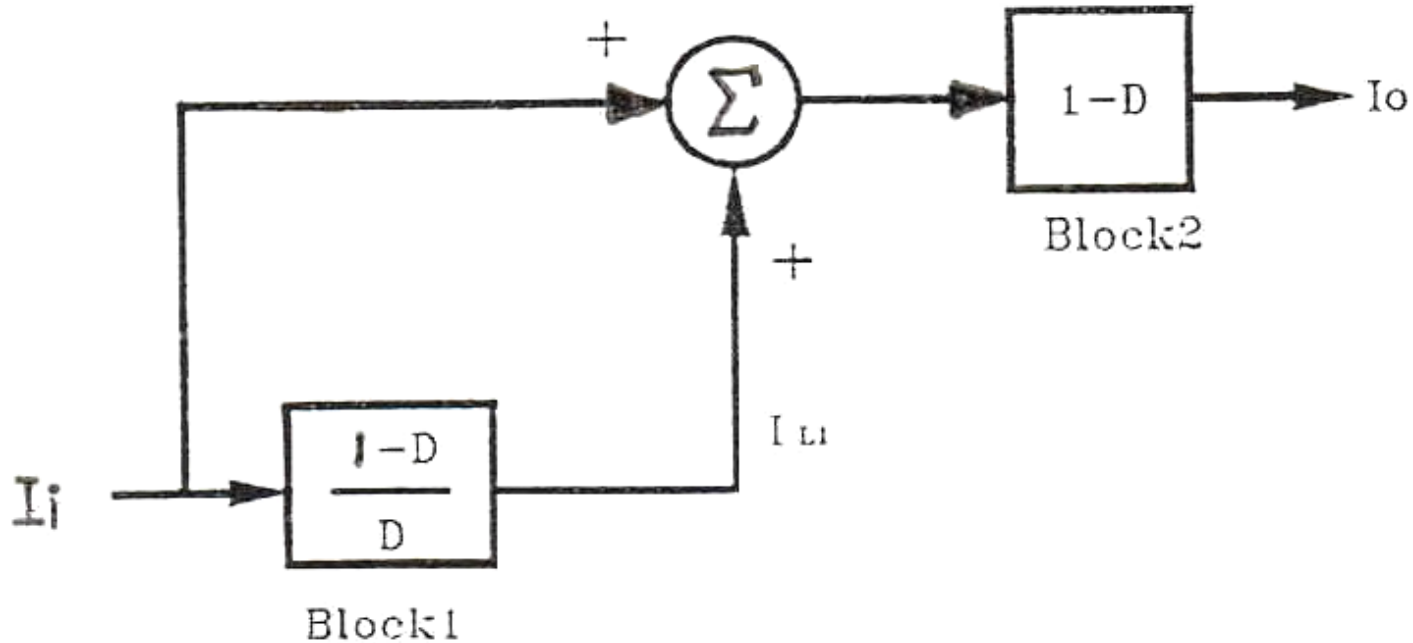


Fig. 18.



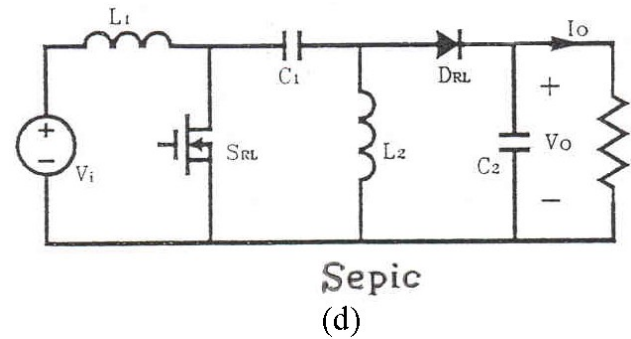
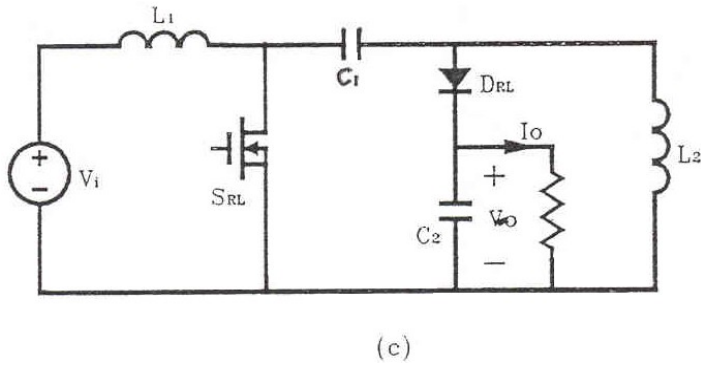



Fig. 18. (continued)

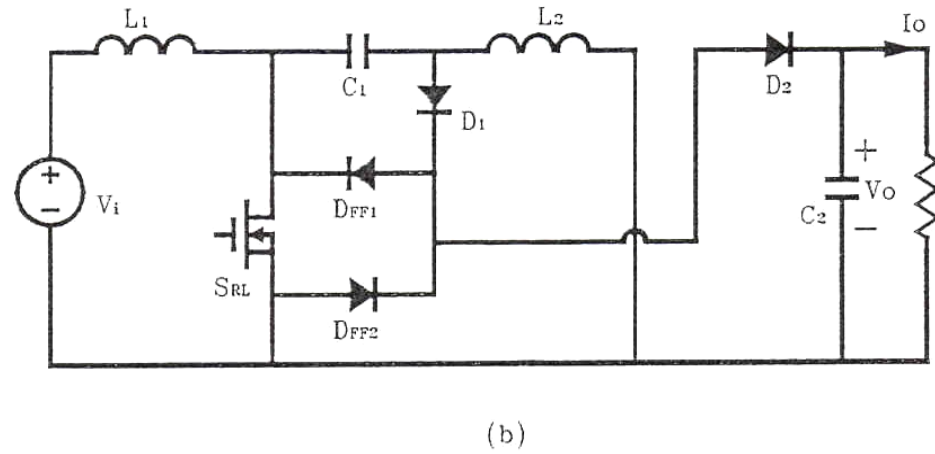

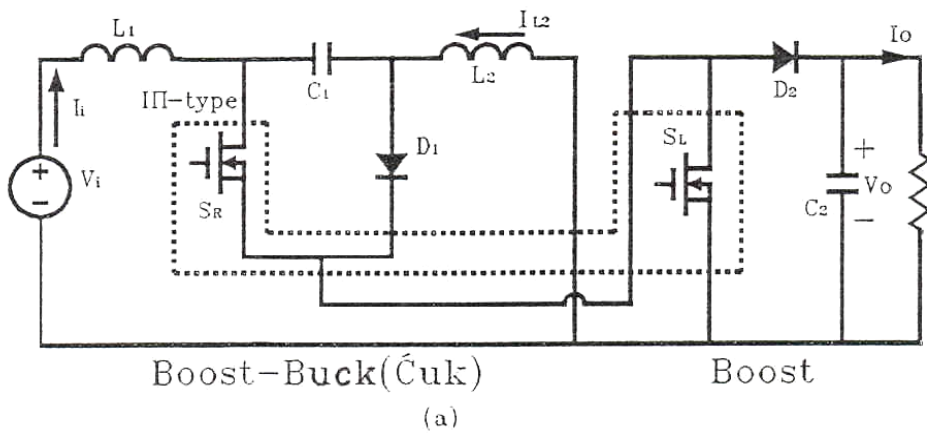


Illustrations
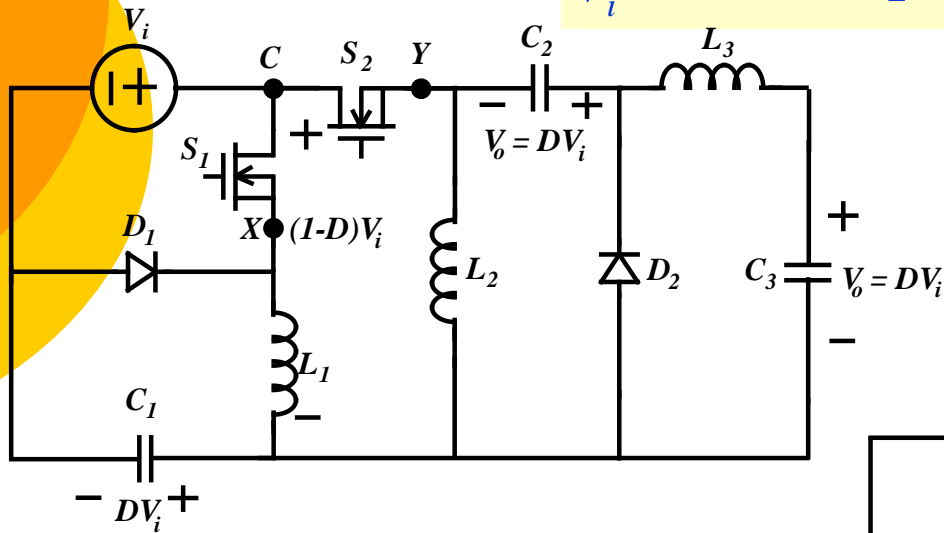
$$\frac{V_o}{V_i} = (1 - D) \cdot \frac{D}{1 - D} = D$$



(A)

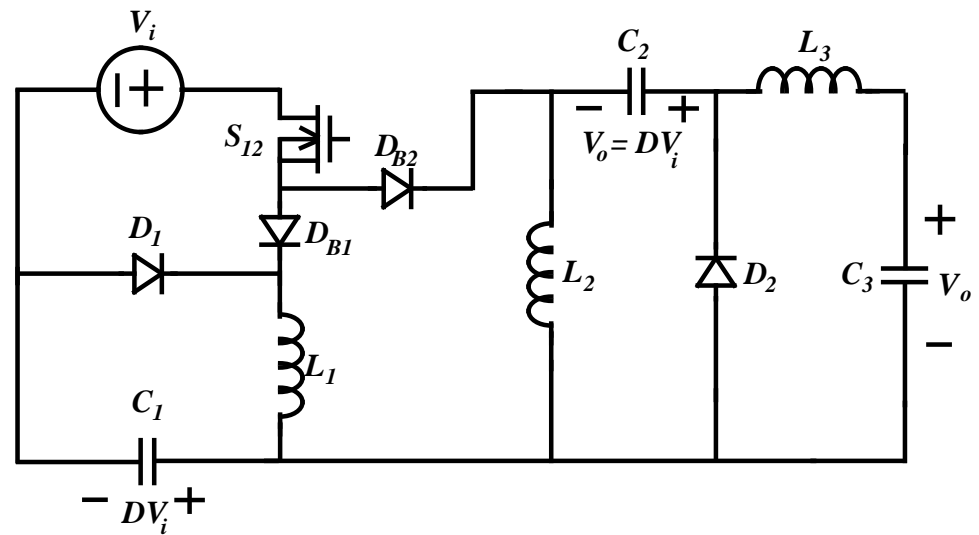

(B)

Fig. 19.

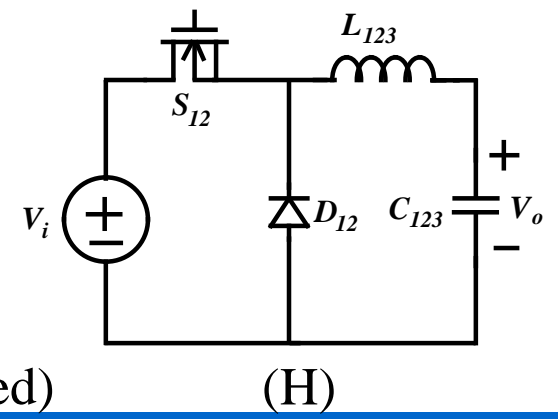
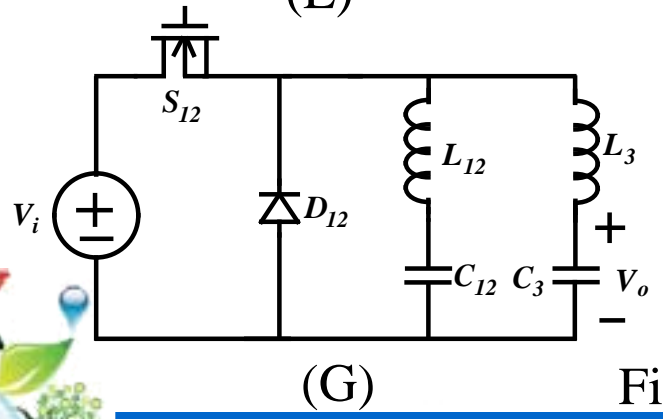
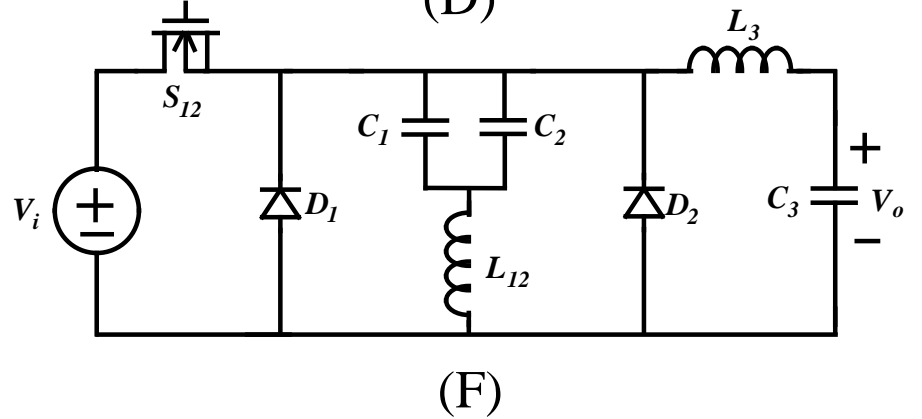
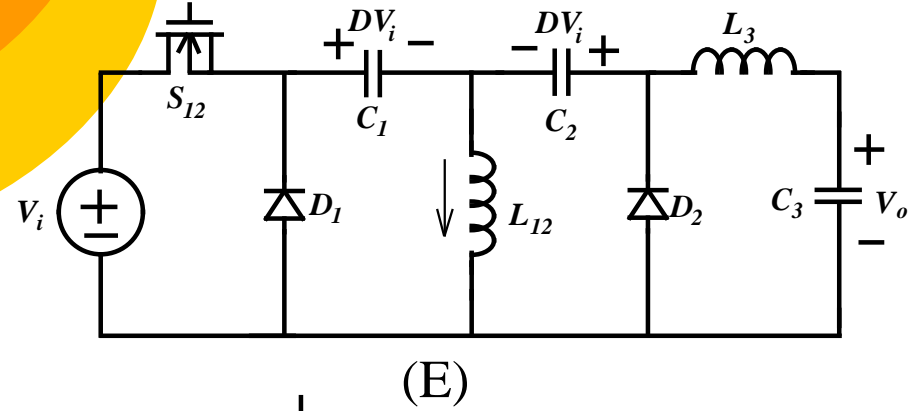
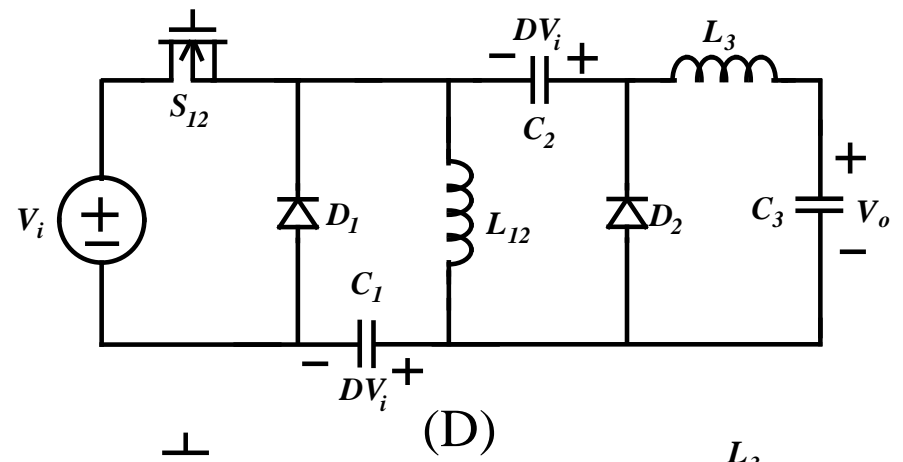
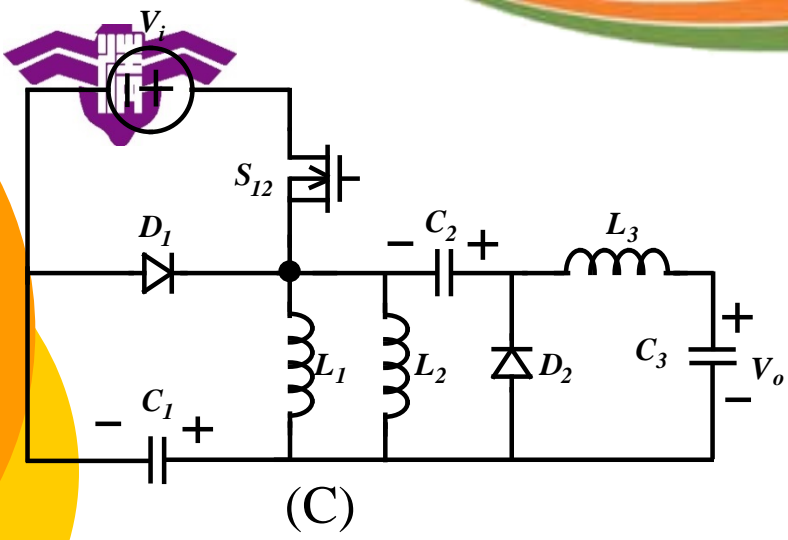


Fig. 19. (continued)

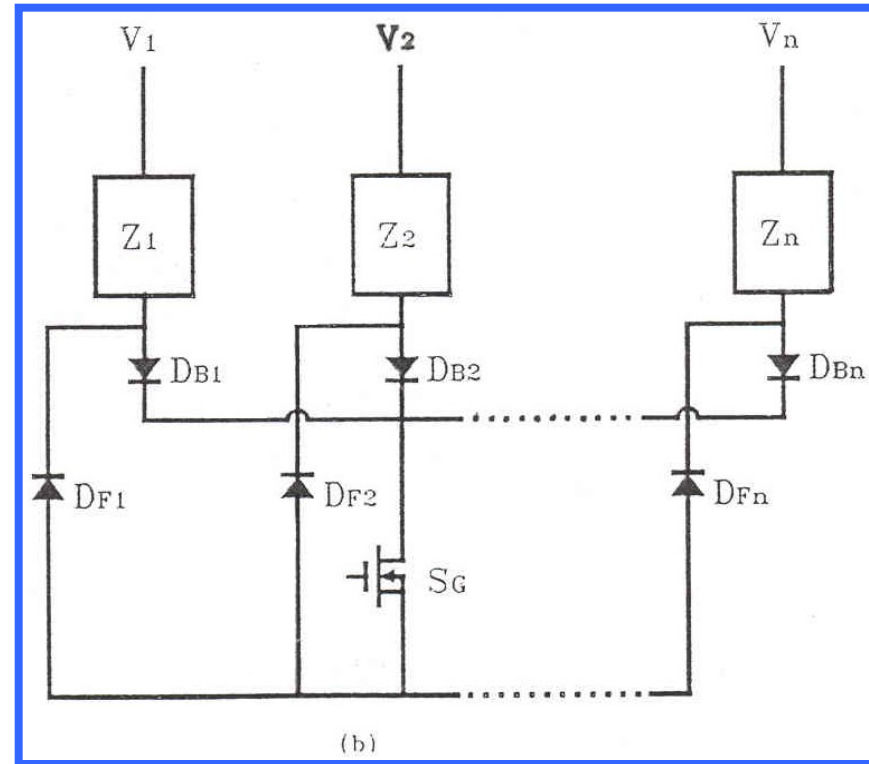
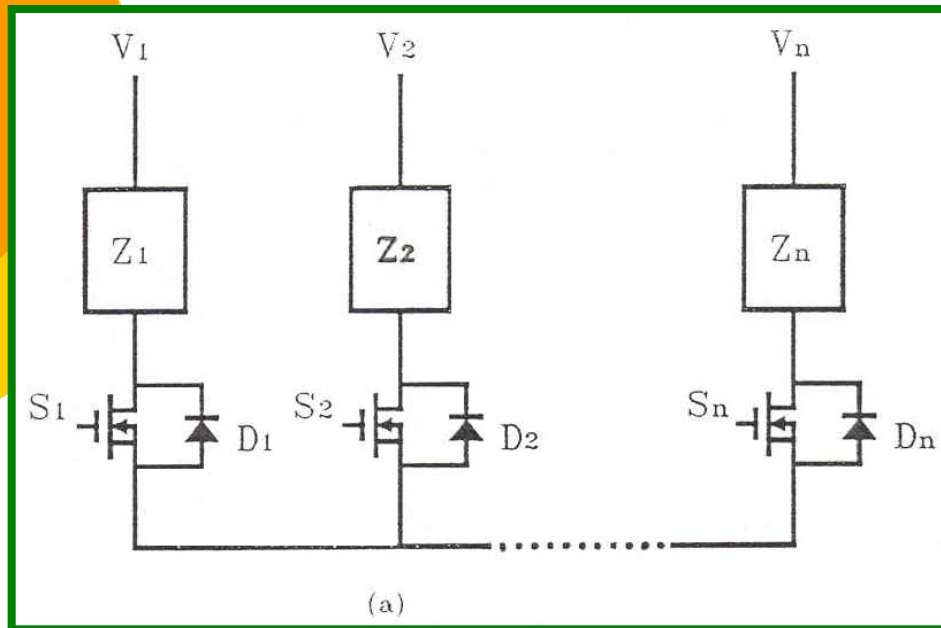


Fig. 20.



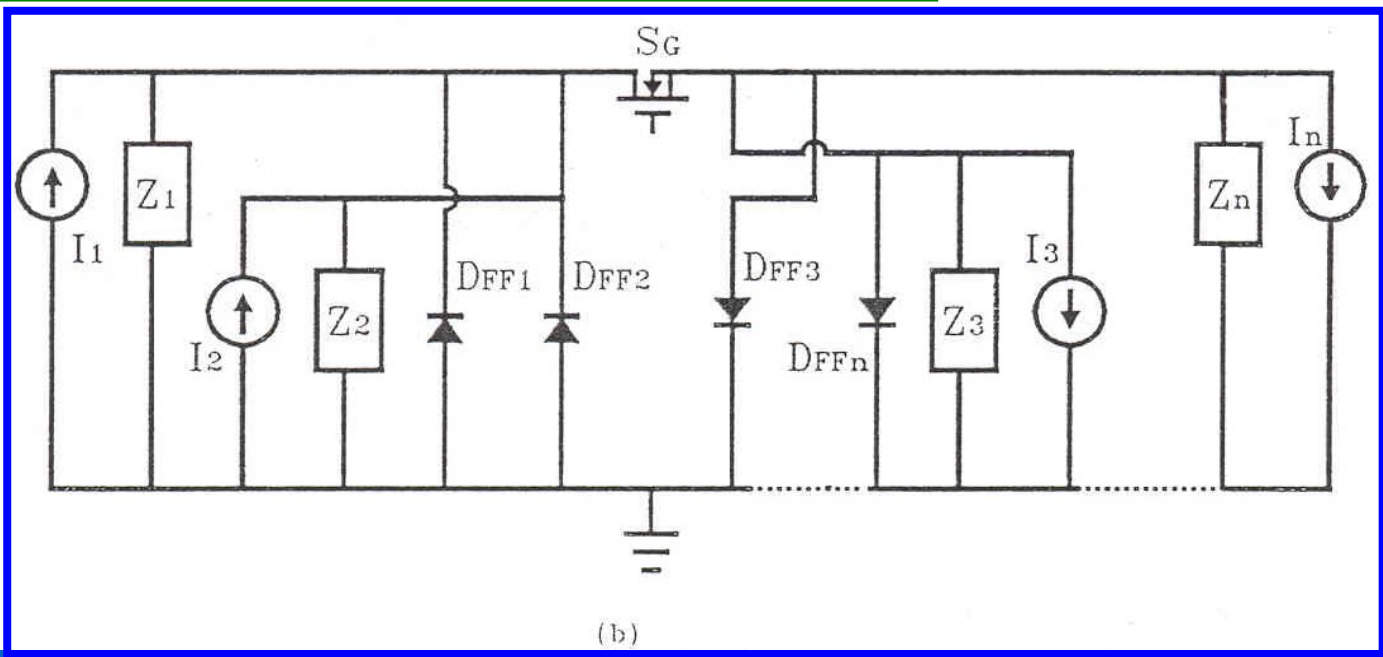


Fig. 21.

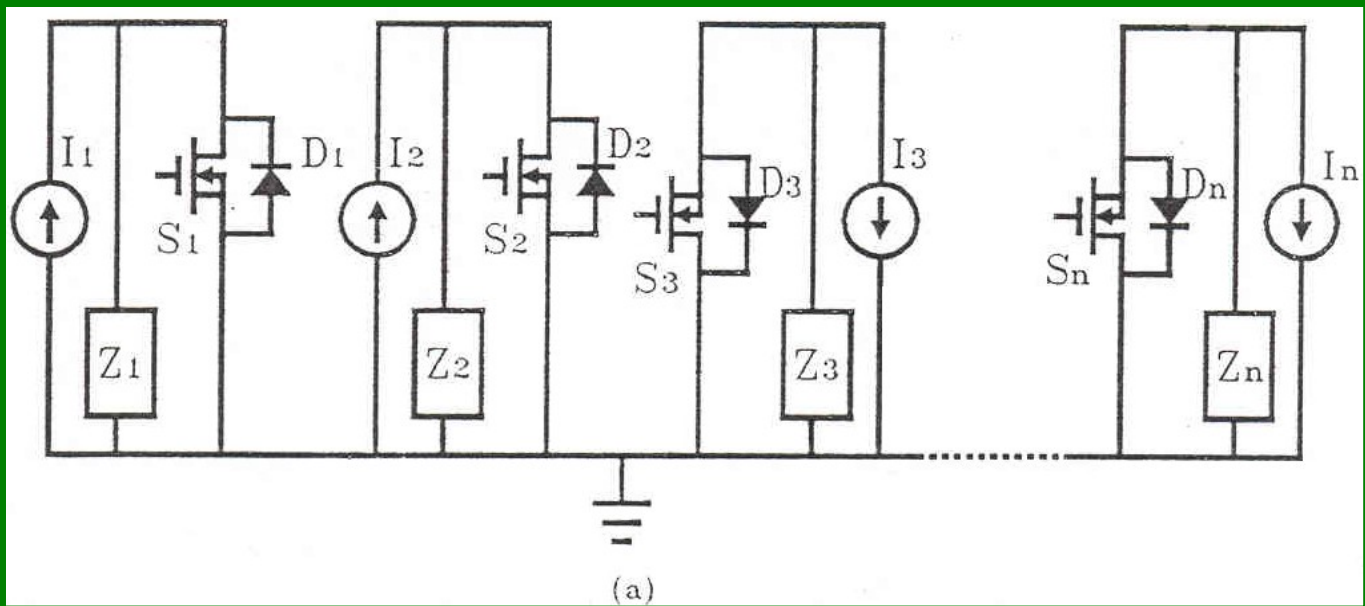


Another Applications with Graft Technique

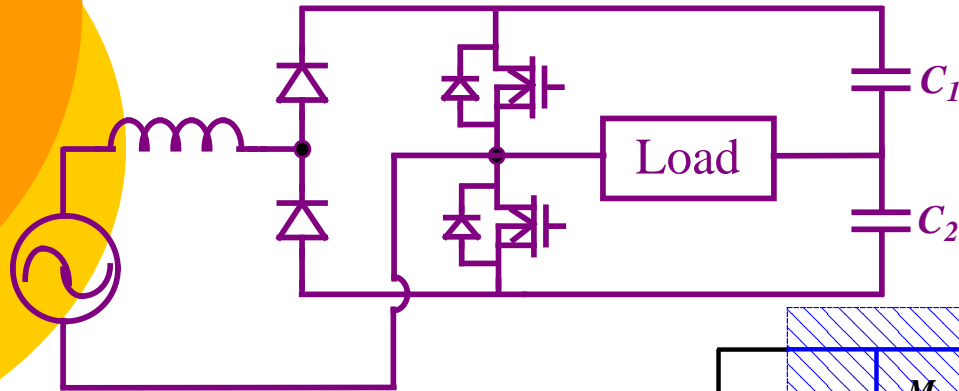- Dither Boost + Half-Bridge Inverter (Isao Takahashi)




(a)

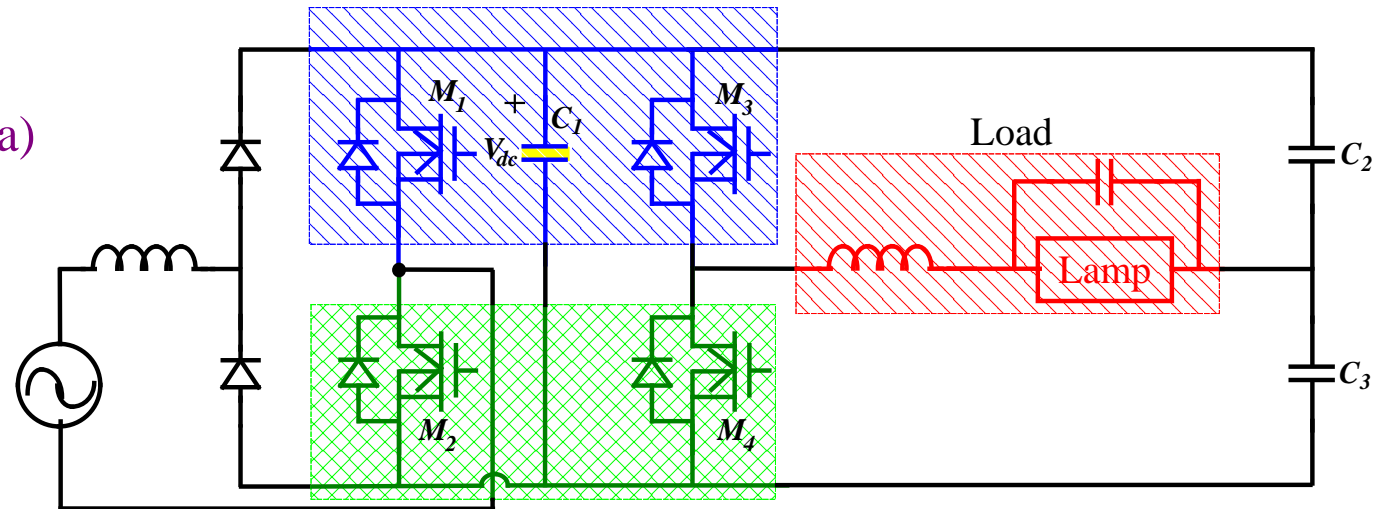


Dither Boost + Half-Bridge

Fig. 22. (b)

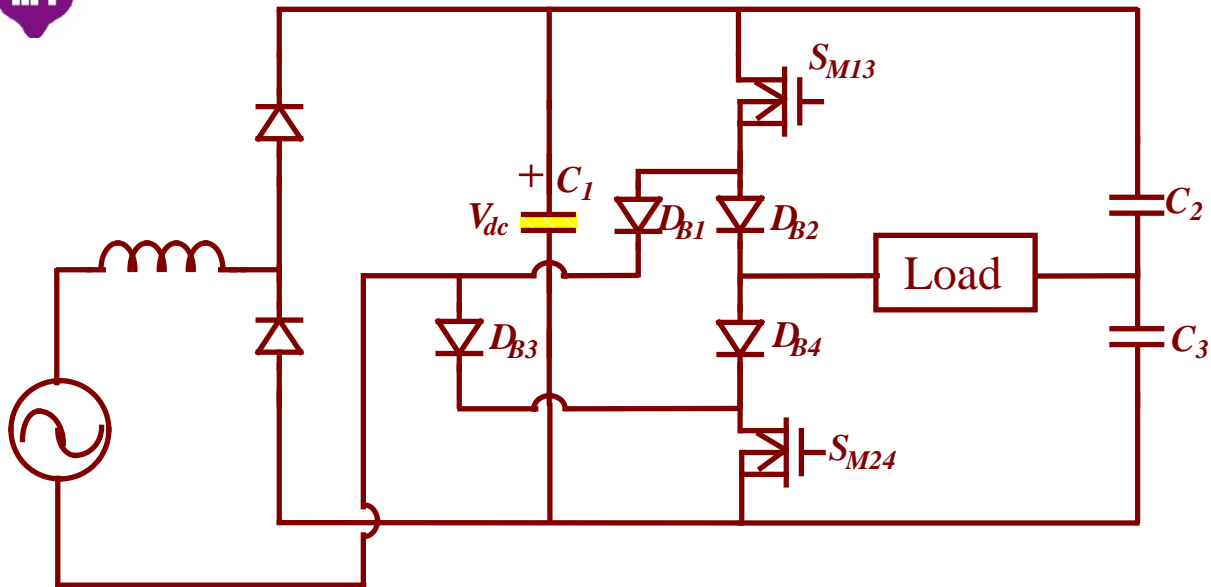

(c)

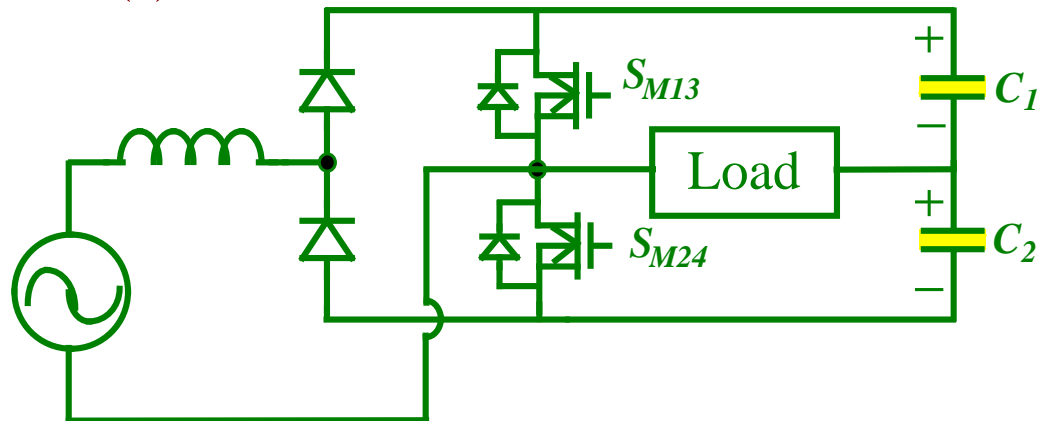


(d)


Fig. 22. (continued)



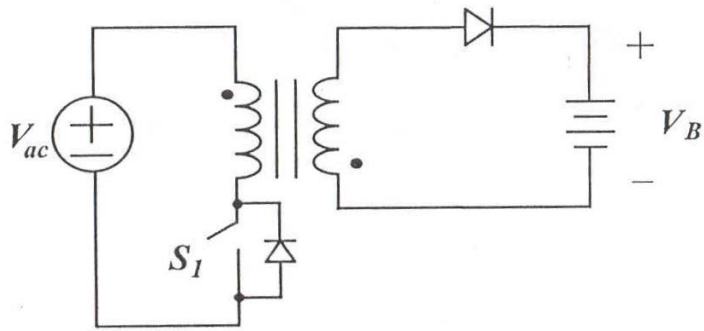
3-in-1 Converter (Charger + Discharger + Ballast)




(a)

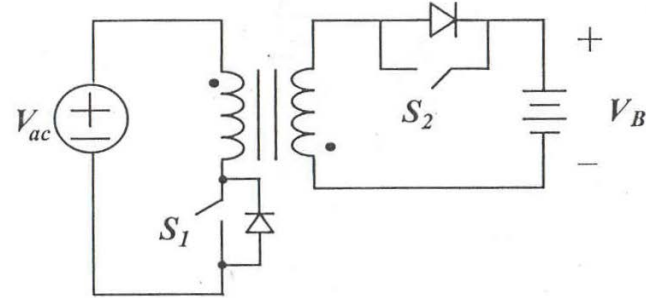


(b)

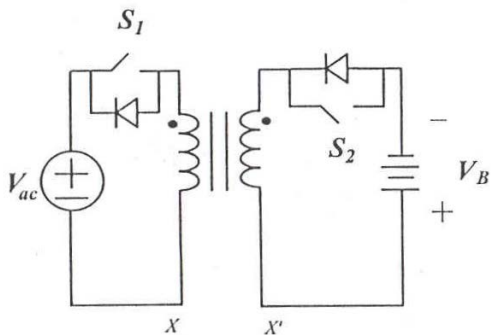

(c)

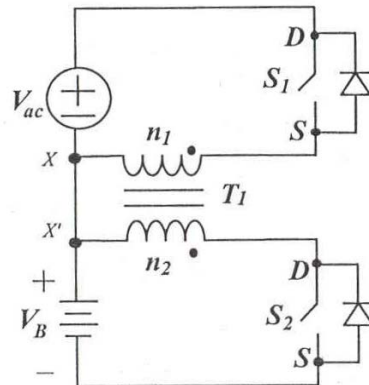


(d)

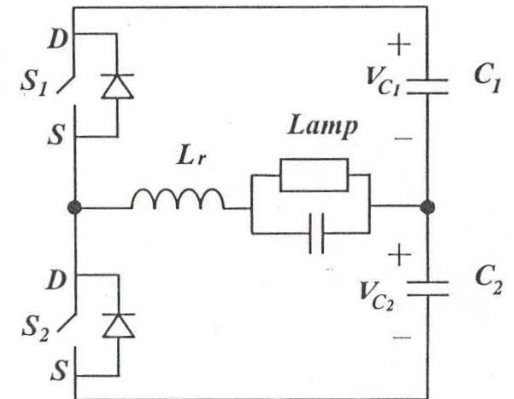


(e)

Fig. 23.

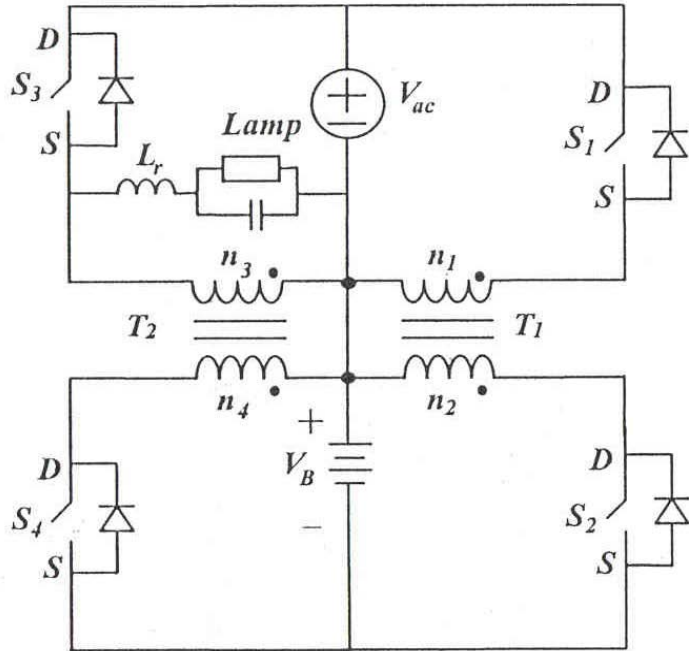


(f)

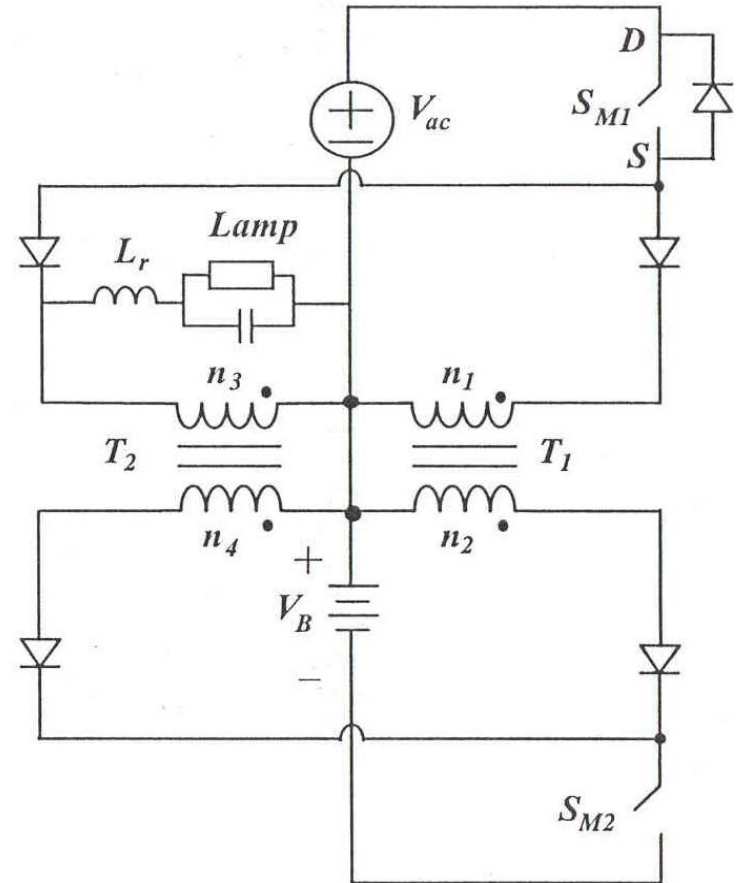


(g)

Fig. 23. (continued)

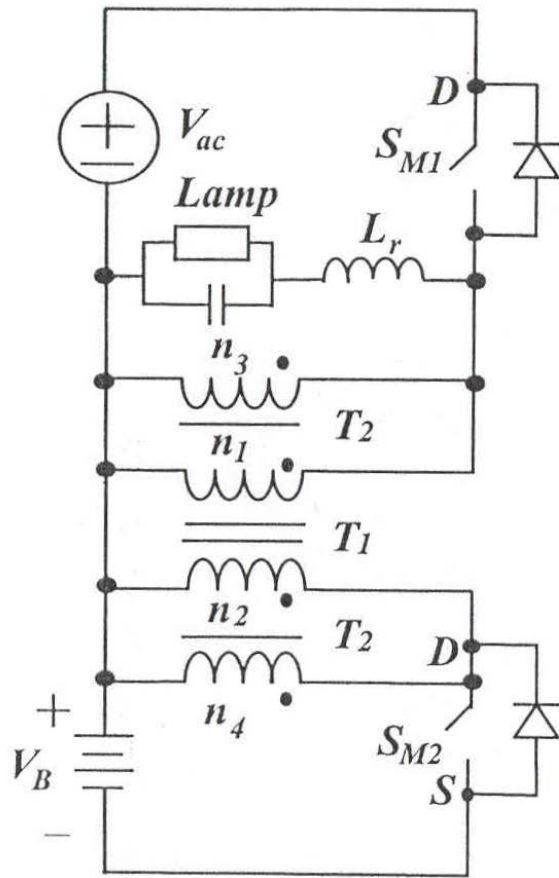

(h)

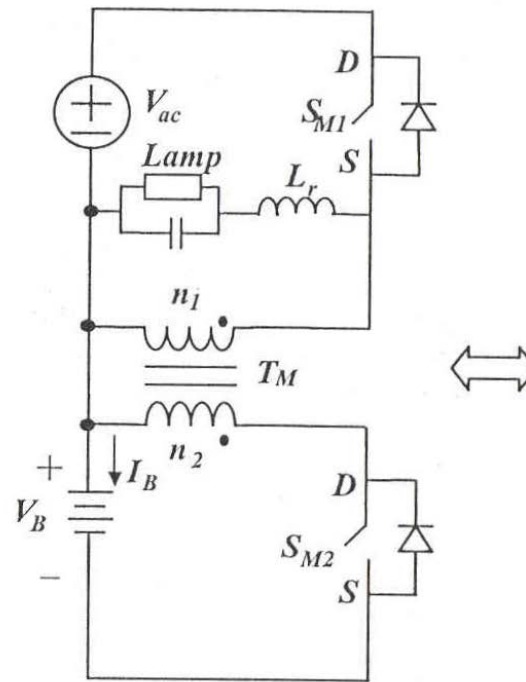

(i)

Fig. 23. (continued)



Boost + Half Bridge (Ćuk)


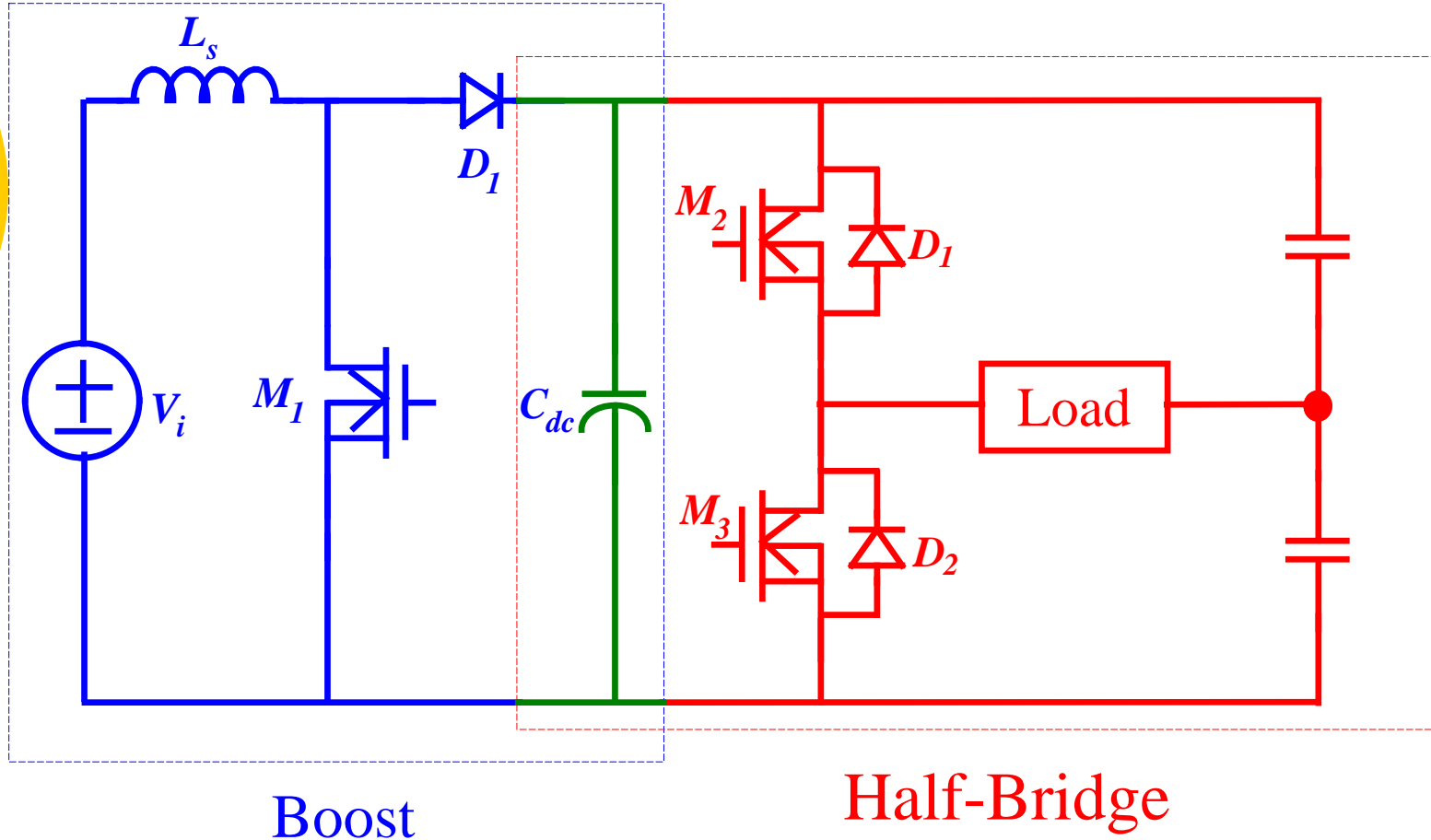


Fig. 24.

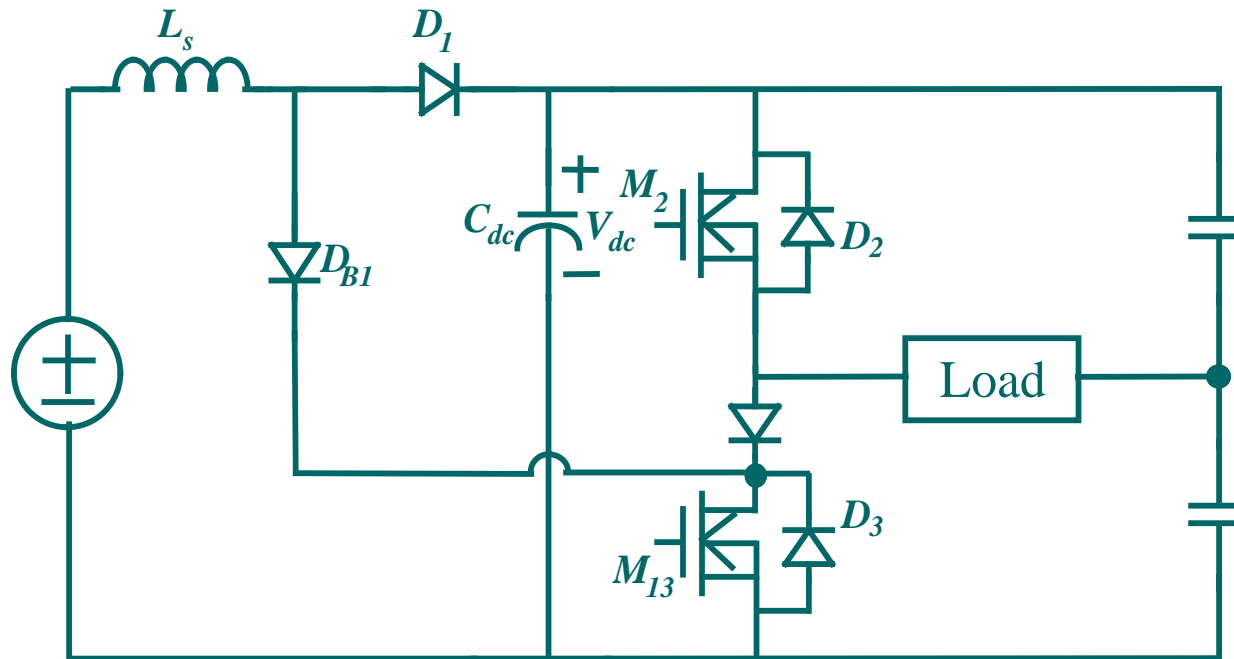

Switches M_1 and M_3 are sharing a common node $s-s$ and they can operated synchronously; thus, we have the following integrated converter:



D_{B2}

Fig. 25.



Since the voltage stresses imposed on M_1 and M_3 are the same and is V_{dc} , diodes D_{B1} and D_{B2} can be removed (*i.e.* shorted). The circuit shown in Fig. 25 can be simplified to the one shown as follows:


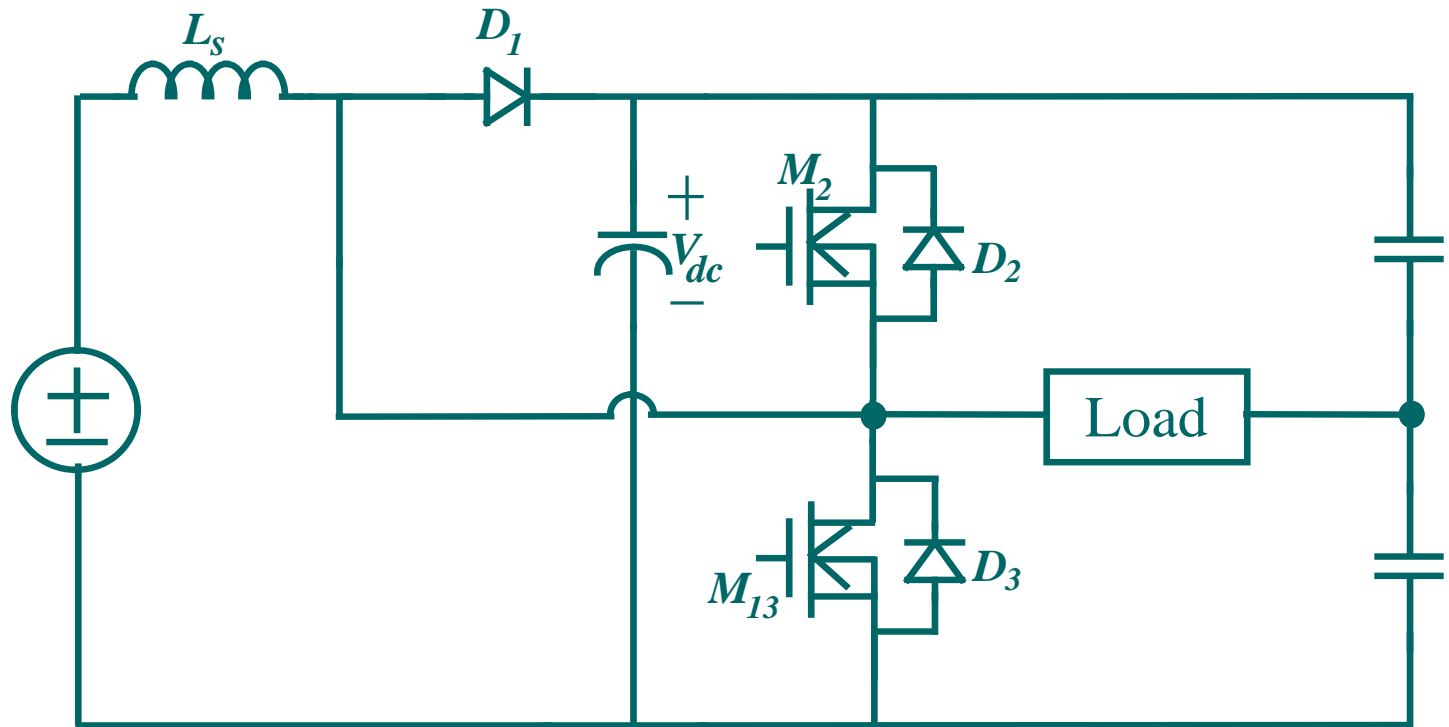


Fig. 26.

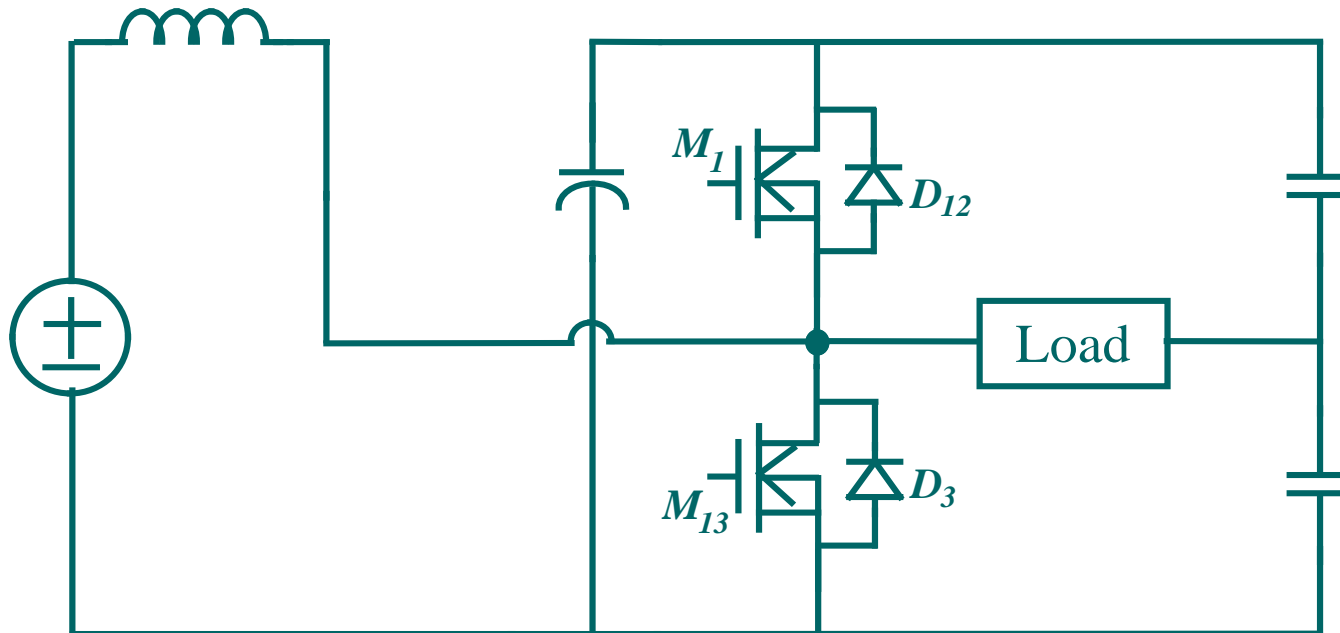

It is obvious that diodes D_1 and D_2 are in parallel. Thus, the circuit shown in Fig. 26 can be further simplified to Fig. 27.




Boost + Half-Bridge

Fig. 27.




Boost + class E (Ćuk)

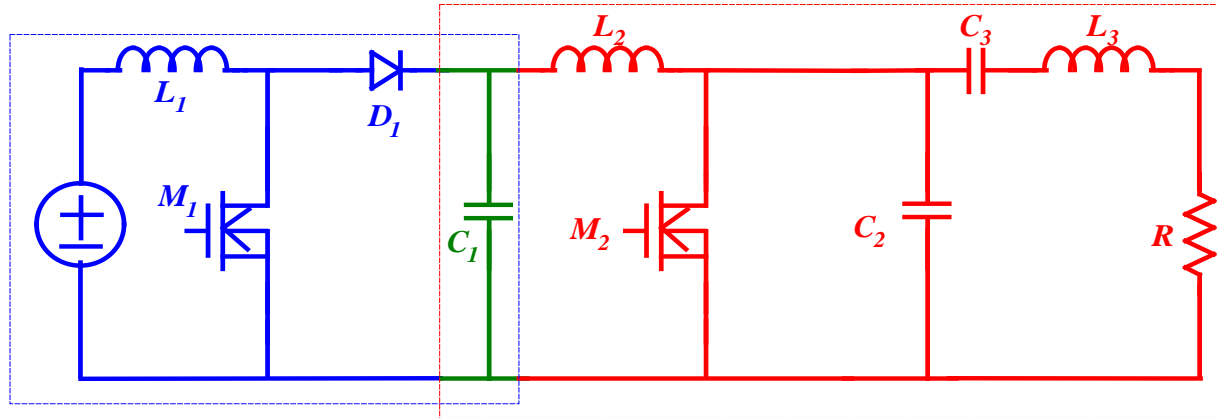

Boost

Class E

(a)

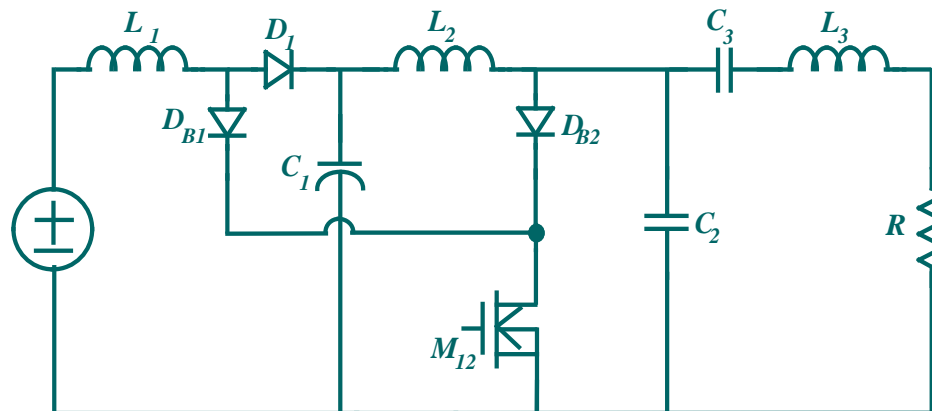


(b)

Fig. 28.



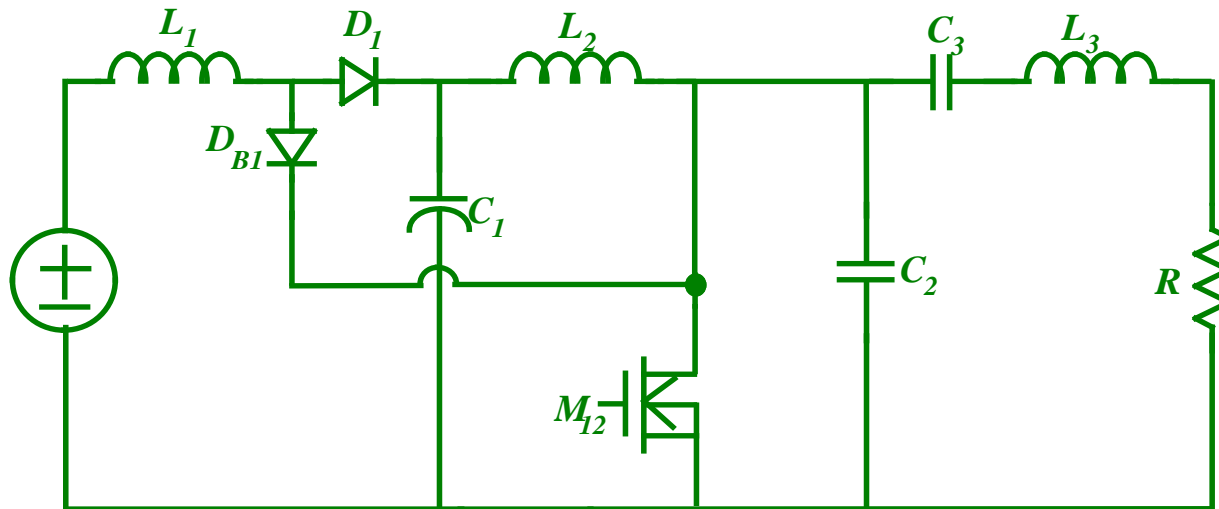Since $V_{ds}(M_2) > V_{dc}(M_1)$ during turn-off, thus we have the following circuit:




Boost + Class E


(c)

Fig. 28. (continued)

Buck//Buck-Boost

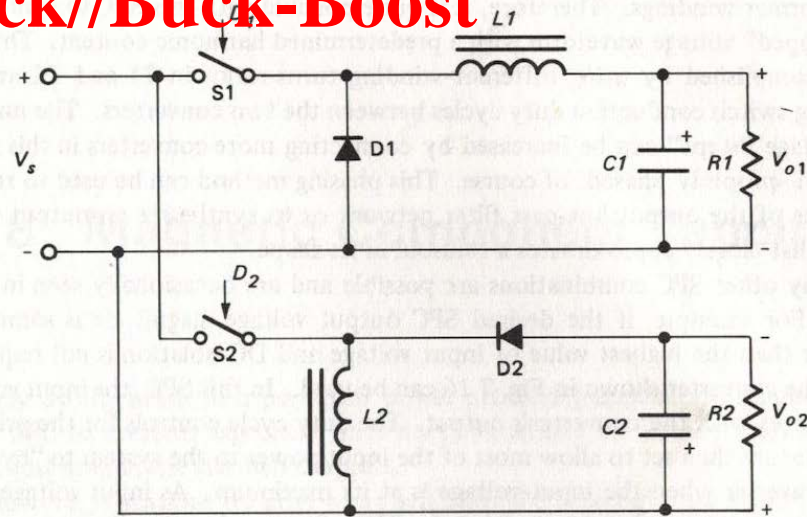

(A)




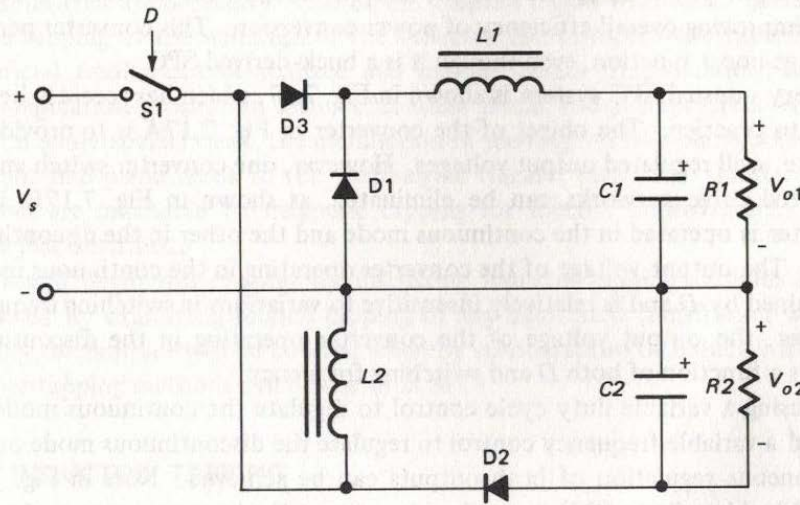


(B)


Fig. 29. A scheme for combining duty cycle and frequency modulation to provide two regulated outputs with one switch.[3]




with Grafted Diodes

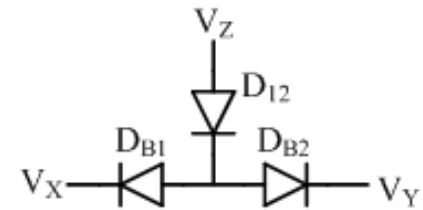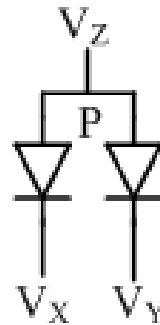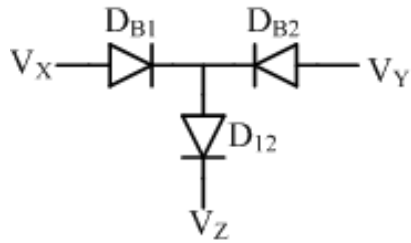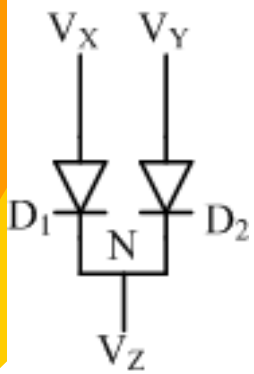





(i) $V_X > V_Y$

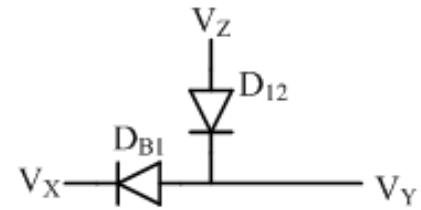

(ii) $V_X < V_Y$

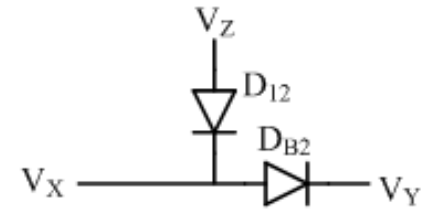


(iii) $V_X = V_Y$

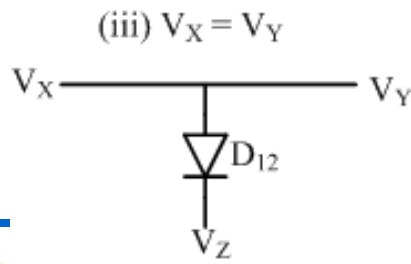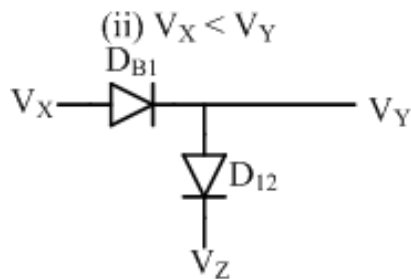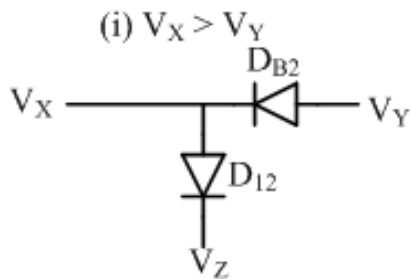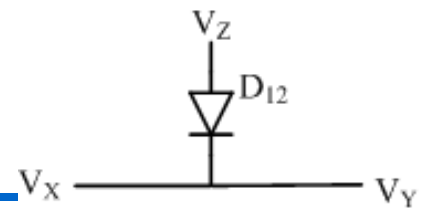

(c) Common P-P

Fig. 30.

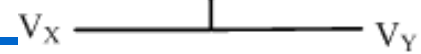


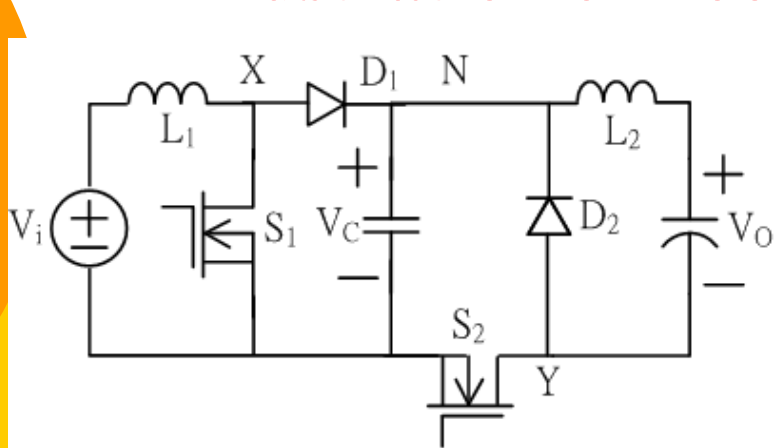(d) L

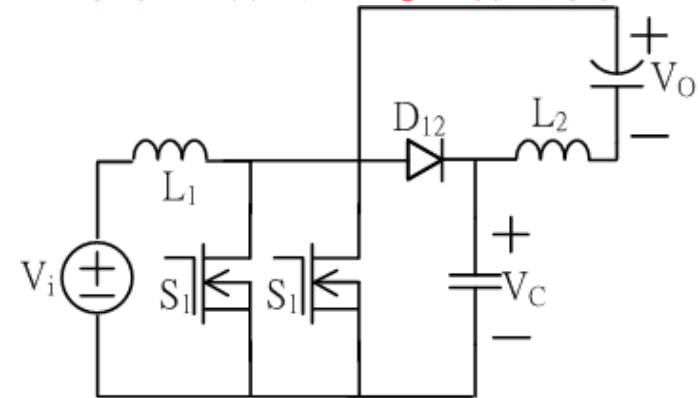





Illustration of Boost + Buck with Grafted Diodes




(a) Boost+Buck



(c)

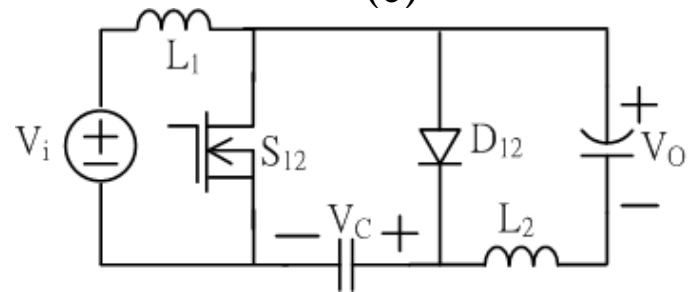

(d)

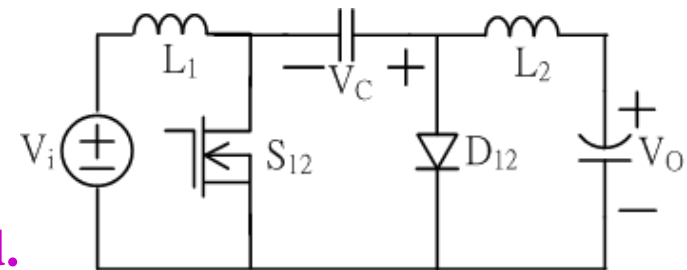

(e) Ćuk (Boost-Buck)

Since $V_X = V_Y$, D_{B1} and D_{B2} can be shorted.

Fig. 31.



V. Layer Scheme

➤ Derivation of Buck-Boost and Zeta Converters



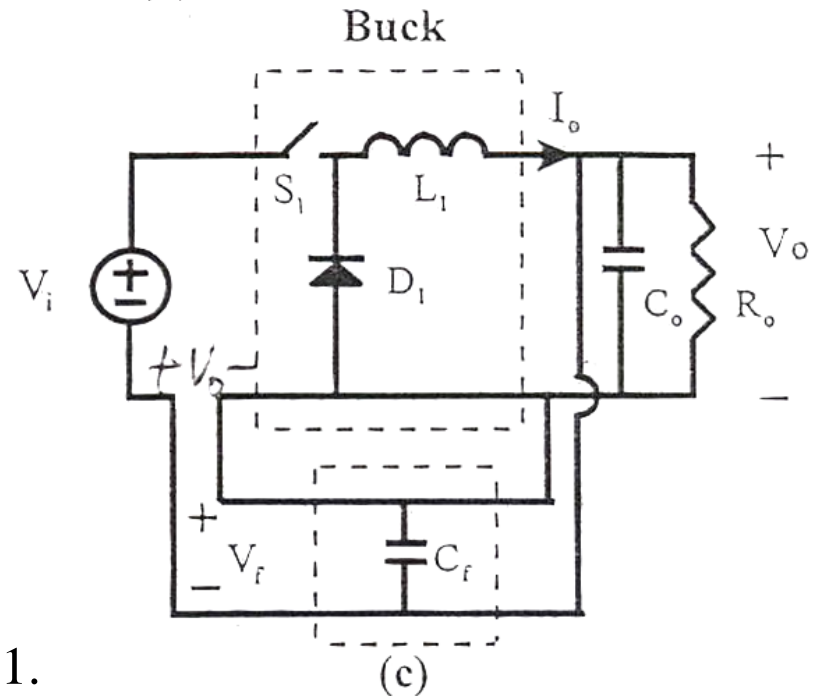
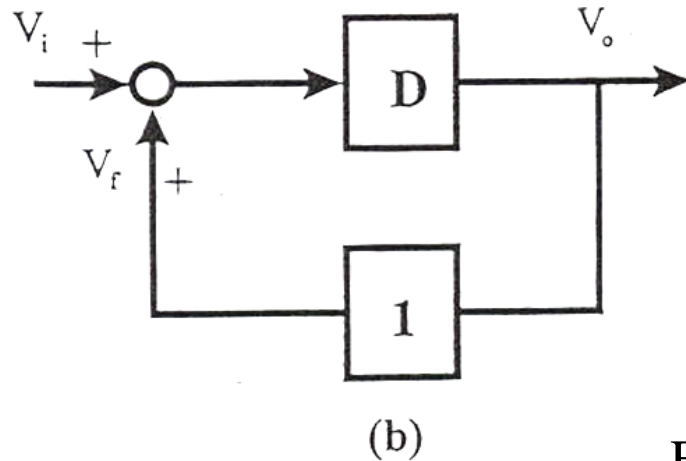
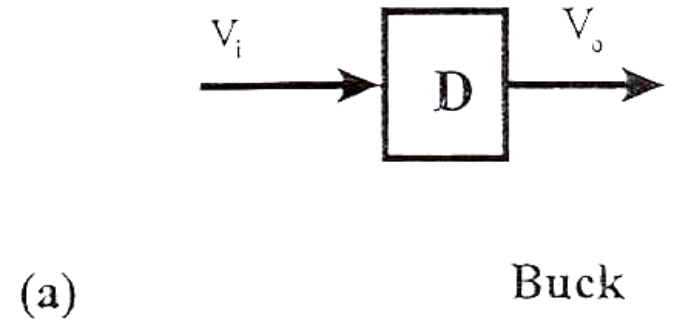
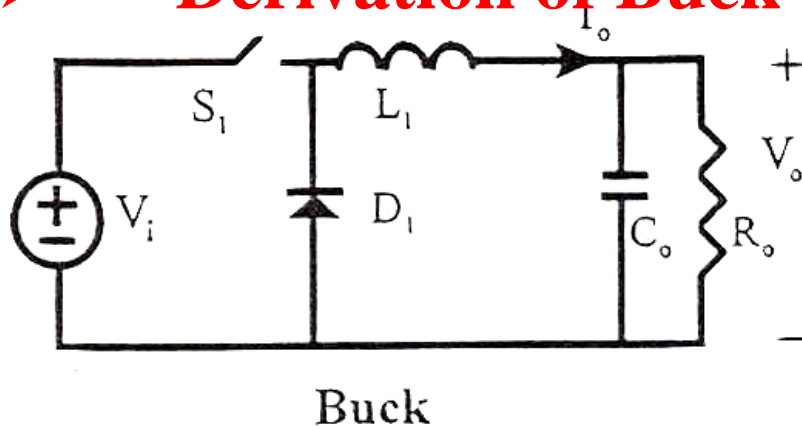
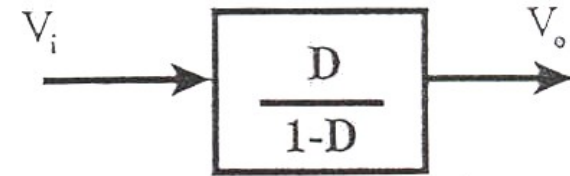



Fig. 1.

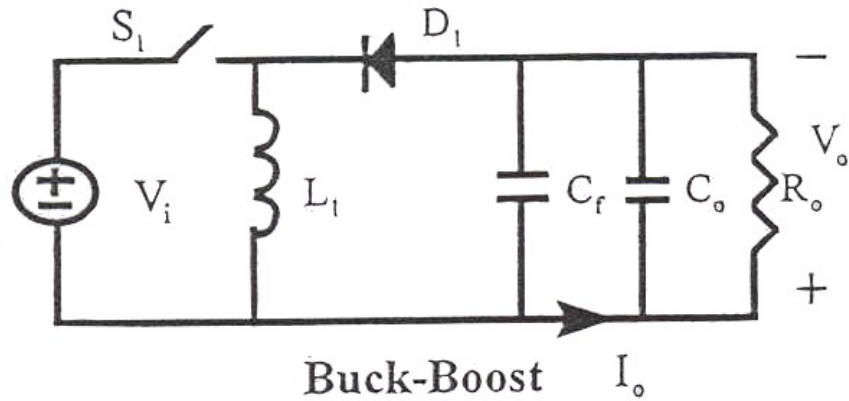

(d)

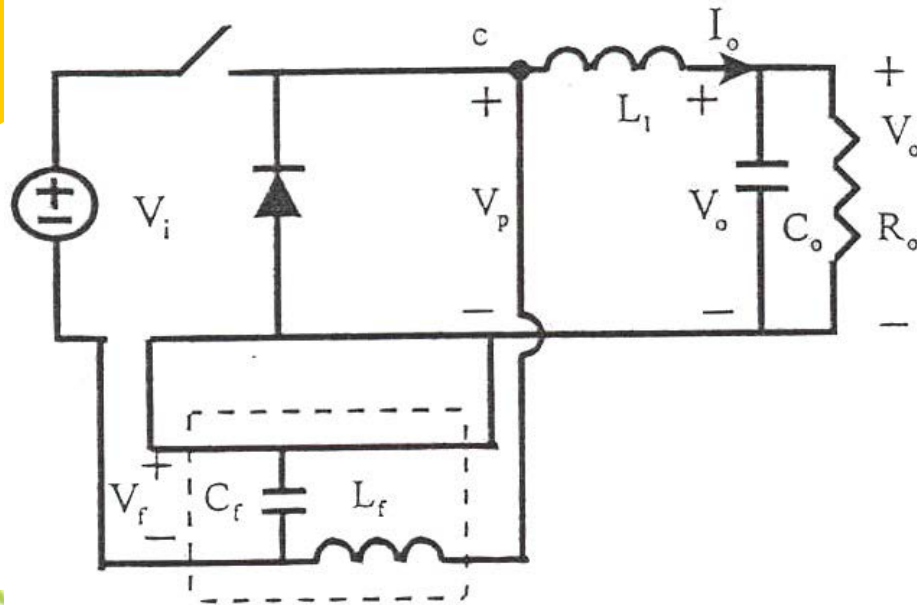

(e)

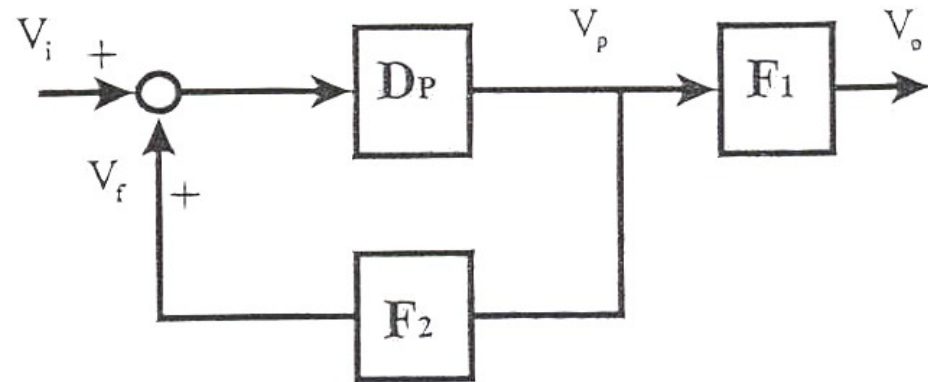

(f)

Fig. 1. (continued)

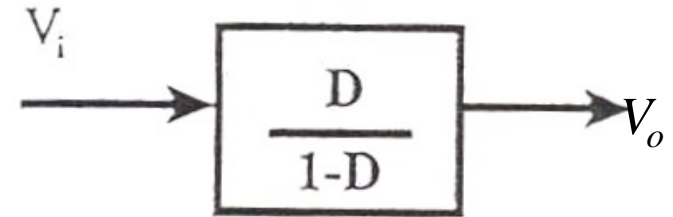
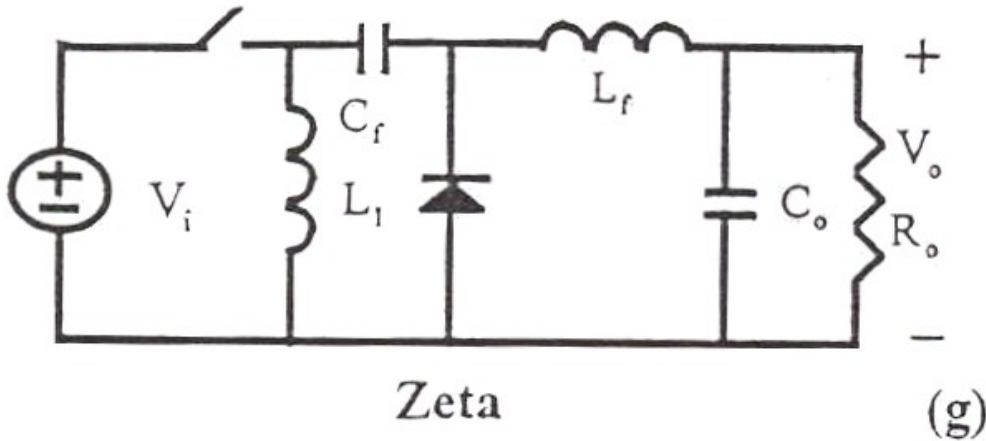


Fig. 1. (continued)

$$\frac{V_o}{V_i} = \frac{D_p F_1}{1 - D_p F_2}$$


Let $F_1 = F_2$,

at dc,


$$\frac{V_o}{V_i} = \frac{D}{1 - D}$$




Derivation of Ćuk and Sepic Converters

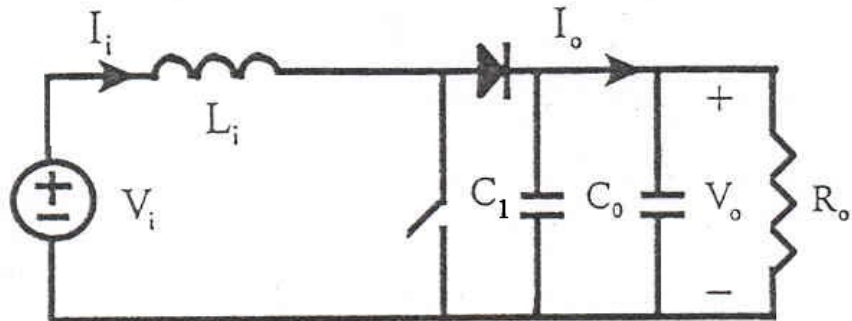


Boost

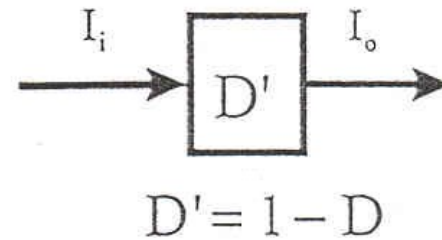

$$D' = 1 - D$$

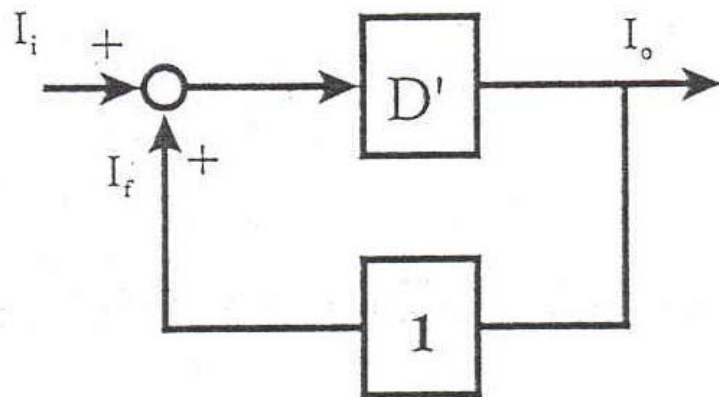


(b)


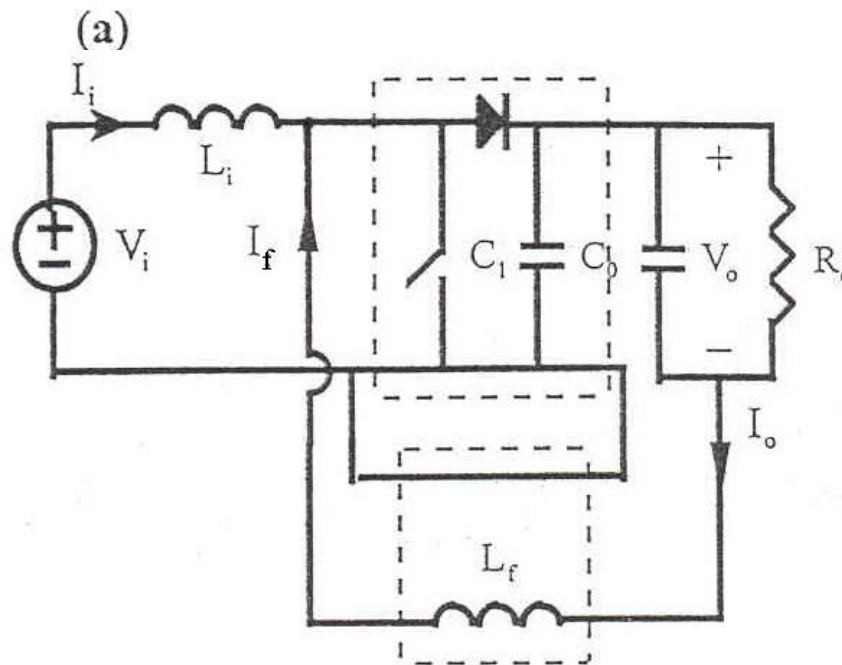


(c)


Fig. 2.

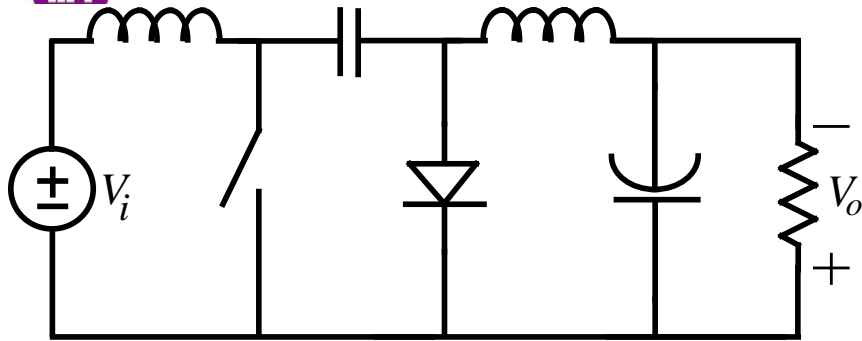

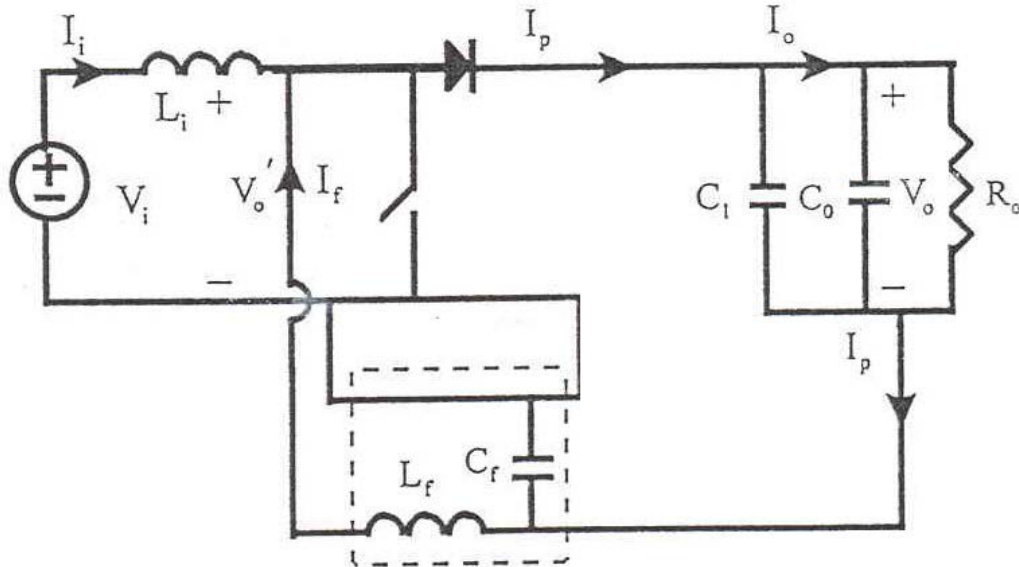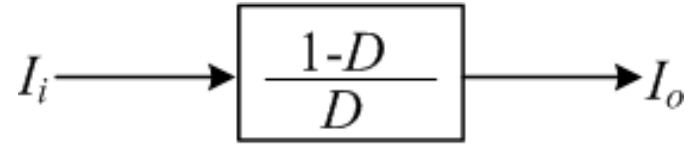Cuk Converter $\frac{V_o}{V_i} = \frac{D}{1-D}$ (d)



(e)

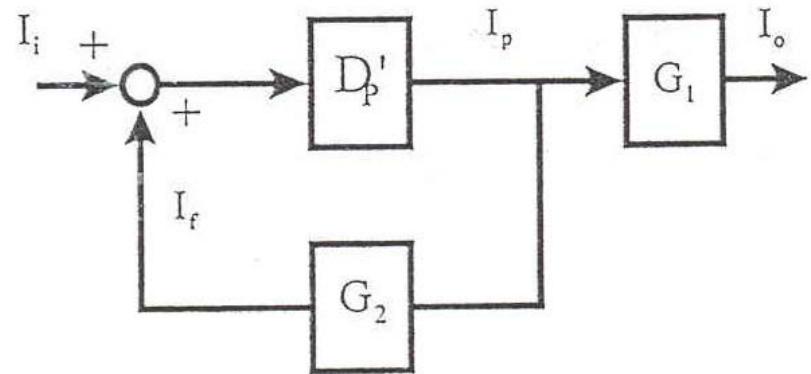

(f)

Fig. 2. (continued)

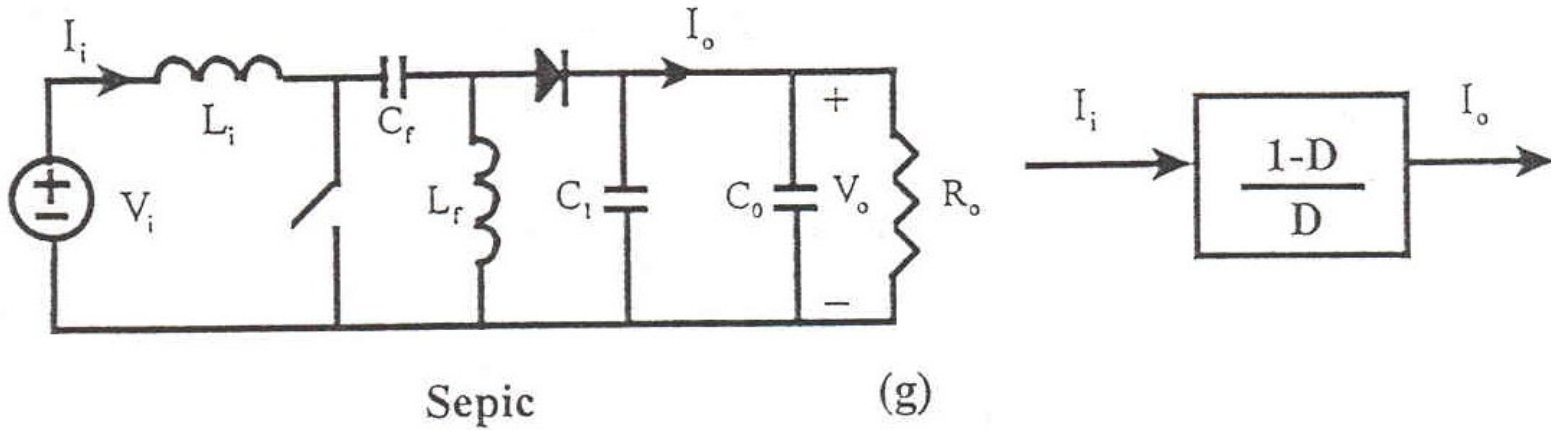


Fig. 2. (continued)

$$\frac{I_o}{I_i} = \frac{D'_p G_1}{1 - D'_p G_2}$$

By power conservation,

$$V_i I_i = V_o I_o,$$

Let $G_1 = G_2$,

we have

at dc,

$$\frac{I_o}{I_i} = \frac{D'}{1 - D'} = \frac{1 - D}{D}.$$

$$\frac{V_o}{V_i} = \frac{D}{1 - D}.$$



Universal forms of buck-family and boost-family Converters

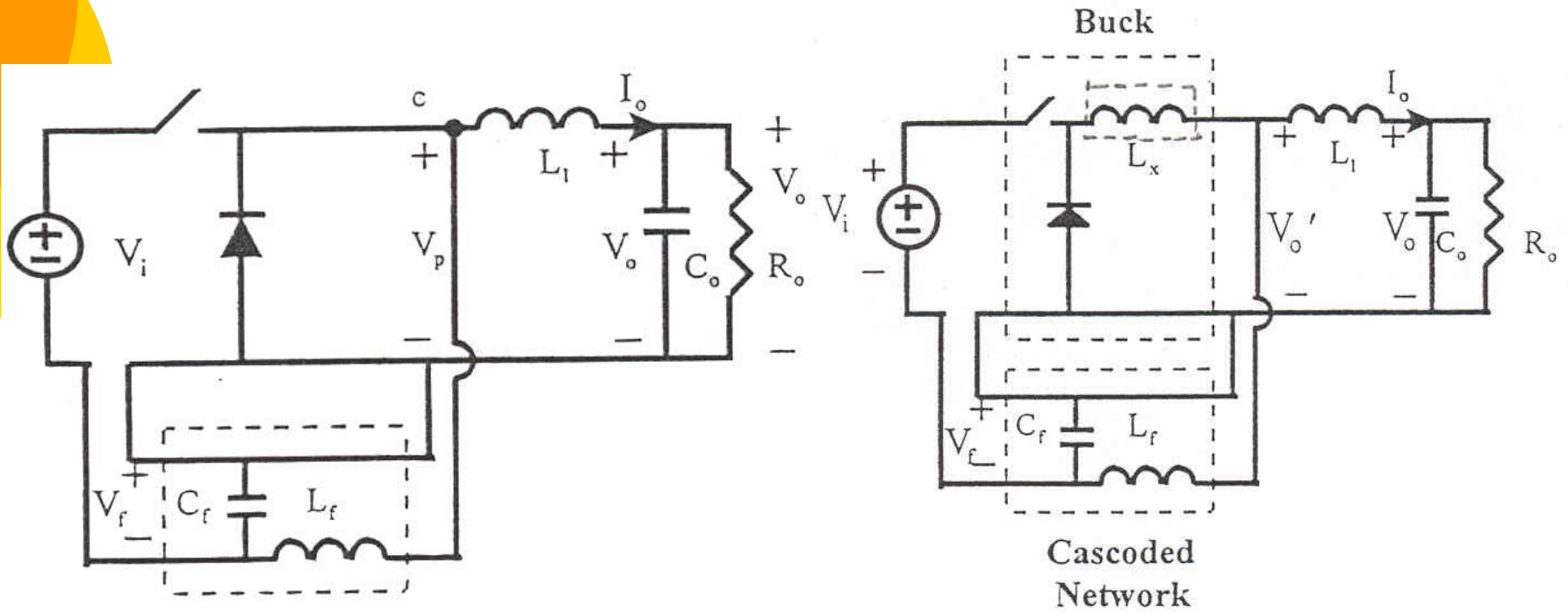


Fig. 3.

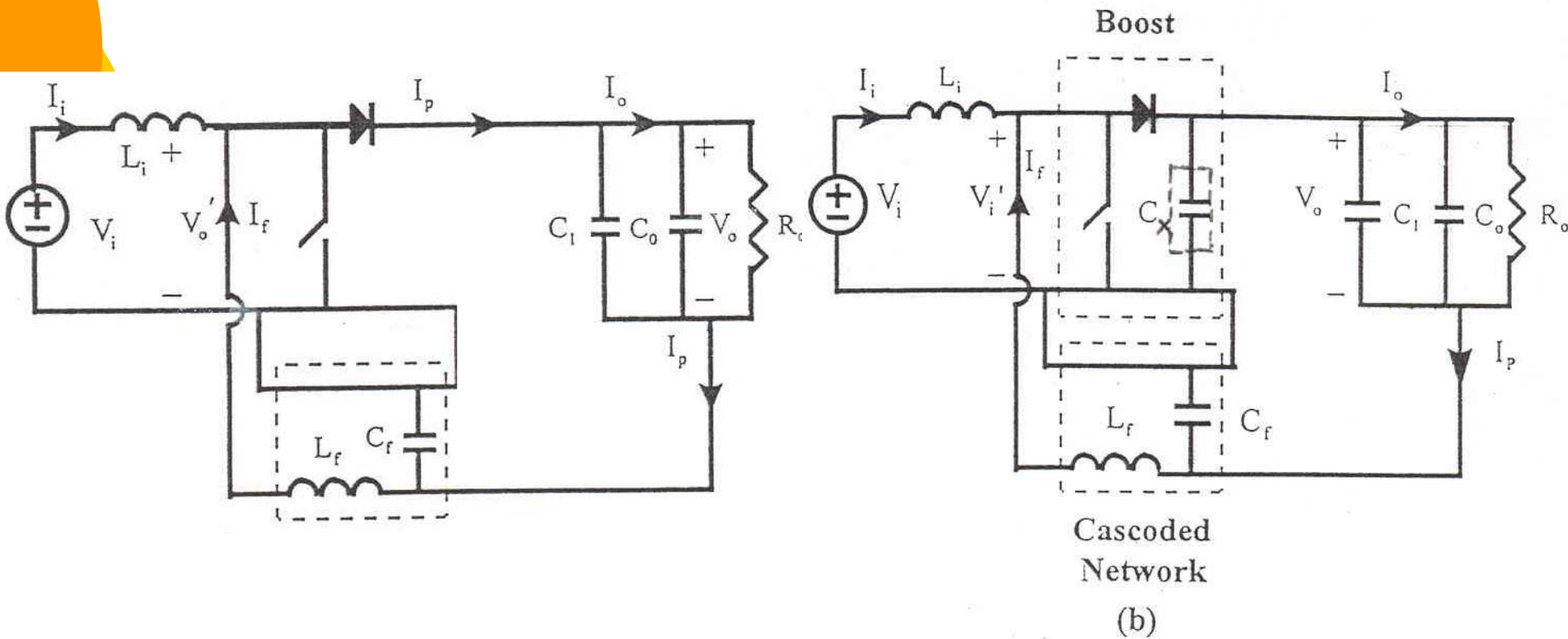



Fig. 3 (continued).




VI. Decoding and Synthesizing PWM Converters

➤ Some Fundamentals

A. Original Converter

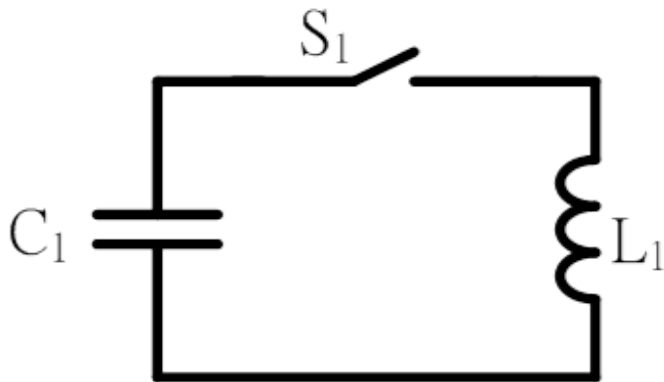

(a)

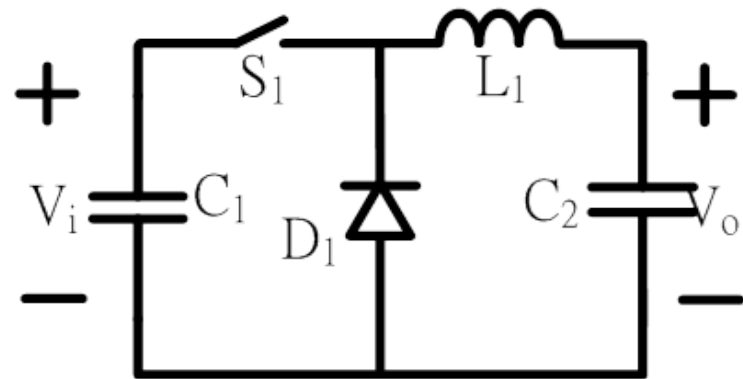


(b)




B. Diode Degeneration





A.

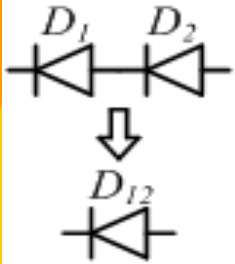





B.

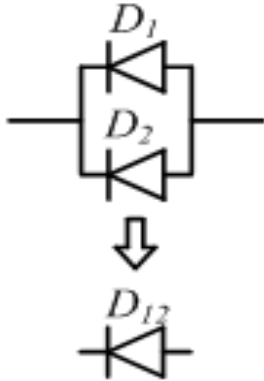

C.

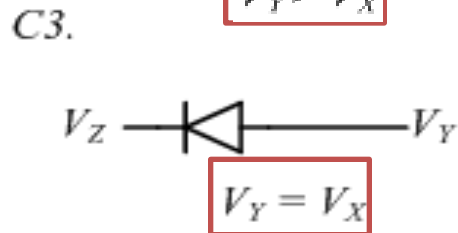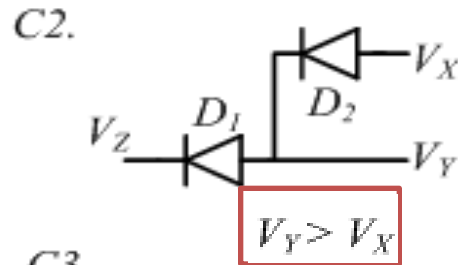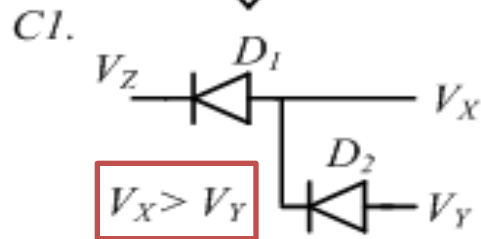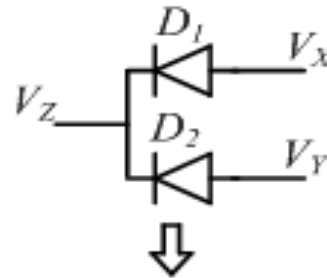

D.

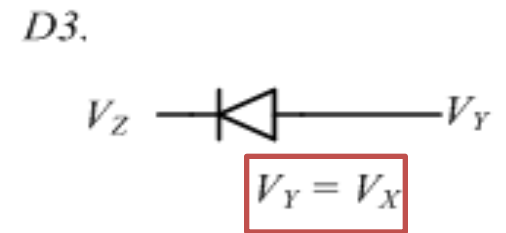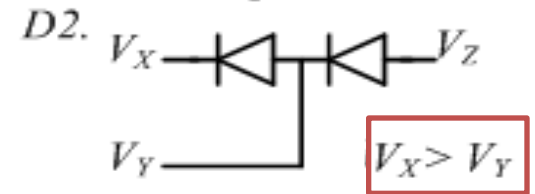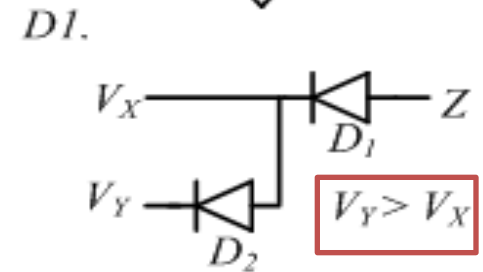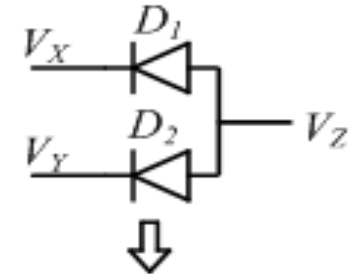



C. DC Voltage/Current Offsetting

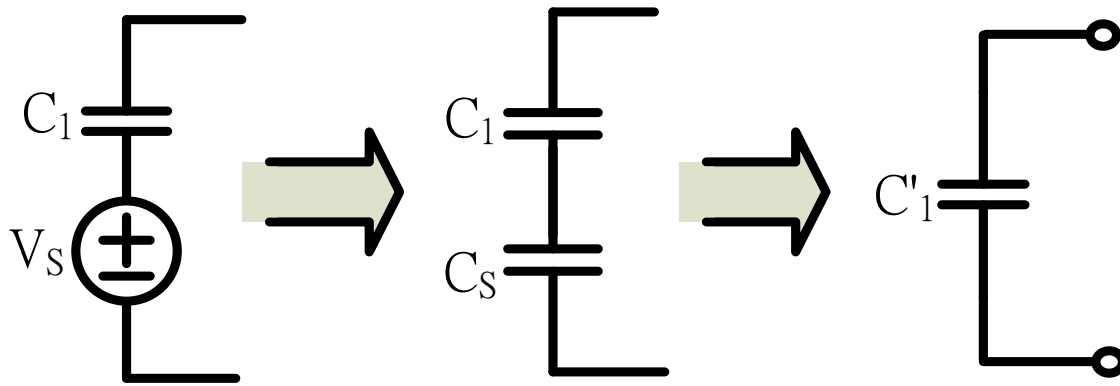


Fig. 4. A voltage source in series with a capacitor is equivalent to a single capacitor with a dc-offset voltage.

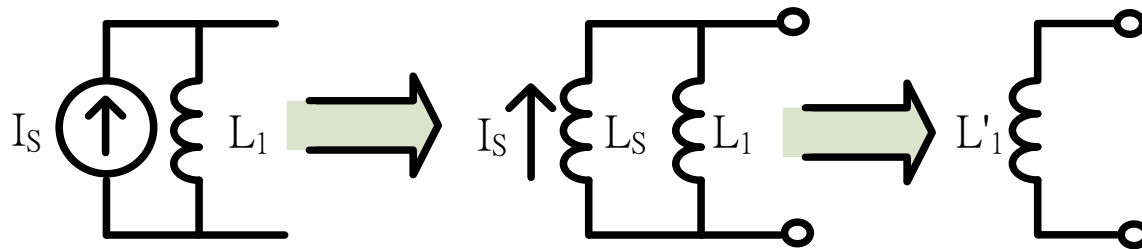


Fig. 5. A current source in parallel with an inductor is equivalent to a single inductor with a dc-offset current.

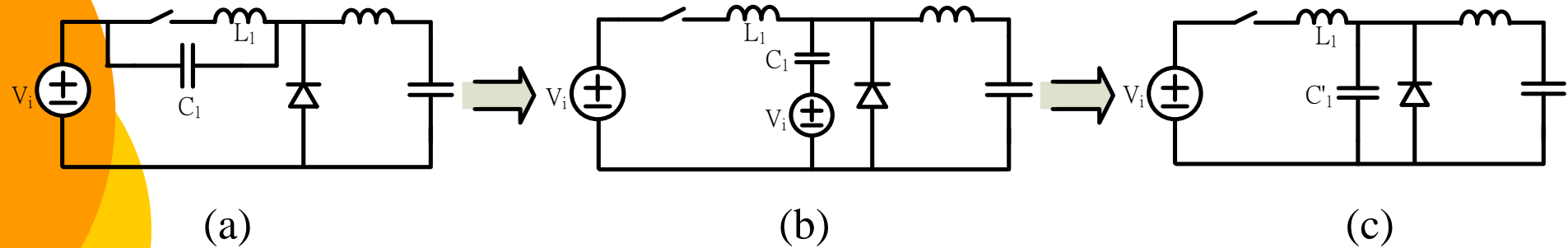


Fig. 6. Illustration of capacitor C_1 with different dc-offset voltages in a quasi-resonant buck converter.

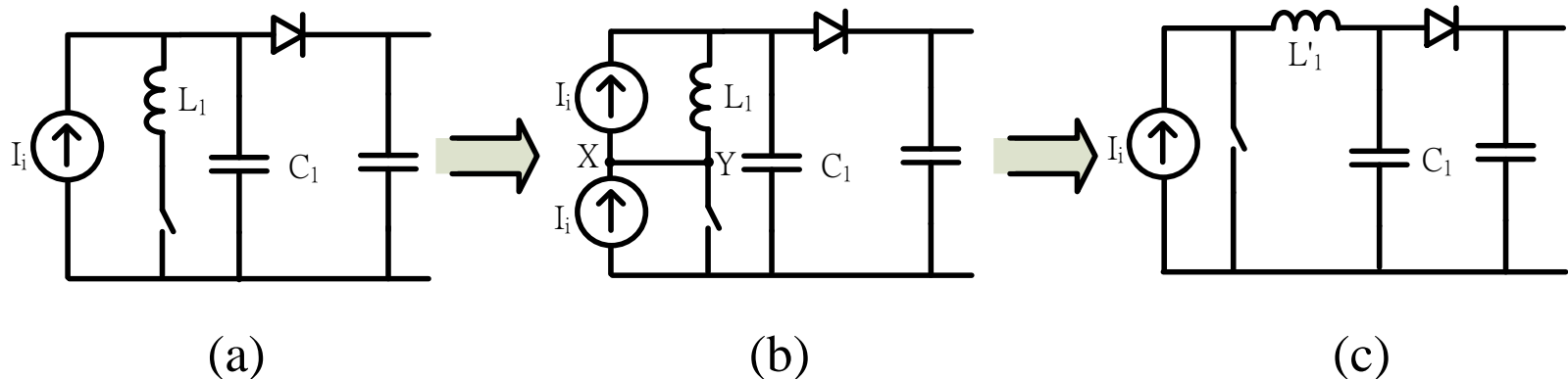


Fig. 7. Illustration of inductor L_1 with different dc-offset currents in a quasi-resonant boost converter.



D. Capacitor/Inductor Component Splitting

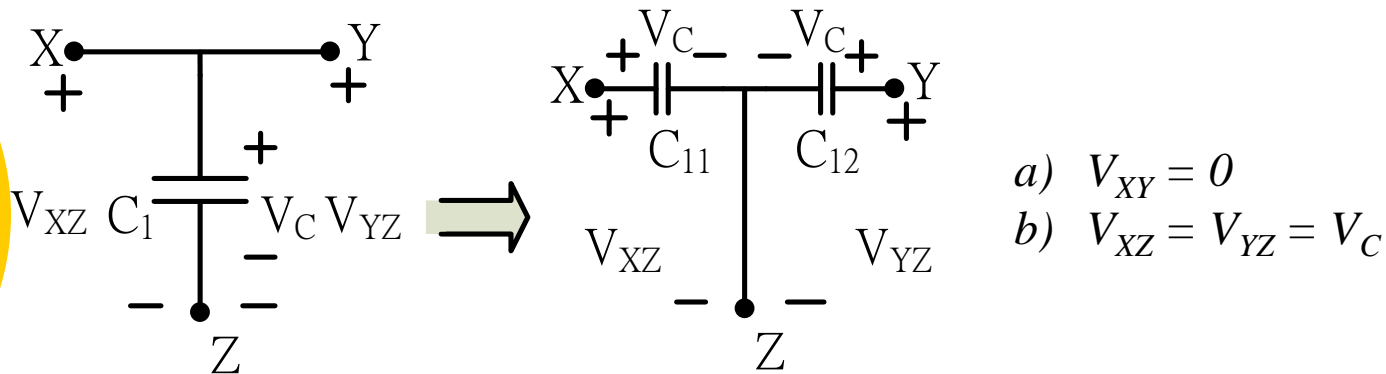


Fig. 8. A capacitor is split into two capacitors with identical node voltages.

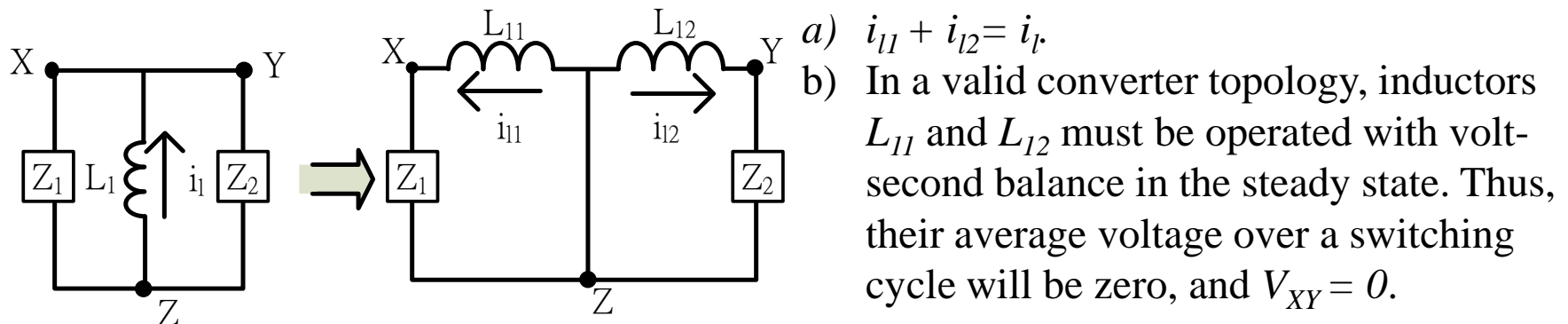



Fig. 9. An inductor is split into two inductors with identical total current and node voltages.




Three Fundamental PWM Converter

A. CCM Operation


$$\frac{V'_o}{V_i} = 1 - D$$

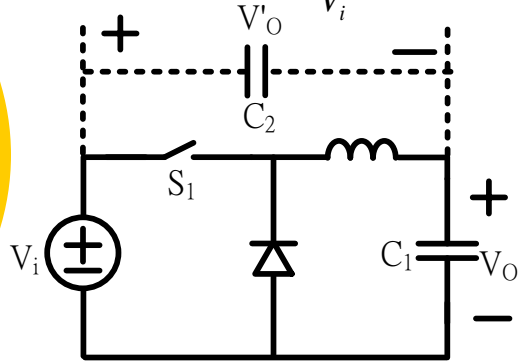


(a) buck: $\frac{V_o}{V_i} = D$

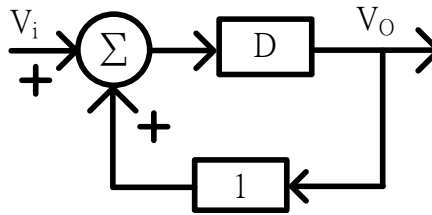

(b) $\frac{V_o}{V_i} = \frac{D}{1 - D}$

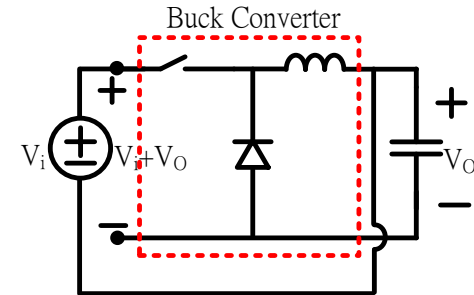


(c)

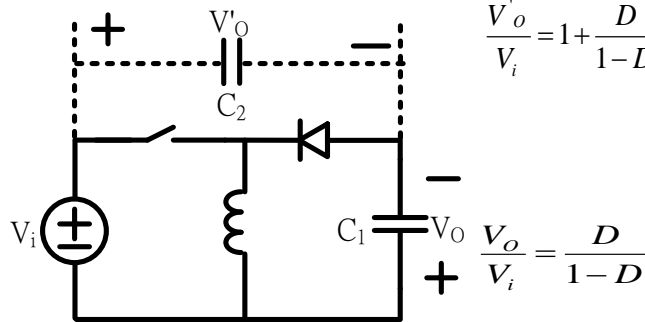

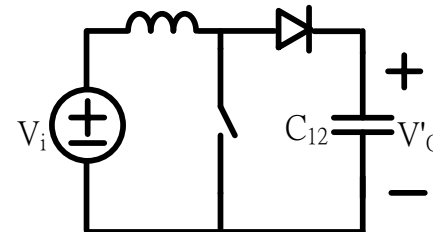(d) buck-boost: $\frac{V_o}{V_i} = \frac{D}{1 - D}$

$$\frac{V'_o}{V_i} = 1 + \frac{D}{1 - D} = \frac{1}{1 - D}$$



(e) $\frac{V'_o}{V_i} = \frac{1}{1 - D}$

Fig. 10. Decoding and evolution of buck-boost and boost converters from the buck converter.



B. DCM Operation

$$\text{Buck} : \frac{d_1}{d_1 + d_2}$$

$$\text{Boost} : \frac{d_1 + d_2}{d_2}$$

$$\text{Buck-Boost} : \frac{d_1}{d_2}$$




If $d_1 + d_2 = 1$, the operation mode will be CCM.

Thus, CCM is a special case of DCM operation.





- **Inverse Buck, Boost and Buck-Boost**

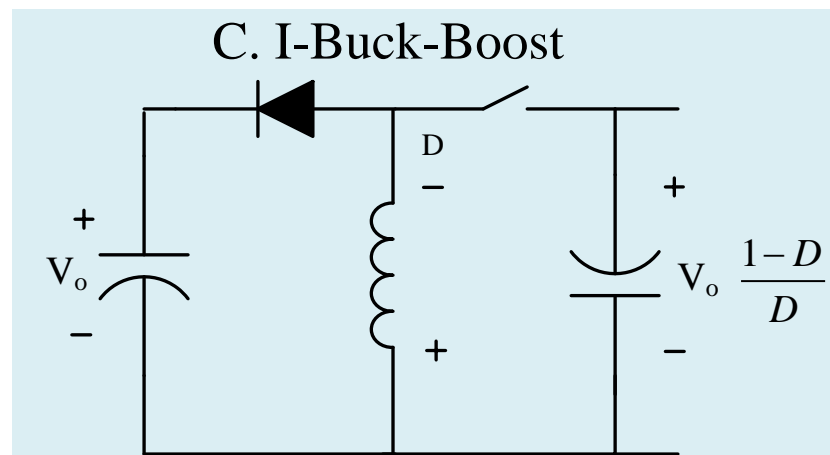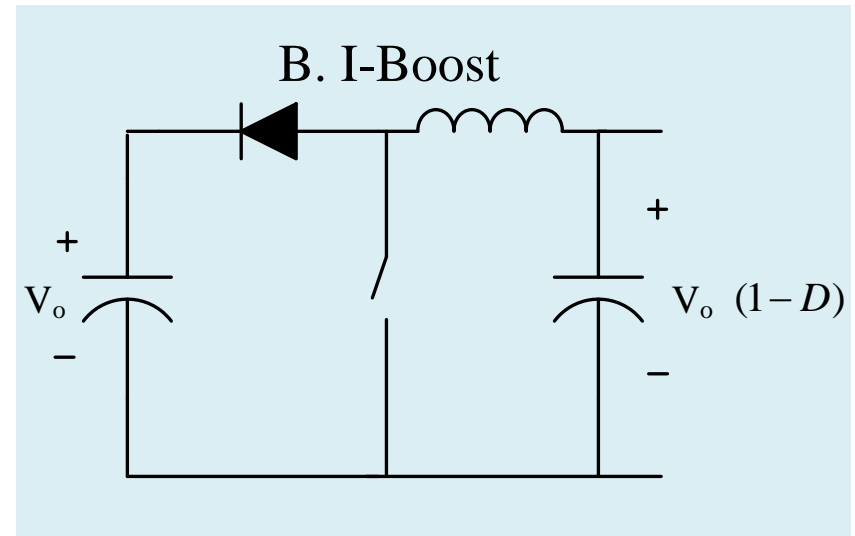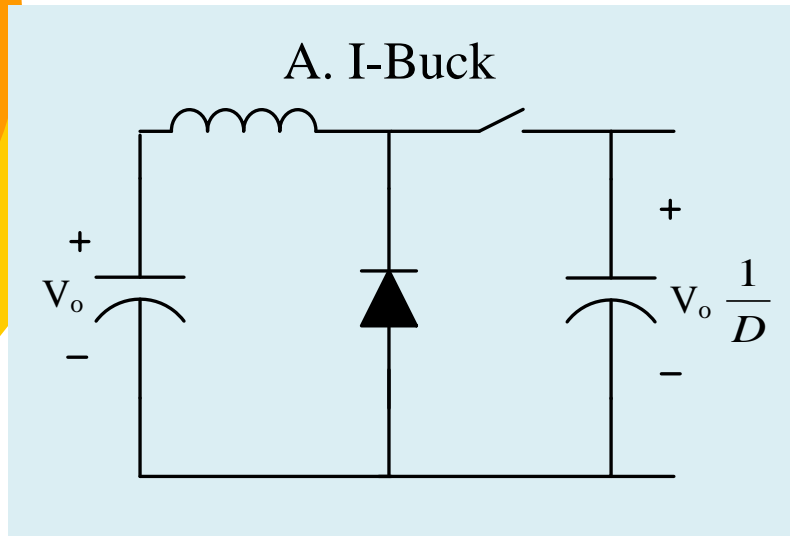



➤ Deduction from Ćuk, SEPIC and Zeta to Buck-Boost Converter (with DC Voltage Offsetting)

A. From Ćuk to Buck-Boost

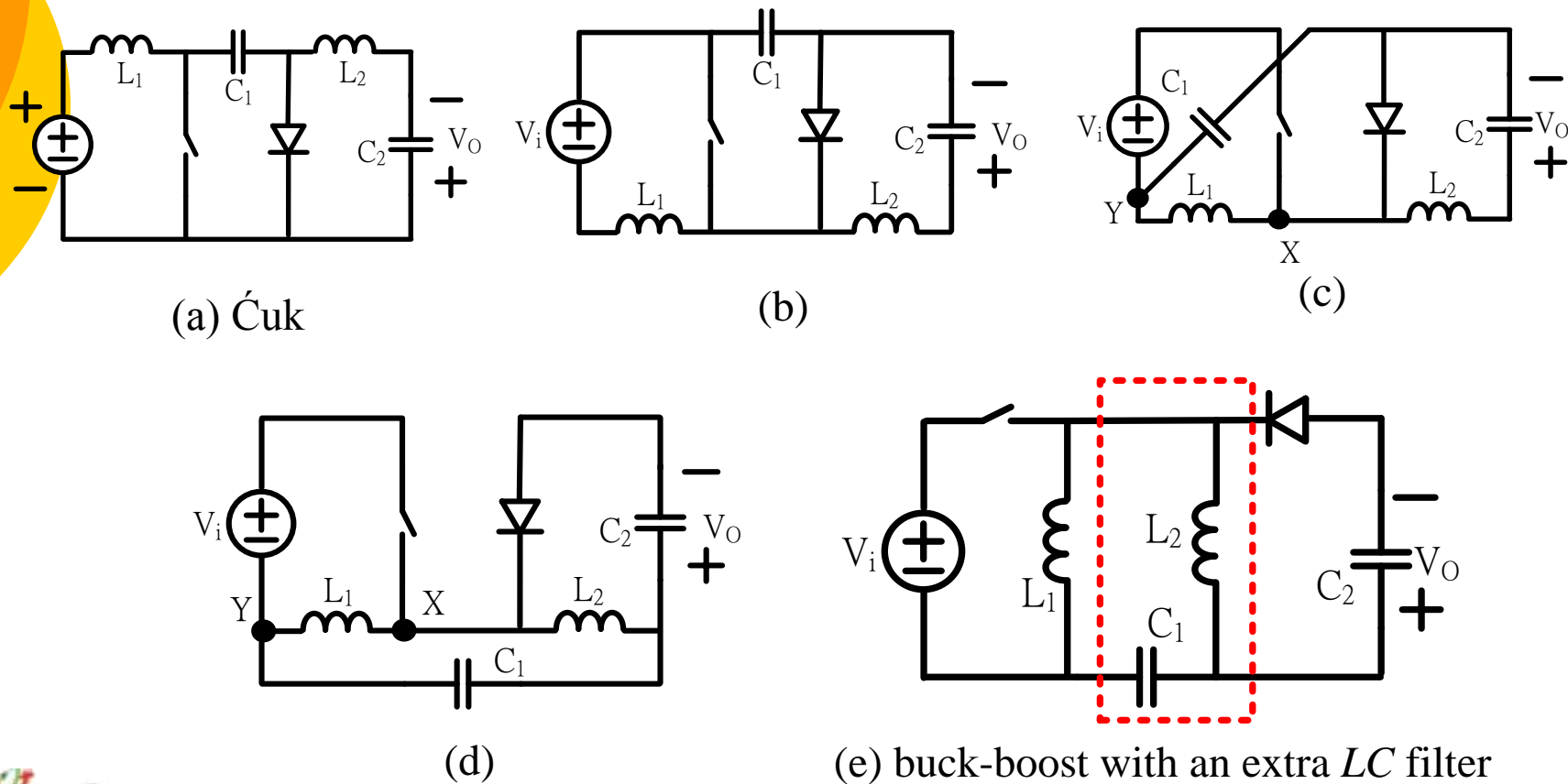


Fig. 11. Deduction from Ćuk to buck-boost converter.



B. From SEPIC to Buck-Boost

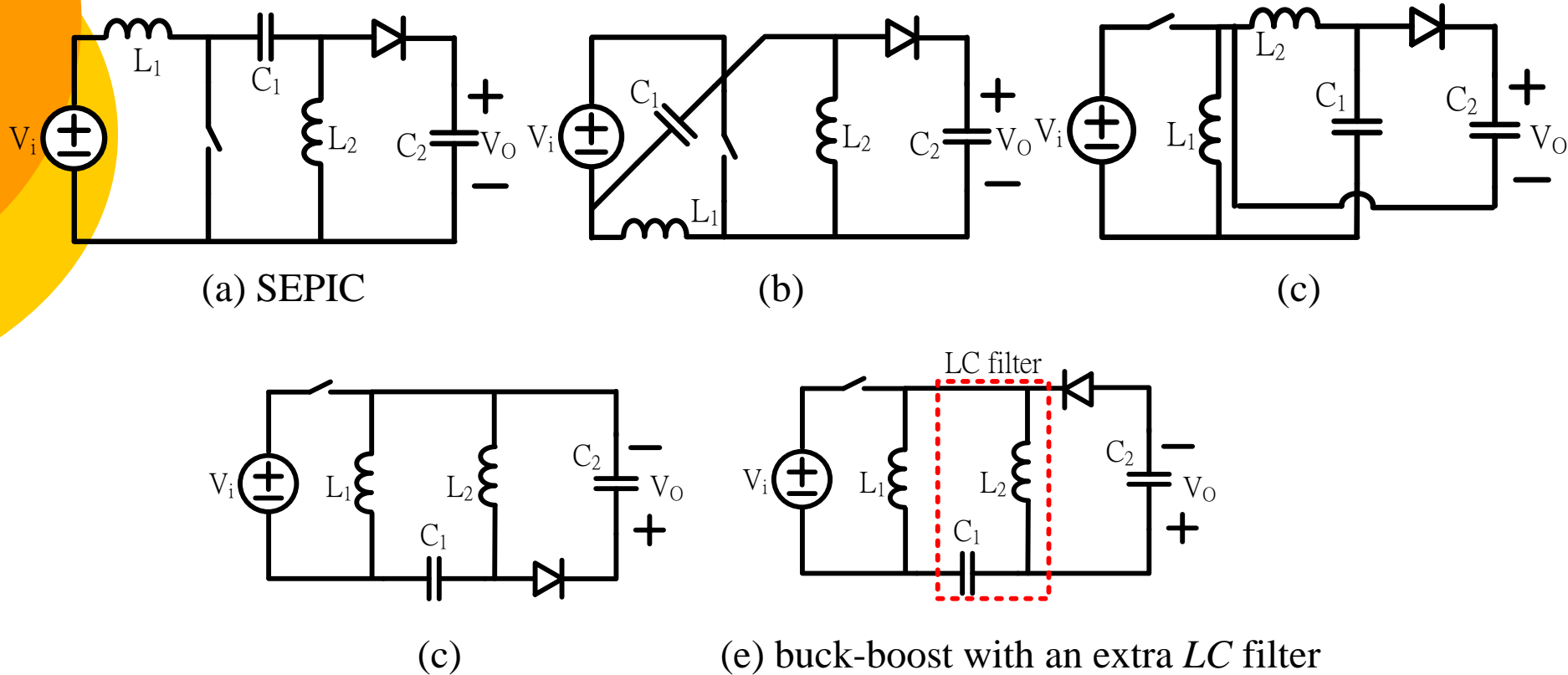


Fig. 12. Deduction from SEPIC to buck-boost converter



C. From Zeta to Buck-Boost

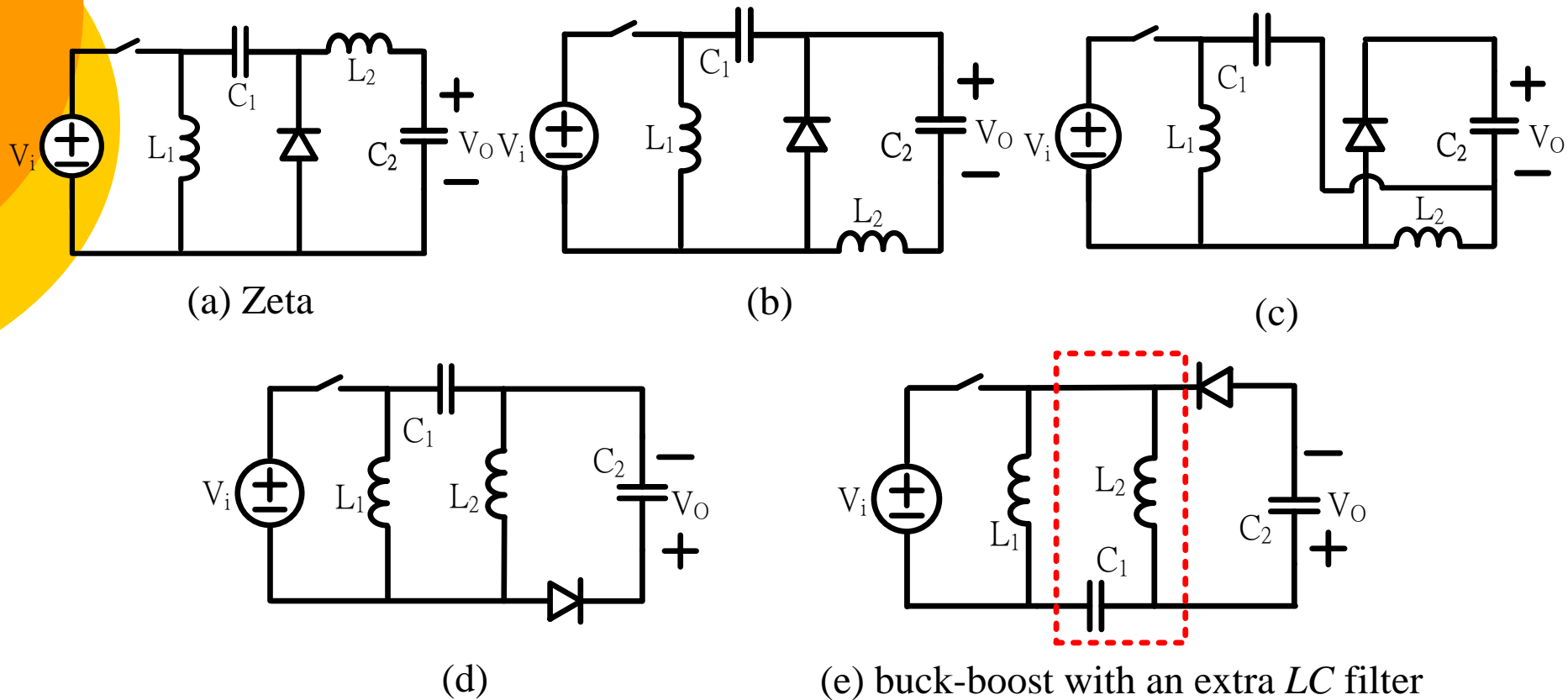


Fig. 13. Deduction from Zeta to buck-boost converter.



D. Deduction from SEPIC to Zeta and Ćuk



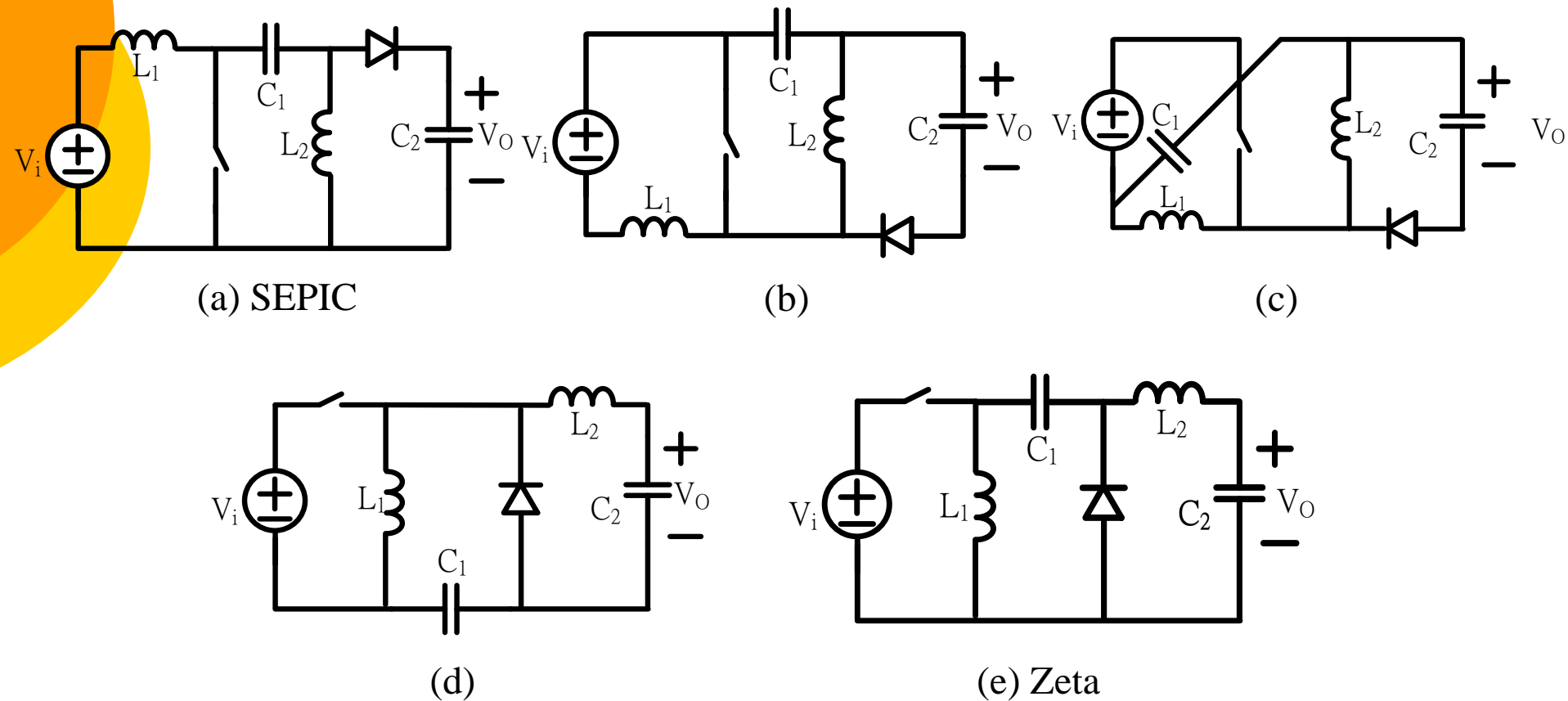



Fig. 14. Evolution of Zeta converter from SEPIC.

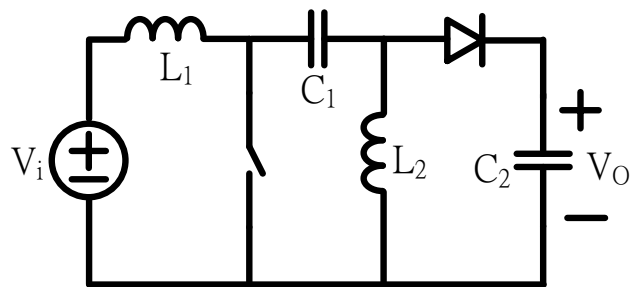


(a) SEPIC

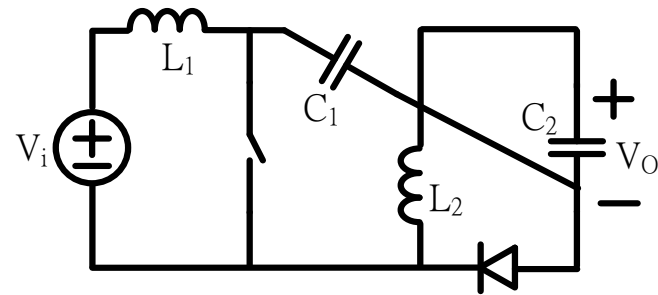

(b)

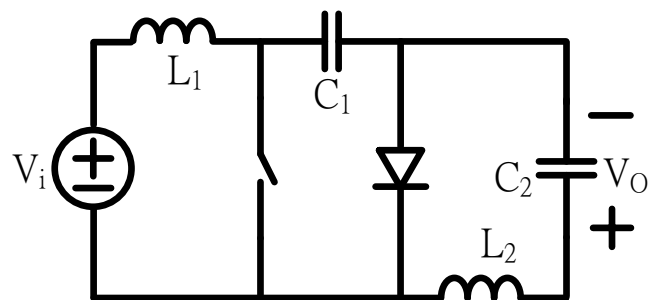

(c)

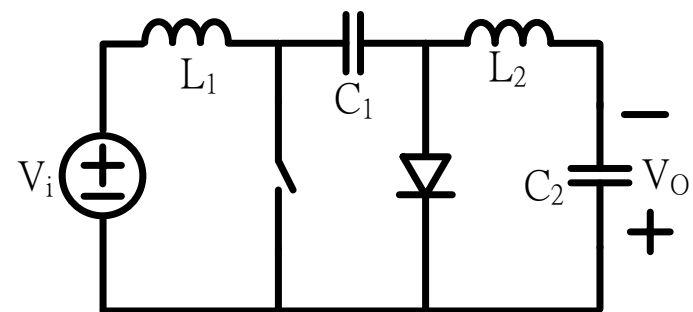

(d) Ćuk

Fig. 15. Evolution of Ćuk converter from SEPIC



➤ Processes of Decoding and Synthesizing

- 1) Using a long division to detach the unity gain from a given transfer gain.

Eg. $f(D) = \frac{V_o}{V_i} = \frac{1-D}{1-2D} = 1 + \frac{D}{1-2D} = 1 + \frac{V'_o}{V_i} = 1 + f_r(D) \quad (1)$

- 2) Conducting a cross multiplication of $V'_o/V_i = f_r(D)$ to find a relationship among V_i , V'_o and D :


$$\frac{V'_o}{V_i} = f_r(D) = \frac{D}{1-2D} \quad \text{Or,} \quad V'_o(1-D) = (V_i + V'_o)D \quad (2)$$

That is,


$$V'_o = (V_i + V'_o) \frac{D}{1-D} \quad (3)$$



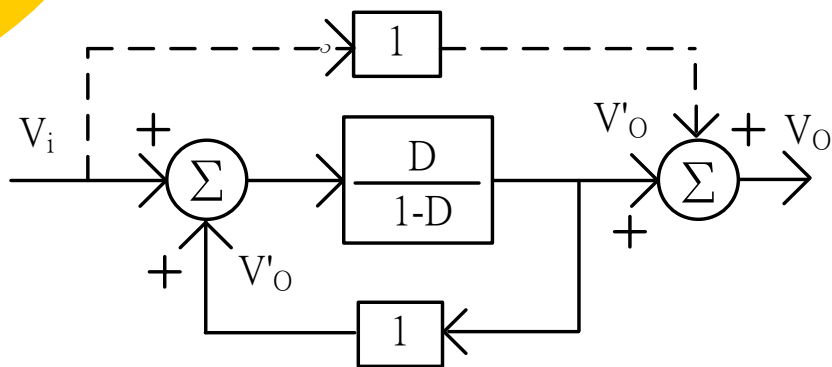- 3) Using a transfer block diagram to illustrate equation (3) and adding up with the unity gain if it exists.
- 4) Synthesizing the transfer block diagram with the original converter and its derived.



(a)

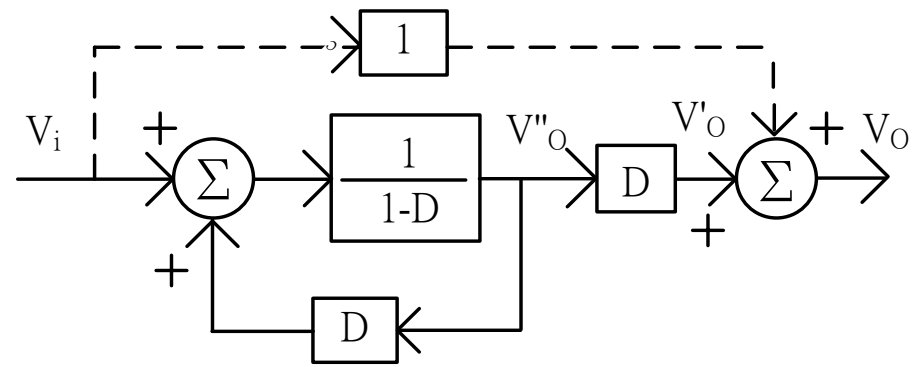

(b)

Fig. 10. Two transfer block diagrams to represent the transfer gain of $V_o/V_i = (1-D)/(1-2D)$.



➤ Decoding and Synthesizing PWM Converters

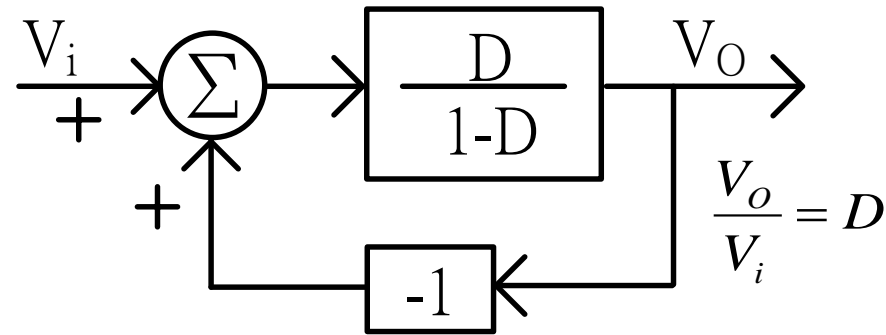


Fig. 16. A buck converter is decoded with $D/(1-D)$ and a negative unity feedback.

1. Synthesizing with Buck-Boost


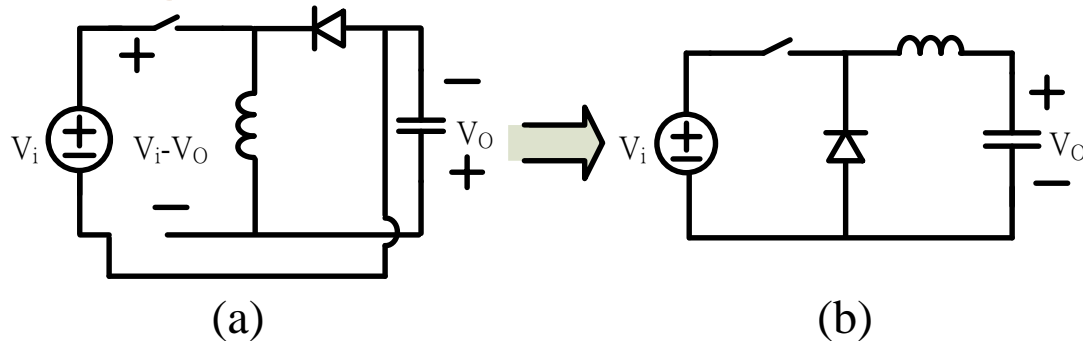



Fig. 17. Derivation of the buck converter from the decoded form shown in Fig. 16 and the buck-boost converter.

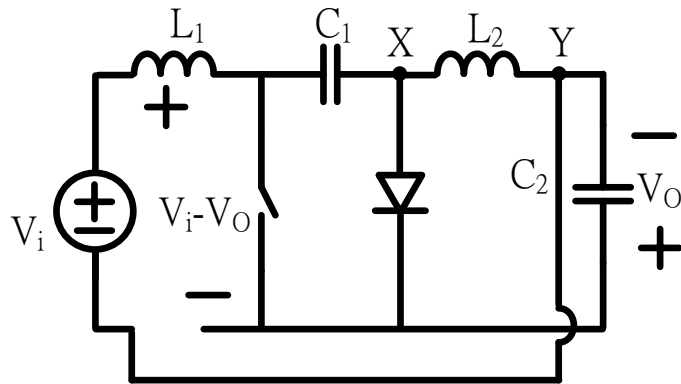


2. Synthesizing with Ćuk




(a)

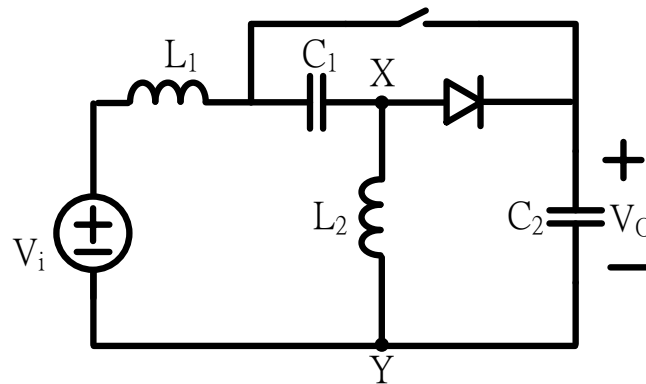

(b)

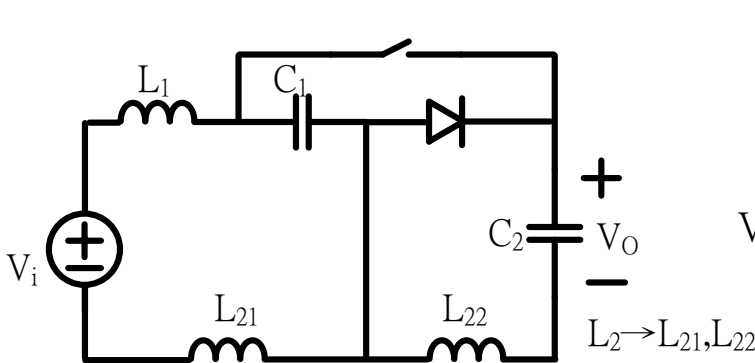

(c)

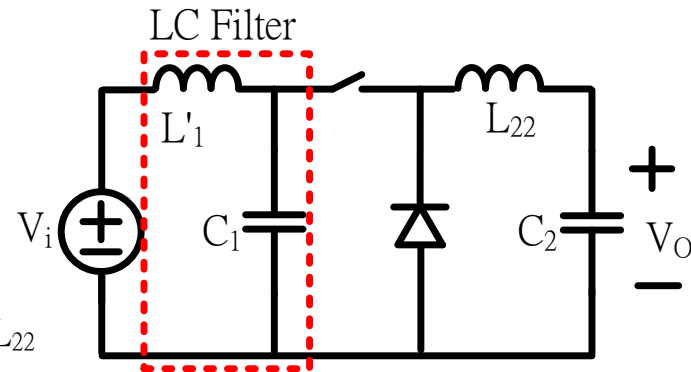

(d) buck with an extra *LC* filter

Fig. 18. Derivation of buck converter from the decoded form shown in Fig. 16 and the Ćuk converter.



A. Voltage-Fed Z-Source Converter

- **Decoding $(1-D)/(1-2D)$**

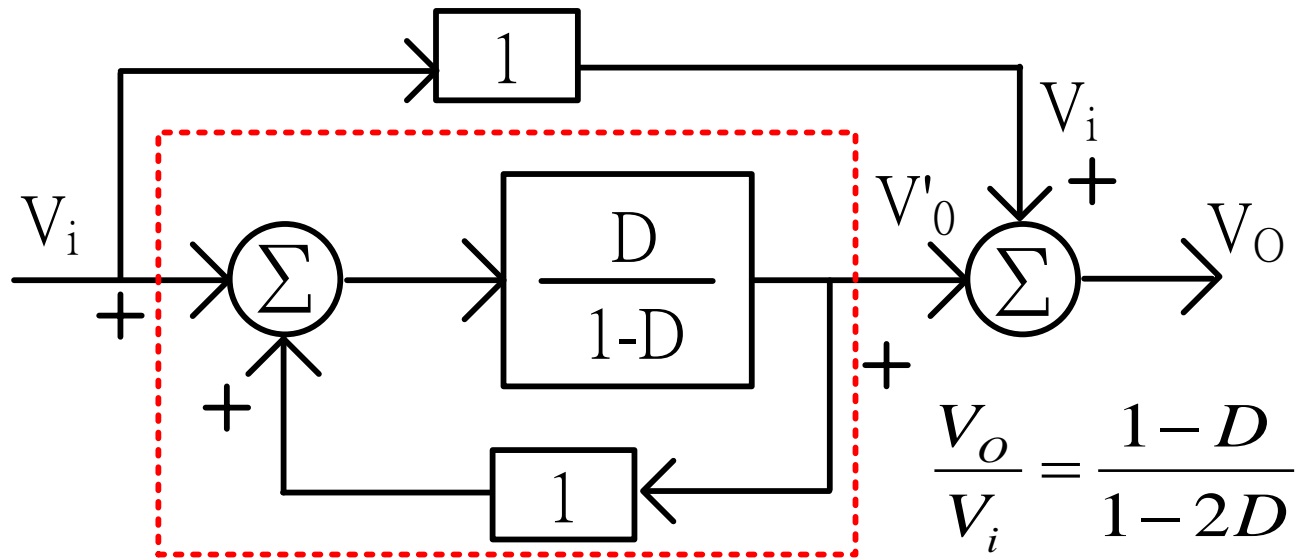


Fig. 19. A transfer block diagram to decode $V_o/V_i = (1-D)/(1-2D)$



• Synthesizing with **SEPIC**


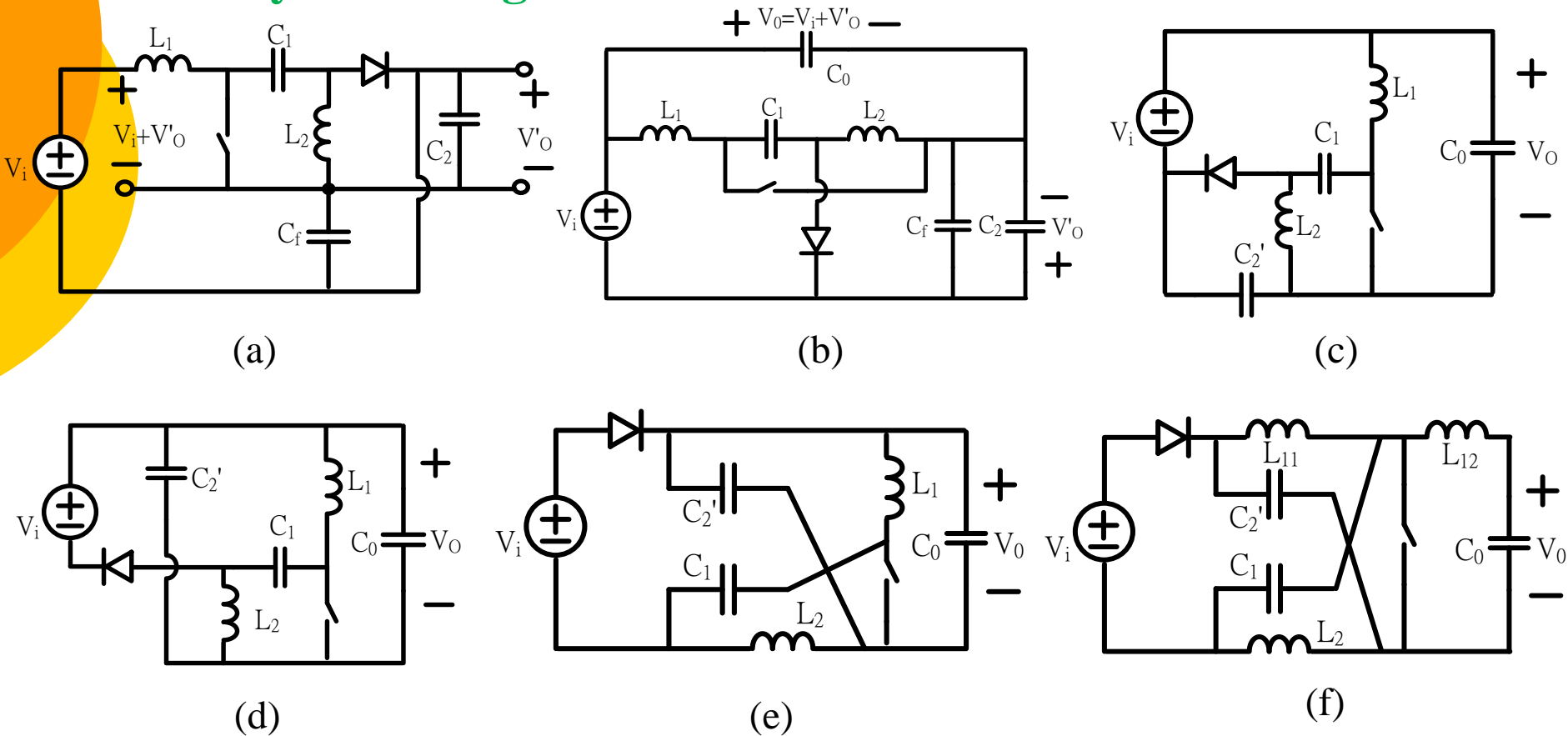



Fig. 20. Synthesizing the transfer block diagram shown in Fig. 19 with the SEPIC converter.

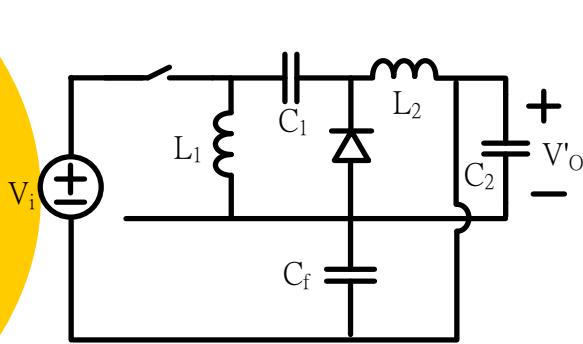


• Synthesizing with **Zeta**




(a)

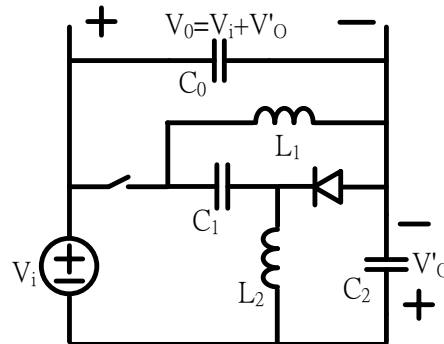


(b)

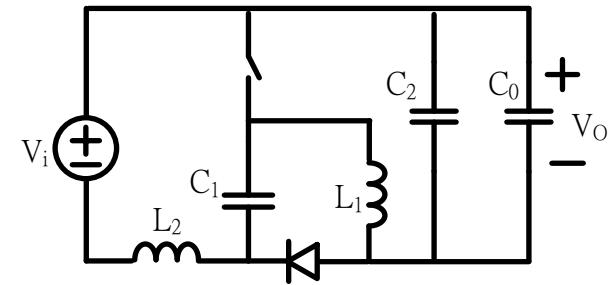


(c)

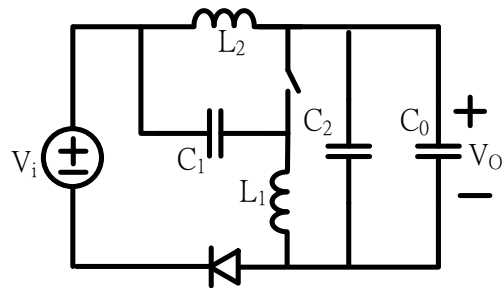

(d)

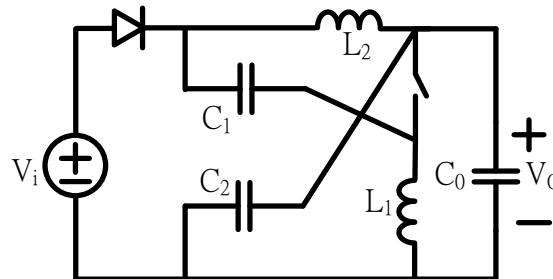

(e)

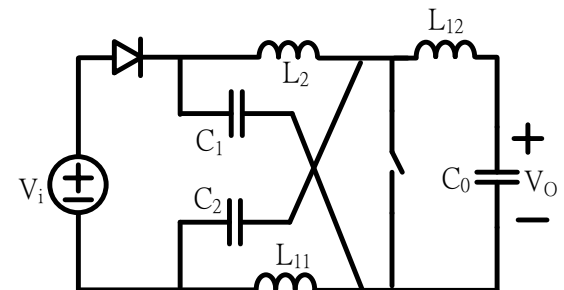

(f)

Fig. 21. Synthesizing the transfer block diagram shown in Fig. 19 with the Zeta converter



B. Current-Fed Z-Source Converter

- Synthesizing with **SEPIC**


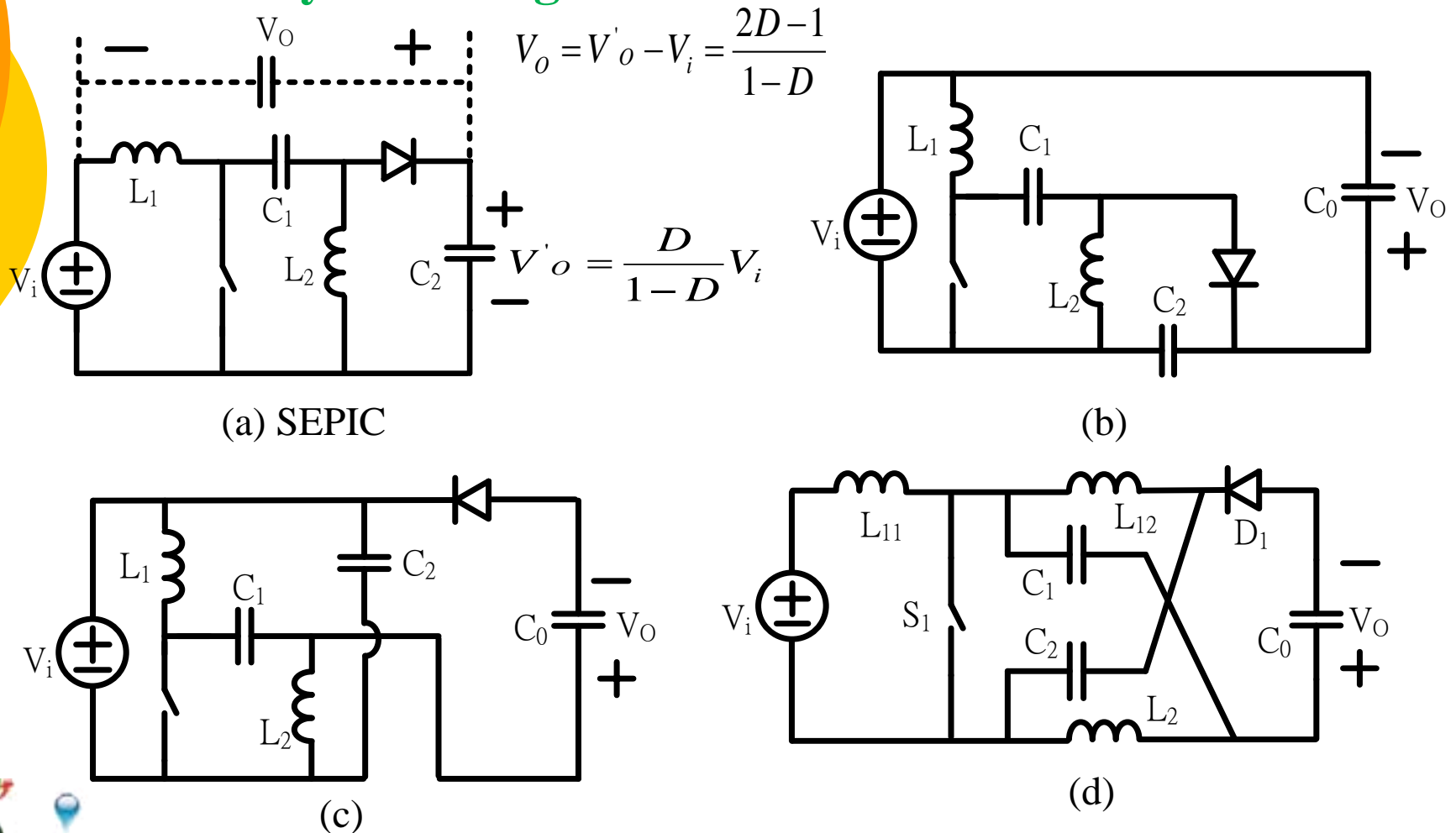



Fig. 22. Synthesizing the transfer gain $V_o/V_i = (2D-1)/(1-D)$ with a SEPIC converter

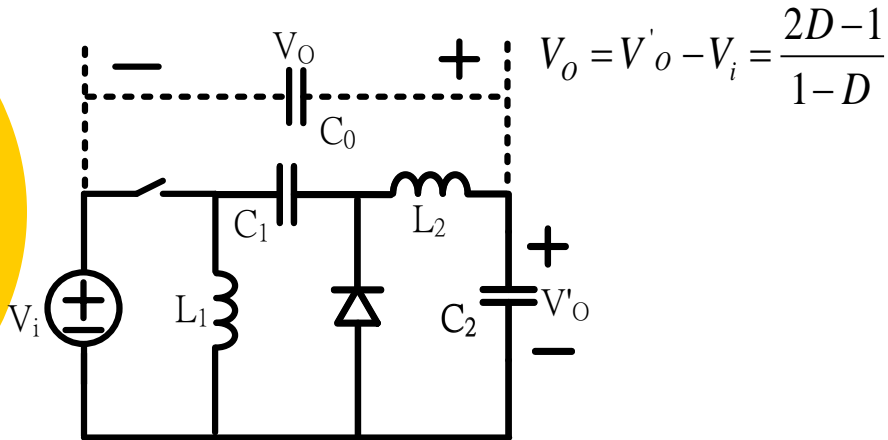


• Synthesizing with Zeta




(a) Zeta

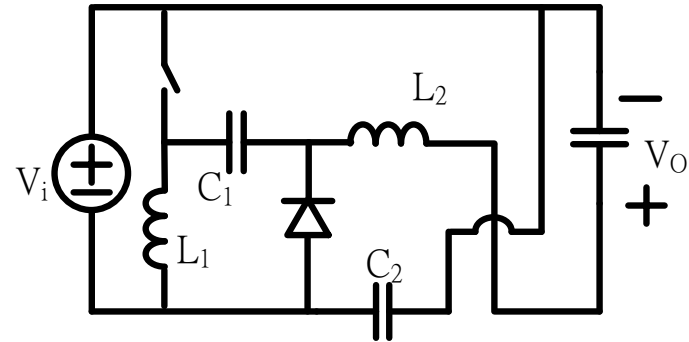

(b)

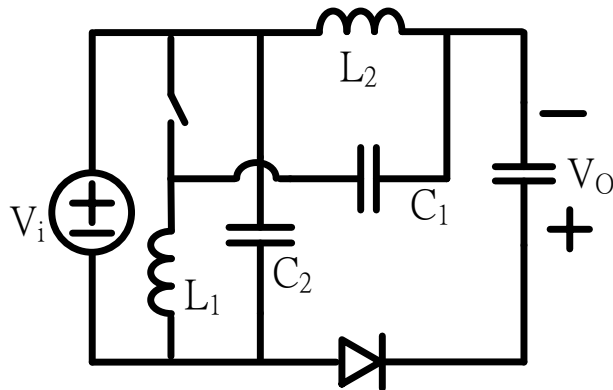

(c)

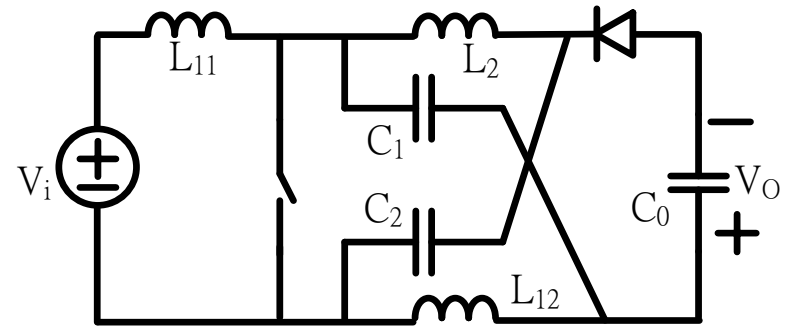

(d)

Fig. 23. Synthesizing the transfer gain $V_o/V_i = (2D-1)/(1-D)$ with a Zeta converter



C. Quasi Z-Source Converter

- Decoding $D/(1-2D)$


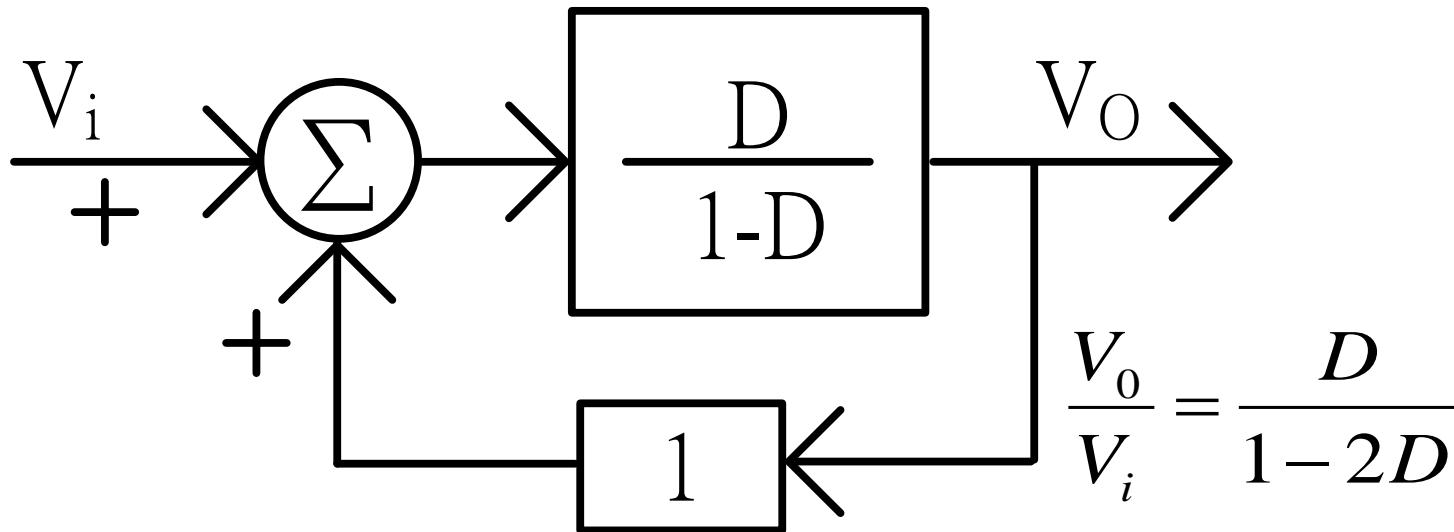



Fig. 24. A transfer gain block of $D/(1-D)$ with a positive unity feedback yielding $V_o/V_i = D/(1-2D)$

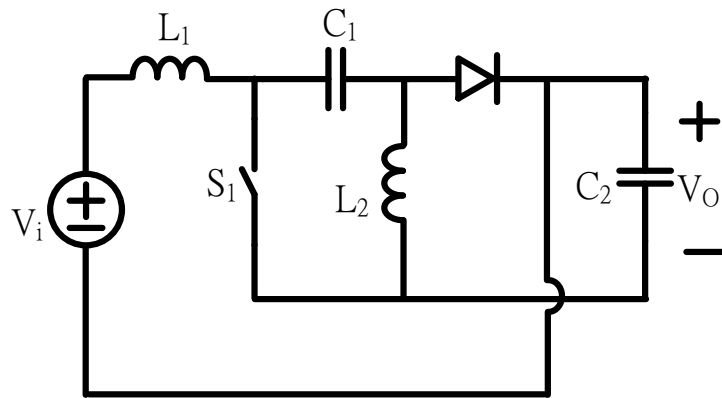


• Synthesizing with **SEPIC**




(a)

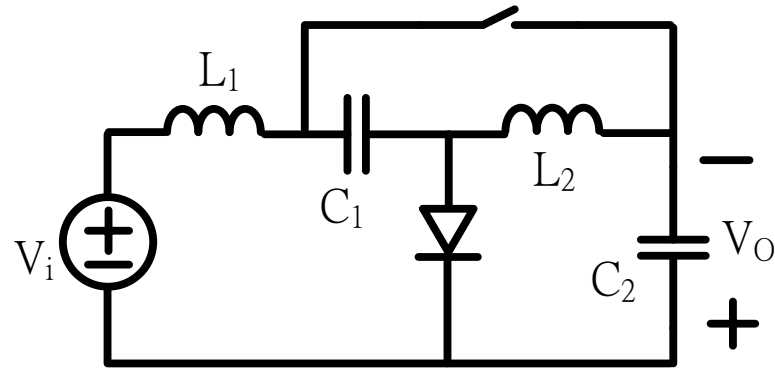

(b)

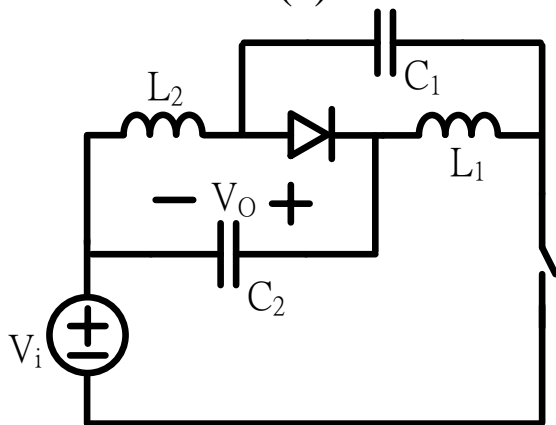

(c)

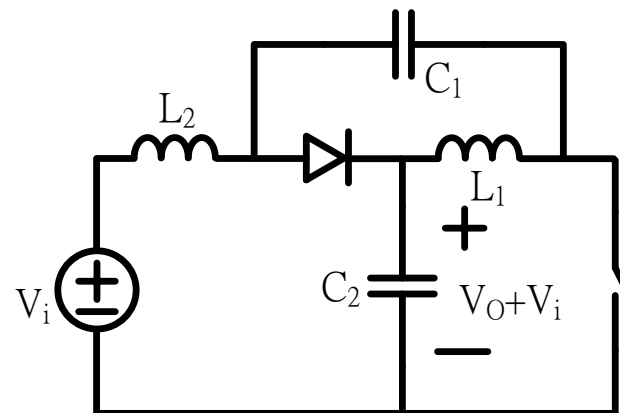


(d)


Fig. 25. Synthesizing $V_o/V_i = D/(1-2D)$ with a SEPIC converter




• Synthesizing with Zeta

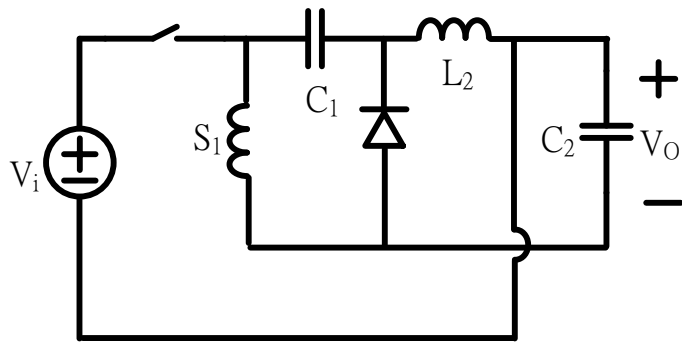


(a)

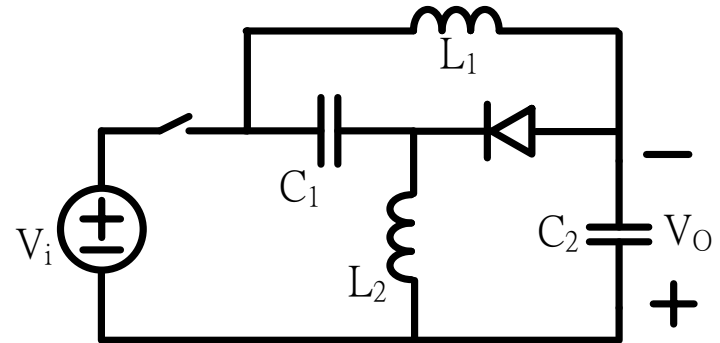

(b)

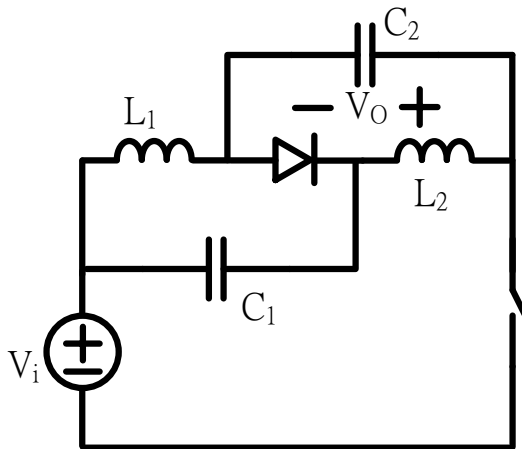

(c)

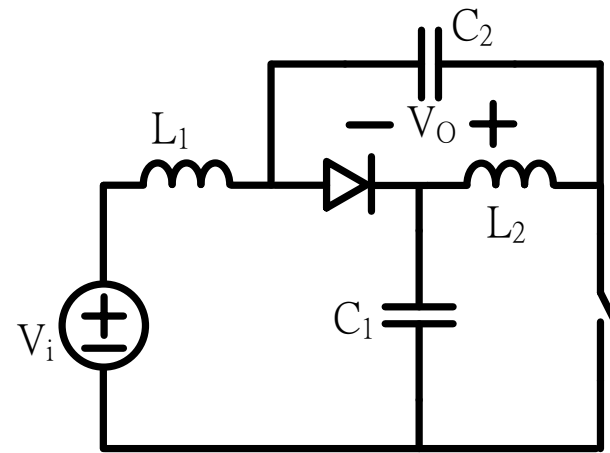


(d)

Fig. 26. Synthesizing $V_o/V_i = D/(1-2D)$ with a Zeta converter




Decoding $D/(2-D)$


1. Synthesizing with Buck +I-Buck-Boost

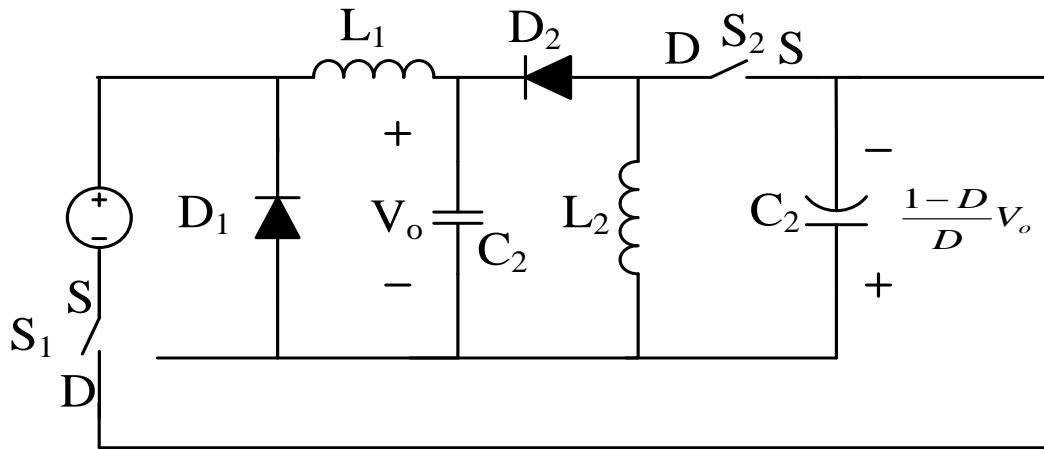


(a)

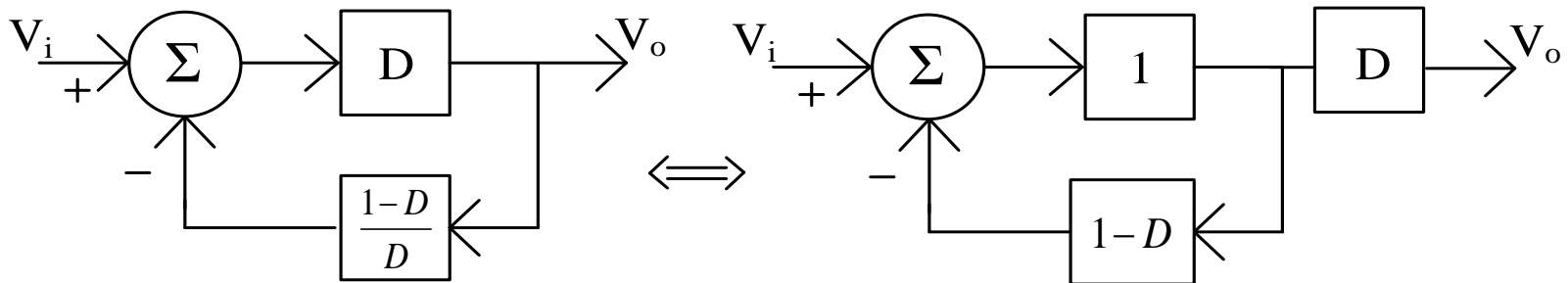

$$\frac{V_o}{V_i} = \frac{D}{2-D}$$

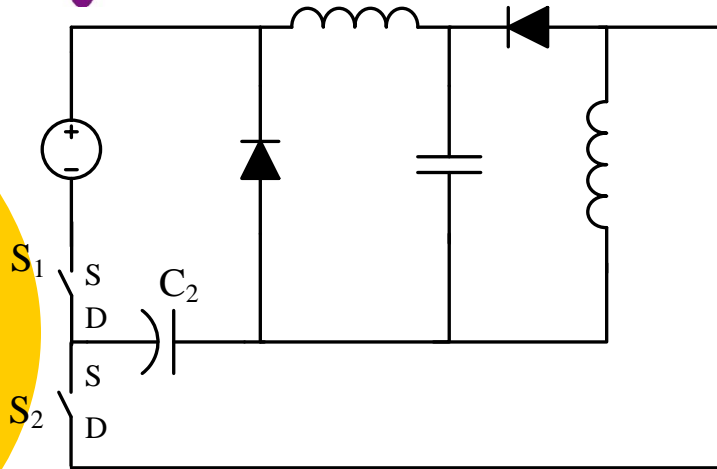


(b)

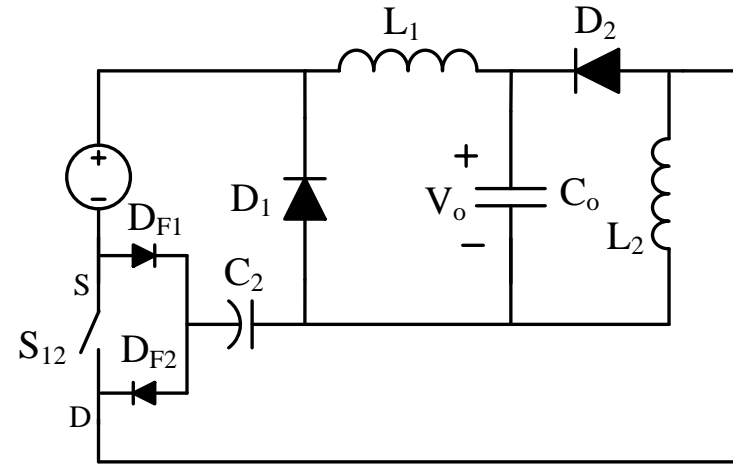


$I_1 = I_2 \rightarrow D_{F1}$ and D_{F2} can be saved (open)

(c)

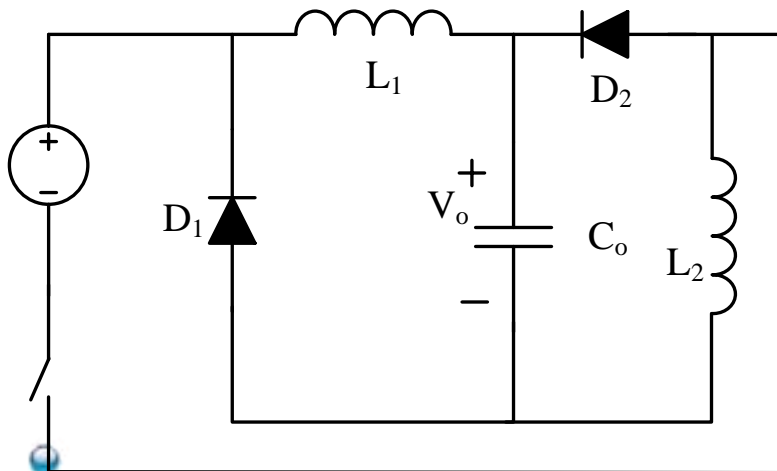


(d)

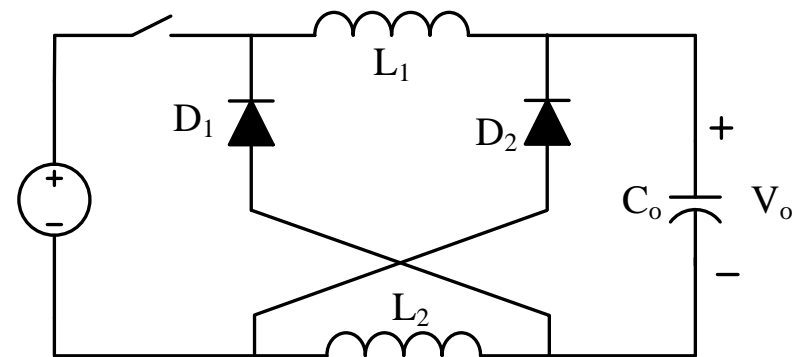


(e) [48]




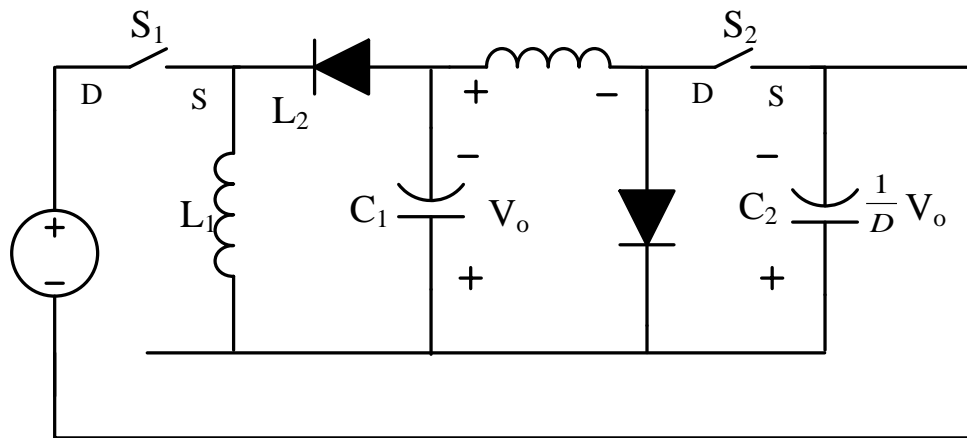2. Synthesizing with **Buck-Boost + I-Buck**




(a)

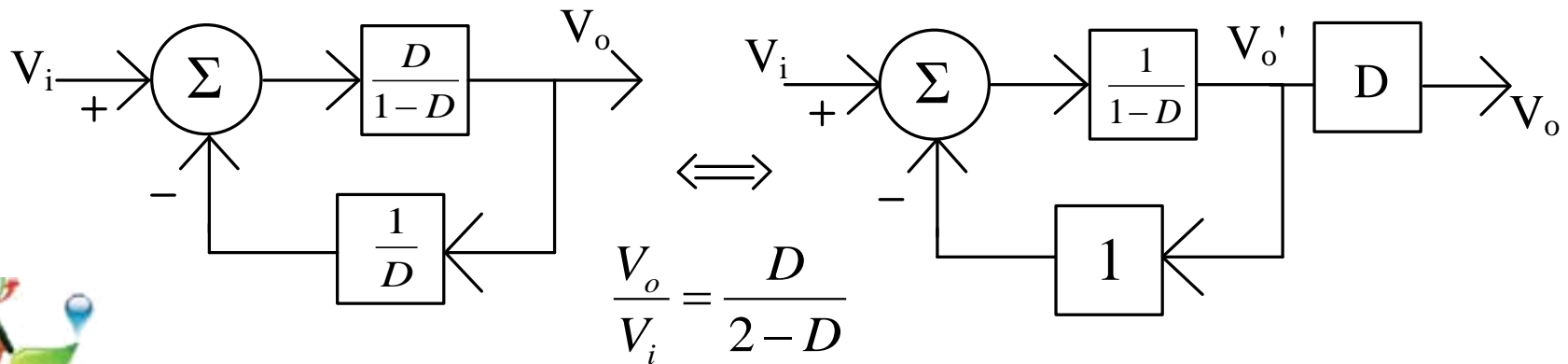


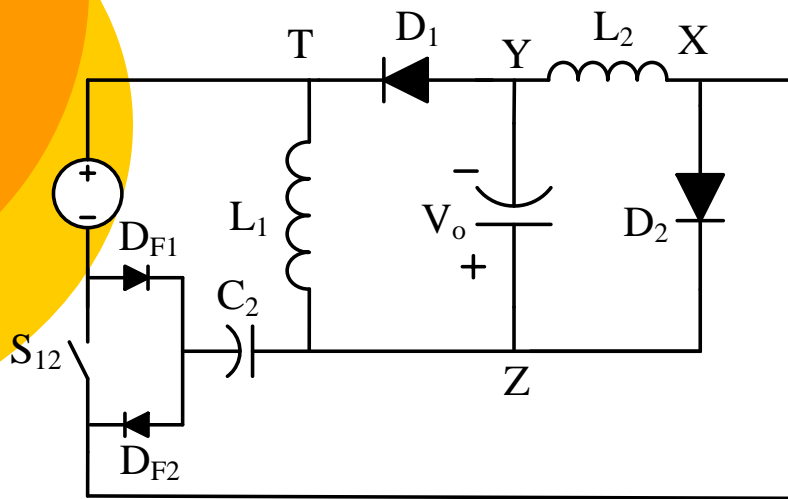


(b)

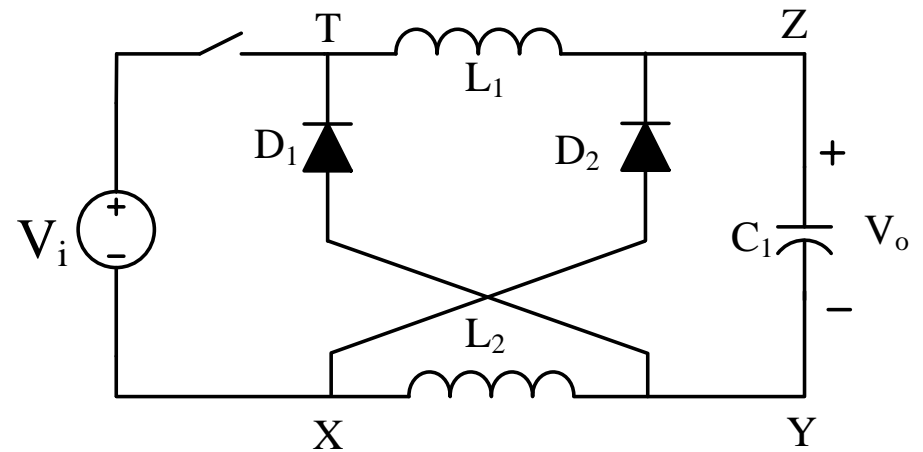


(c) [48]

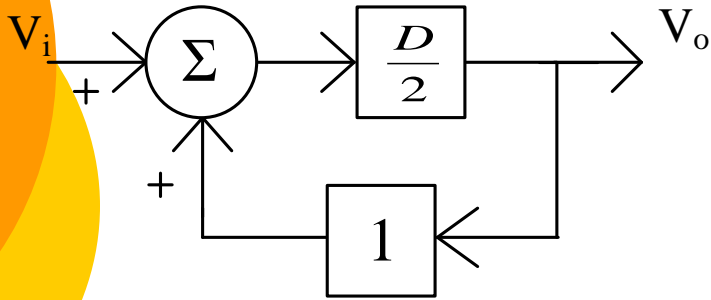

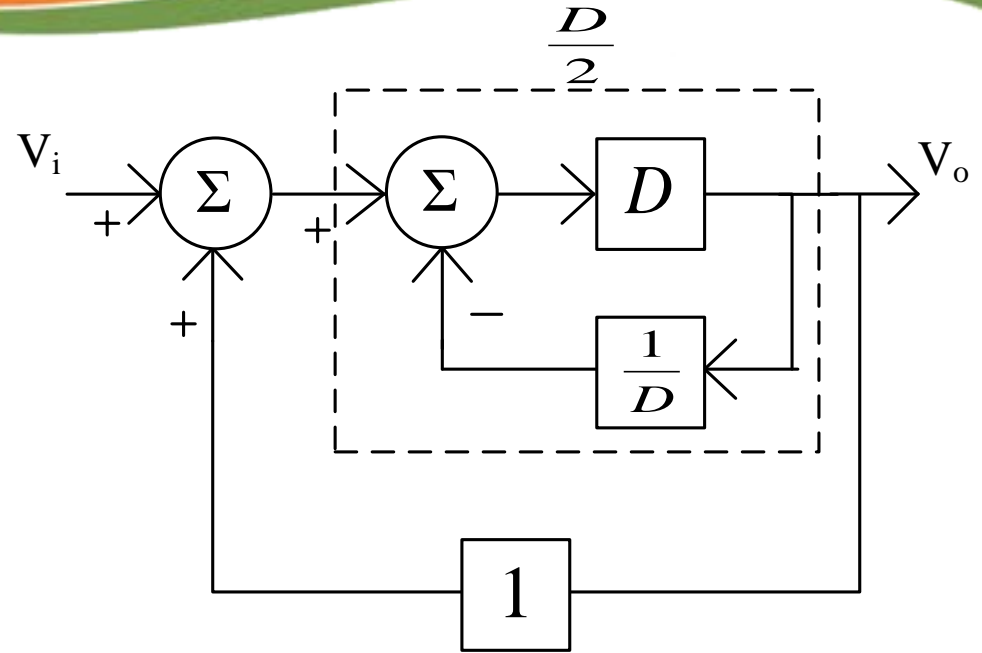(a) no converter to realize $\frac{D}{2}$



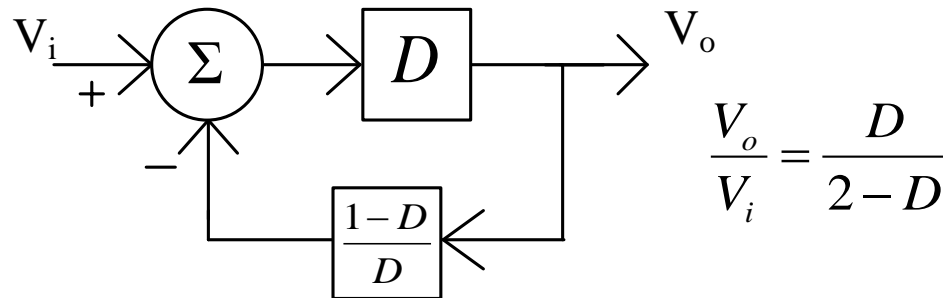(b) no converter to realize the negative feedback path of $\frac{1}{D}$





(c) Combine the two feedback paths into a single one.

This block diagram can be synthesized by the converters shown in eg. 1.




Decoding $D/2(1-D)$
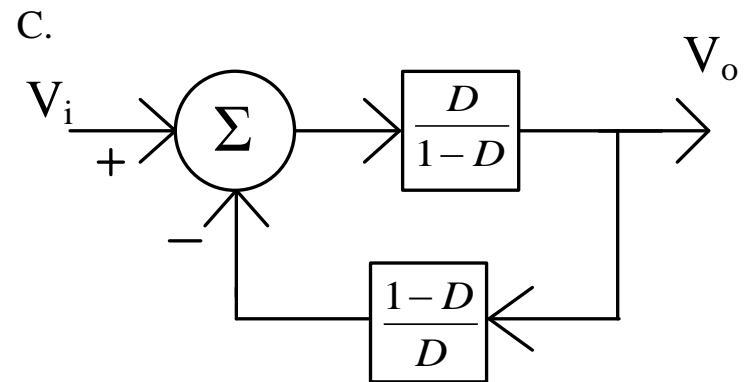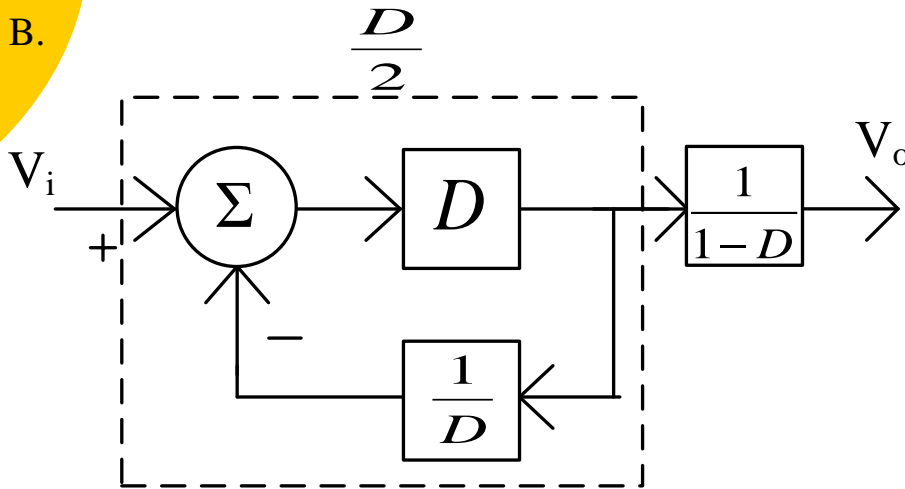
$$A. \frac{V_o}{V_i} = \frac{D}{2(1-D)} = \frac{D}{2} \times \frac{1}{1-D}$$







1. Synthesizing with Zeta + I-Buck-Boost

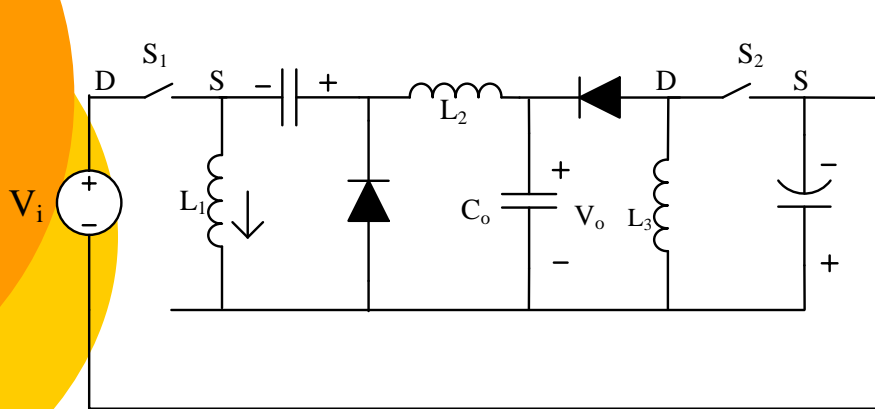

(a)

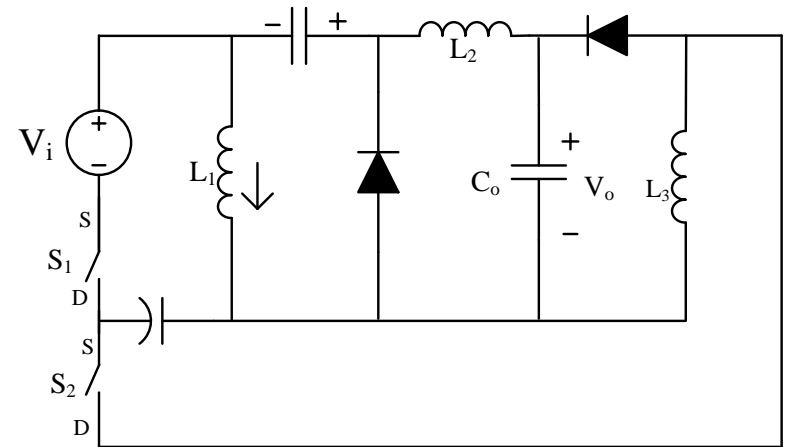


(b)

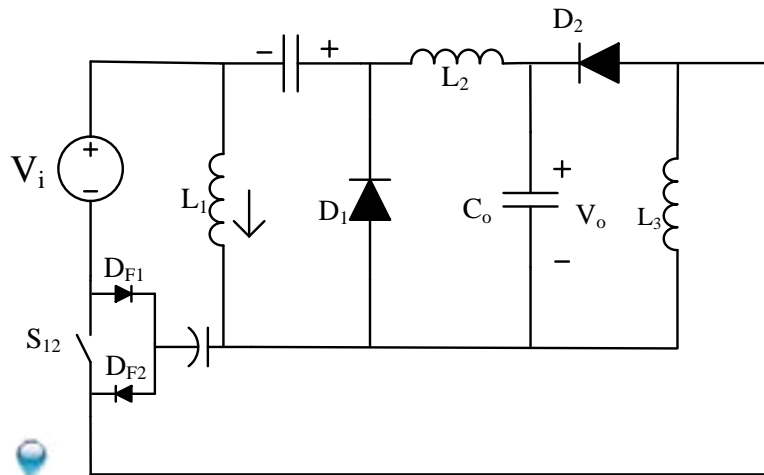


$I_1 = I_2 \rightarrow D_{F1}$ and D_{F2} can be saved


(c)

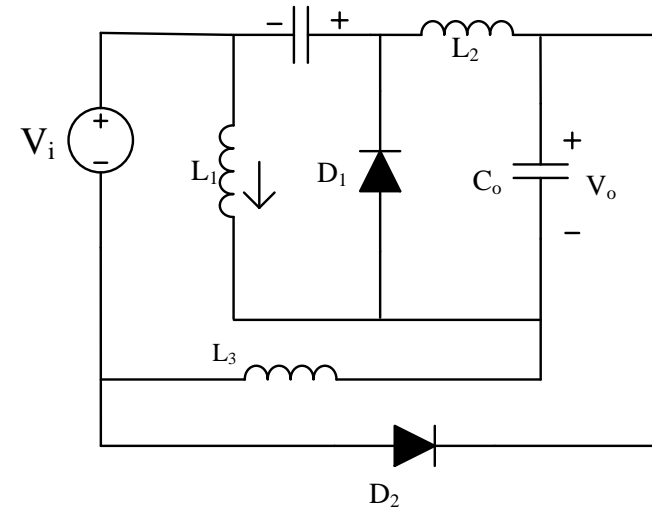



(d)

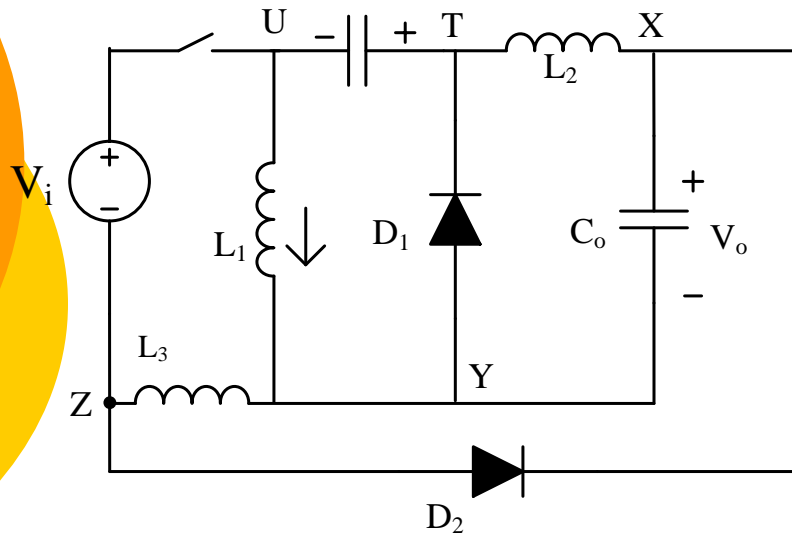

(e)

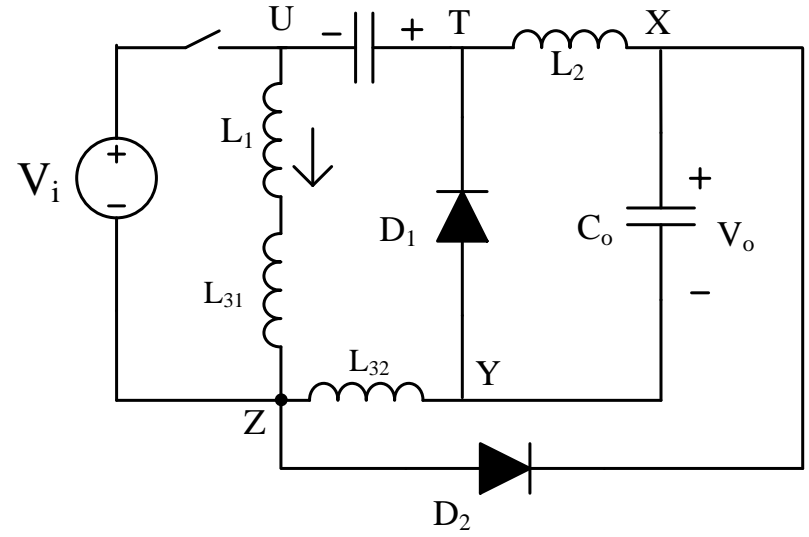

(f)

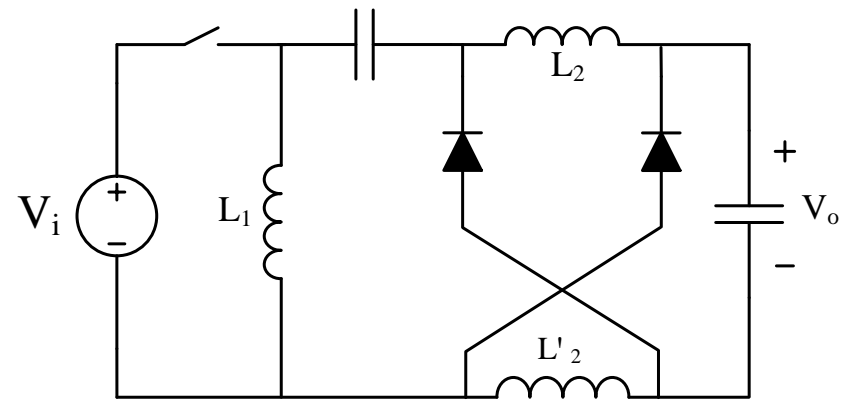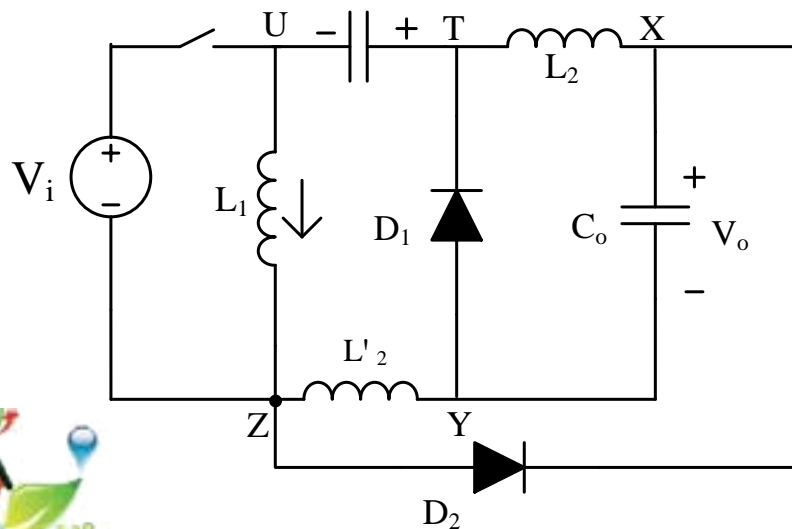


$$(h) \quad \frac{V_o}{V_i} = \frac{D}{2(1-D)} \quad [48]$$



2. Synthesizing with **SEPIC + I-Ćuk**


SEPIC+I-Cuk

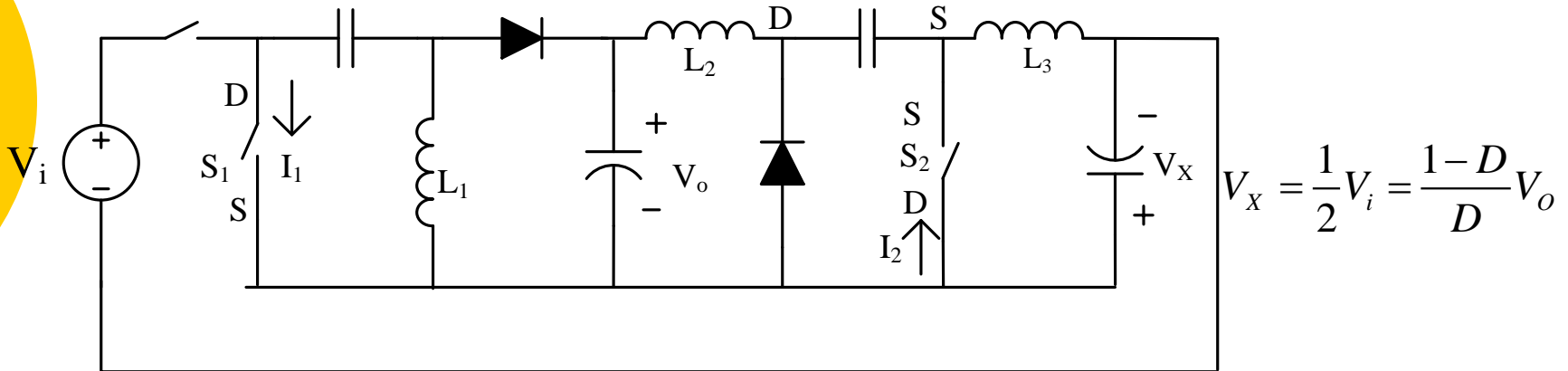


Let $L_S = L_1 = L_2 = L_3$, and we have $I_1 = I_2$

(a)




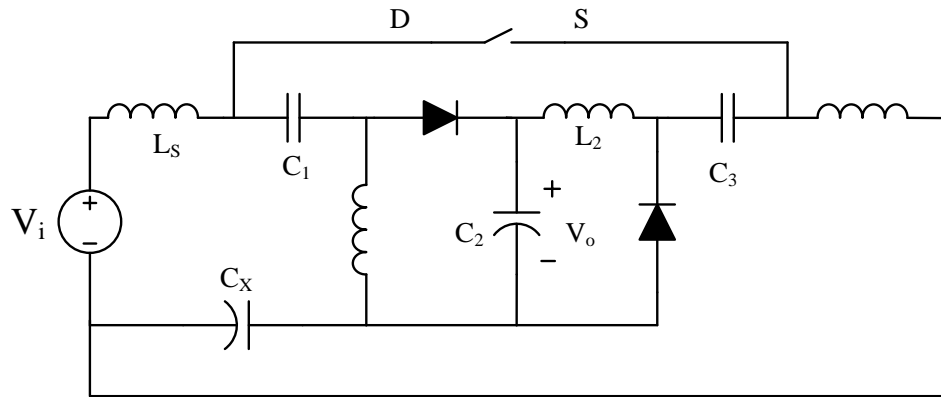






(b)

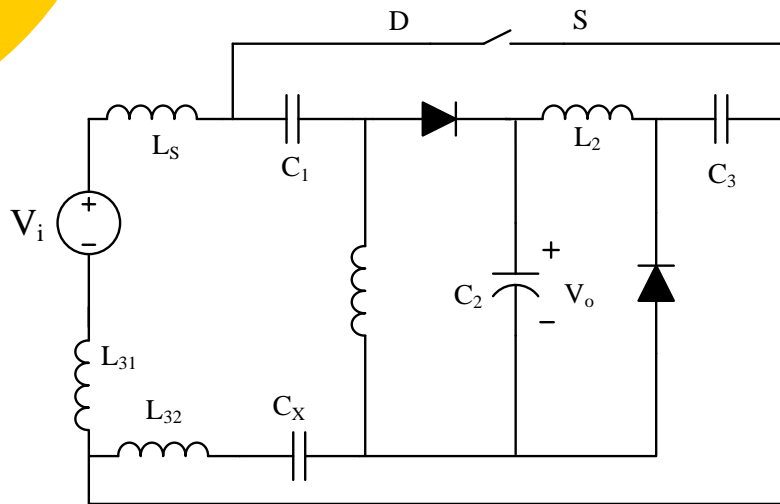


(c)

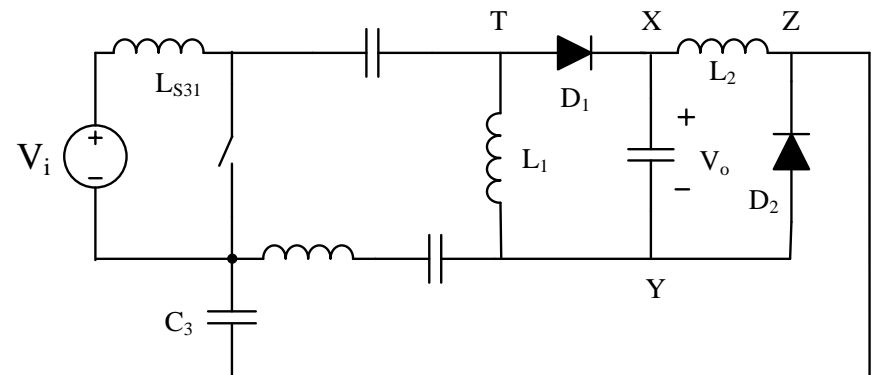

(d)

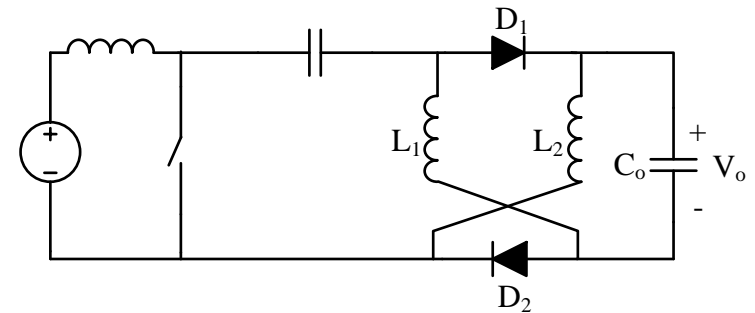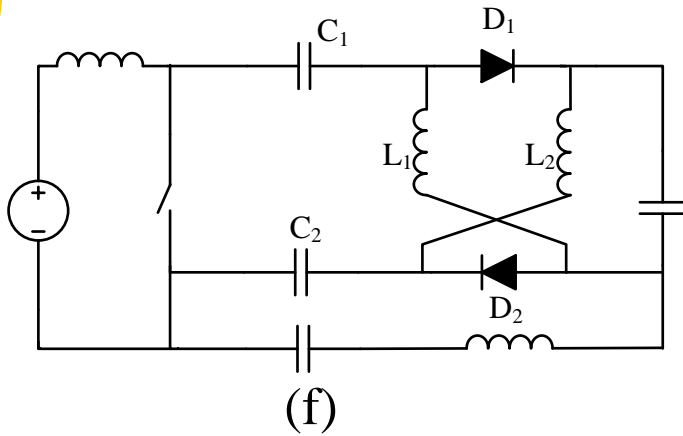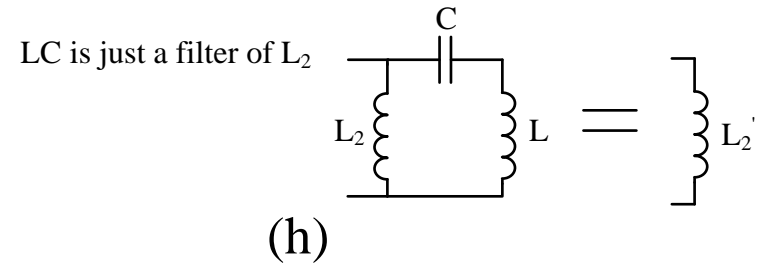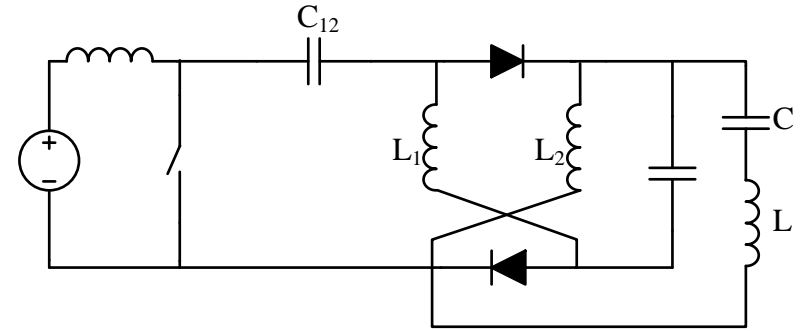
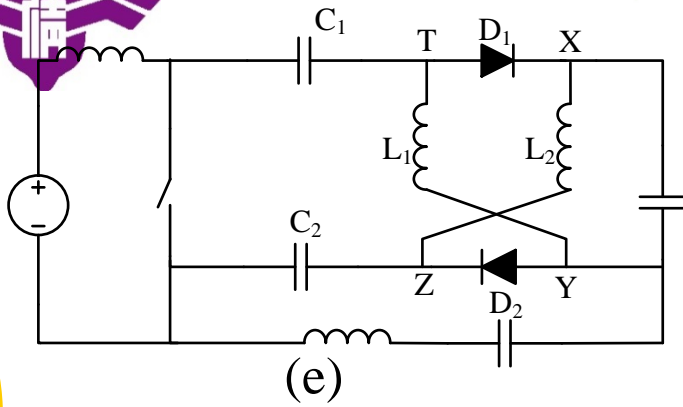

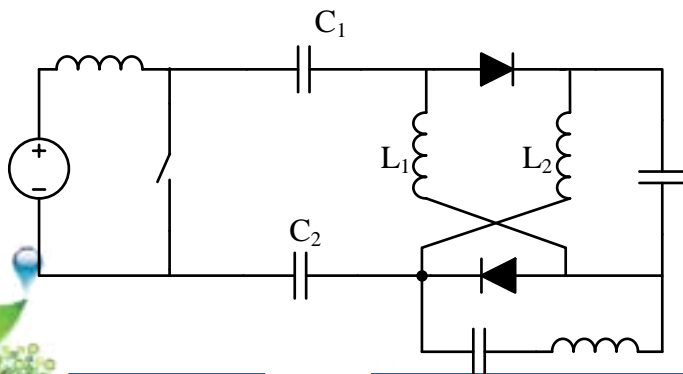
$$(i) \quad \frac{V_o}{V_i} = \frac{D}{2(1-D)} \quad [48]$$






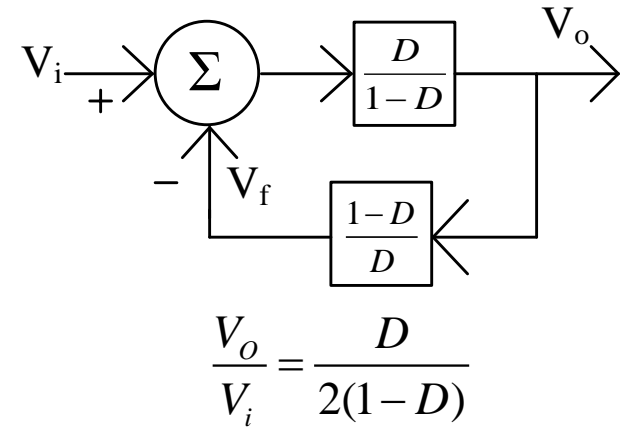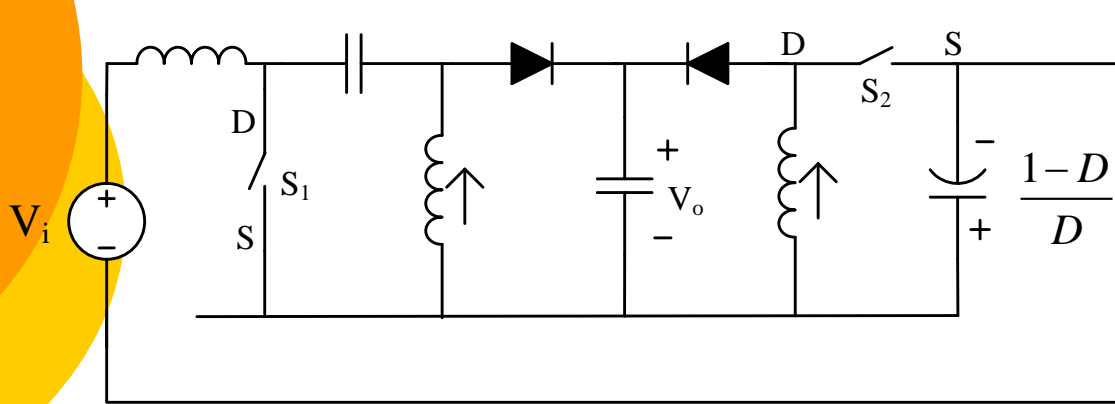3. Synthesizing with **SEPIC** + **I-Buck-Boost**



(a)

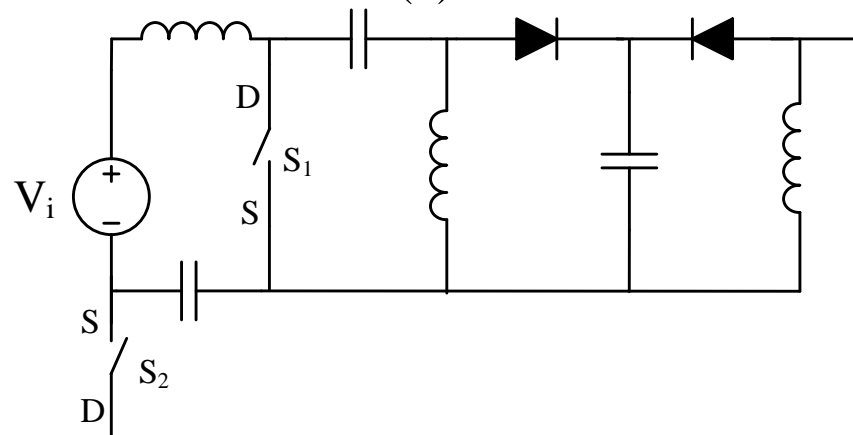


No common node between S_1 and S_2


(b)



4. Synthesizing with Zeta + I-Ćuk

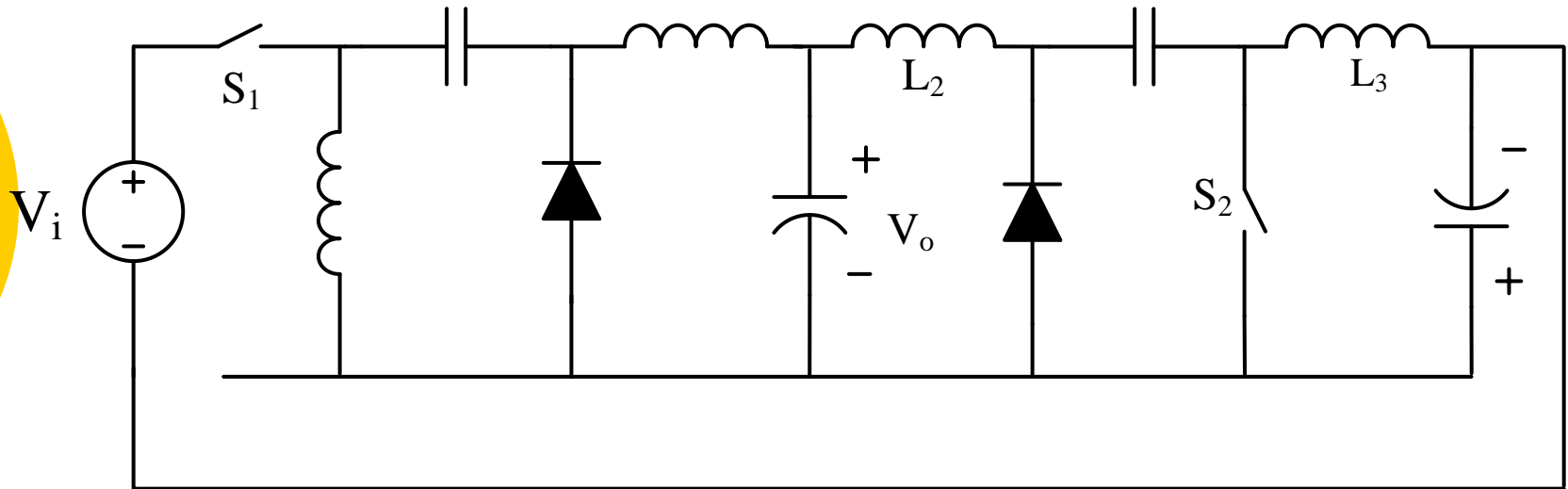


No common node between S_1 and S_2

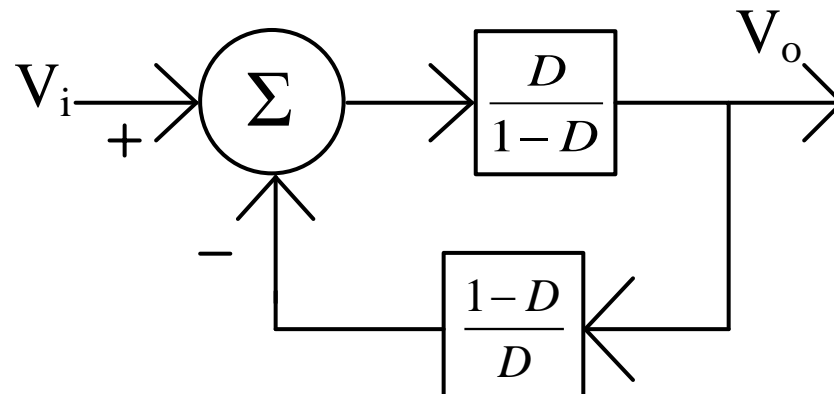




Decoding $(1+D)/(1-D)$


Synthesizing with **Cuk** + **Boost**

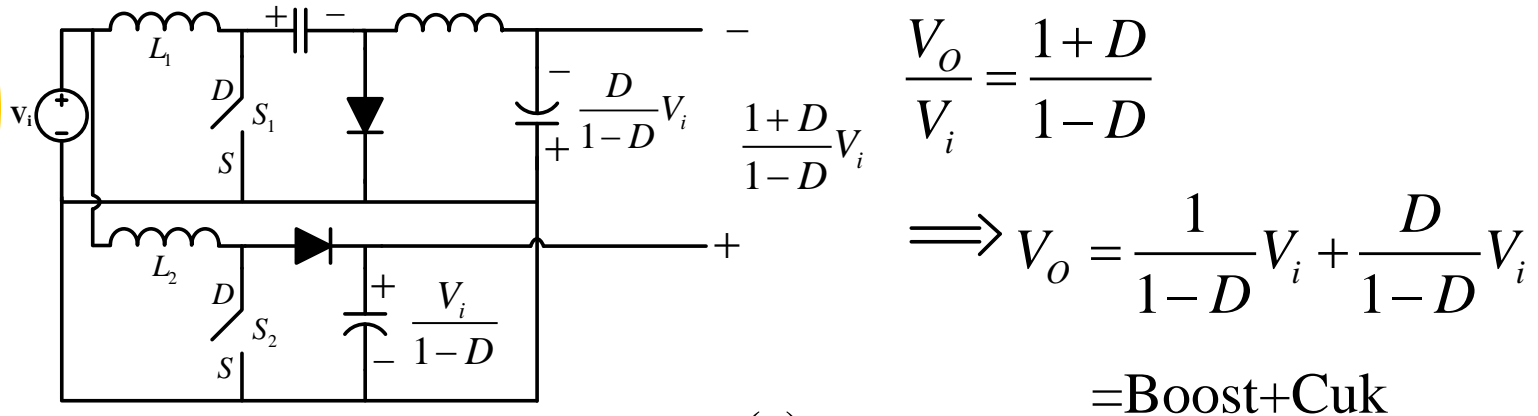


(a)

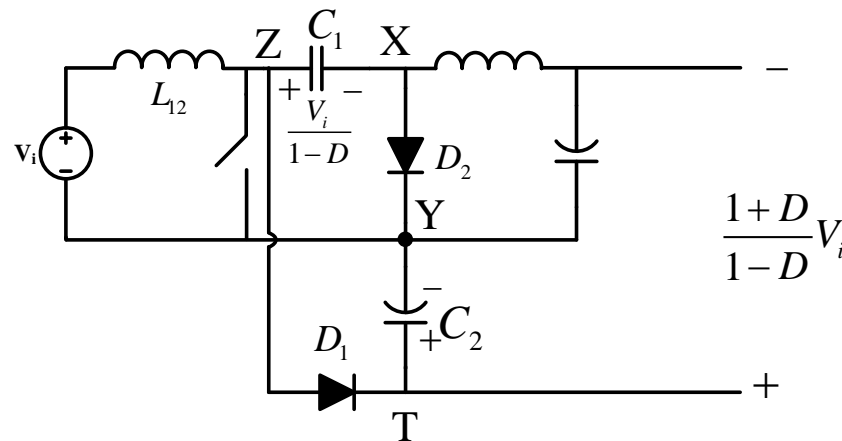

(b)

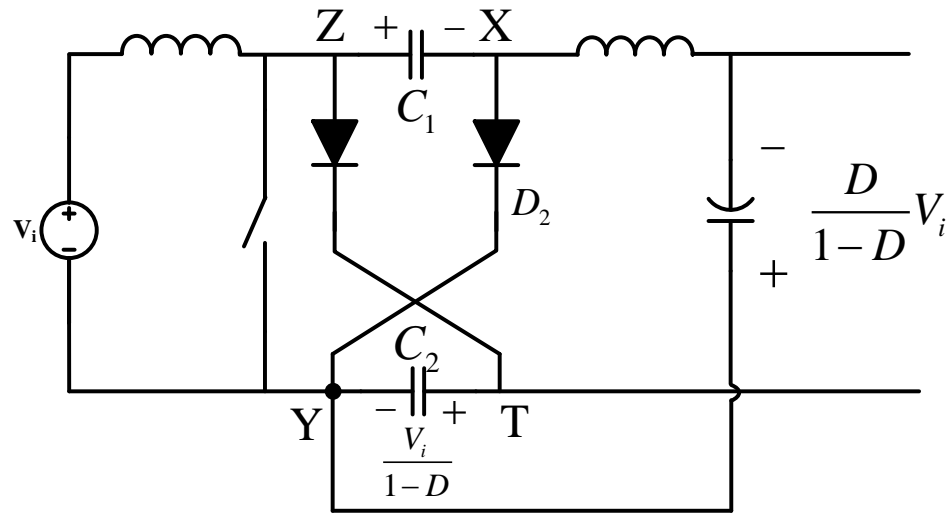



(c)

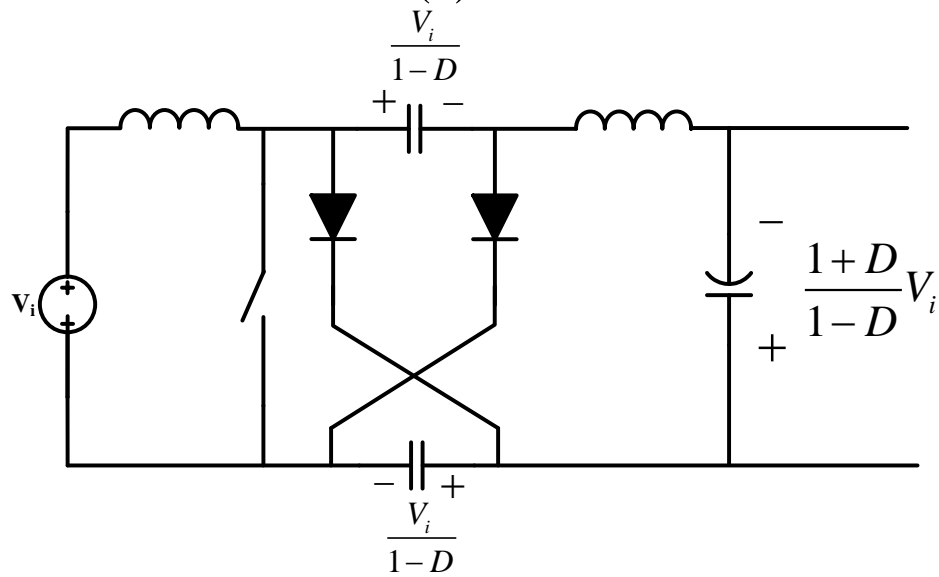

(d) [48]



Decoding $D/(1-2D)$

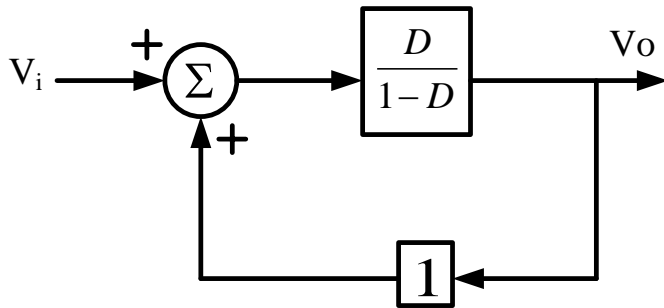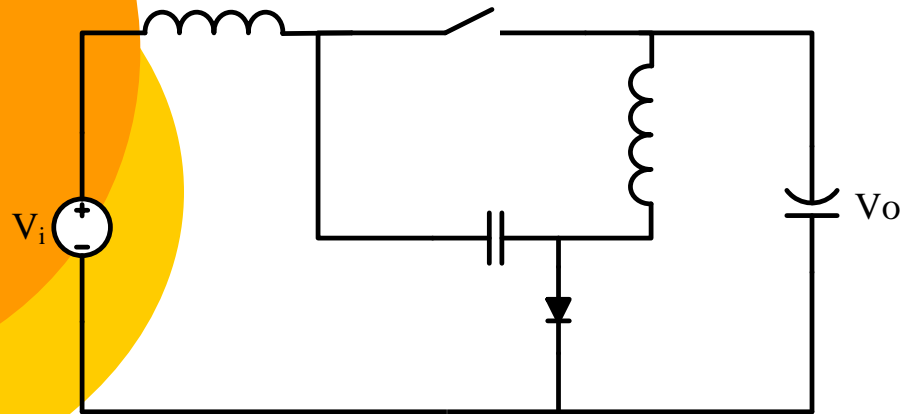

$$\frac{V_o}{V_i} = \frac{D}{1-2D} \Rightarrow (1-2D)V_o = DV$$

$$\Rightarrow V_o(1-D) = (V_i + V_o)D$$

$$\Rightarrow V_o = \frac{(V_i + V_o)D}{1-D}$$


$$= \frac{V_i D}{1-D} + \frac{V_o D}{1-D}$$

$$\Rightarrow V_o \left(1 - \frac{D}{1-D}\right) = V_i \left(\frac{D}{1-D}\right)$$


$$\Rightarrow \frac{V_o}{V_i} = \frac{\frac{D}{1-D}}{1 - \frac{D}{1-D}}$$



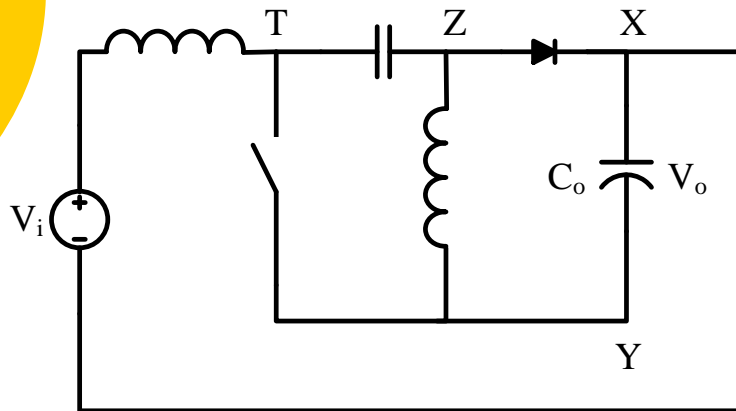Synthesizing with **SEPIC** + positive feedback




(a)

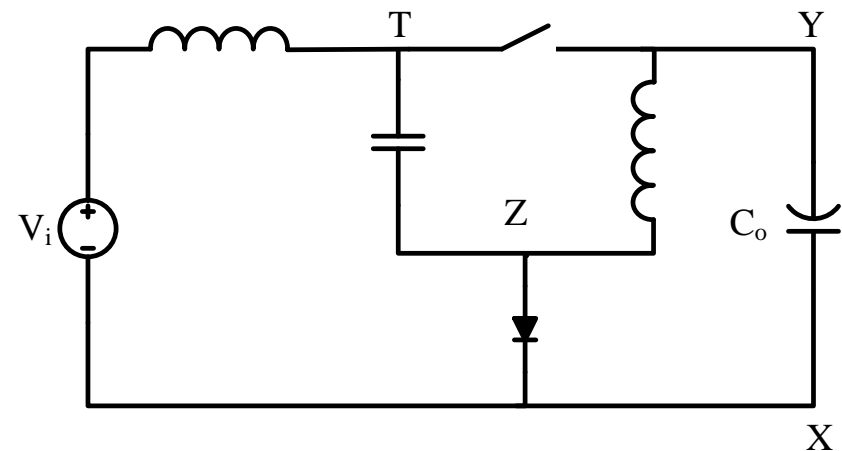


(b) [29]




➤ Synthesizing PWM Converters

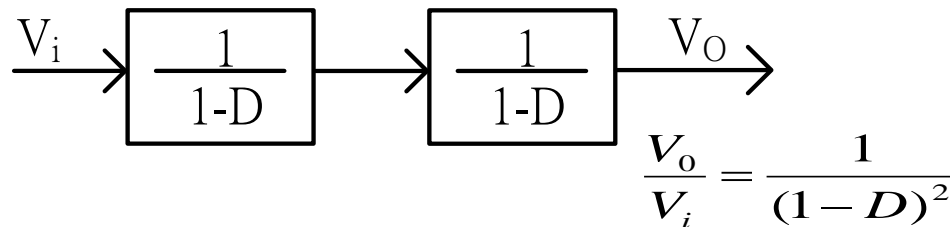


(a)

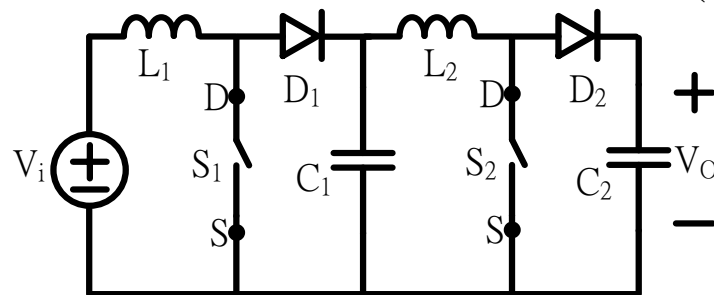


(b) boost + boost

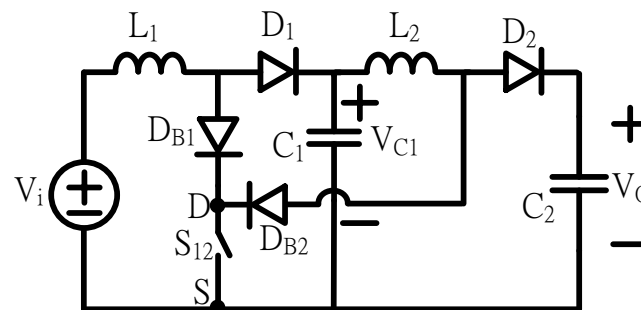

(c)


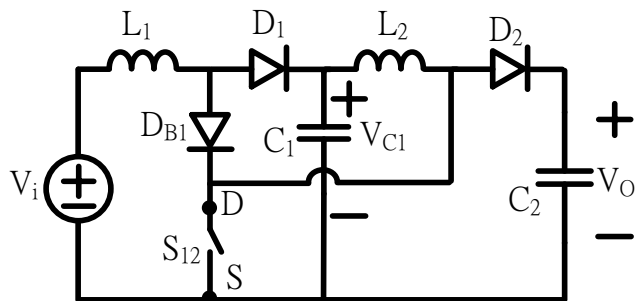


(d)

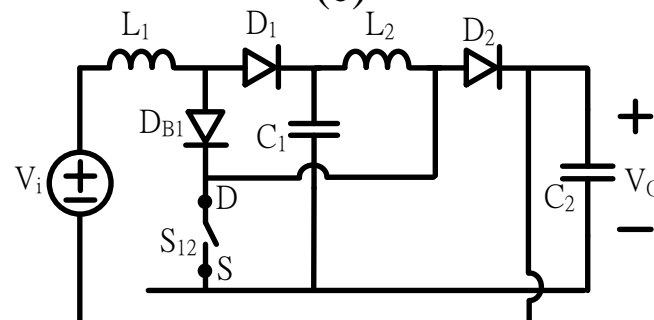


(e)


Fig. 27. Decoding and evolution of the boost-boost grafted PWM converter from two boost converters in cascade.

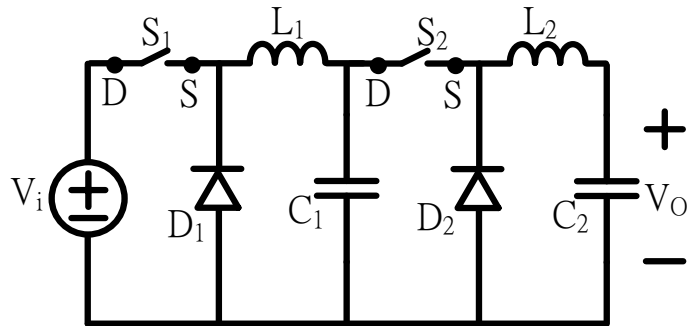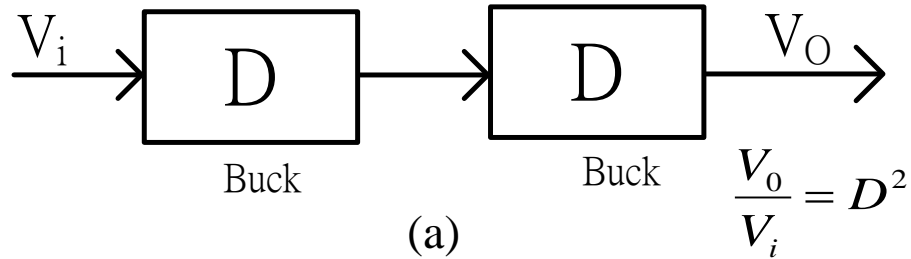


(b) buck + buck

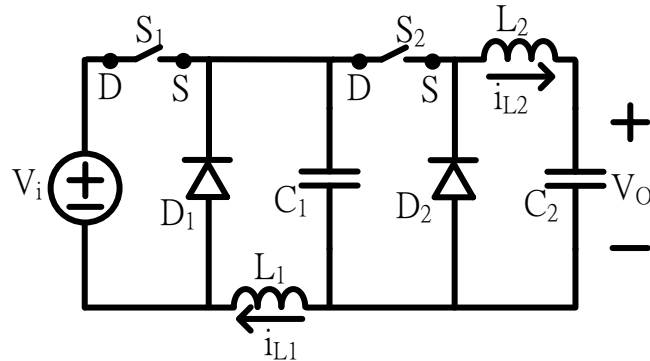

(c)

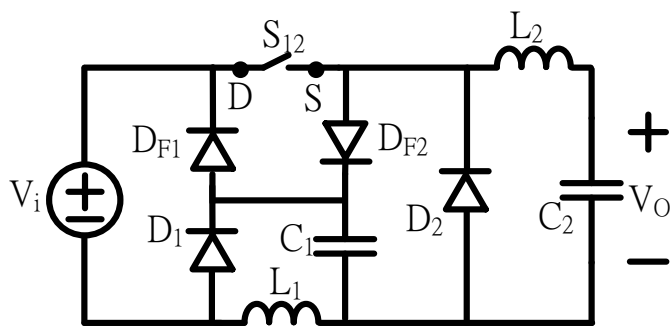

(d)

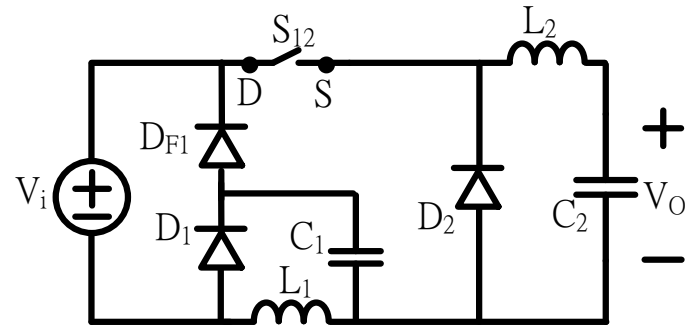


(e)


Fig. 28. Decoding and evolution of the buck-buck grafted PWM converter from two buck converters in cascade.



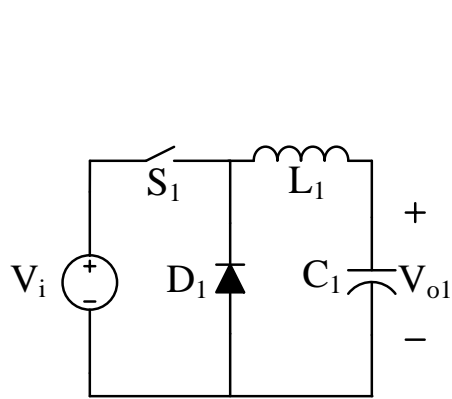
➤ Buck Converter with a Second Output V_{o2}




(a)

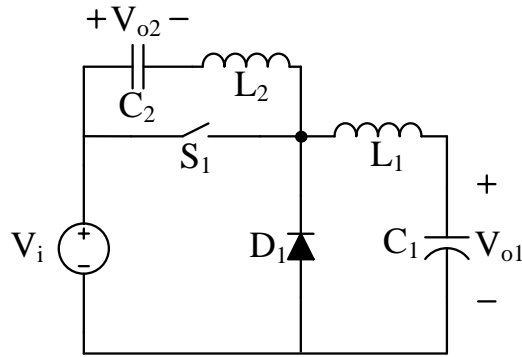



(b)

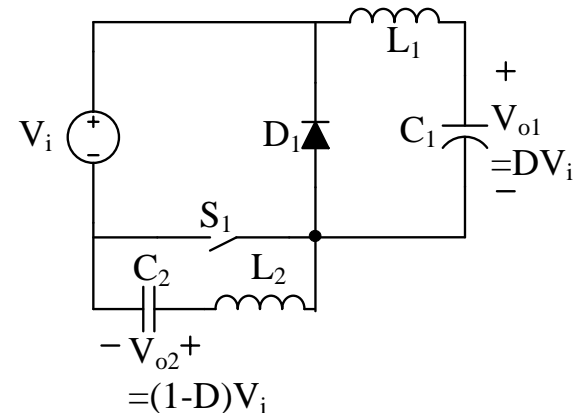


(c)

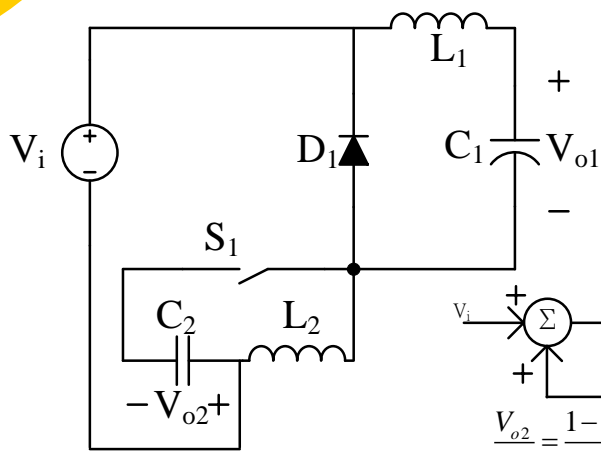

(d)

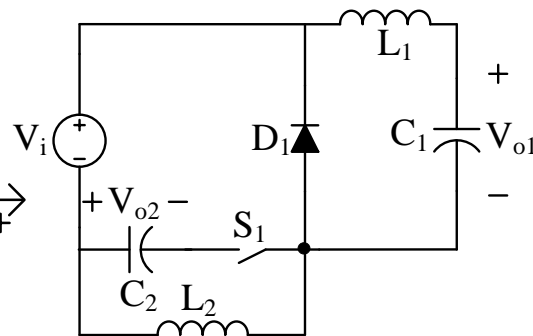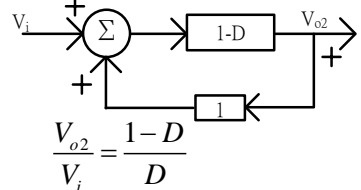

(e) $V_{o2}/V_i = (1-D)/D$

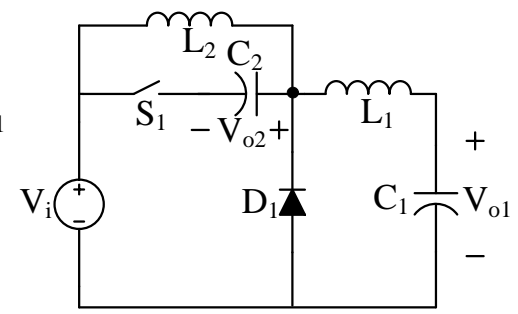


(f) $V_{o2}/V_i = (1-D)/D$




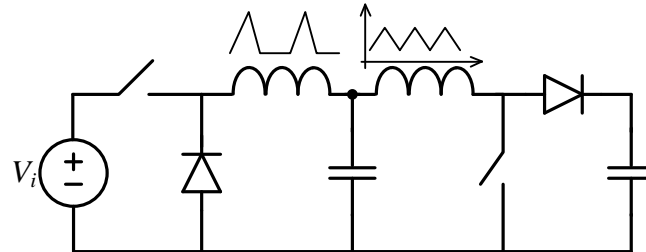A. Buck (DCM) + Boost (CCM)


$$\frac{d_1}{(d_1 + d_2)} \times \frac{1}{(1 - d_2)} = \frac{d_1}{(d_1 + d_2)(1 - d_2)}$$



(a)

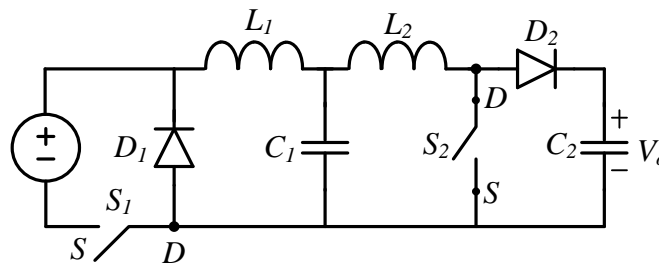

(b)

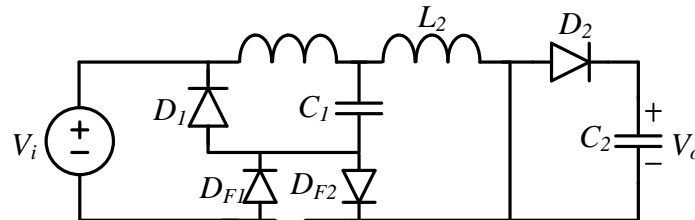


(c)



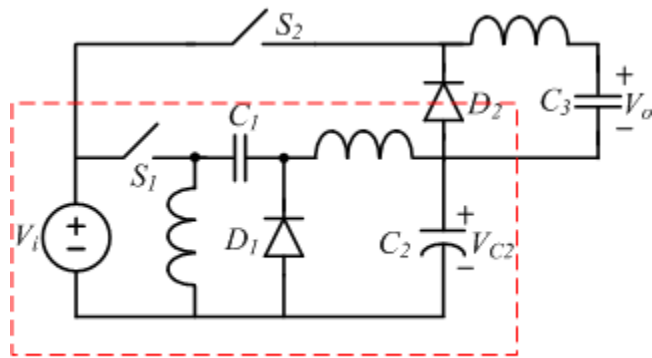
B. Zeta cascoded with Buck

$$\frac{V_o}{V_i} = \left(1 - \frac{D}{1-D}\right) \times D = \left(\frac{1-2D}{1-D}\right) \times D$$




Zeta


(a)

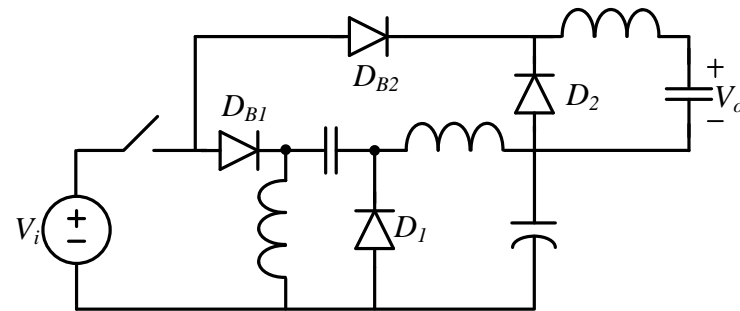

(b)

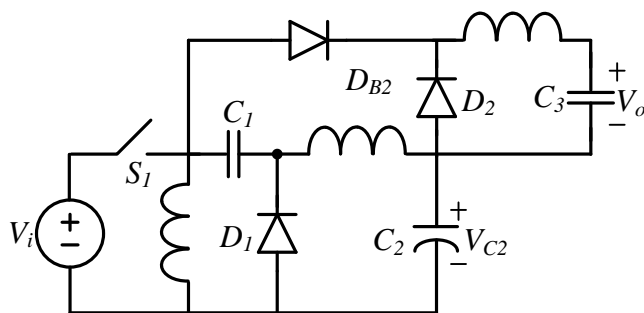

(c)


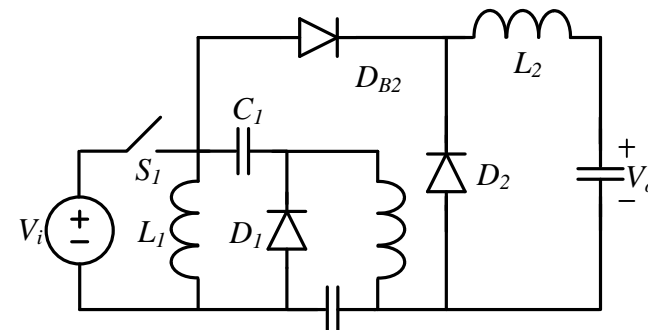


(d)



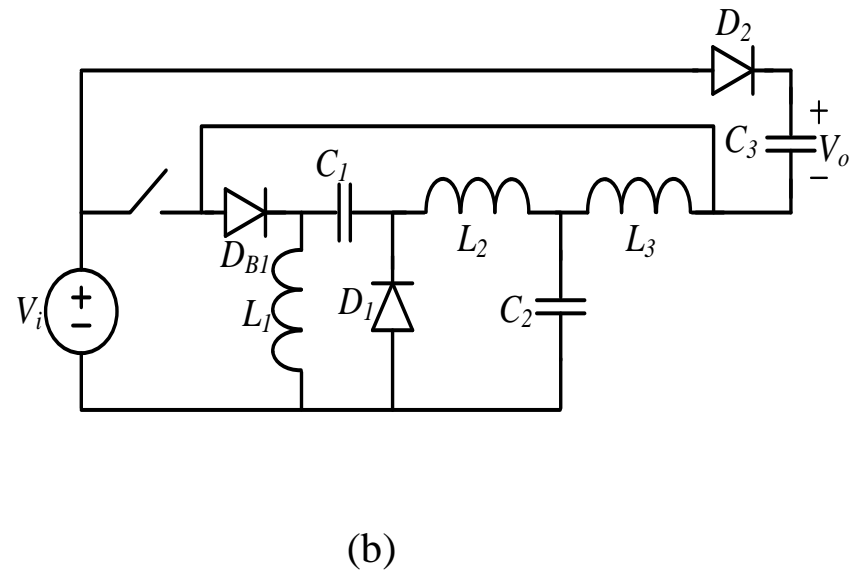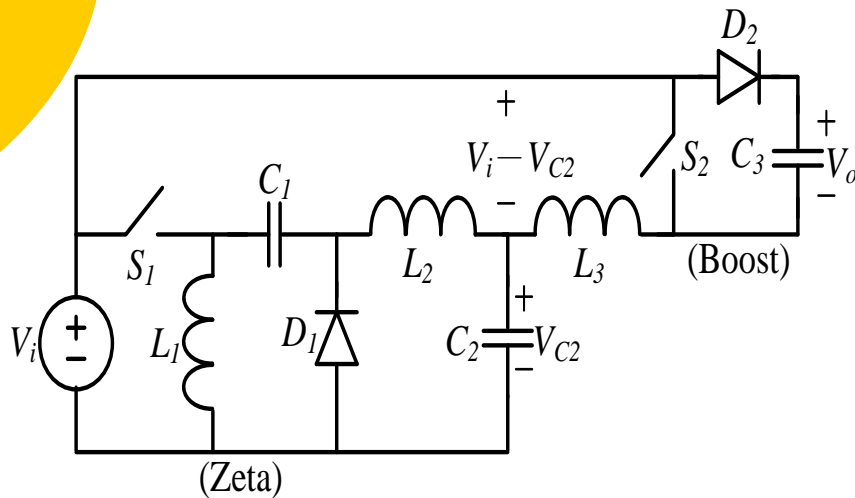C. Zeta cascoded with Boost

$$\frac{V_o}{V_i} = \left(1 - \frac{D}{1-D}\right) \times \frac{1}{(1-D)} = \frac{1-2D}{(1-D)^2}$$





VII. Other PWM Converters

➤ PWM Converters with DC-transformer

A. Buck-Derived Circuits [3]

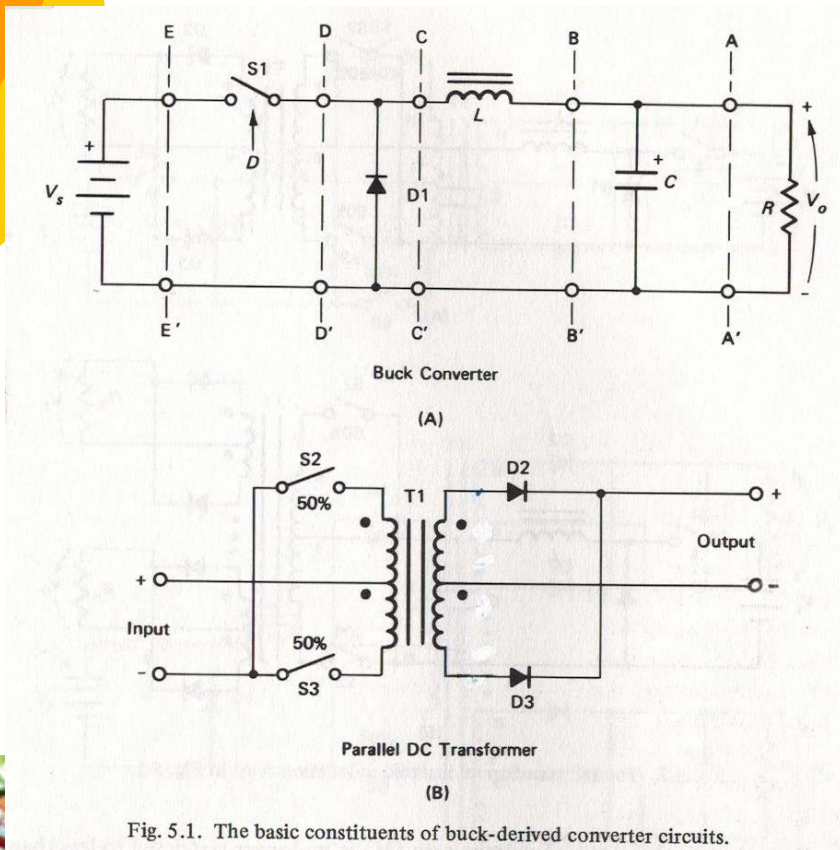


Fig. 5.1. The basic constituents of buck-derived converter circuits.

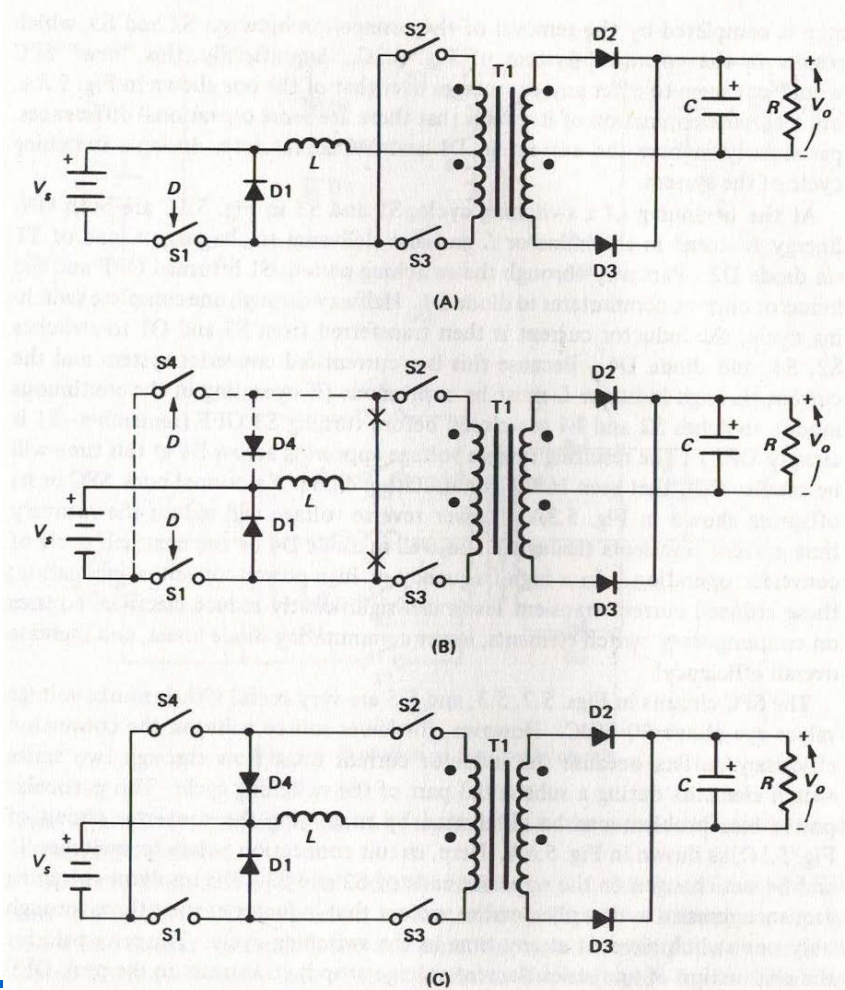


Fig. 5.5. Evolution of the IBM circuit.



B. Boost-Derived Circuits [3]



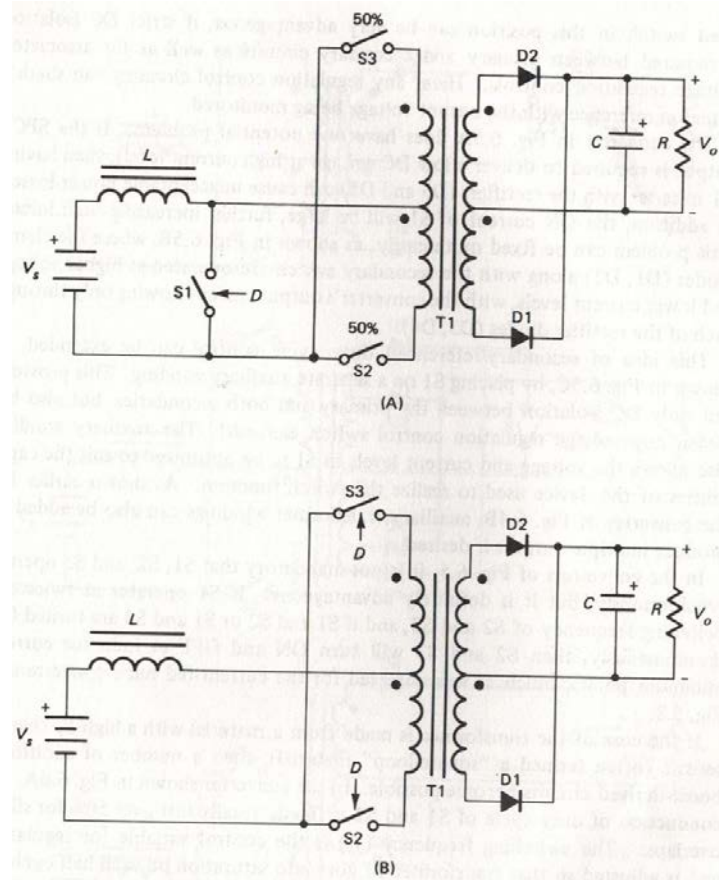



Fig. 6.4. The Clarke circuit.

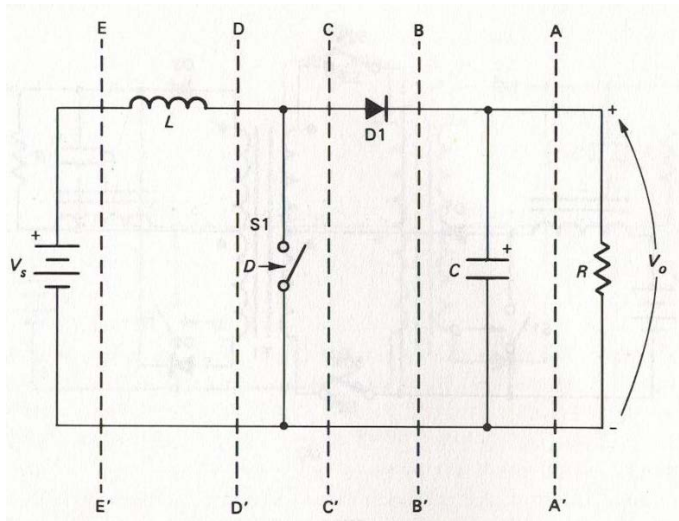


Resonant Converters

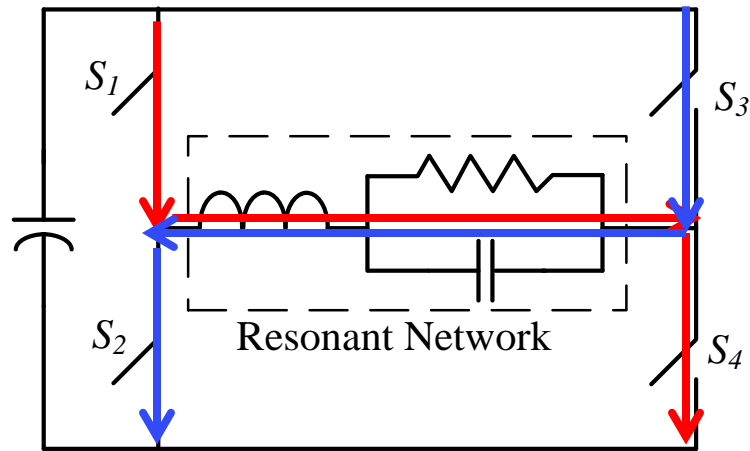

(a) Two buck converters in DCM operation

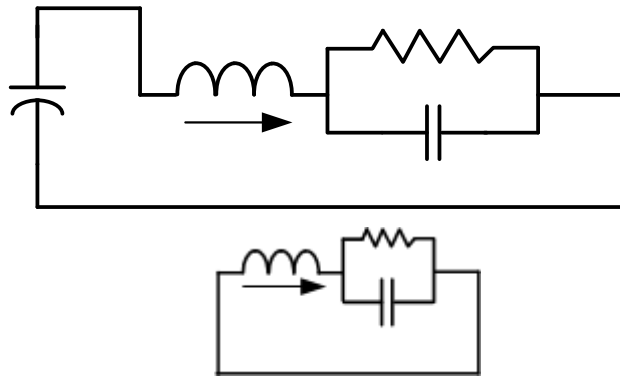


(b) Positive half cycle

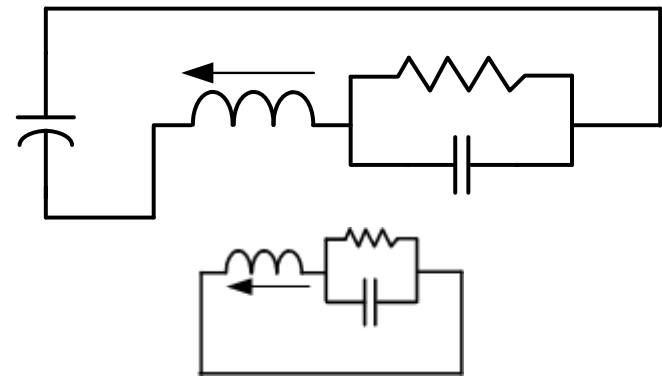

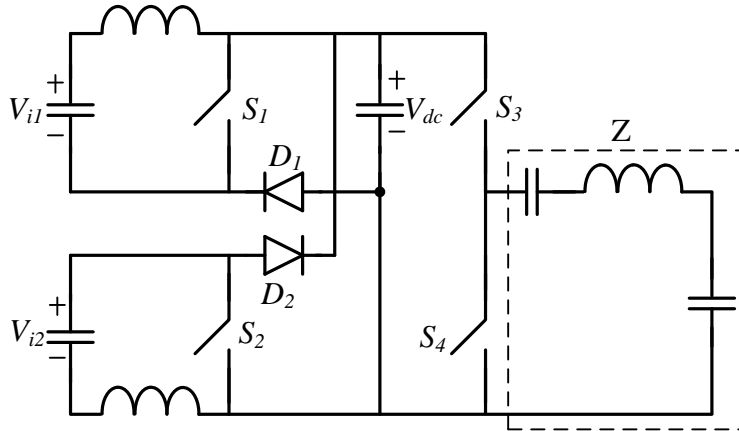
(c) Negative half cycle




Single-stage Interleaved with Grafted Switch and Diode [41],[42]




(a)

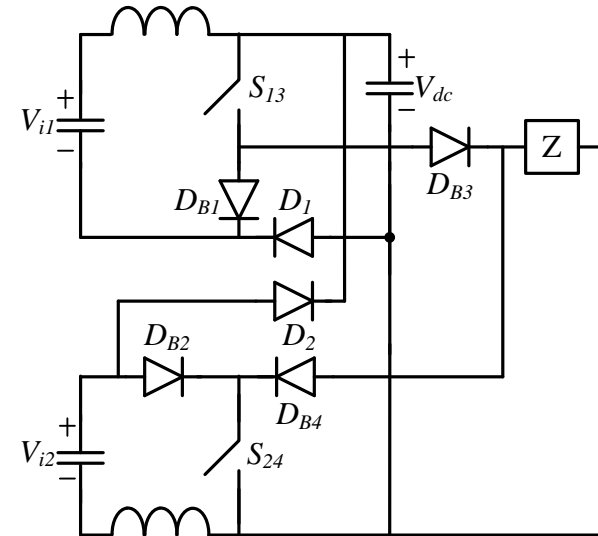


(b)

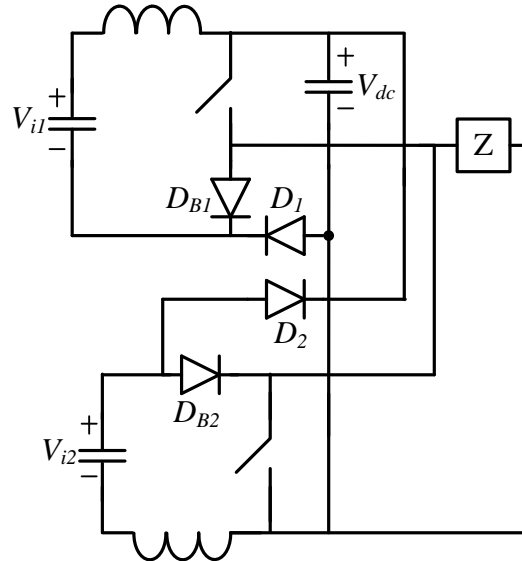


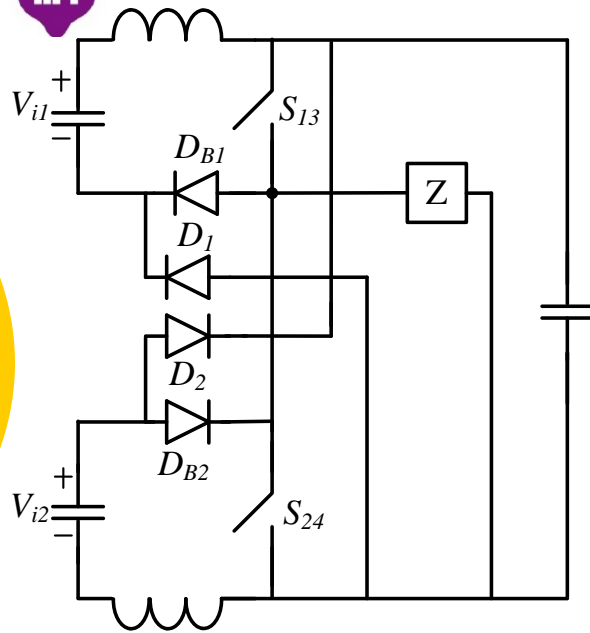
(c). Boost in DCM, and $V_{dc} > V_{i1}$ or $V_{dc} > V_{i2}$



(d)

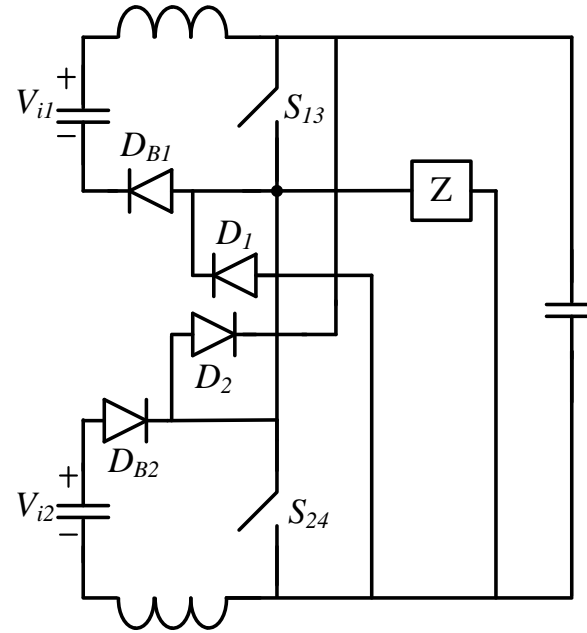

(e)

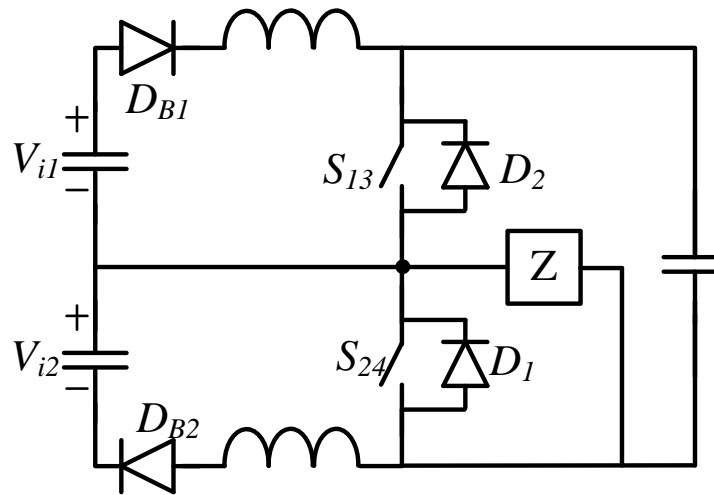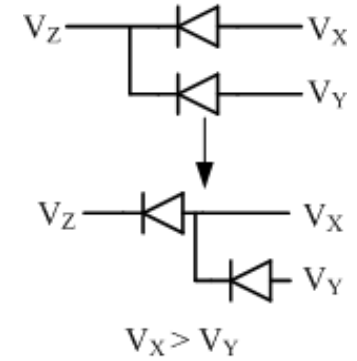

(f) D_1 and D_2 are the body diodes of switches S_{24} and S_{13} , respectively.



Interleaved Single-Stage High PFC [43] – Buck + Zeta (with isolation)

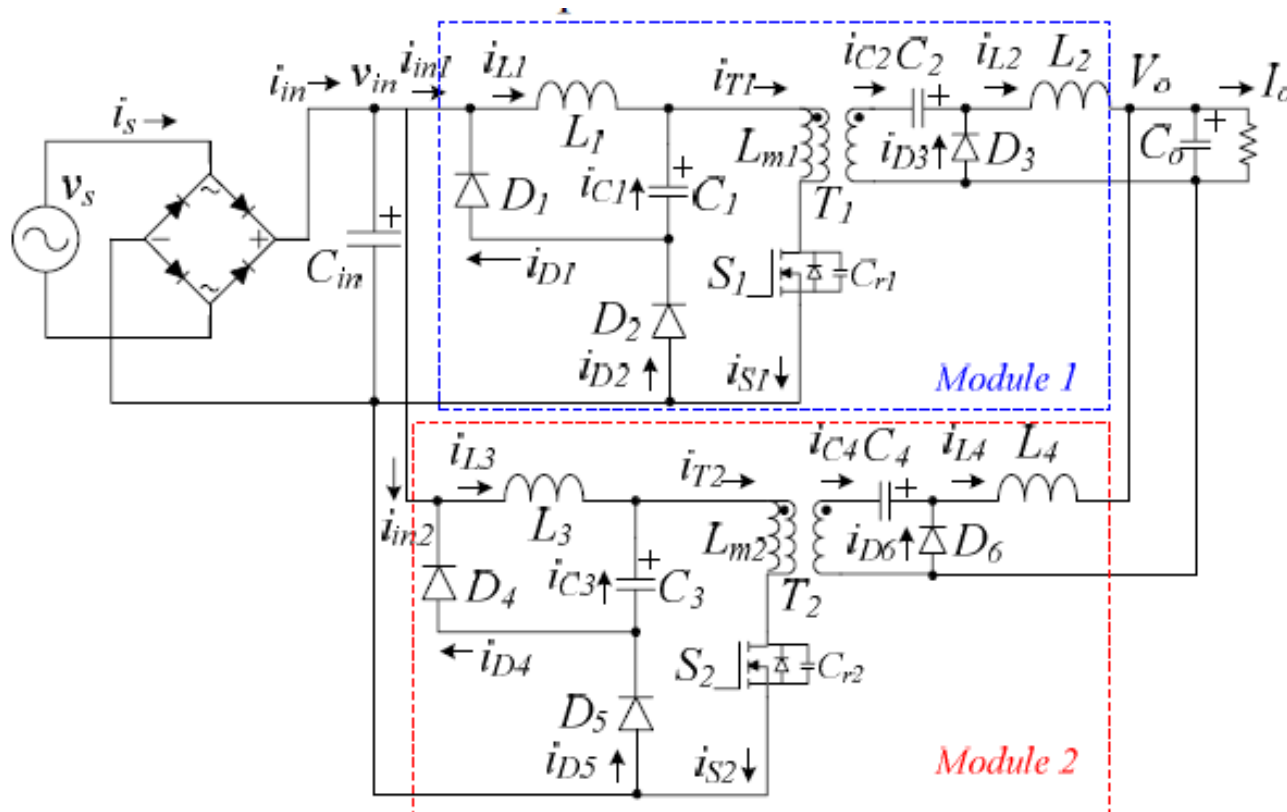


Fig. 1 Circuit configuration of the proposed converter.



Interleaved Single-Stage Full-Bridge Converter [44] – Boost+ Full-Bridge

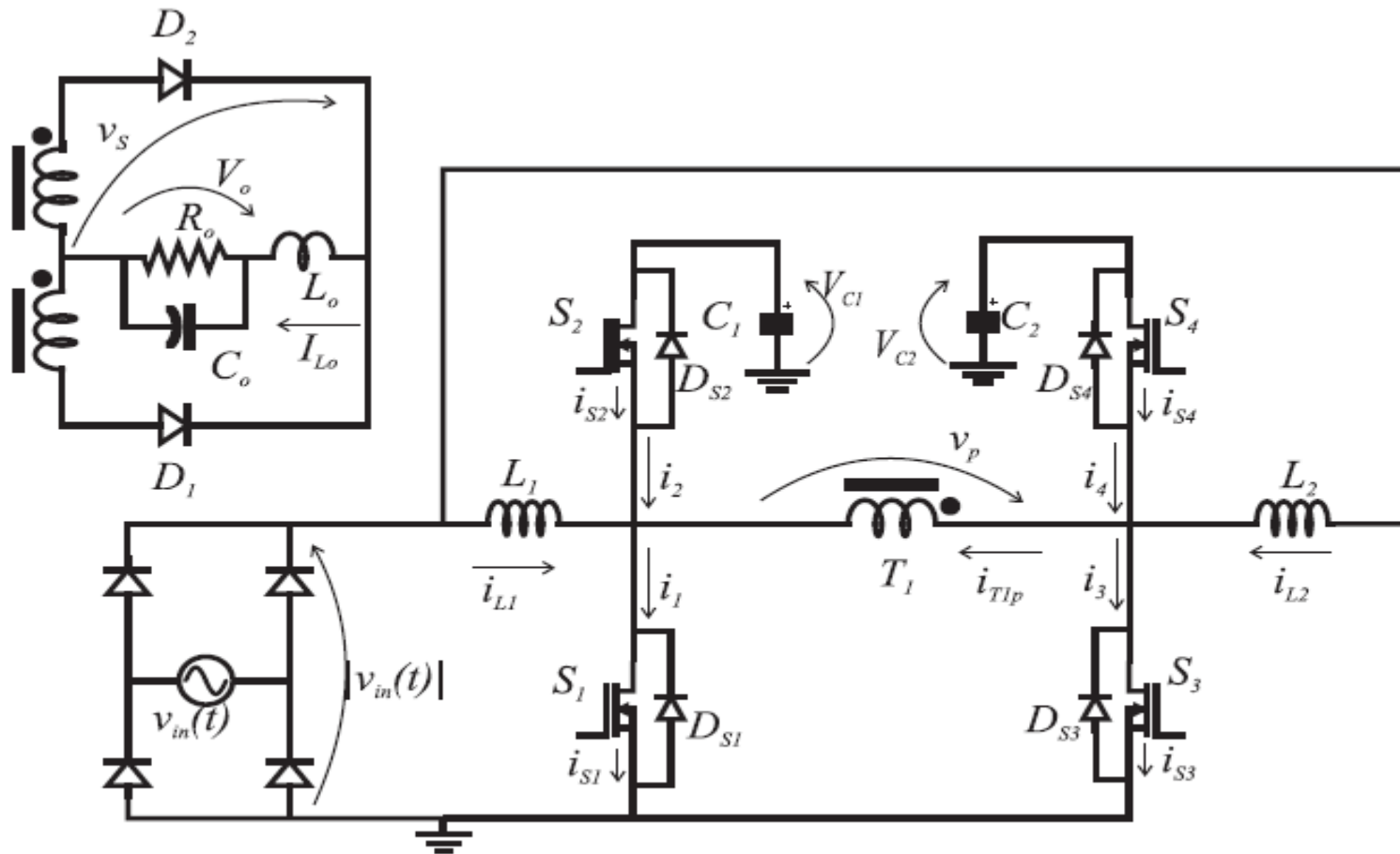


Figure 1. Topology proposed in



Interleaved Single-Stage AC-DC Converter [45] – Boost+ Flyback

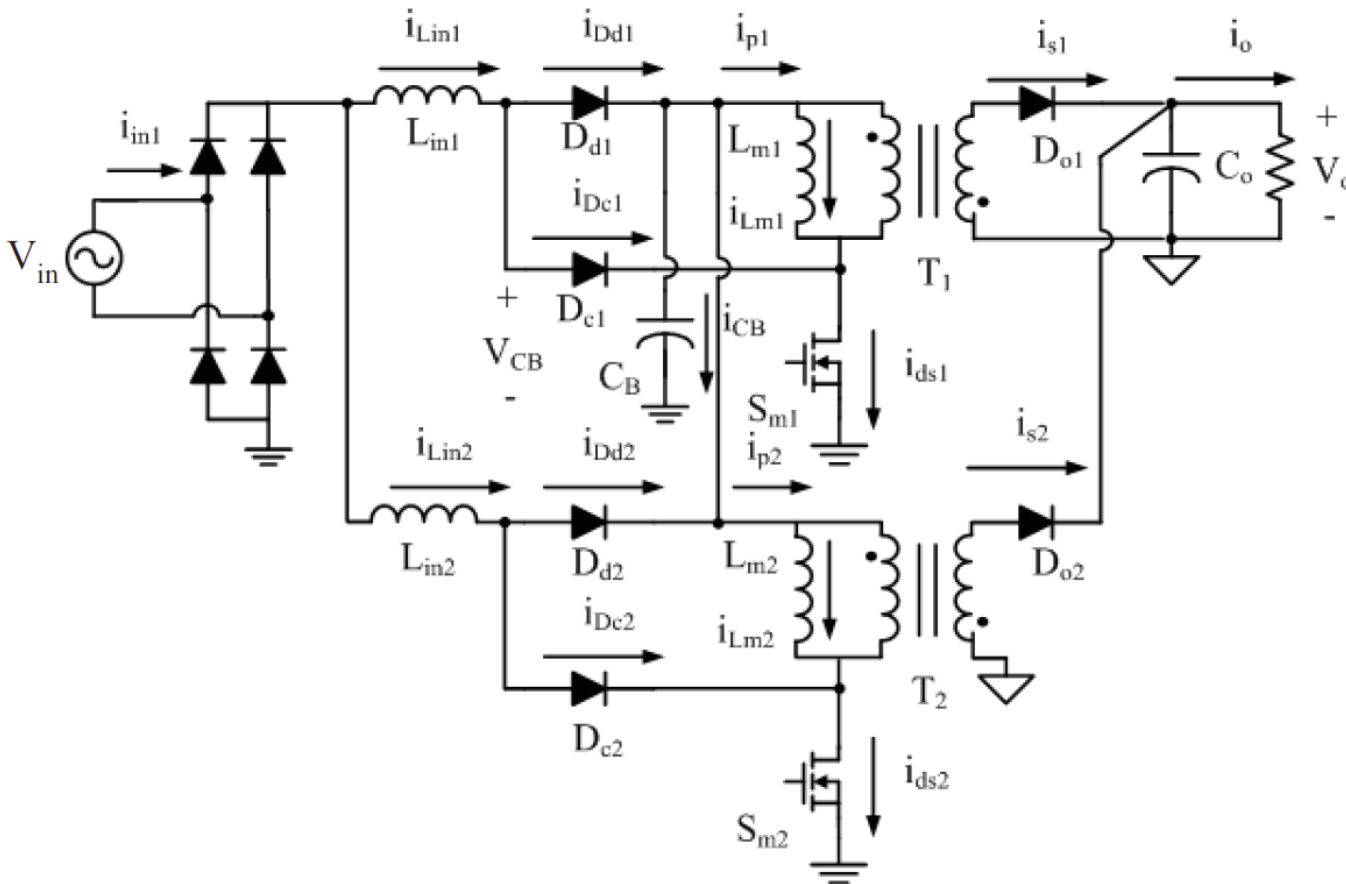


Fig. 2 circuit configuration of the proposed AC-DC boost-flyback converter.



Single-Stage PFC [46]

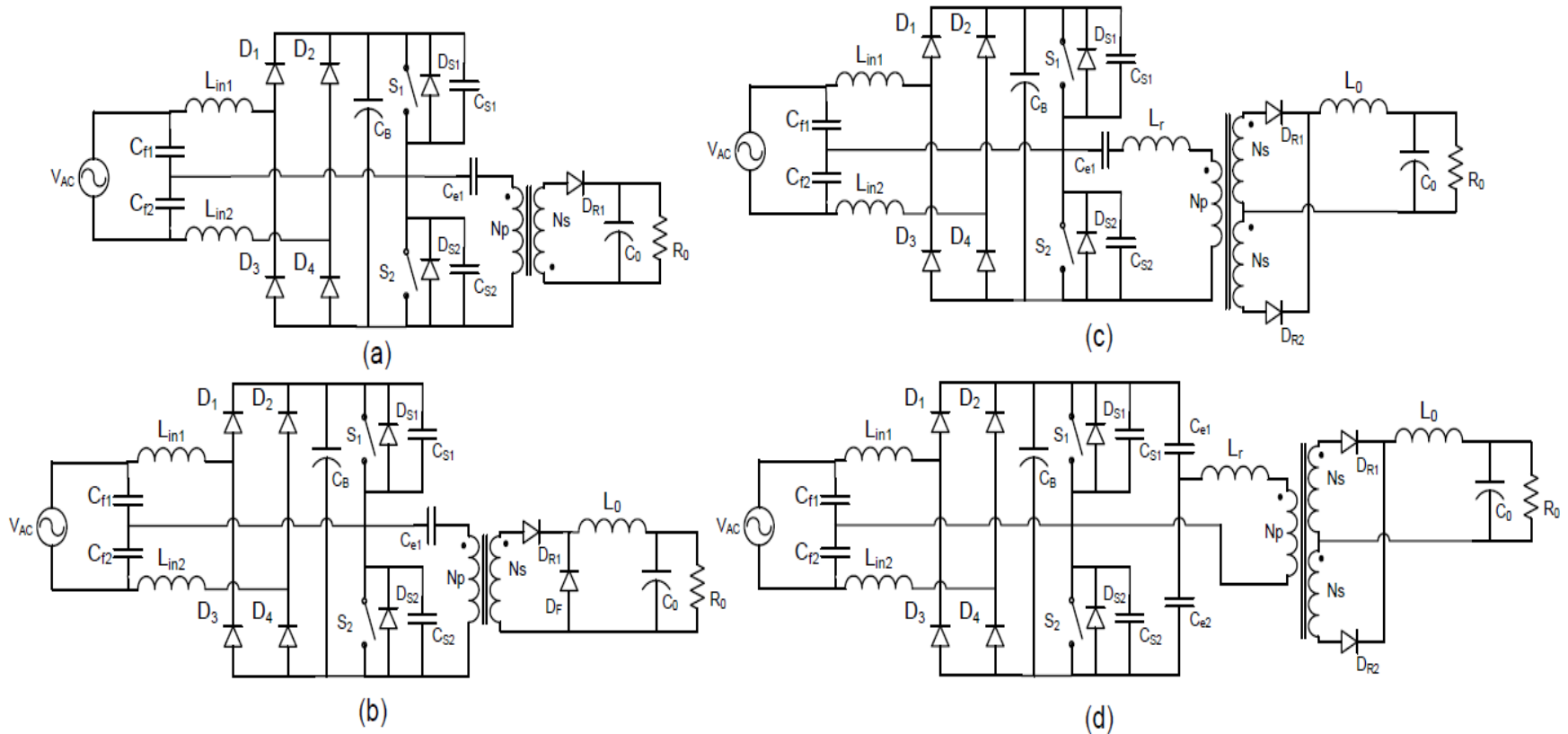


Figure 1. Proposed AC-DC converters: (a) PFC integrated with a flyback converter, (b) PFC integrated with a forward converter, (c) PFC integrated with an AHB converter, and (d) PFC integrated with a SHB converter.



Interleaved Single-Stage LLC Resonant Converter [47]



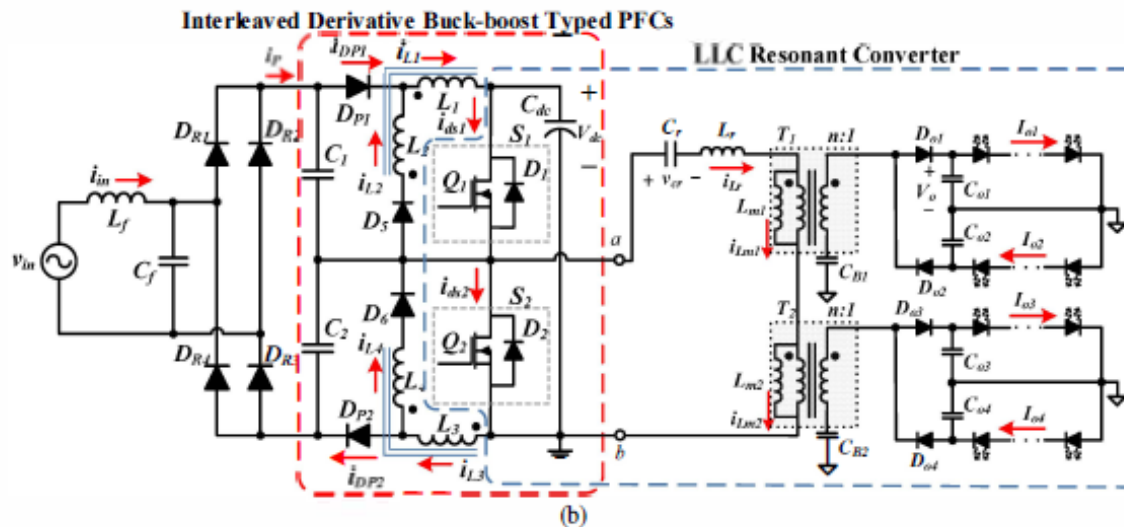


Fig. 3. Circuit derivation of the proposed single-stage LED driver.

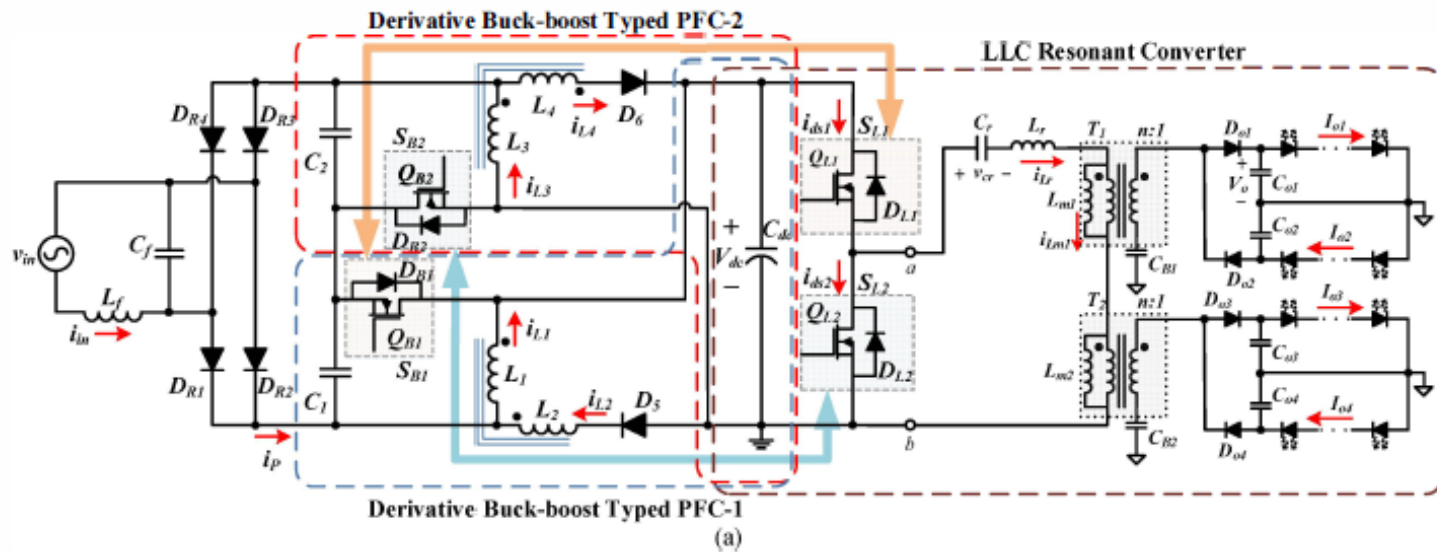


Discussion

A. Duality

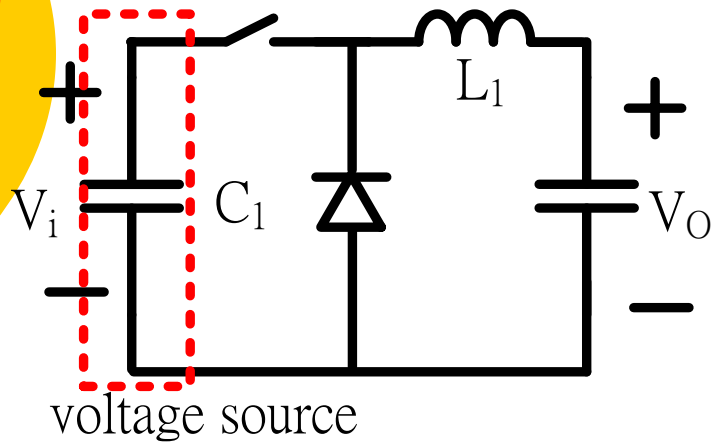

(a)

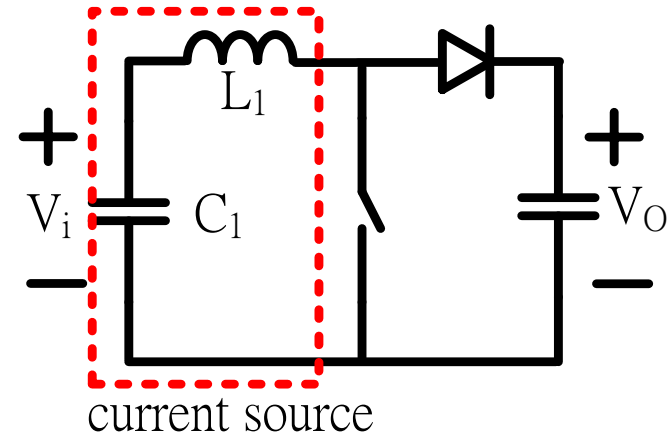


(b)

Fig. 30. Illustration of non-one-to-one correspondence of the duality between voltage source and current source.



What kind of dual is this?

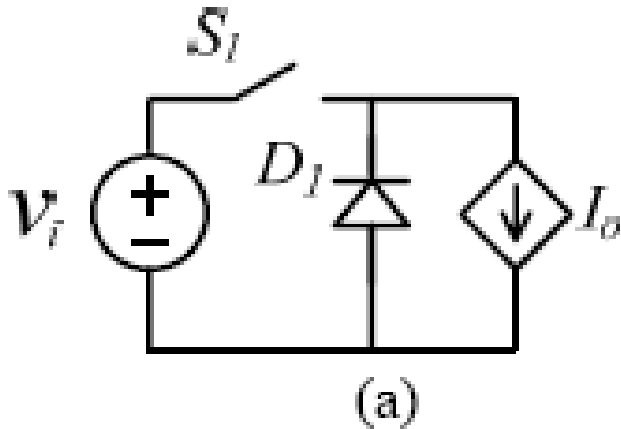

**Topological
Duality**


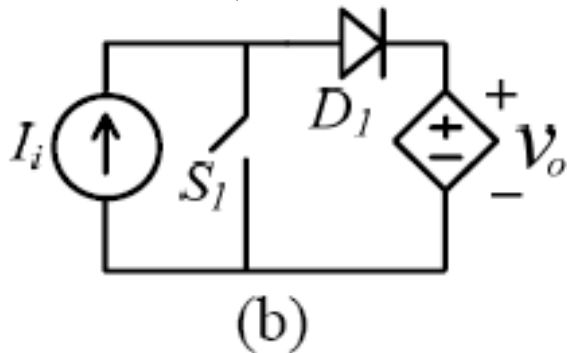


Fig. 31. (a) buck converter, and (b) boost converter in topological configuration

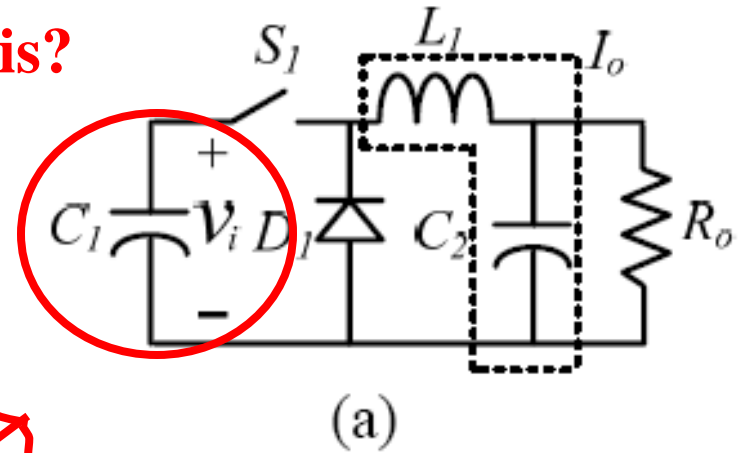

?



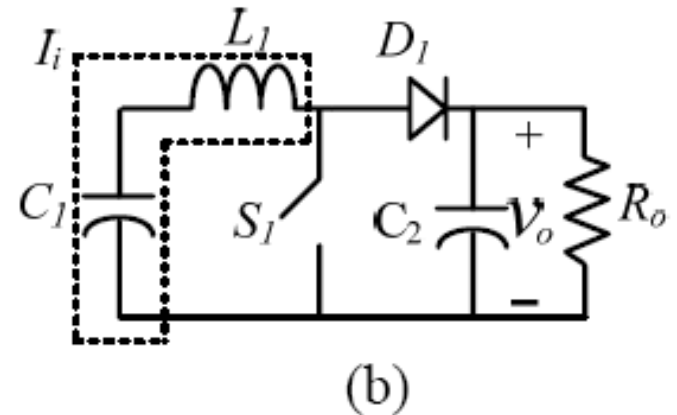


Fig. 32. (a) buck converter, and (b) boost converter in circuit configuration

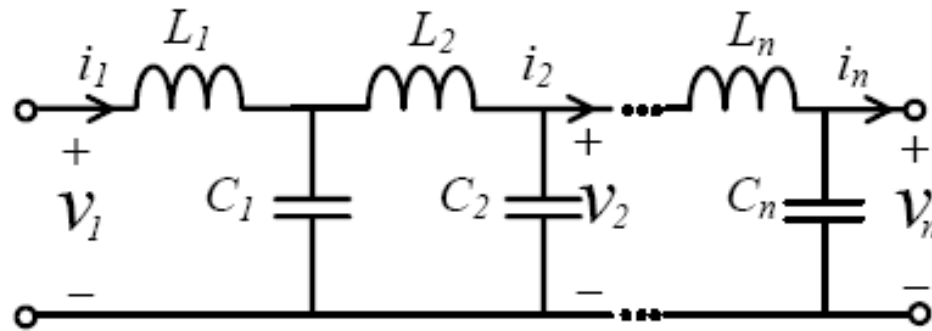


(a)

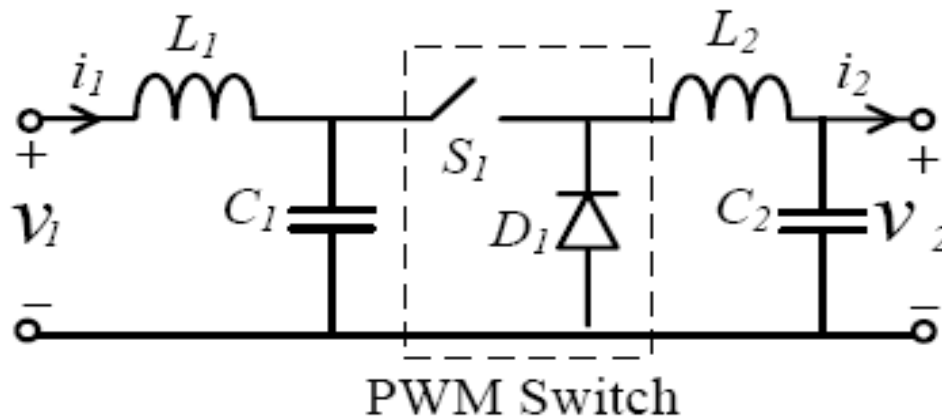


(b)

Fig. 33. (a) a transmission line modeled with L-C network
(b) a buck converter configured from resonance philosophy

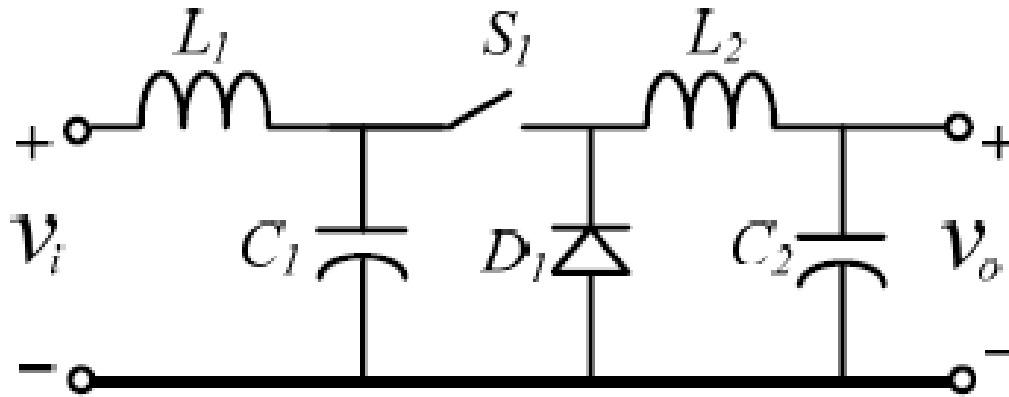

(a) Buck Converter

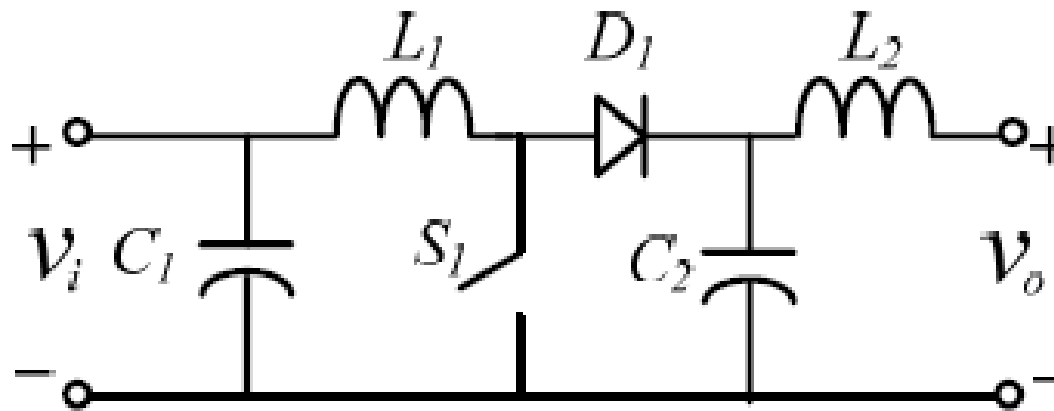

(b) Boost Converter

Fig. 34.



B. Analogy of PWM Converters to DNA

DNA雙螺旋結構發現人 1953年

佛朗西斯·克里克 | 羅莎琳·富蘭克林 | 雷蒙·葛斯林 | 艾力克·斯托克斯 | 莫里斯·威爾金斯 | 賀伯特·威爾森 | 詹姆斯·沃森


The Nobel Prize Winners in 1962.




James Dewey
Watson




Maurice Hugh
Frederick Wilkins

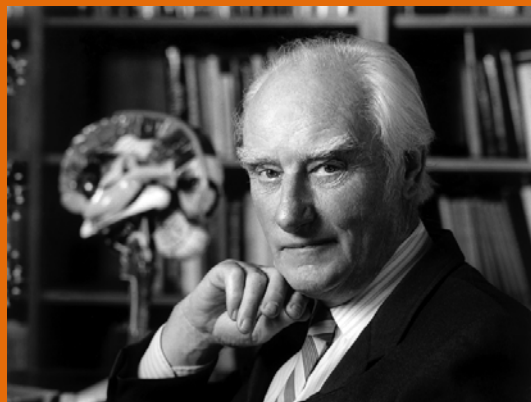


Francis Harry Compton
Crick

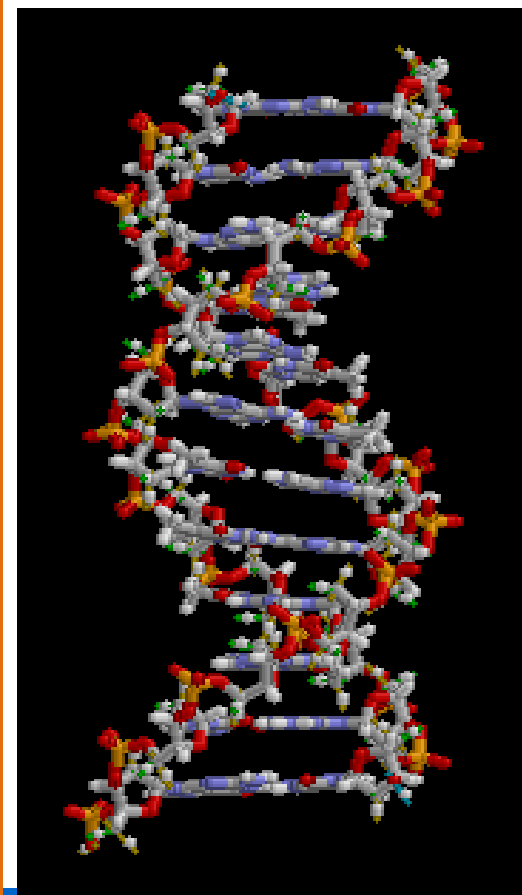


(EPEARL)

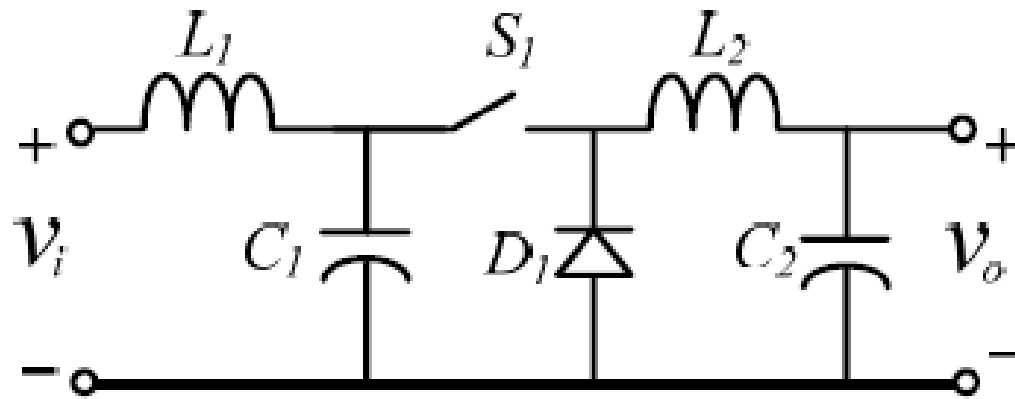

Two-port network

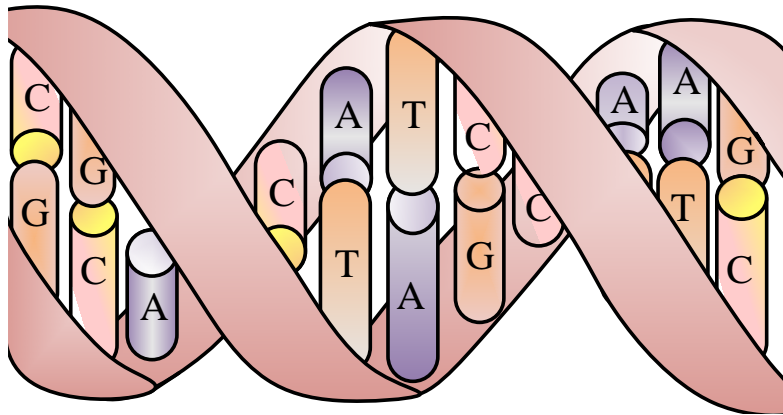

(a)

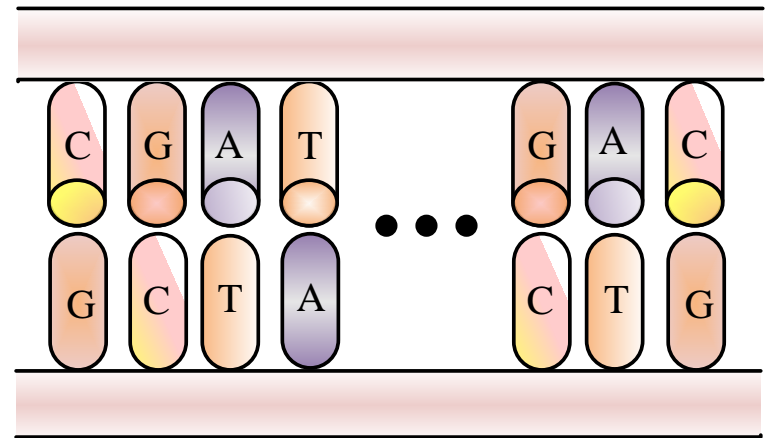


(b)

Fig. 65. (a) DNA in double helix structure
(b) stretched DNA in two-port network like structure.



- Converter ↔ DNA

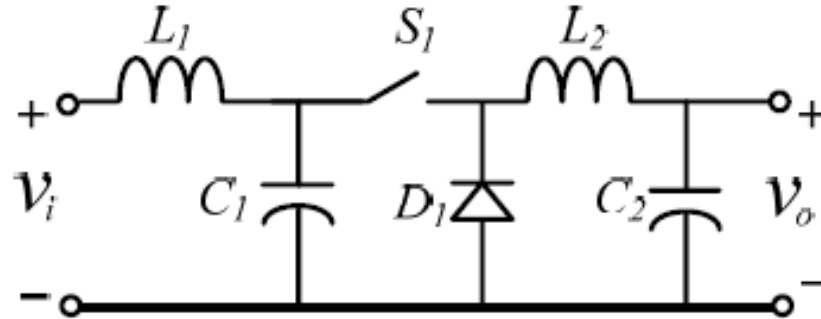

L, C, S, D



A(adenine), T(thymine),
G(guanine), C(cytosine)


L ↔ C

A ↔ T

S ↔ D




G ↔ C

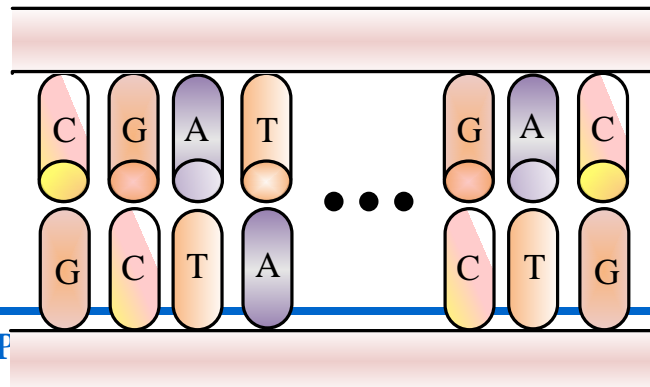




- Converter \leftrightarrow DNA

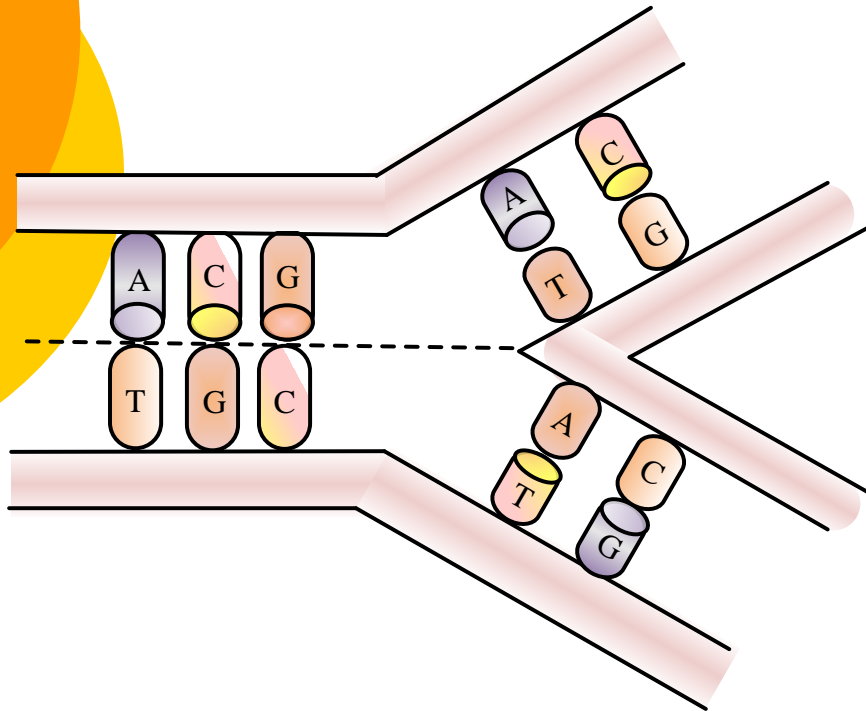

(a)

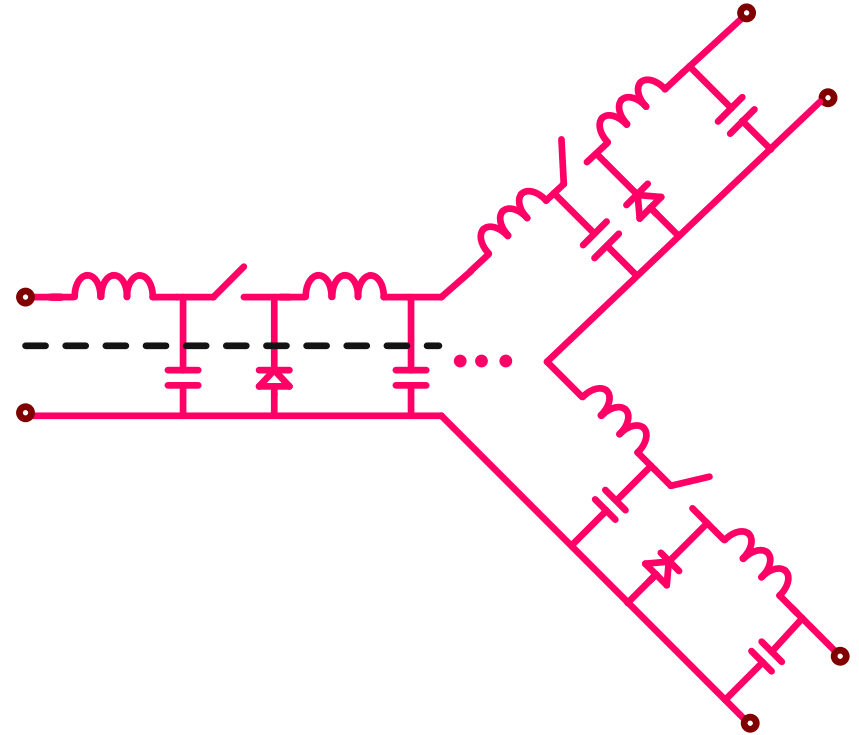

(b)

Fig. 35. Replication of (a) DNA and (b) PWM buck converter.



- **Converters**

1. formed from codes L, C, S and D
2. transfer power

- **DNA**

1. formed from codes A, T, G and C
2. transmit signal





跳脫本業窠臼 妙趣橫生
跨越領域鴻溝 海濶天空
馳騁學術疆場 創意無窮
究竟天下道理 萬源歸宗

1. Jumping out the trapped area, we will find a lot of fun.
2. Crossing the gap between fields, our mind can soar in the sky freely.
3. Based on this kind of mind, we can gallop free in academic field and have unlimited innovation.
4. After realizing the natural rules, we recognize that all of them just deduce from a simple principle.



Thanks for your attention





References

1. S. Ćuk, "General Topological Properties of Switching Structures," *Proceedings of the IEEE PESC*, pp. 109-130, 1979.
2. R. W. Erickson, "Synthesis of Switched-Mode Converters," *Proceedings of the IEEE PESC*, pp. 9-22, 1983.
3. R. P. Severns and G. E. Bloom, *Modern DC-to-DC Switch Mode Power Converter Circuits*, Van Nostrand Reinhold Co., New York, 1985.
4. R. Tymerski and V. Vorperian, "Generation, Classification and Analysis of Switched-Mode DC-to-DC Converters by the Use of Converter Cells," *Proceedings of INTELEC*, pp. 181-195, 1986.
5. K.-H. Liu and F. C. Lee, "Topological Constraints of Basic PWM Converters," *Proceedings of the IEEE PESC*, pp. 164-172, 1988.
6. M. S. Makowski, "On Topological Assumptions on PWM Converters—A Re-Examination," *Proceedings of IEEE Power Electronics Specialists Conference 1993*, pp. 141-147.
7. D. Maksimovic and S. Ćuk, "General Properties and Synthesis of PWM DC-to-DC Converters," *Proceedings of the IEEE PESC*, pp. 515-525, 1989.
8. F. C. Lee, *High-Frequency Resonant, Quasi-Resonant and Multi-Resonant Converters*, Virginia Power Electronics Center, 1989.
9. A. K. S. Bhat and F. D. Tan, "A Unified Approach to Characterization of PWM and Quasi-PWM Switching Converters: Topological Constraints, Classification, and Synthesis," *IEEE Trans. On Power Electronics*, Vol. 6, No. 4, pp. 719-726, Oct., 1991.
10. S. D. Freeland, "Techniques for the Practical Applications of Duality to Power Circuits," *IEEE Trans. on Power Electronics*, Vol. 7, No. 2, pp. 374-384, April 1992.
11. M. S. Makowski, "On Topological Assumptions on PWM Converters—A Re-Examination," *Proceedings of IEEE Power Electronics Specialists Conference 1993*, pp. 141-147.
12. D. C. Hopkins and D. W. Root, Jr., "Synthesis of a New Class of Converters That Utilize Energy Recirculation," *Proceedings of the IEEE PESC*, pp. 1167-1172, 1994.
13. T.-F. Wu and Y.-K. Chen, "A Systematic and Unified Approach to Modeling PWM DC/DC Converters Using the Layer Scheme," *Proceedings of IEEE Power Electronics Specialists Conference 1996*, pp. 575-580.
14. T.-F. Wu and T.-H. Yu, "Unified Approach to Developing Single-Stage Power Converters," *IEEE Trans. on Aerospace and Electronic Systems*, Vol. 34, No. 1, pp. 221-223, Jan. 1998.
15. T.-F. Wu and Y.-K. Chen, "A Systematic and Unified Approach to Modeling PWM DC/DC Converter Based on the Graft Scheme," *IEEE Trans. on Industrial Electronics*, Vol. 45, No. 1, pp. 88-98, Feb. 1998.



16. T.-F. Wu and Y.-K. Chen, "Modeling PWM DC/DC Converter Out of Basic Converter Units," *IEEE Trans. on Power Electronics*, Vol. 13, No. 5, pp. 870-881, Sept. 1998.
17. T.-F. Wu, Y.-K. Chen and S.-A. Liang, "A Structural Approach to Synthesizing, Analyzing and Modeling Quasi-Resonant Converters," *Power Electronics Specialists Conference 1999*, pp. 1024-1029.
18. T.-F. Wu, Shih-An Liang and Yu-Kai Chen, "A Structural Approach to Synthesizing Soft Switching PWM Converters," *IEEE Trans. On Power Electronics*, Vol. 18, No. 1, pp. 38-43, January, 2003.
19. M. Ogata and T. Nishi, "Topological Criteria for Switched Mode Dc-Dc Converters," *Proceedings of ISCAS 2003*, Vol. 3, pp. 184-187.
20. F. Z. Peng, L. M. Tolbert, and F. H. Khan, "Power Electronic Circuit Topology—The Basic Switching Cells," *Proceeding of IEEE Power Electronics Education Workshop 2005*, pp. 52-57.
21. Y. Berkovich, A. Shenkman, A. Loinovici, and B. Axelrod, "Algebraic Representation of DC-DC Converters and Symbolic Method of Their Analysis," *Proceeding of IEEE Convention. Electrical and Electronics Engineers 2006*, pp. 47-51.
22. F. H. Khan, L. M. Tolbert, and F. Z. Peng, "Deriving New Topologies of DC-DC Converters Featuring Basic Switching Cells," *Proceeding of IEEE COMPEL 2006*, pp. 328-332.
23. Y. Berkovich, B. Axelrod, S. Tapuchi, and A. Ioinovici, "A family of four-quadrant, PWM DC-DC converters", *Proceedings of IEEE Power Electronics Specialists Conference 2007*, pp. 1878-1883.
24. B. W. Williams, "Basic DC-to-DC converters," *IEEE Trans. on Power Electronics*, Vol. 23, No. 1, pp. 387-401, Jan., 2008.
25. J. Anderson and F. Z. Peng, "Four Quasi-Z source Inverters", *Proceedings of IEEE Power Electronics Specialists Conference 2008*, pp. 2743-2749.
26. J. Anderson and F. Z. Peng, "A Class of Quasi-Z source Inverters", *Proceedings of IEEE Industrial Application Meeting 2008*, pp. 1-7.
27. D. Cao and F. Z. Peng, "A family of Z source and quasi-Z source DC-DC converters" , *Proceedings of IEEE Applied Power Electronics Conference 2009*, pp. 1097-1101.
28. L. M. Tolbert, F. Z. Peng, F. H. Khan, and S. Li, "Switching Cells and Their Implications for Power Electronic Circuits," *Proceeding of IEEE IPEMC 2009*, pp. 773-779.
29. B. W. Williams, "Generation and Analysis of Canonical Switching Cell DC-to-DC Converters," *IEEE Trans. on Industrial Electronics*, Vol. 61, pp. 329-346, 2014.
30. F. Z. Peng, "Z source Inverter", *IEEE Trans. On Industrial Application*, vol. 39, No. 2, pp. 504-510, Mar./Apr. 2003.



31. W. Qian, F. Z. Peng, and H. Cha, “Trans-Z source Inverters” , *IEEE Trans. On Power Electronics*, Vol. 26, No. 12, pp. 3453–3463, Dec. 2011.
32. F. Z. Peng, A. Joseph, J. Wang, M. Shen, L. Chen, Z. Pan, E. Ortiz-Rivera, and Y. Huang, “Z source Inverter for Motor Drives” , *IEEE Trans. On Power Electronics*, Vol. 20, No. 4, pp. 857–863, Jul. 2005.
33. Y. Huang, M. Shen, F. Z. Peng, and J. Wang, “Z source Inverter for Residential Photovoltaic Systems” , *IEEE Trans. On Power Electronics*, Vol. 21, No. 6, pp. 1776–1782, Nov. 2006.
34. F. Z. Peng, M. Shen, and K. Holland, “Application of Z source Inverter for Traction Drive of Fuel Cell Battery Hybrid Electric Vehicles” , *IEEE Trans. On Power Electronics*, Vol. 22, No. 3, pp. 1054–1061, May 2007.
35. M. Shen, A. Joseph, J. Wang, F. Z. Peng, and D. J. Adams, “Comparison of Traditional Inverters and Z source Inverter for Fuel Cell Vehicles” , *IEEE Trans. On Power Electronics*, Vol. 22, No. 4, pp. 1453–1463, Jul. 2007.
36. U. Supatti and F. Z. Peng, “Z source Inverter Based Wind Power Generation System” , *Proceeding of IEEE International Conference Sustainable Energy Technologies*, pp. 634–638, Nov. 2008.
37. J.-H. Park, H.-G. Kim, E.-C. Nho, T.-W. Chun, and J. Choi, “Grid Connected PV System Using a Quasi-Z source Inverter,” *Proceedings of IEEE Applied Power Electronics Conference 2009*, pp. 925–929.
38. Z. J. Zhou, X. Zhang, P. Xu, and W. X. Shen, “Single-phase Uninterruptible Power Supply Based on Z source Inverter,” *IEEE Trans. on Industrial Electronics*, Vol. 55, no. 8, pp. 2997–3004, Aug. 2008.
39. D. Vinnikov and I. Roasto, “Quasi-Z source Based Isolated DC/DC Converters for Distributed Power Generation,” , *IEEE Trans. on Industrial Electronics*, Vol. 58, pp. 192–201, 2011.
40. F. L. Luo, “Double-output Luo converters, an advanced voltage-lift,” *IEE Proceedings on Electric Power Applications*, Vol. 147, No. 6, pp. 469-485, 2000.





41. Fengfeng Tao and Fred C. Lee, “An Interleaved Single-Stage Power-Factor-Correction Electronic Ballast”, *IEEE Applied Power Electronics Conf.*, 2000, pp. 617–623.
42. Chun-An Cheng, Hung-Liang Cheng, Chien-Hsuan Chang, Fu-Li Yang and Tsung-Yuan Chung, “A Single-Stage LED Driver for Street-Lighting Applications with Interleaving PFC Feature”, *IEEE 2nd International Symposium on Next-Generation Electronics (ISNE)*, 2013.
43. B. R. Lin, C. H. Chao and L. A. Lin, “Implementation of an Interleaved Single-Stage High Power Factor Converter”, *Industrial Electronics and Applications*, 2011, pp. 1209-1214.
44. P. C. S. Ficagna * and J. R. Pinheiro, “A Single-Stage LED Driver for Street-Lighting Applications with Interleaving PFC Feature.”, *IEEE* 2008.
45. J. Y. Lee, L. S. Yang, T. J. Liang, and M. Y. Cheng, “Analysis and Implementation of Interleaved Single-Stage Single-Phase AC-DC Boost-Flyback Converter”, *IEEE Power Electronics and Motion Control Conference*, 2009, pp. 678-682.
46. C. S. Postiglione, A. L. Fuerback, D. C. Martins, A. J. Perin, C. B. Nascimento, “Single-Stage PFC AC-DC Converter Based on Serial- Interleaved Boost”, *10th IEEE/IAS International Conference on Industry Applications*, 2012, pp 1-8.
47. C. H. Chang, C. A. Cheng, Masahito Jinno, and H. L. Cheng, “An Interleaved Single-Stage LLC Resonant Converter Used for Multi-Channel LED Driving”, *IEEE Power Electronics Conference*, 2014, pp.3333-3340.
48. B. Axelrod, Y. Berkovich, and A. Ioinovici, “Switched-capacitor/switched-inductor structures for getting transformerless hybrid dc-dc PWM converters,” *IEEE Trans. on Circuits and Systems-I*, Vol. 55, No. 2, pp. 687-696, 2008.